



Lab 2

Circuit Analysis


1. Introduction:

The purpose of this lab is to verify the findings of Thevenin's and Norton's Theorems

A- Thevenin's and Norton's theorems verification

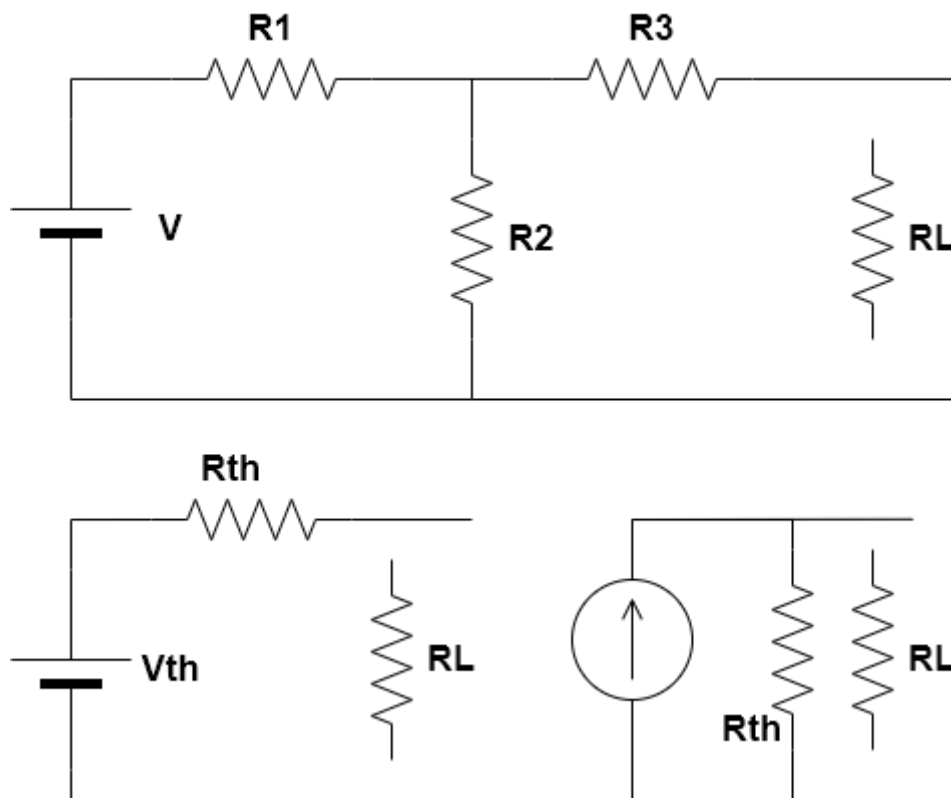I. Experiment:

- 1- Consider the first circuit in Fig. 1 where $R_L = 2K\Omega$, and calculate its Thevenin's and Norton's equivalent circuits as depicted in Fig. 2.



- 2- Measure the voltage across R_L and the current passing through it, in the three circuits, and fill in the below table.






	V across R_L	I in I_L
Original cct.		
Thevenin's equivalent		
Norton's equivalent		



3- Comment on how this verifies Thévenin's and Norton's theorems.



II. Simulation Procedures:

➤ Draw schematic:

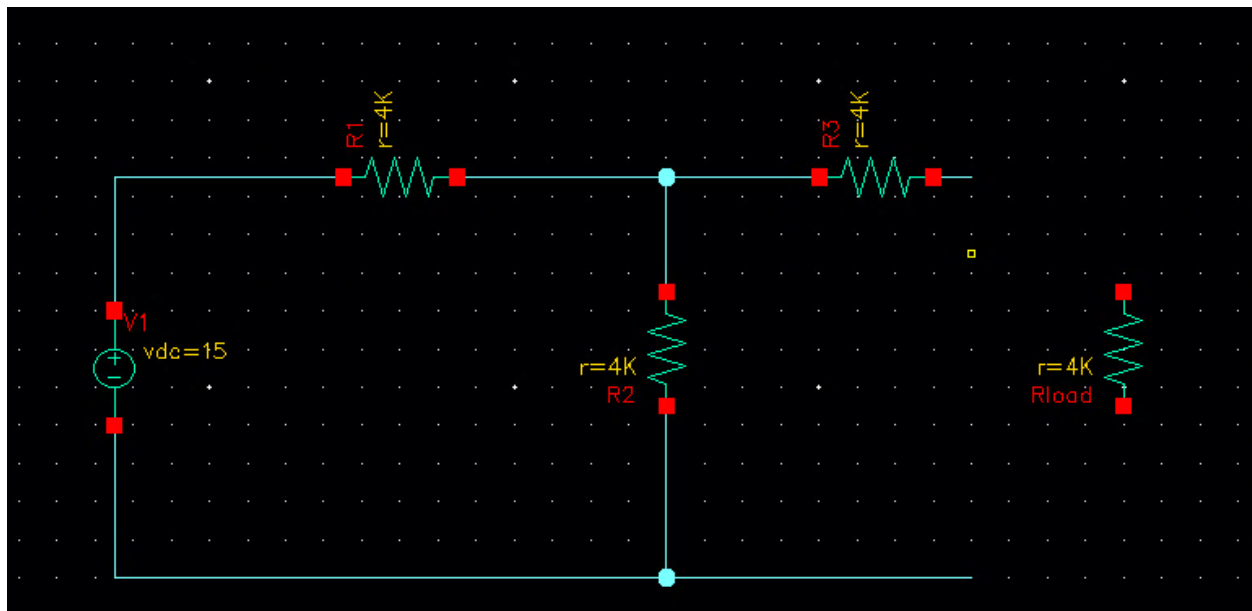

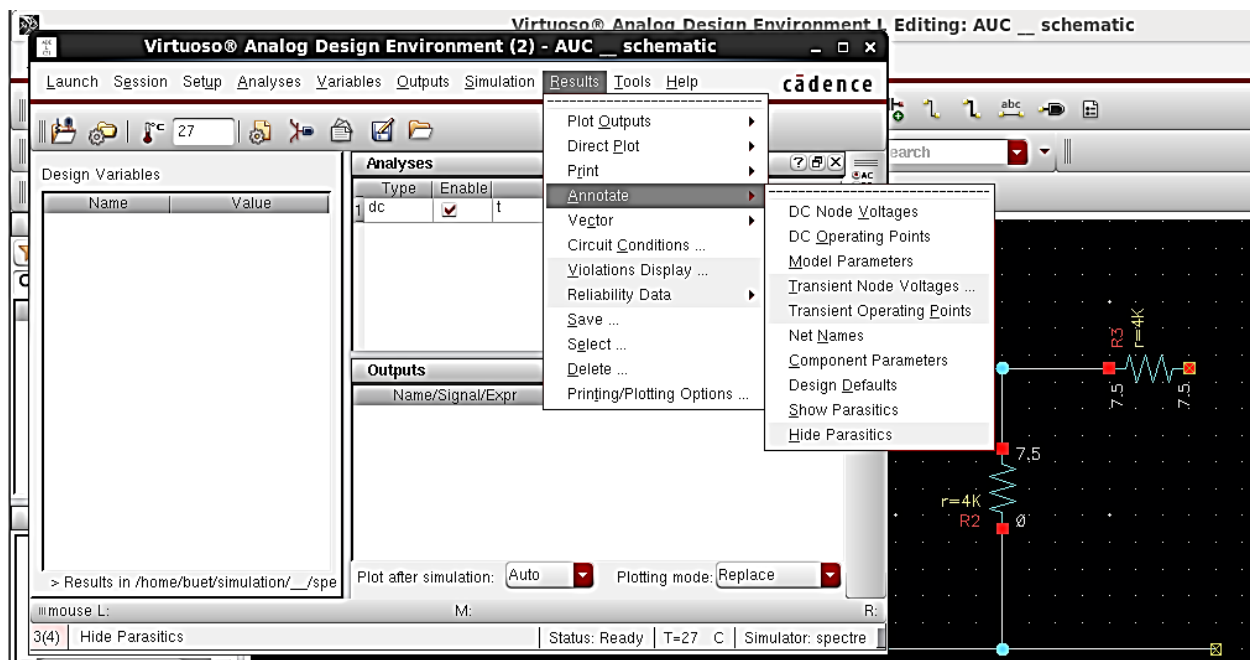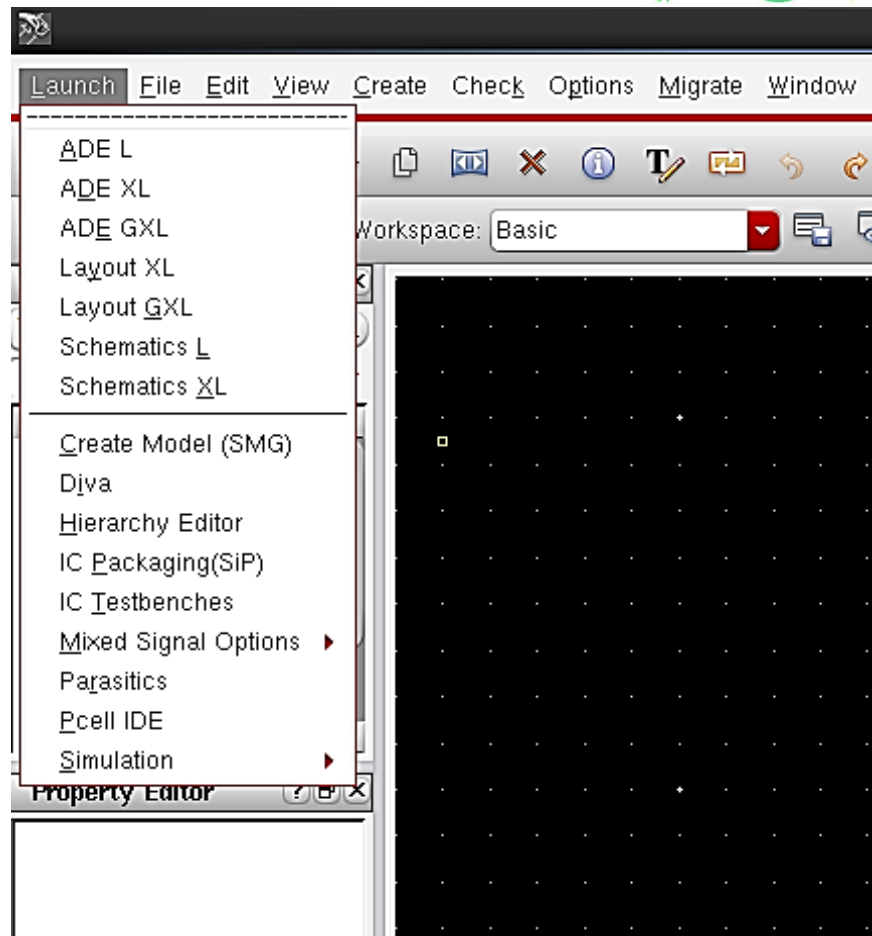

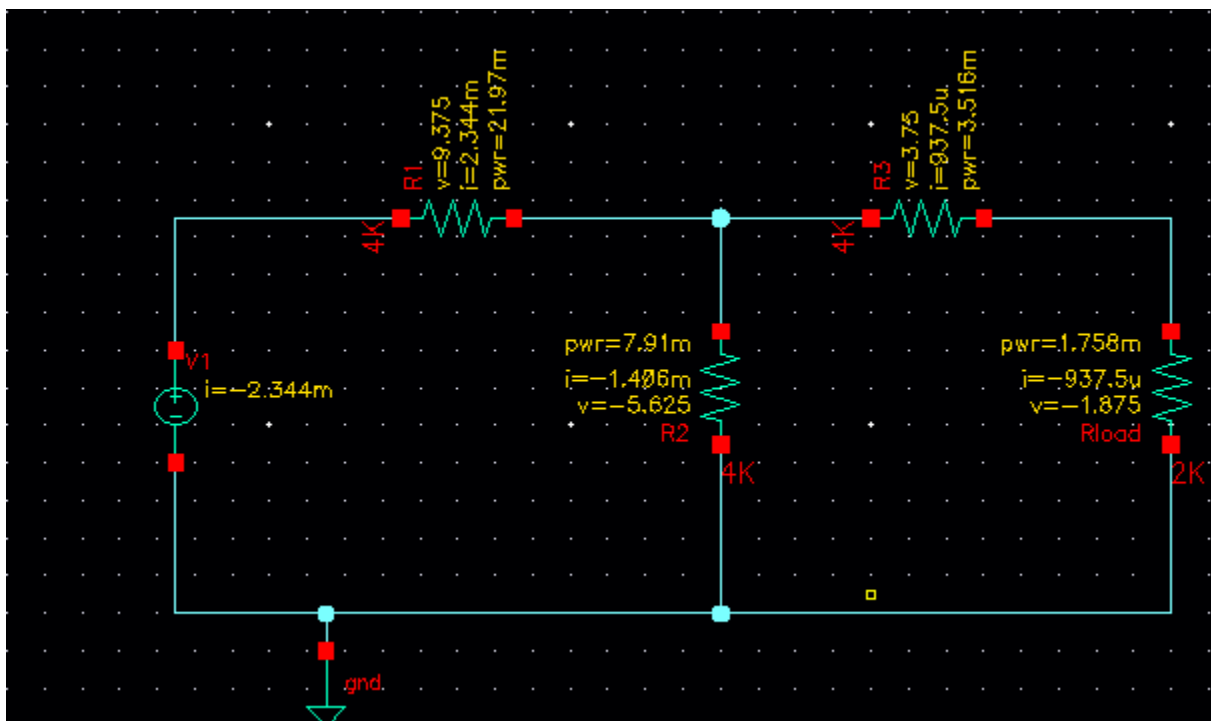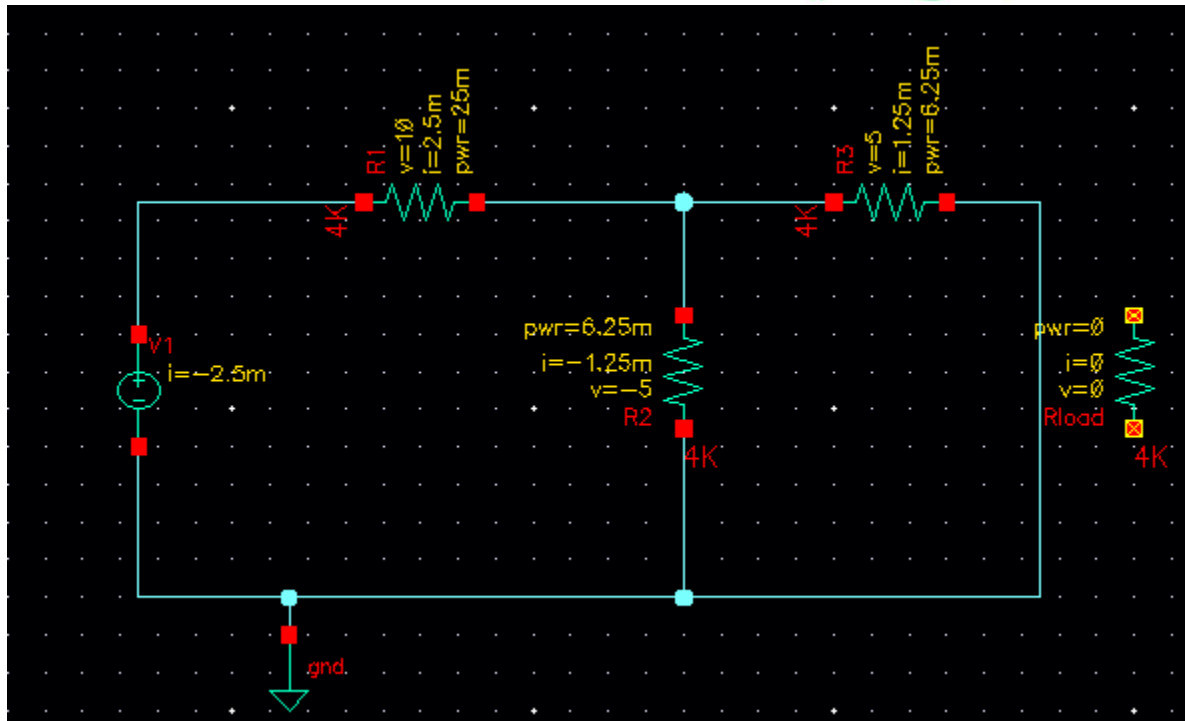

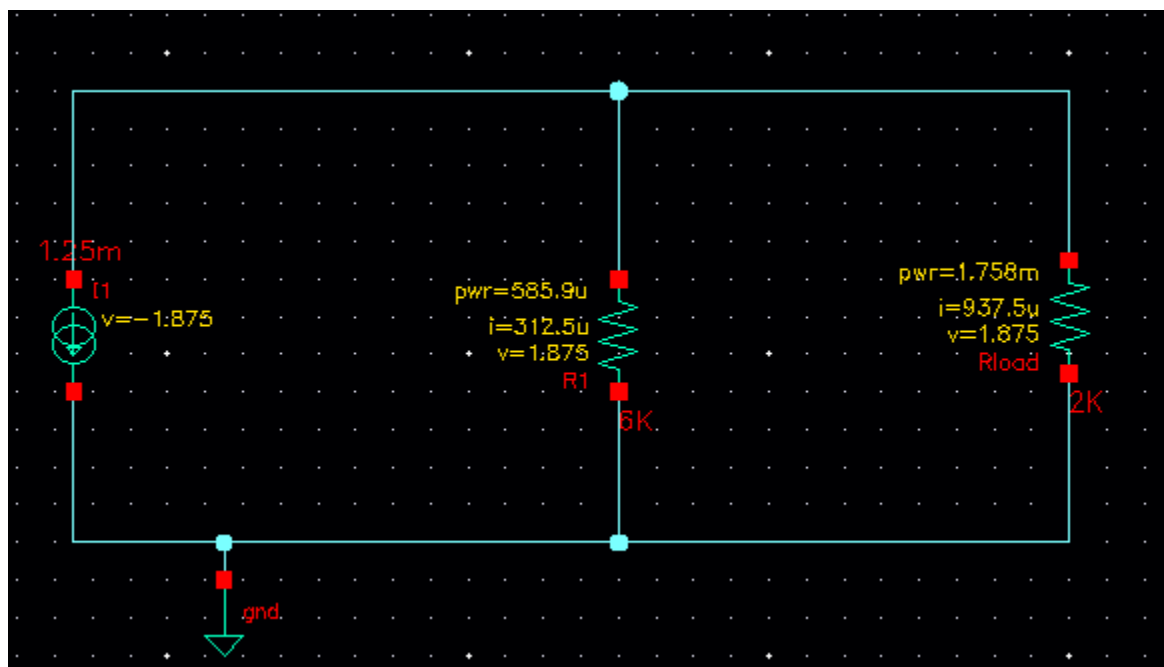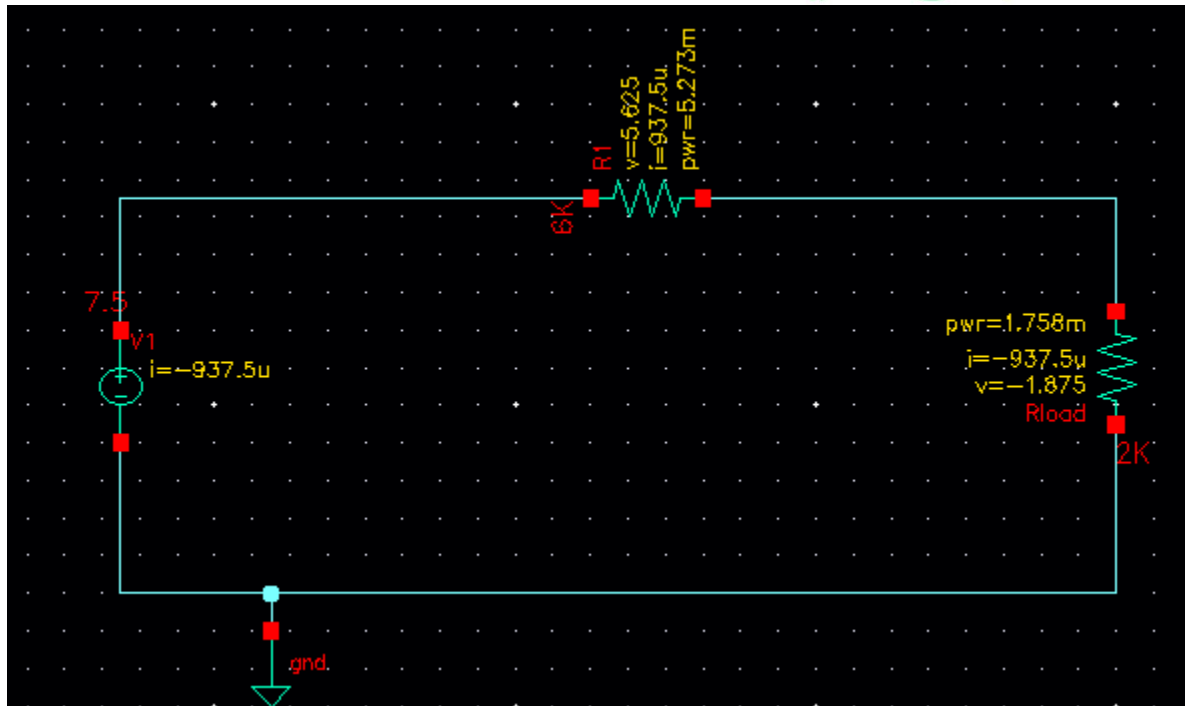

B- Nodal-Analysis Technique:

Multi-source DC circuits may be analyzed using the nodal analysis technique. The process involves identifying all of the circuit nodes, a node being a point where various branch currents combine. A reference node, usually ground, is included. Kirchhoff's Current Law is then applied to each node. Consequently, a set of simultaneous equations are created with an unknown voltage for each node with the exception of the reference.

1. Experiment:

- Connections are made as shown in Fig.1
- Measure actual values Table.1.

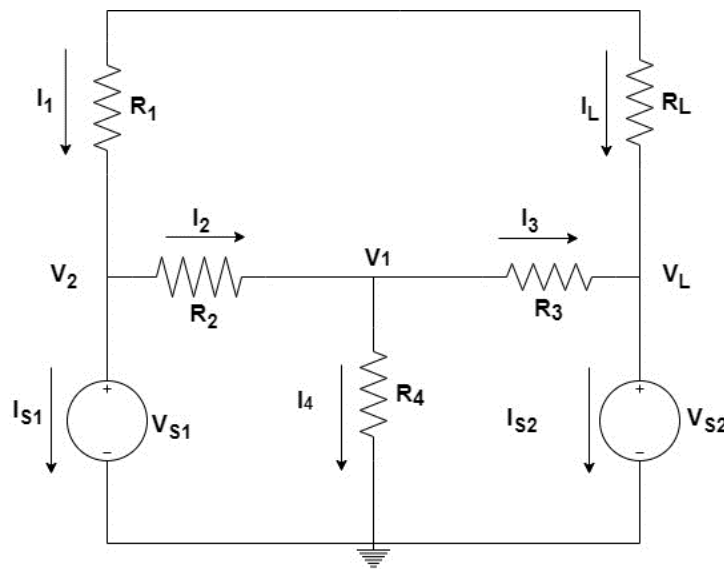


Figure 1: Connection Diagram for the Dual Voltage Supply Experimental Network.

Vs1 = 13V(nominal), Vs2 = 5V (nominal), R1 = 1.4-2.4 kΩ, R2 = 2.9-5.1 kΩ, R3 = 6.5-8 kΩ, R4 = 9.5-16 kΩ, RL = 2.6-3.6 kΩ (3.3 kΩ nominal)

Table 1 Component Actual values

	Vs1	Vs2	R1	R2	R3	R4	RL
Value							

- Calculate Node Voltages using the component's actual-values

$$\Delta\% = \frac{V_{j,meas} - V_{j,calc}}{V_{j,calc}} \times 100$$

Table 2 Node Voltages



	V1	V2	VL
Calculated			
Measured			
$\Delta\%$			

- Calculate Branch Currents using the component's actual-values

$$\Delta\% = \frac{I_{j,meas} - I_{j,calc}}{I_{j,calc}} \times 100$$

Table 3 Branch Currents:

	I1	I2	I3	I4	Is1	Is2	IL
Calculated							
Measured							
$\Delta\%$							

- For ALL power calculations assume that the PASSIVE Sign convention relates component voltage-polarities and current-directions.
- Calculation-1: Use the component's actual values.
- Calculation-2: Use the measured values of V-across, and I-through for the two supplies from the previous tables 2-3.

$$\Delta\% = \frac{P_{j,meas} - P_{j,calc}}{P_{j,calc}} \times 100$$

Table. 4 Power from sources

	Pvs1	Pvs2	$\sum P_{vsj}$
Calculated			
Measured			
$\Delta\%$			

Table. 5 Power absorbed by resistors.

	P_{R1}	P_{R2}	P_{R3}	P_{R4}	P_{RL}	$\sum P_{Rj}$
Calculated						
Measured						
$\Delta\%$						




$$\Delta_{OB} \% = \frac{\sum P_{Vsj} - \sum P_{Rj}}{|\sum P_{Vsj}| + |\sum P_{Rj}|} \times 100$$

Table 6 Power balance


	$\sum P_{Vsj}$	$\sum P_{Rj}$	% out of balance
Calculated			
Measured			

2. Simulation Procedures:

➤ Draw SCHEMATIC

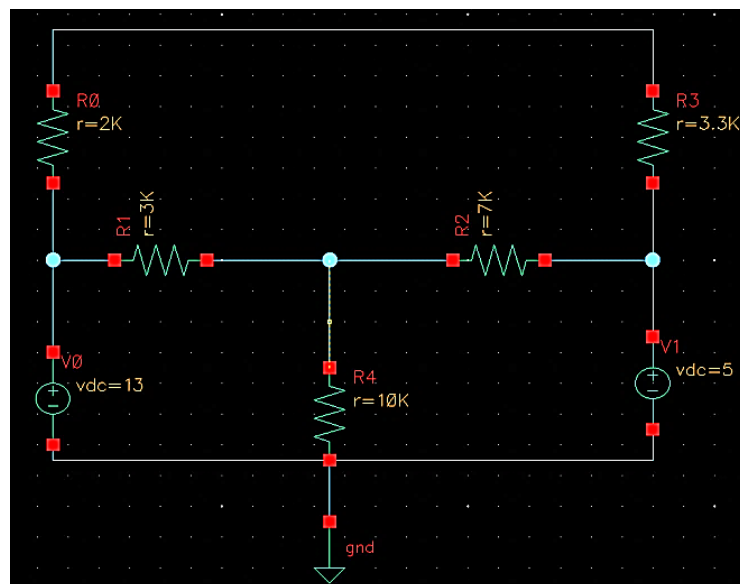


➤ Check and save.

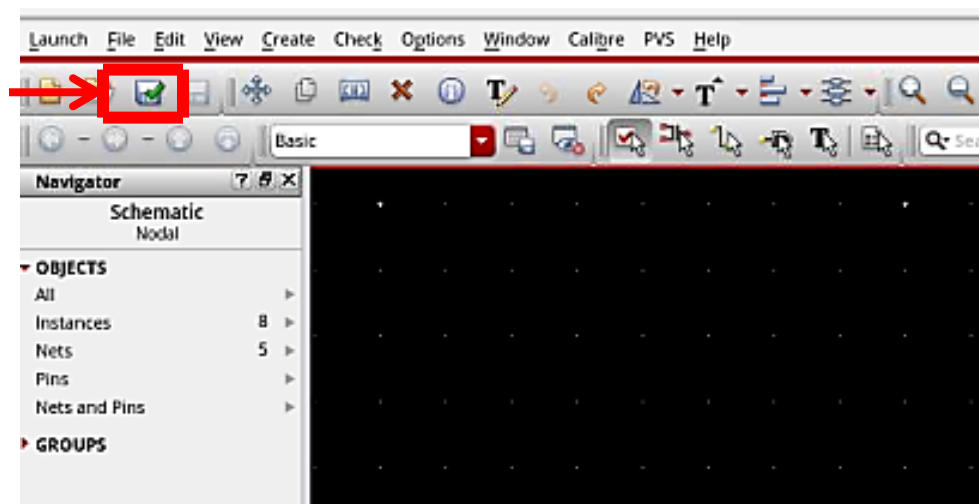





➤ **Lunch => ADE XL**

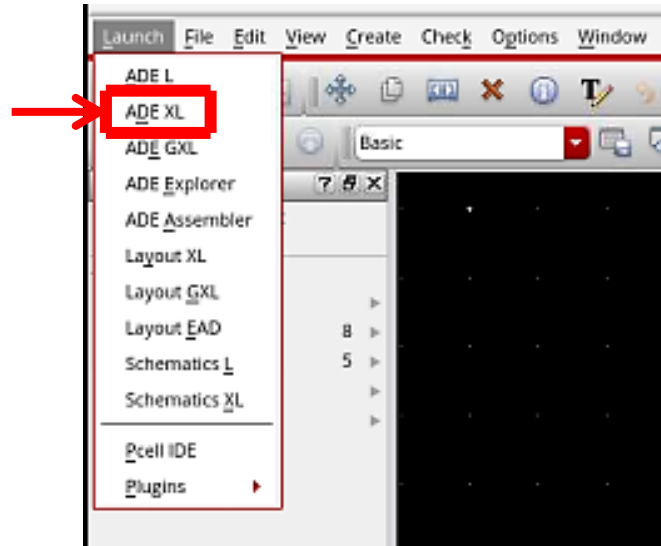


➤ **Create New View => OK**

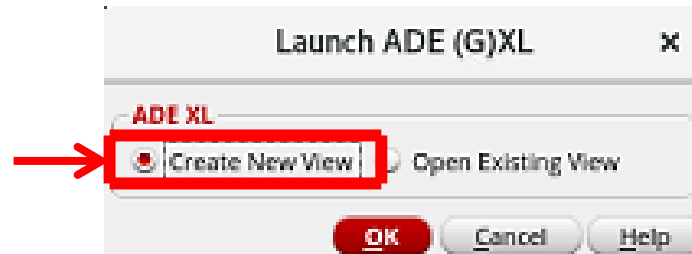


➤ **Cell => “nodel” => OK**

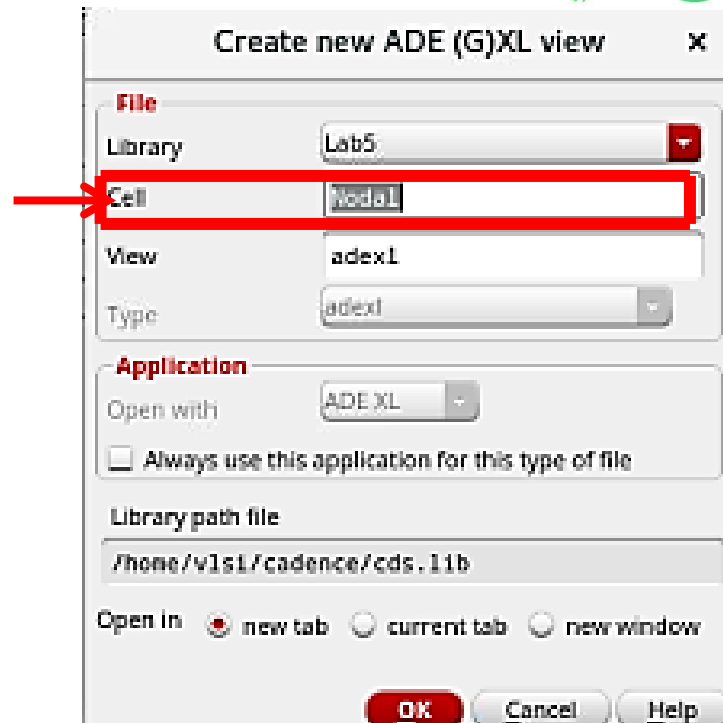

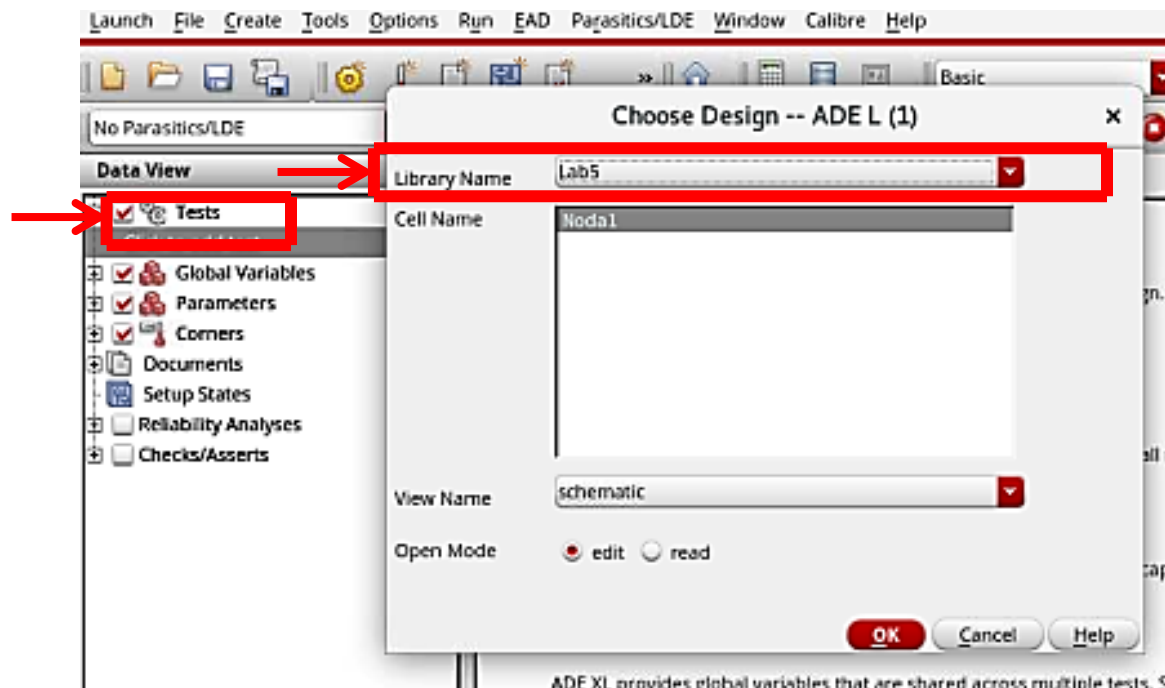
➤ Click “Tests” => Cell Name “nodal” => OK



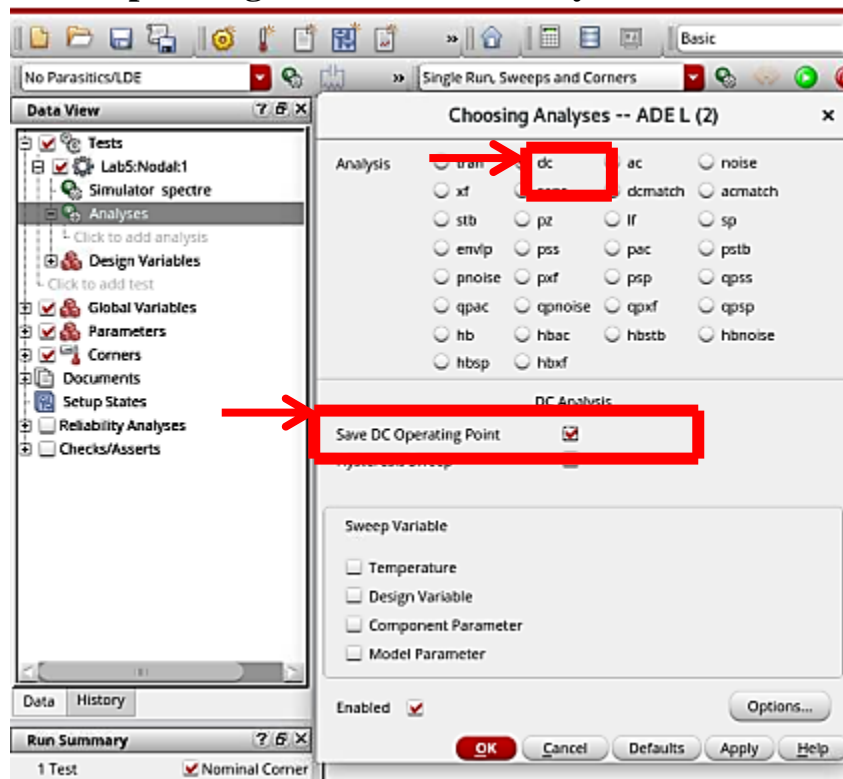- Analysis => dc
- Save DC Operating Points => DC Analysis




- Annotate => DC Operating Points

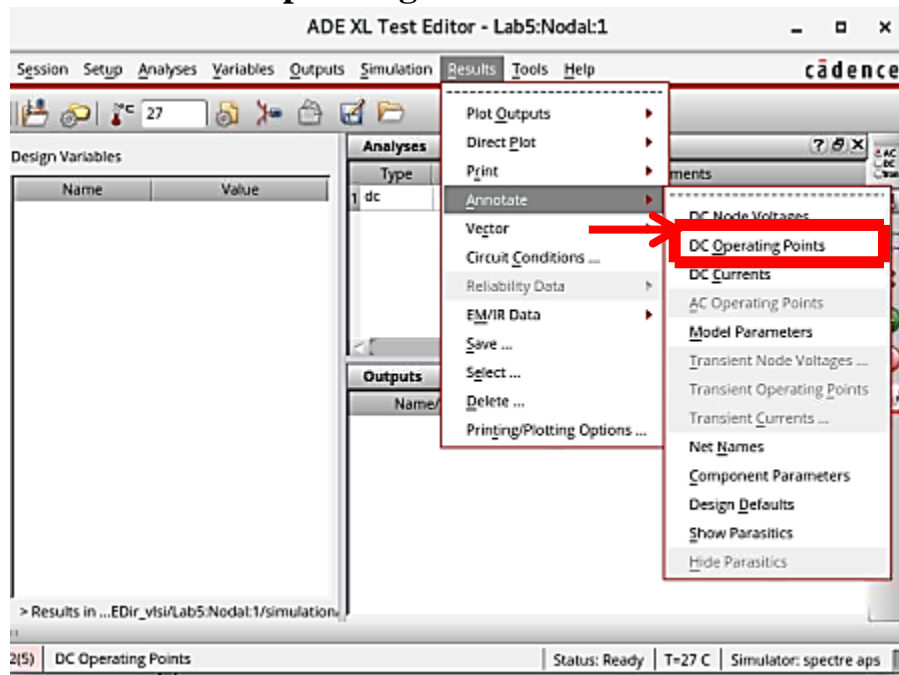




➤ The Result

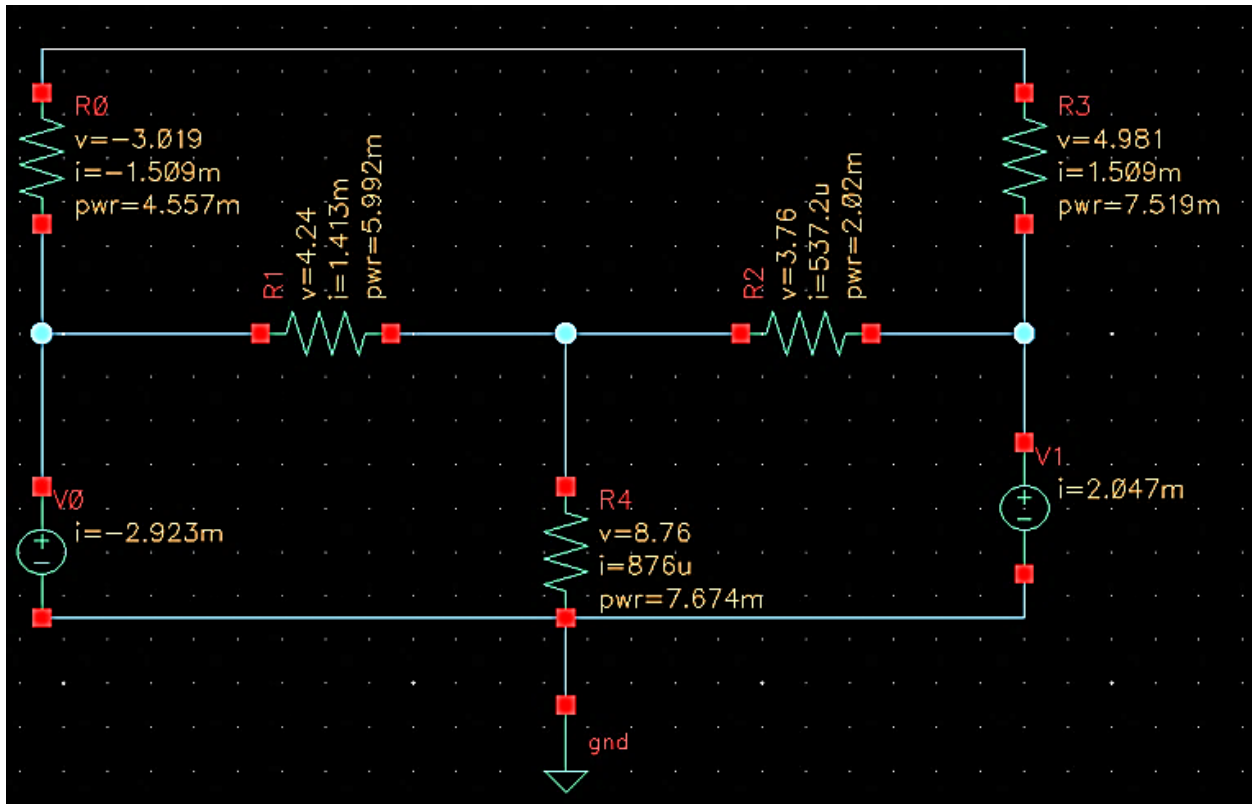


C- Maximum Power Transfer Verification



Using the simulator, add a potentiometer (variable resistor) as a load to terminals a-b in the circuit of Figure 3 (use the V_{th} and R_{th} values from the previous part of this lab). Then, measure the load average power using the wattmeter for different load values. Specify and connect the load that results in the maximum power transfer. Then, verify the max power transfer theory. Record your observations in the table below.

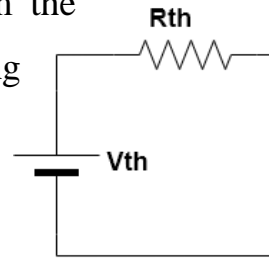

Q: Did the maximum power transfer to the load when R_L was equal to R_{th} ?

R_L												
P_L												

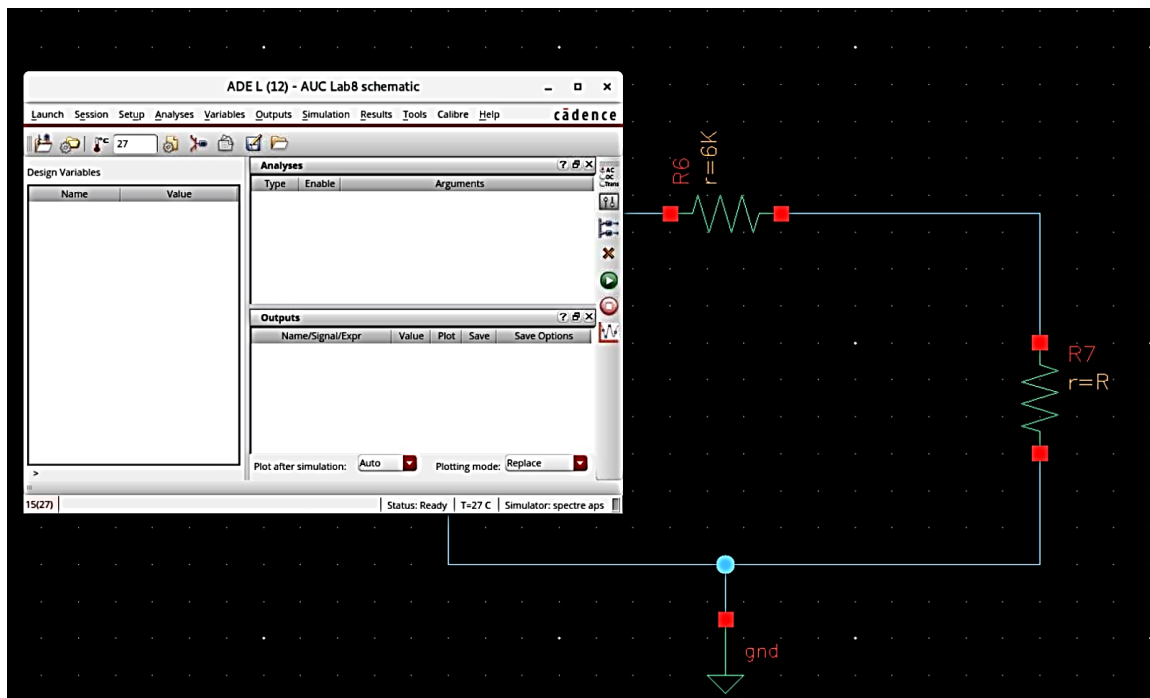

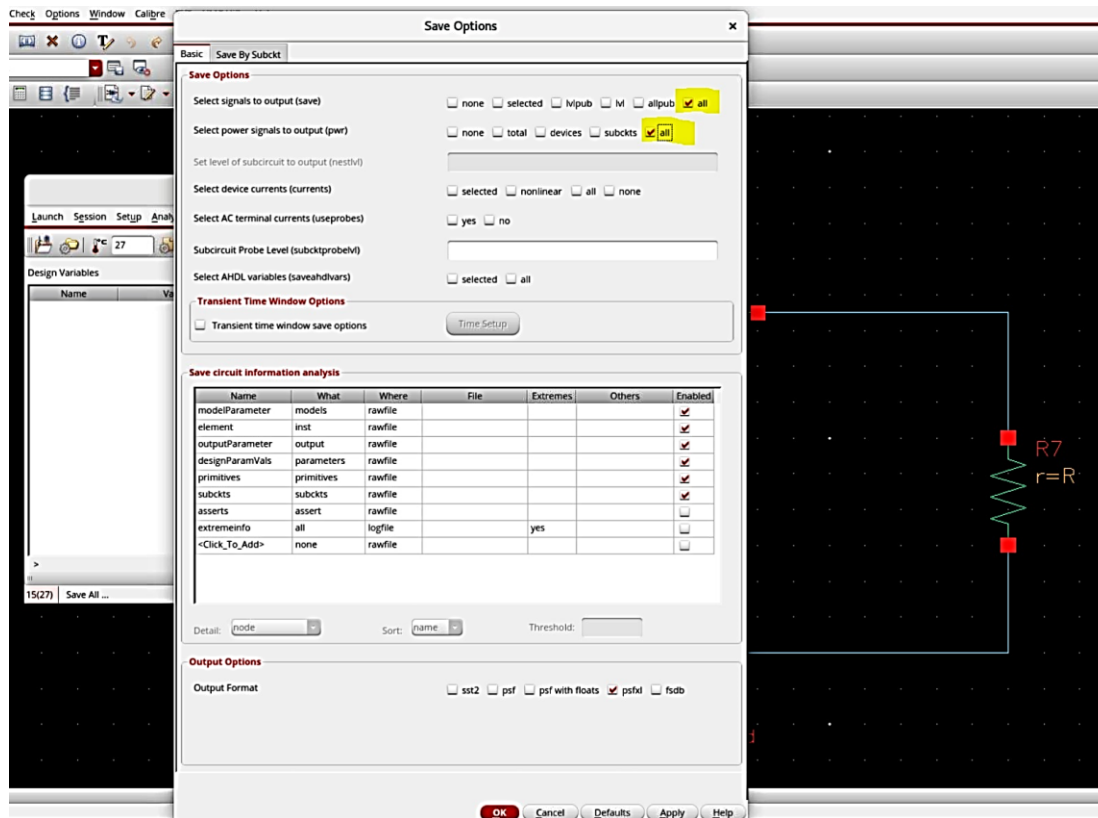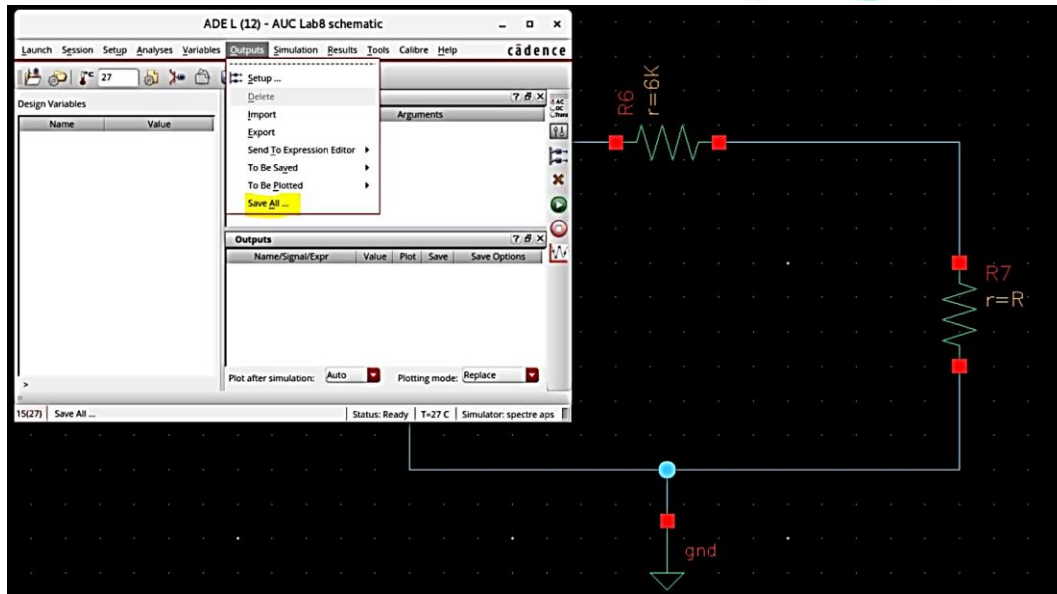



Choosing Analyses -- ADE L (12)

Analysis

☒ dc ☐ ac ☐ noise

☐ xf ☐ sens ☐ dcmatch ☐ acmatch

☐ stb ☐ pz ☐ lf ☐ sp

☐ envlp ☐ pss ☐ pac ☐ pstb

☐ pnoise ☐ pxf ☐ psp ☐ qpss

☐ qpac ☐ qpnoise ☐ qpxf ☐ qpssp

☐ hb ☐ hbac ☐ hbstb ☐ hbnoise

☐ hbsp ☐ hbxf

DC Analysis

Save DC Operating Point ☒

Hysteresis Sweep ☒

Sweep Variable

☐ Temperature

☒ Design Variable

☐ Component Parameter

☐ Model Parameter

Variable Name

Select Design Variable

Sweep Range

☒ Start-Stop

Start Stop

☐ Center-Span

Sweep Type

Automatic ☒

Add Specific Points ☐

Add Points By File ☐

Enabled ☒

Options...

OK Cancel Defaults Apply Help

Direct Plot Form

Plotting Mode

Analysis

☒ dc

Function

☐ Voltage ☐ Voltage Ratio

☐ Current ☐ Current Ratio

☒ Power ☐ Power Ratio



☐ Transresistance ☐ Transconductance


Select

Add To Outputs ☐

> Select Instance Terminal on schematic...

Close Help

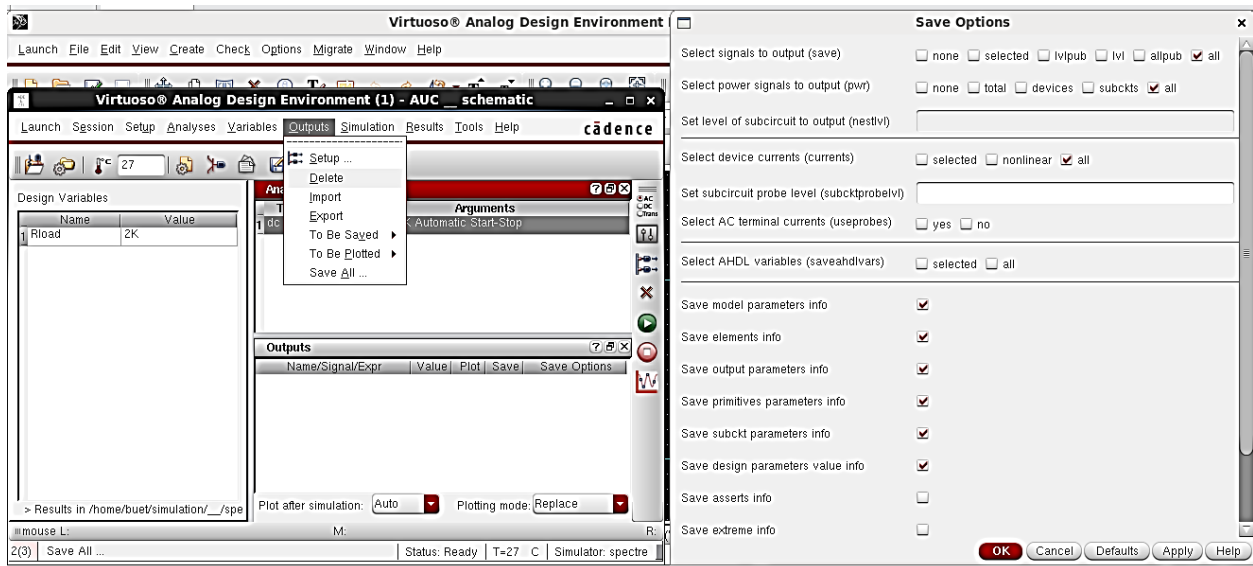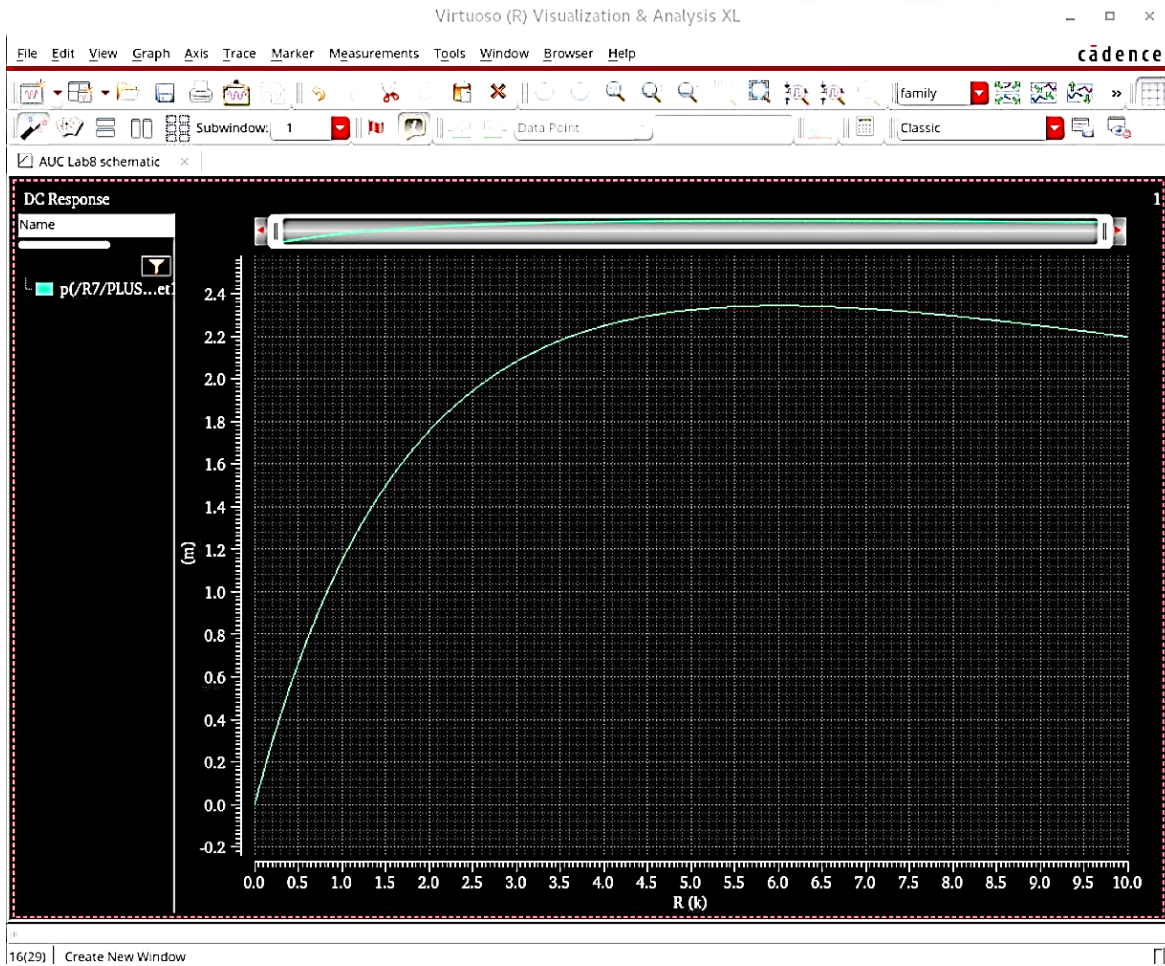

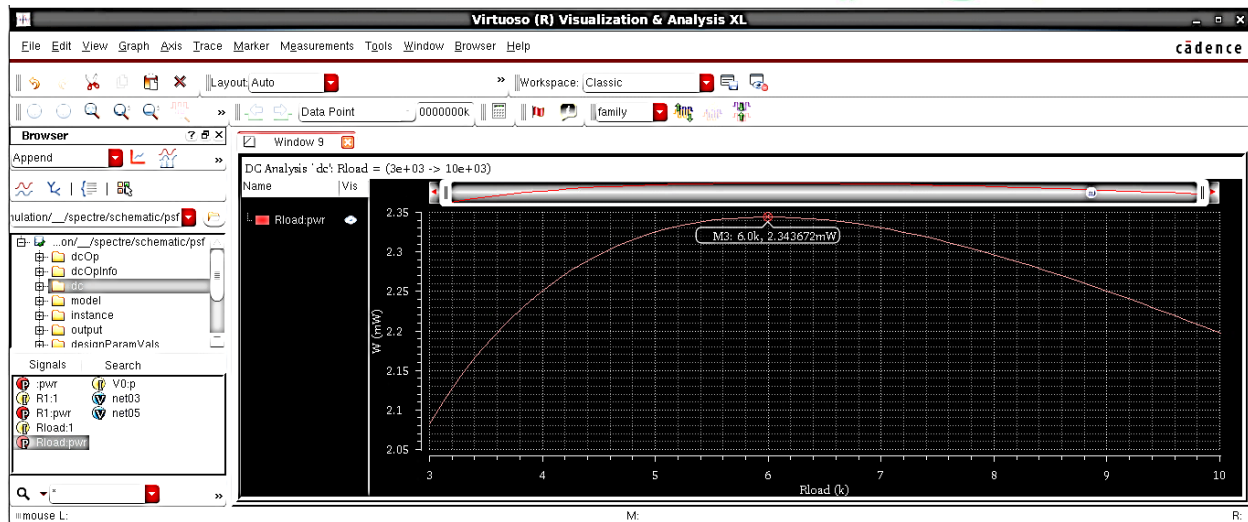

Assignment 2

- Find the Thevenin and Norton equivalent for the following circuit at $R_{load} = 6K$. Also, verify that the maximum power transfer happens when $R_L = R_{th}$.

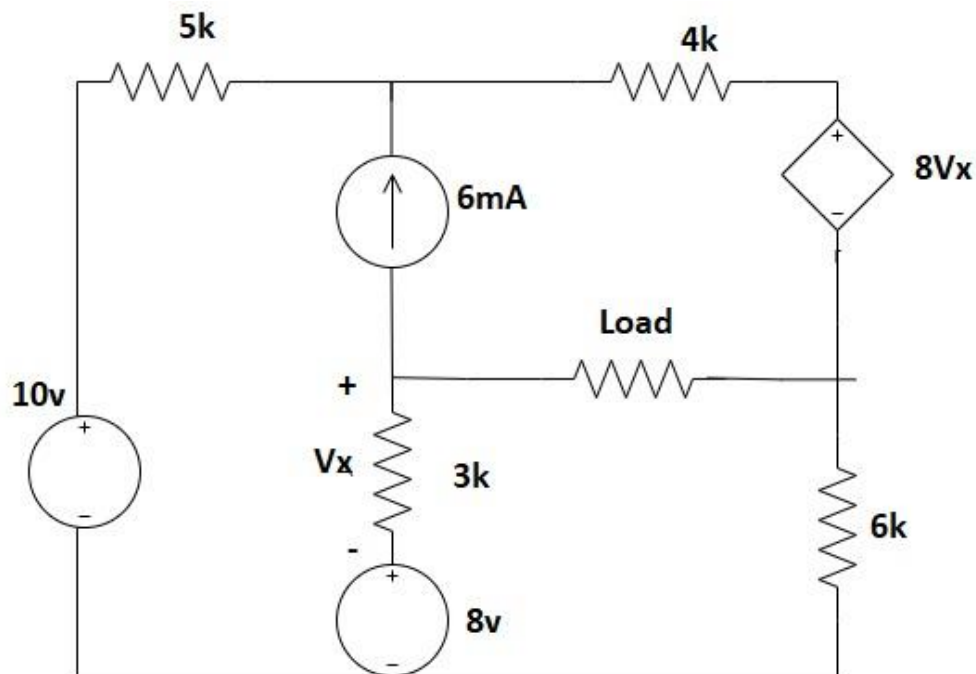


Figure 2 applied circuit



Bonus Questions of Lab 2

- Using Cadence, Find the Thevenin equivalent for the following circuit at $R_L=2\text{ohm}$
- Also, verify that the maximum power transfer happens when $R_L = R_{th}$.

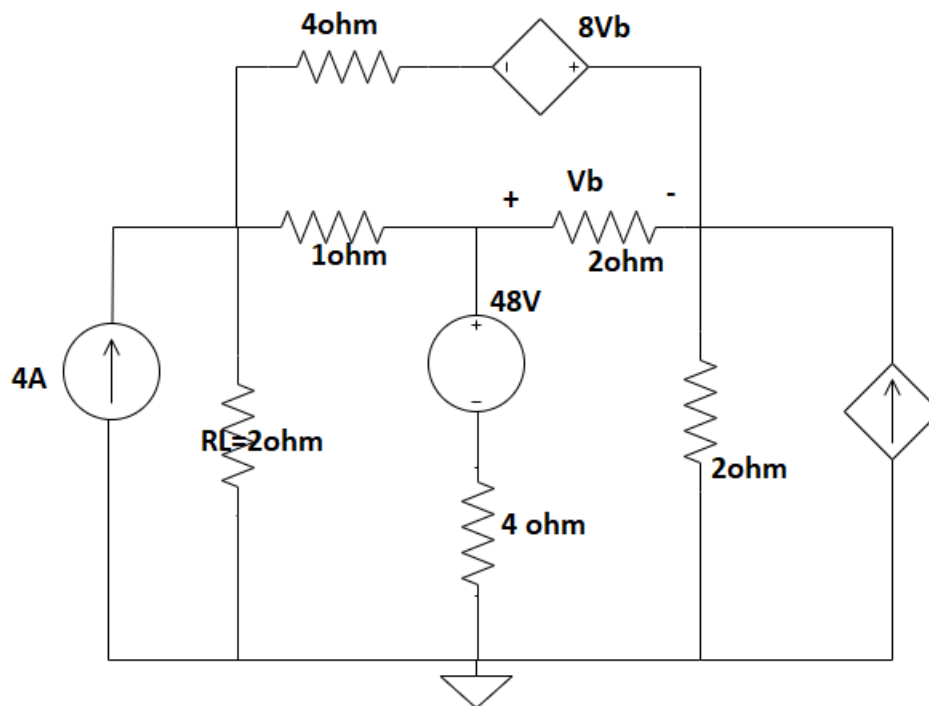


Figure 3 applied circuit 2