

Transient Effect of AC source

Calculate i_L

$$15i_L + 0.01 \frac{di_L}{dt} + \frac{1}{100 \times 10^{-6}} \int_0^t i_L(x) dx = \cos(120\pi t)$$

$$15I_L + 0.01sI_L + 10^4 \frac{I_L}{s} = \frac{1}{s^2 + (120\pi)^2}$$

$$= \frac{100s^2}{[s^2 + 1500s + 10^6][s^2 + (120\pi)^2]}$$


K_1^*

$$K_1 = 0.07357 / 97.89$$


$$K_2 = -1.8345$$

$$1s + 750 + 661.44j$$

$$156.6^\circ$$

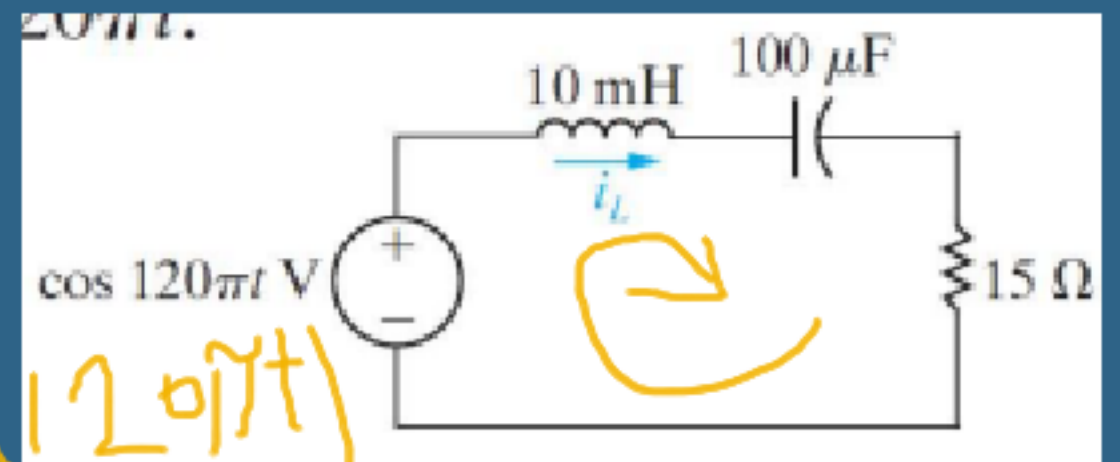

$$(s + 750 - 661.44j)$$

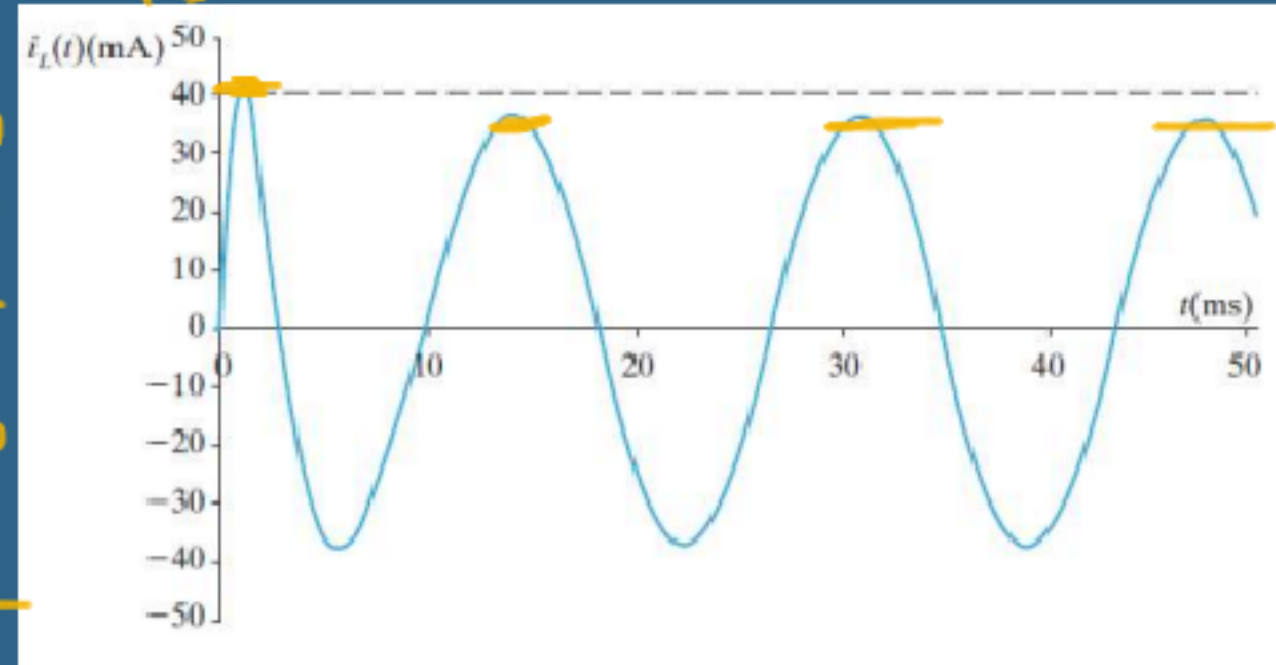

$$\begin{aligned}
 & 147.14 e^{-750t} \cos(661.44t - 97.89^\circ) \\
 & + 36.69 \cos(120.41t + 56.61^\circ)
 \end{aligned}$$

mA

Poles and Zeros

Poles ==> The roots of the denominator polynomial [$F(s)$ becomes infinitely large].

Zeros ==> The roots of the numerator polynomial [$F(s)$ becomes zero].


$$F(s) = \frac{K(s + z_1)(s + z_2) \cdots (s + z_n)}{(s + p_1)(s + p_2) \cdots (s + p_m)}$$

Circuit Elements in the s-Domain

Resistor

$$v = iR \rightarrow$$

$$V = IR$$

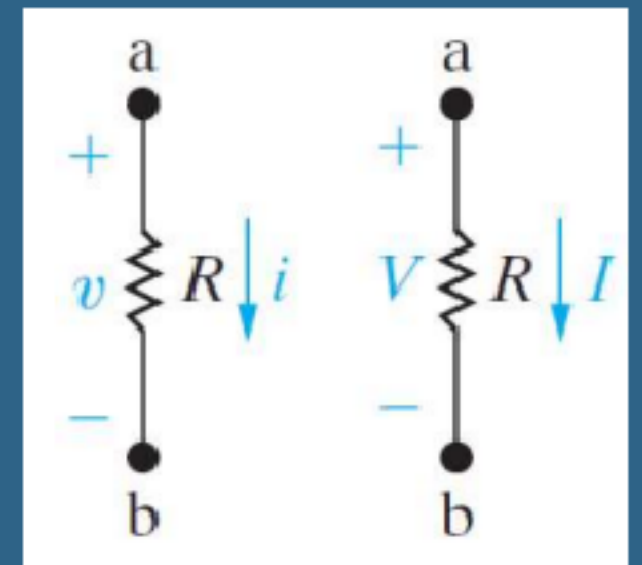

Inductor

$$V = L \frac{di}{dt} \rightarrow V = L \left[sI - \cancel{I(0)} \right]$$


$$V = \underline{LIS - LI_0}$$

$$I = \frac{V + LI_0}{sL}$$

$$= \frac{V}{sL} + \frac{I_0}{s}$$



the initial current
is zero.


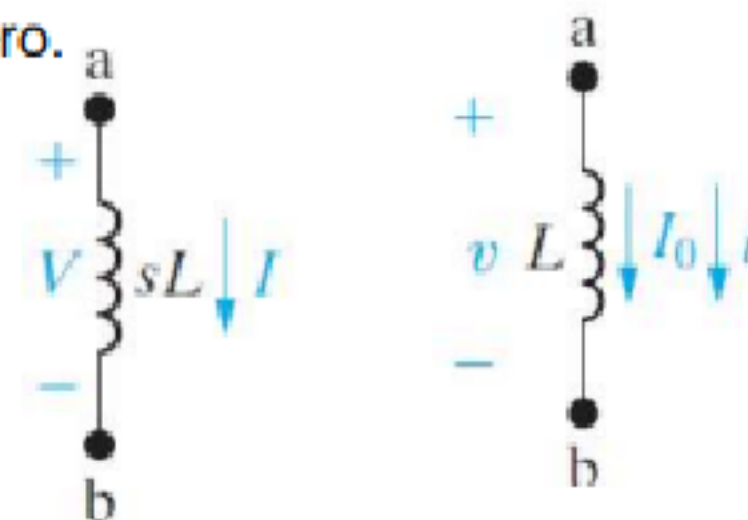


Capacitor

$$I = C \frac{dV}{dt} \rightarrow I = C \frac{dV - V_0}{dt}$$

$$V = \frac{I + CV_0}{Cs} = \frac{I}{Cs} + \frac{V_0}{s}$$


the initial voltage is zero.

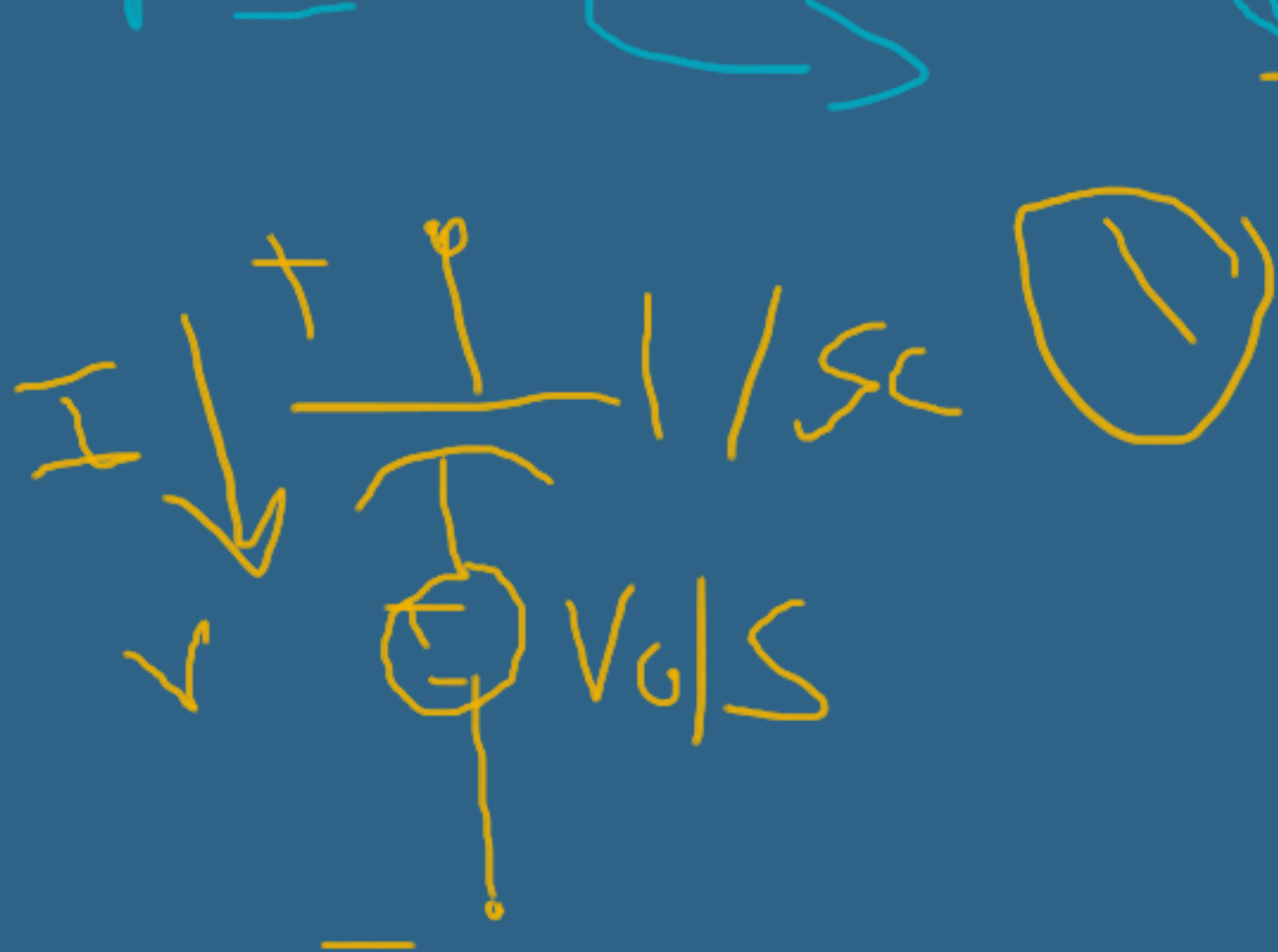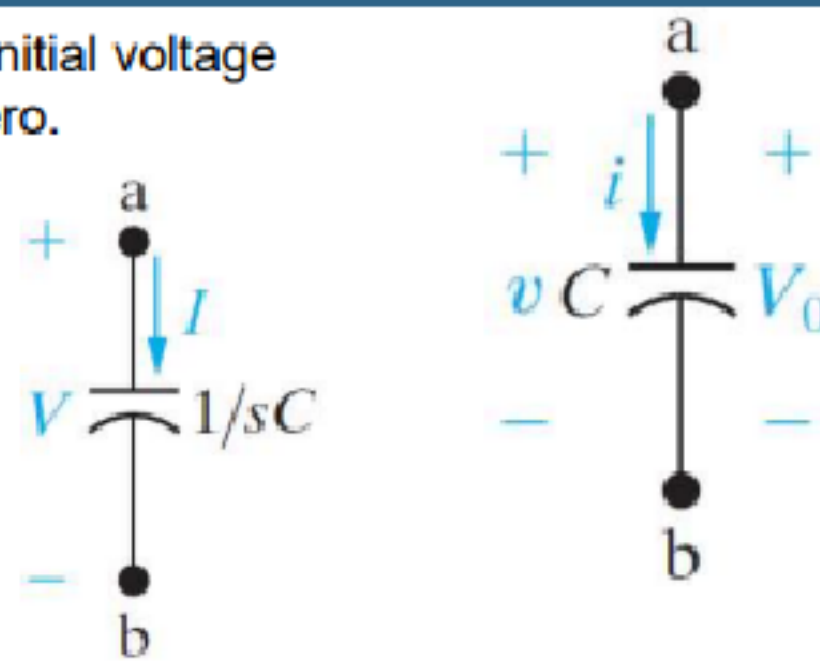

LAPLACE TRANSFORM METHOD

Steps:

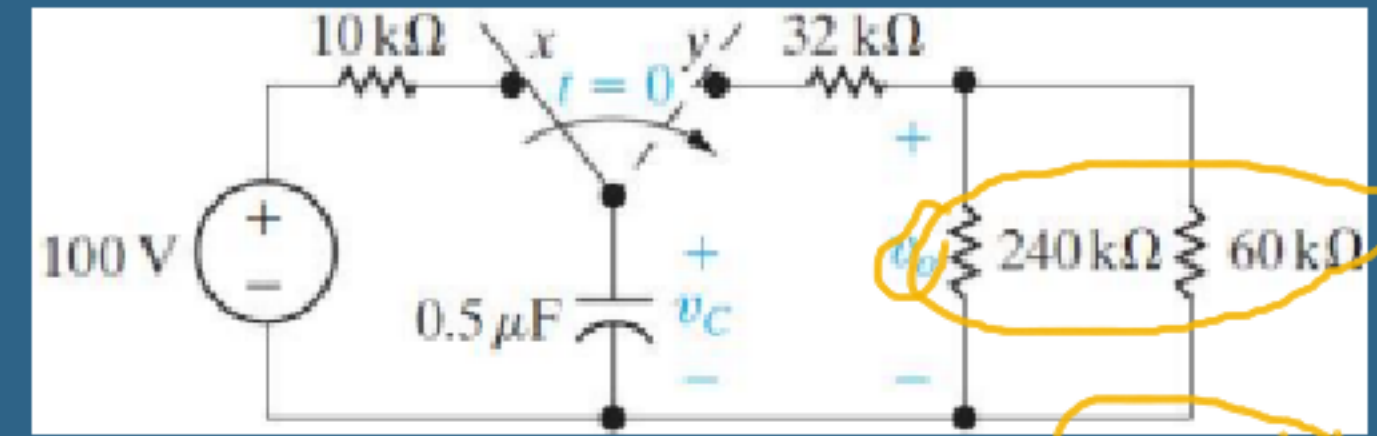- 1- Initial conditions for ind & cap.
- 2- Laplace-transform (Tables) \Rightarrow I, V, and other components.
- 3- Analyze the s-domain circuit using resistive circuit analysis techniques.
- 4- Inverse-Laplace-transform the s-domain voltages and currents using partial fraction expansion.



The Natural Response of an RC Circuit

using first-order circuit analysis techniques.

Use the Laplace Transform to find $v(t)$ for $t > 0+$.

① $V_0 = 100V$

② s-domain $Z_C = \frac{1}{sC}$

$\frac{24 \times 10^6}{s}$

③ $V_0 = \frac{100}{s + 32 + \frac{2 \times 10^6}{s}}$

$\left(\frac{100}{s} \right)$

$\frac{60}{s + 25}$

$\rightarrow 60 e^{-25t} u(t)$




The Step Response of an RLC Circuit

=> the initial current in the inductor is 29 mA

=> the initial voltage across the capacitor is 50 V

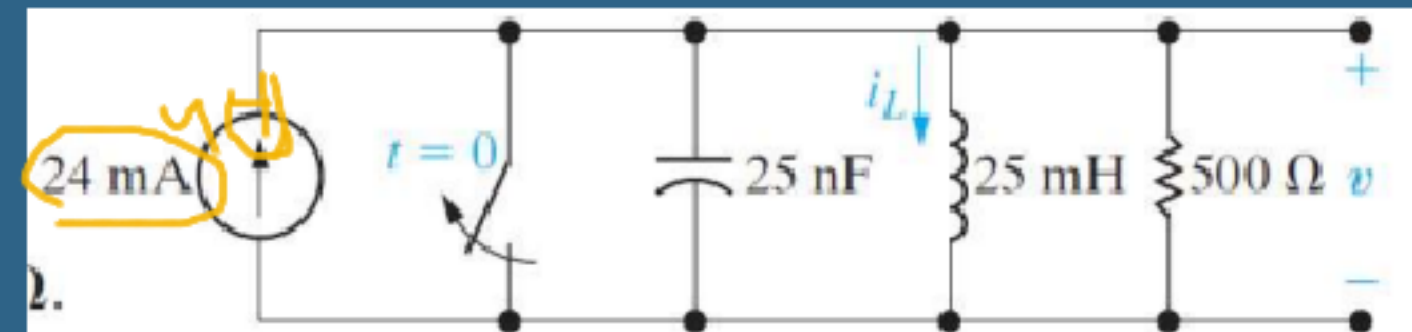Use the Laplace transform method to find $v(t)$ for $t > 0$.



$$Z_C = \frac{1}{sC} = \frac{1}{s \times 25 \times 10^{-9}} = \frac{4 \times 10^6}{s} \Omega$$

$$Z_L = sL = 0.025s$$




$$V = Z_{eq} \left(\frac{-0.24}{s} + 1.25 \times 10^{-6} - \frac{0.024}{s} \right) = \frac{5.5 - 2.04 \times 10^4}{s^2 + 8000s + 16 \times 10^6}$$

$$\frac{1}{Z_{eq}} = \frac{1}{Z_C} + \frac{1}{Z_L} + \frac{1}{Z_R} \quad Z_{eq} = \checkmark$$

$$v(t) = \mathcal{L}^{-1} \left\{ \frac{-2.2 \times 10^6}{(s + 40,000)^2} + \frac{50}{(s + 40,000)} \right\}$$

$$= (-2.2 \times 10^6 t e^{-40,000t} + 50 e^{-40,000t}) u(t) \text{ V.}$$

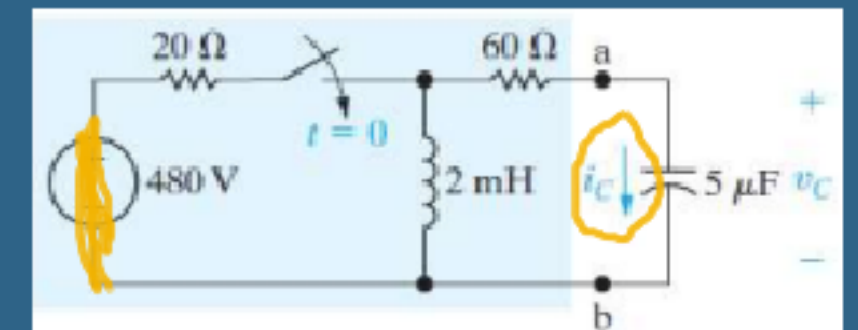
Creating a Thévenin Equivalent in the s Domain



$$\begin{aligned}
 1) \quad Z_L &= sL = 500 \Omega \\
 2) \quad Z_C &= \frac{1}{sC} = \frac{2 \times 10^5}{s} \Omega \\
 V_{Th} &= \frac{(480/s)(0.0025)}{20 + 0.0025s} \times \frac{48}{5} \\
 Z_{Th} &= (20 || 2mH) + 60 \\
 &= \frac{20(5 + 7500)}{s + 10^4}
 \end{aligned}$$

$$i_C = (-30,000te^{-5000t} + 6e^{-5000t})u(t) \text{ A.}$$
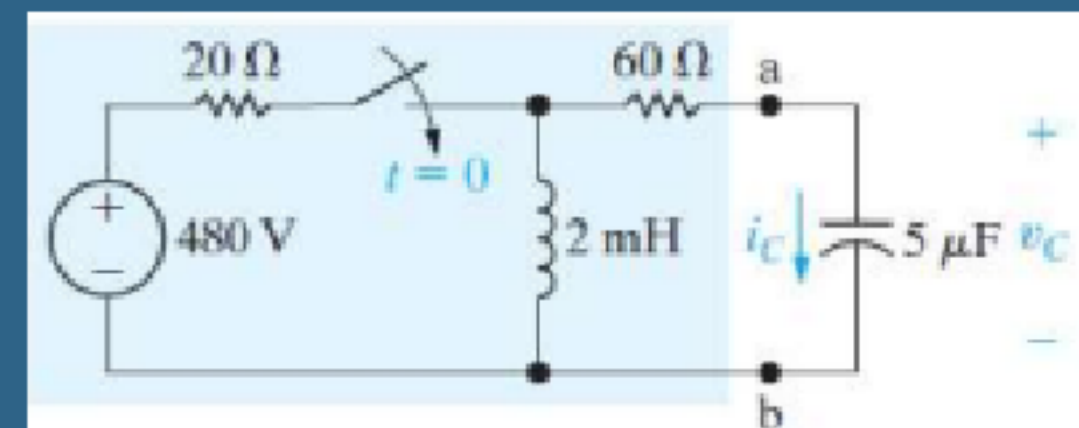
$$v_C = 12 \times 10^5 te^{-5000t} u(t) \text{ V.}$$



$$\begin{aligned}
 & \text{Handwritten notes: } V_{th} \\
 & \text{Circuit equation for } t > 0: \\
 & \frac{480}{s + 10^4} \\
 & i_C = \frac{80(s + 7500)}{s + 10^4} + \frac{2 \times 10^5}{s} \\
 & = \frac{6s}{(s + 5000)^2}
 \end{aligned}$$



$$\lim_{s \rightarrow \infty} sI(s) \equiv \lim_{t \rightarrow \infty} i(t) \rightarrow \text{initial current}$$

$$\lim_{s \rightarrow \infty} sI(s) = \lim_{s \rightarrow \infty} \frac{6s^2 / s^2}{\left(\frac{s}{s} + \frac{5000}{s}\right)^2} = \lim_{s \rightarrow \infty} \frac{6}{\left(1 + \frac{5000}{s}\right)^2}$$

$$= \boxed{6}$$

$$\boxed{0}$$

$$\lim_{s \rightarrow 0} sI(s) \equiv \lim_{t \rightarrow \infty} i(t) \Rightarrow \text{final current}$$