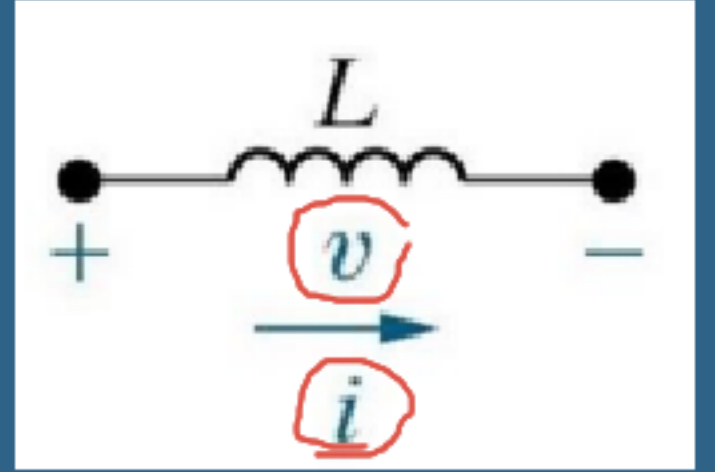



Inductance

$$V \propto \frac{di}{dt} \rightarrow V = L \frac{di}{dt}$$




- The voltage across the terminals of an inductor is proportional to the time rate of change of the current in the inductor.
- First, if the current is constant, the voltage across the ideal inductor is zero. Thus, the inductor behaves as a ~~short circuit~~ in the presence of a constant, or dc current.
- Second, current cannot change instantaneously in an inductor; that is, the current cannot change by a finite amount in zero time.
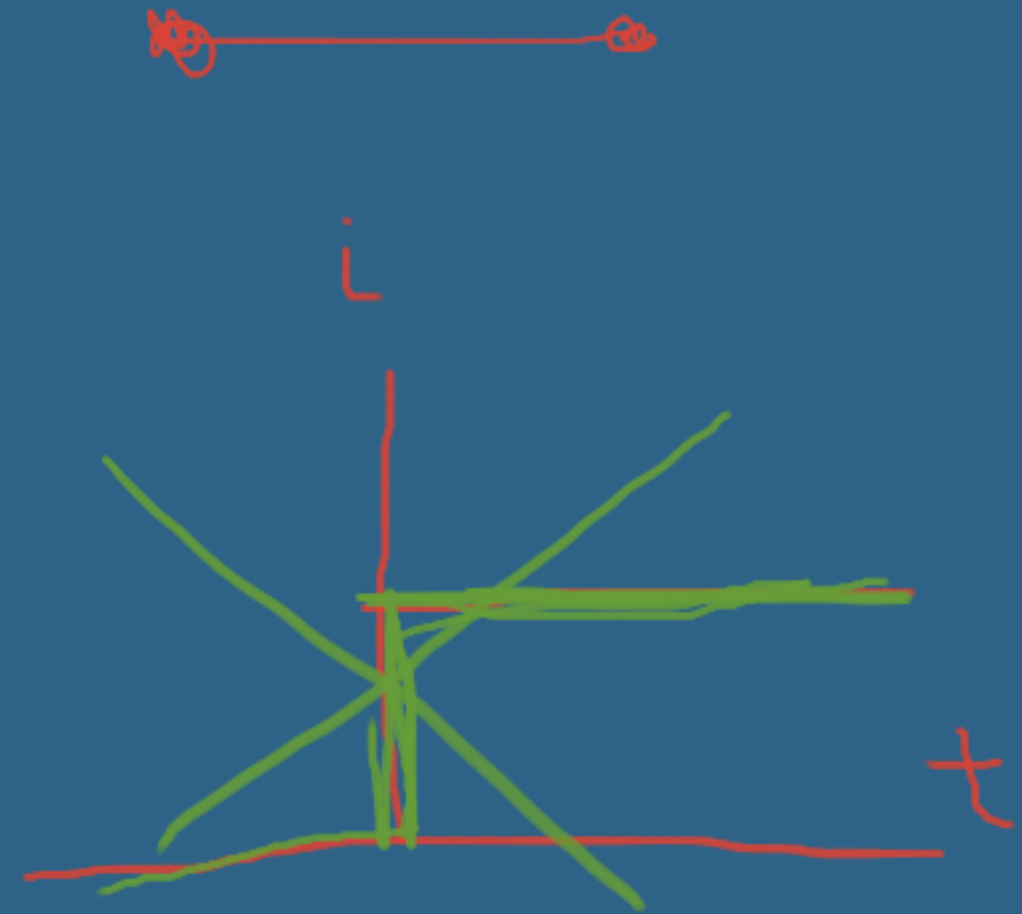
$$i = \text{constant} \rightarrow V = 0$$



Voltage Across an Inductor


a) Sketch the current waveform.

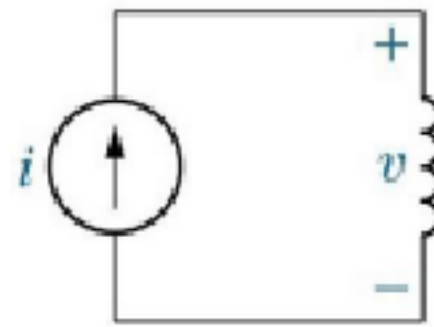

$$i = 0, \quad t < 0$$

$$t < 0$$
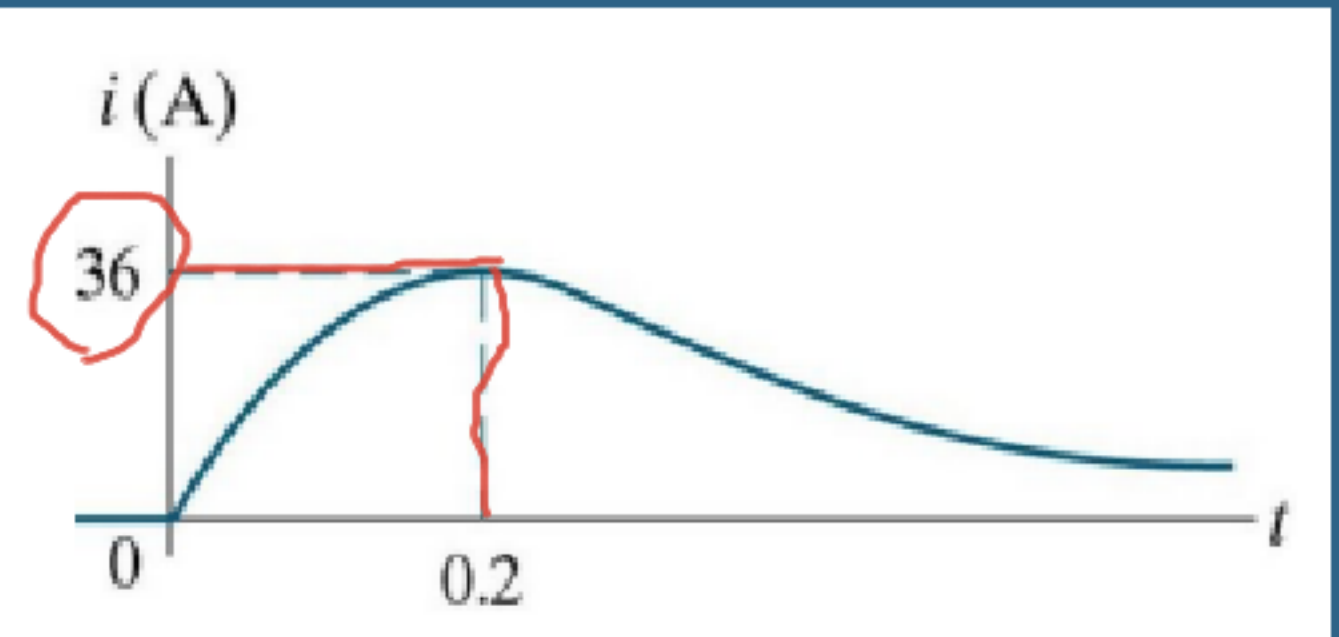
$$i = 10te^{-5t} \text{ A}, \quad t > 0$$




a) At what instant of time is the current maximum?

$$\frac{di}{dt} = 0 \rightarrow (10t)(-5)e^{-5t} + e^{-5t}(10) = 0 \rightarrow t = 0.2 \text{ s}$$


- Express the voltage across the terminals of the 100 mH inductor as a function of time.
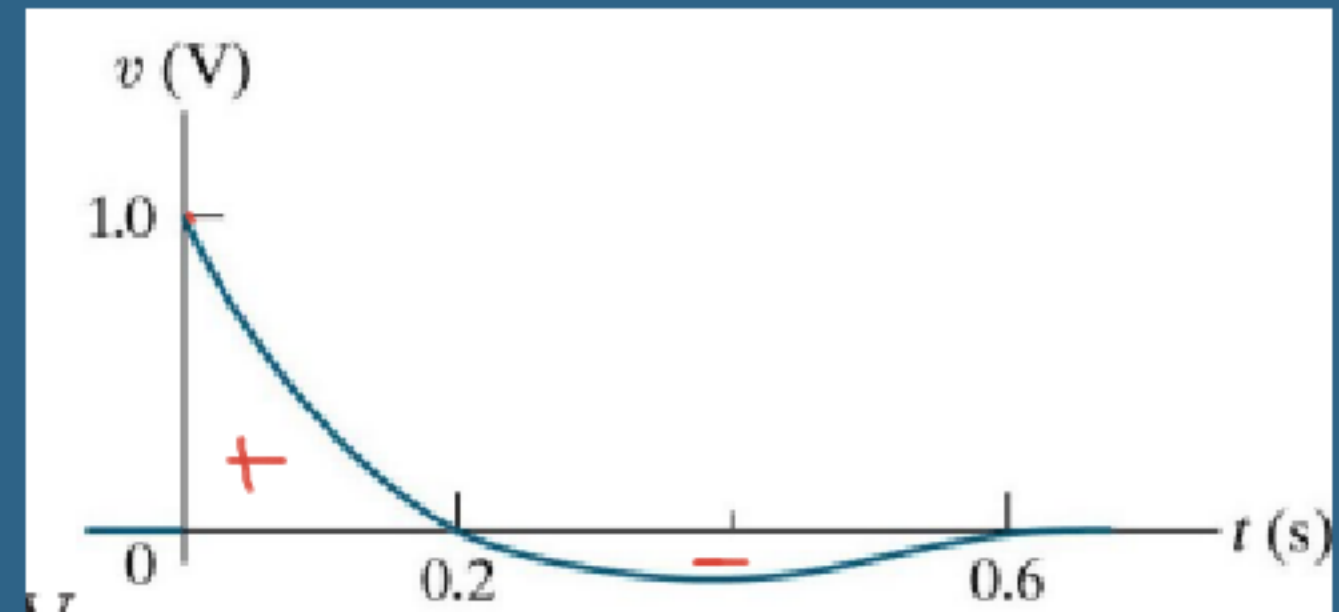
$$v = L \frac{di}{dt} = 0.1 \left[-5e^{-5t}(10t) + e^{-5t}(10) \right] = 0.1 e^{-5t} (10 - 50t)$$



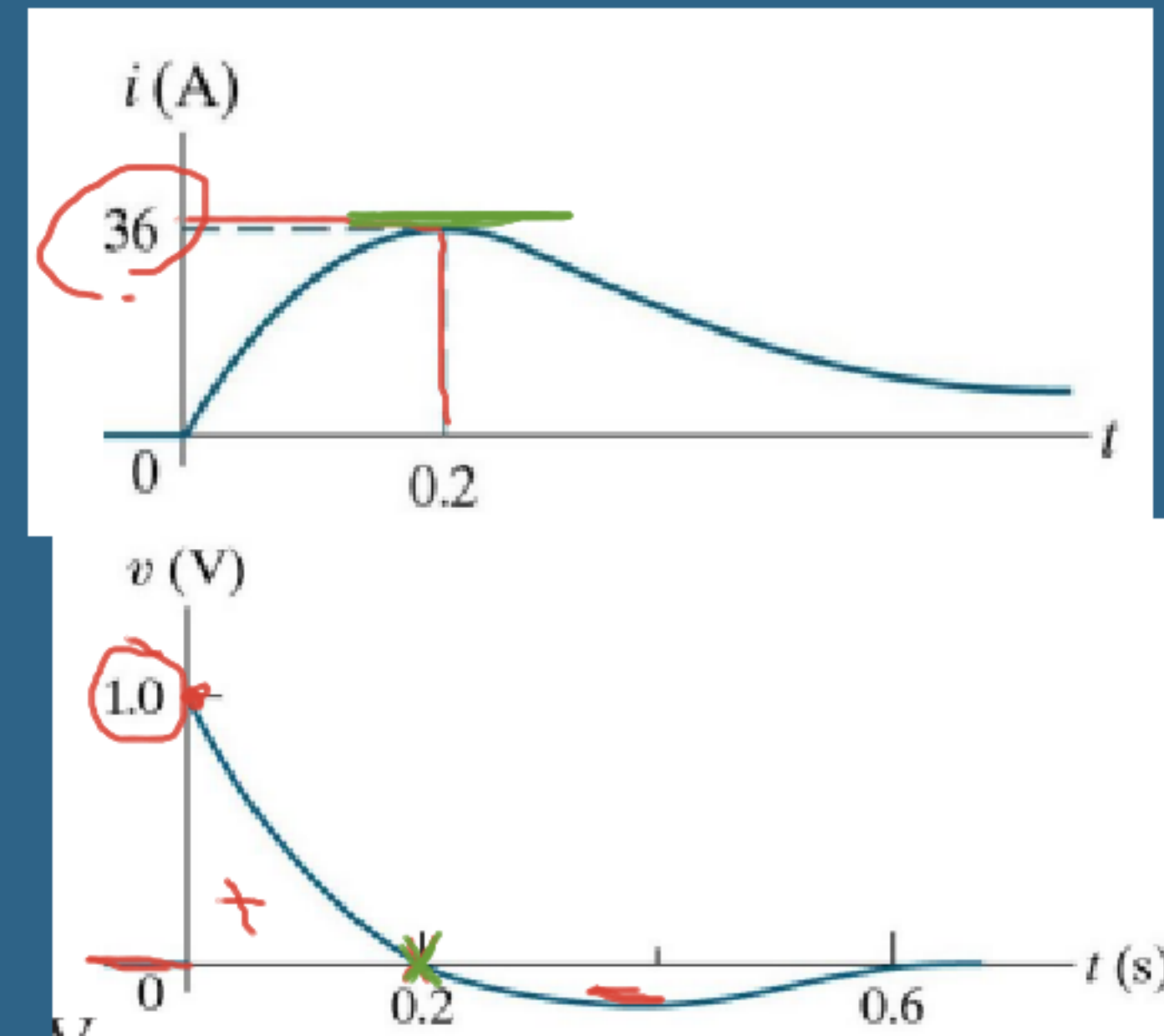e) Are the voltage and the current at a maximum at the same time?

$$V \propto \frac{di}{dt} \Rightarrow V \propto i \text{ not } \propto i \quad \text{No}$$




f) At what instant of time does the voltage change polarity?

@ 0.2 s

g) Is there ever an instantaneous change in voltage across the inductor? If so, at what time?



Yes @ $t = 0$ but not

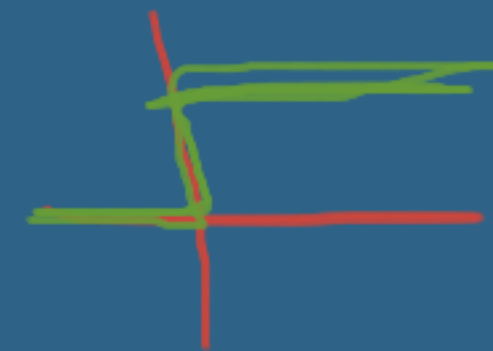

Current across an inductor

Assume an ideal dc current source connected to an inductor at $t=0$,
current cannot change instantaneously across an inductor, where
does the current go ?

HYACTUAL

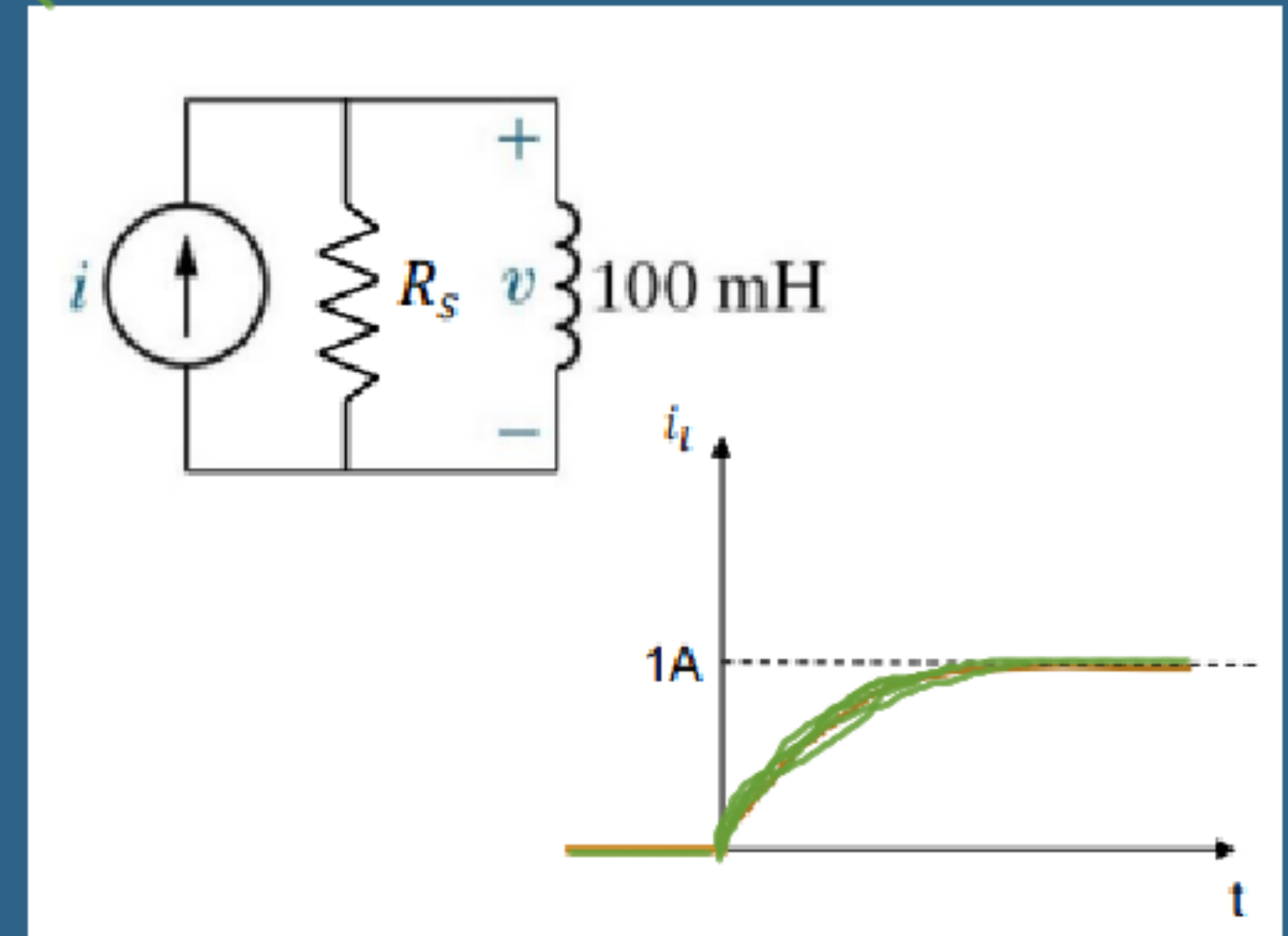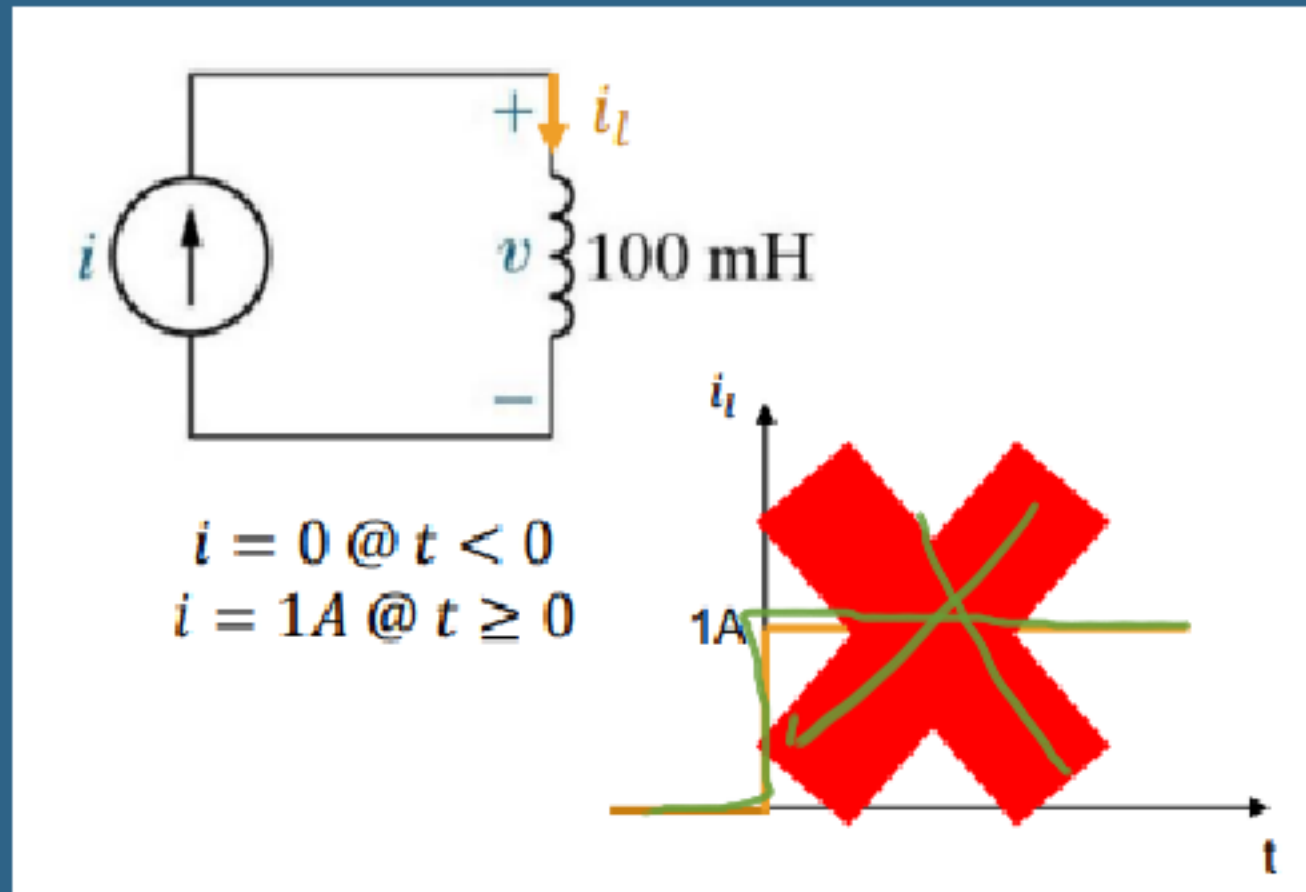

Current in an inductance

To find i as a function of v :

$$v = L di/dt$$

$$v = L \frac{di}{dt} \quad \text{(* } dt \text{)}$$

$$\int v dt = \int L di$$

$$\int_{i_0}^{i_f} di = \frac{1}{L} \int_{t_0}^{t_f} v dt$$

$$i_f - i_0 = \frac{1}{L} \int_{t_0}^{t_f} v dt$$

$$i = \frac{1}{L} \int_{t_0}^t v dt + i(t_0)$$

$$i = \frac{1}{L} \int_0^t v dt$$



$$i(t) = \frac{1}{L} \int_{t_0}^t v d\tau + i(t_0),$$

Most of the time $t_0 = 0$

Current in an Inductor

$$v(t) = 20te^{-10t} \text{ V}$$

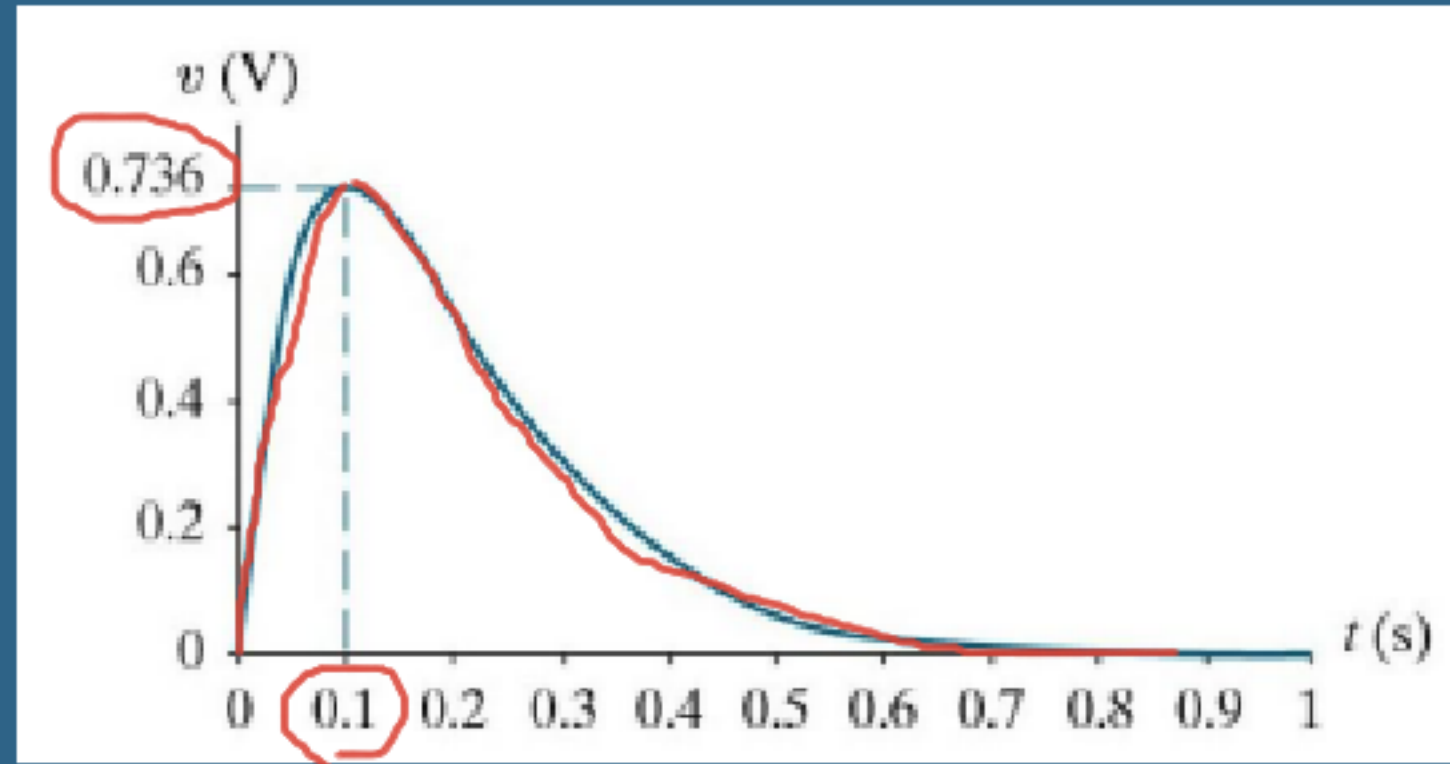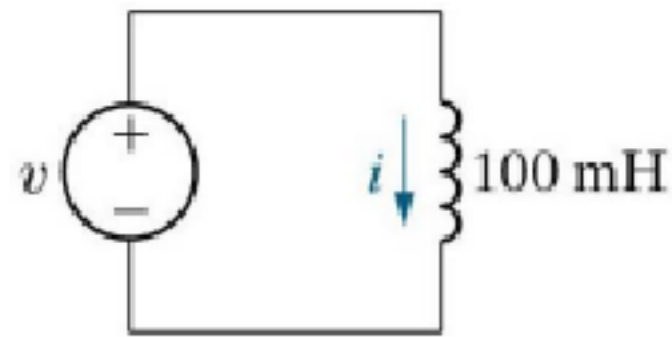for $t > 0$. Also assume $i = 0$ for $t \leq 0$.



Get the i equation, then draw it:

$$i = \frac{1}{L} \int v dt + K e^{-10t}$$

100 mH


$$20te^{-10t}$$

$$2(1 - 10te^{-10t} - e^{-10t}) \text{ A}$$

$t > 0$

$$20t e^{-10t}$$
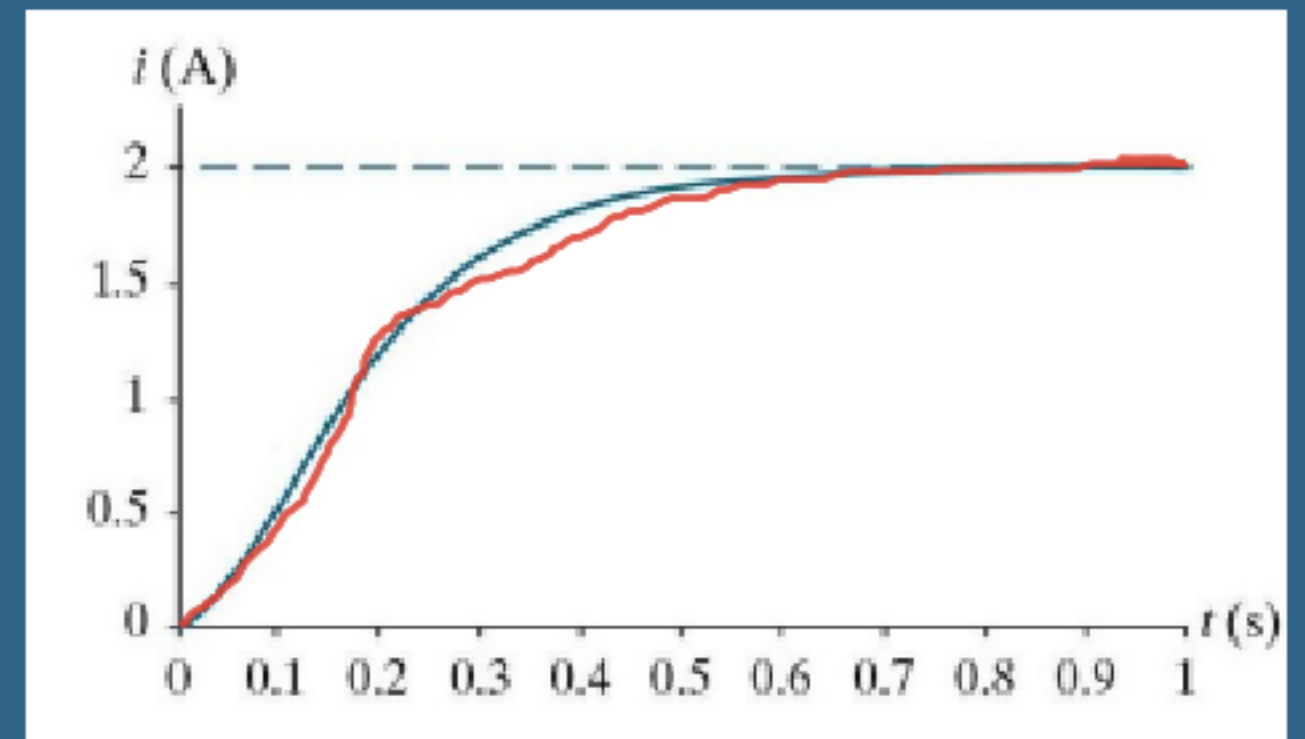
$$20 \left(\frac{-1}{10} \right) e^{-10t} - \frac{1}{10} e^{-10t}$$



Power and Energy in the Inductor

Power

$$p = v i = L i \frac{di}{dt} = v \left[\frac{1}{L} \int_0^t v dt + i_0 \right] = \frac{w}{t}$$

$$w = \frac{1}{2} L i^2$$

#

$$v = L \frac{di}{dt} = L (-5) e^{-5t}$$

$$p = v i$$

