

## **Lab 3 Analog**

**Name: Karim Mahmoud Kamal**

**AUC ID: V23010174**


**Section:16**

**Eng. Mariam Mamdoh**


## A- DC Analysis Passive components:

### I. Experiment:


	$VC1$	$VR1$ (right)	$VR2$ (top)	$VL1$
Value	2v	2v	6v	0v
	$IC1$	$IR1$ (right)	$IR2$ (top)	$IL1$
Value	0	2m	2m	-2m

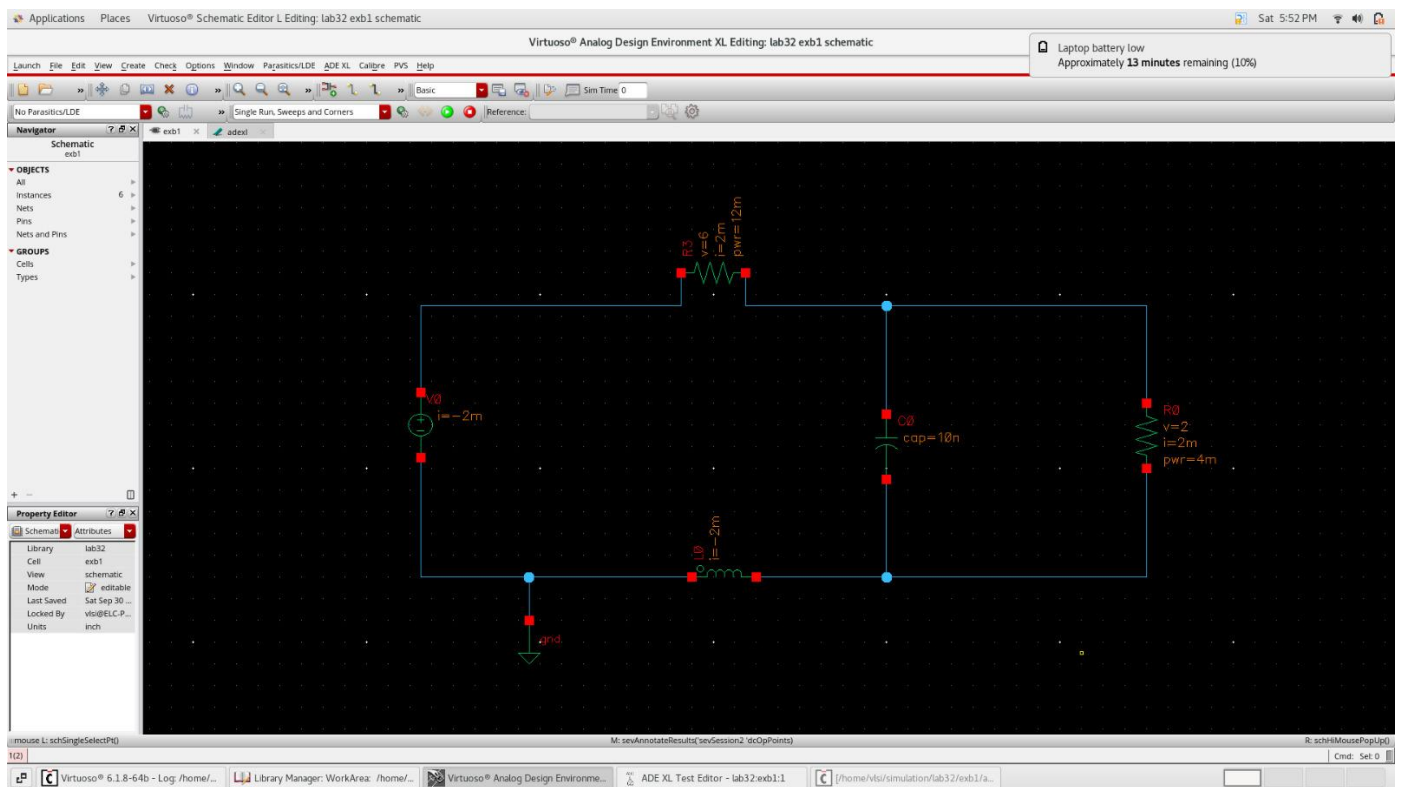


## B- Transient RLC analysis:

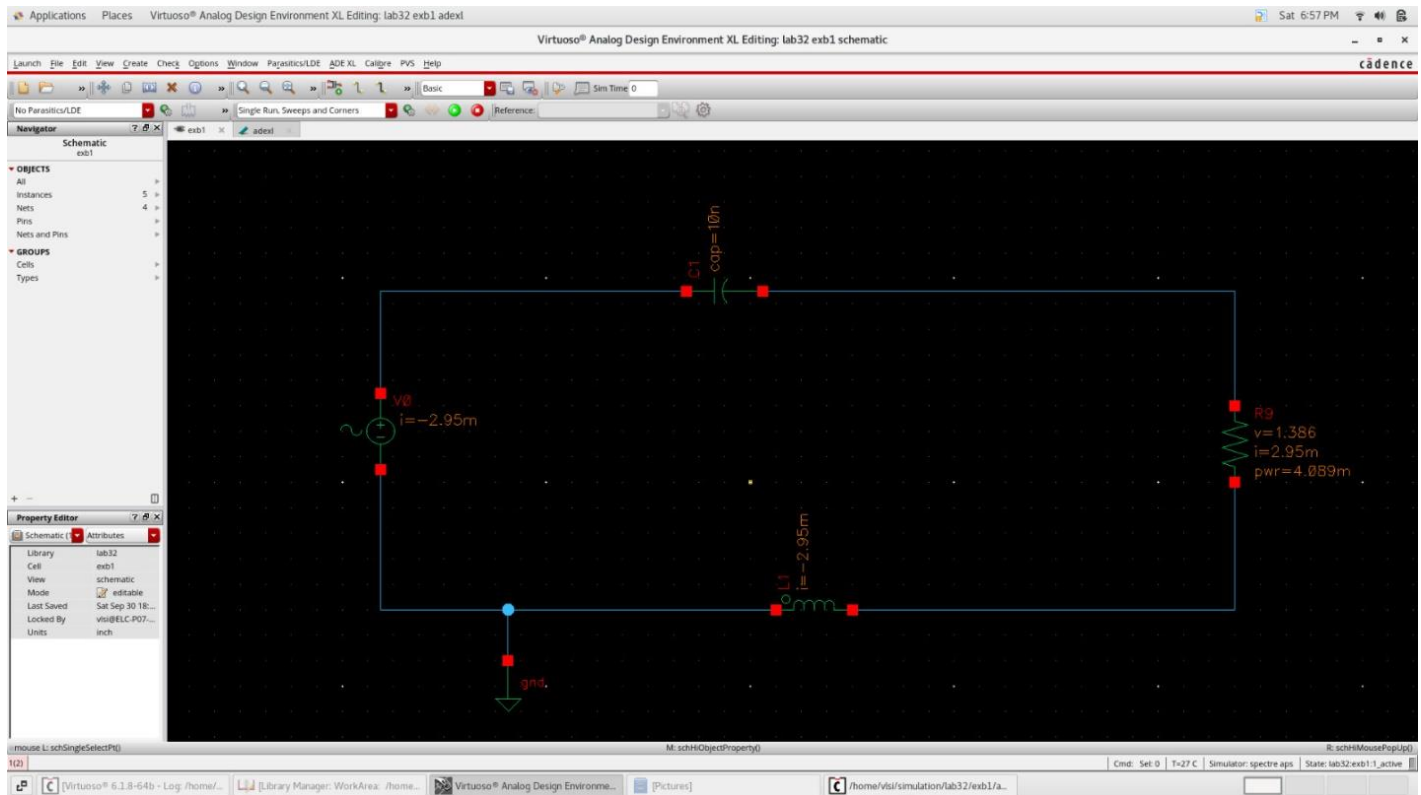

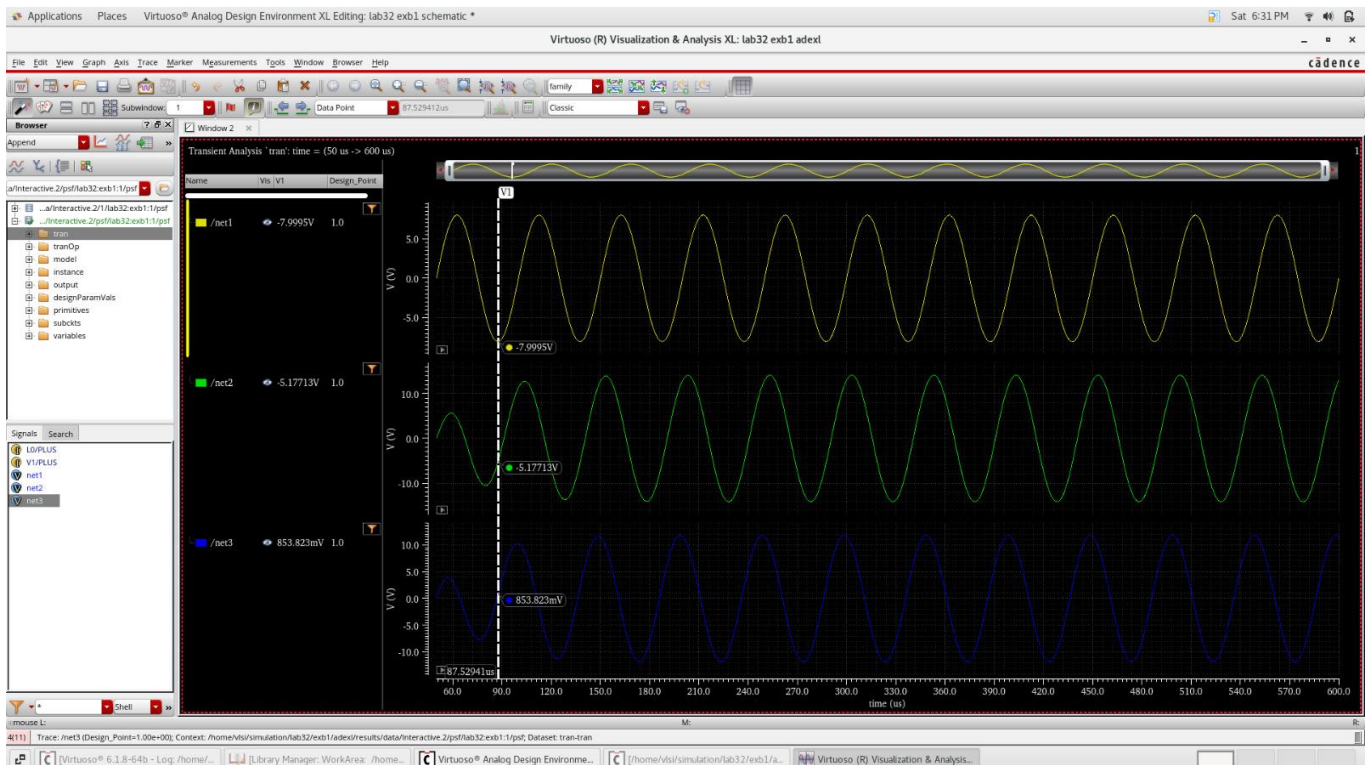
We can see that signals of V1 and V2 are phase-shifted from the input signal.




## C- Transients in RC circuit:

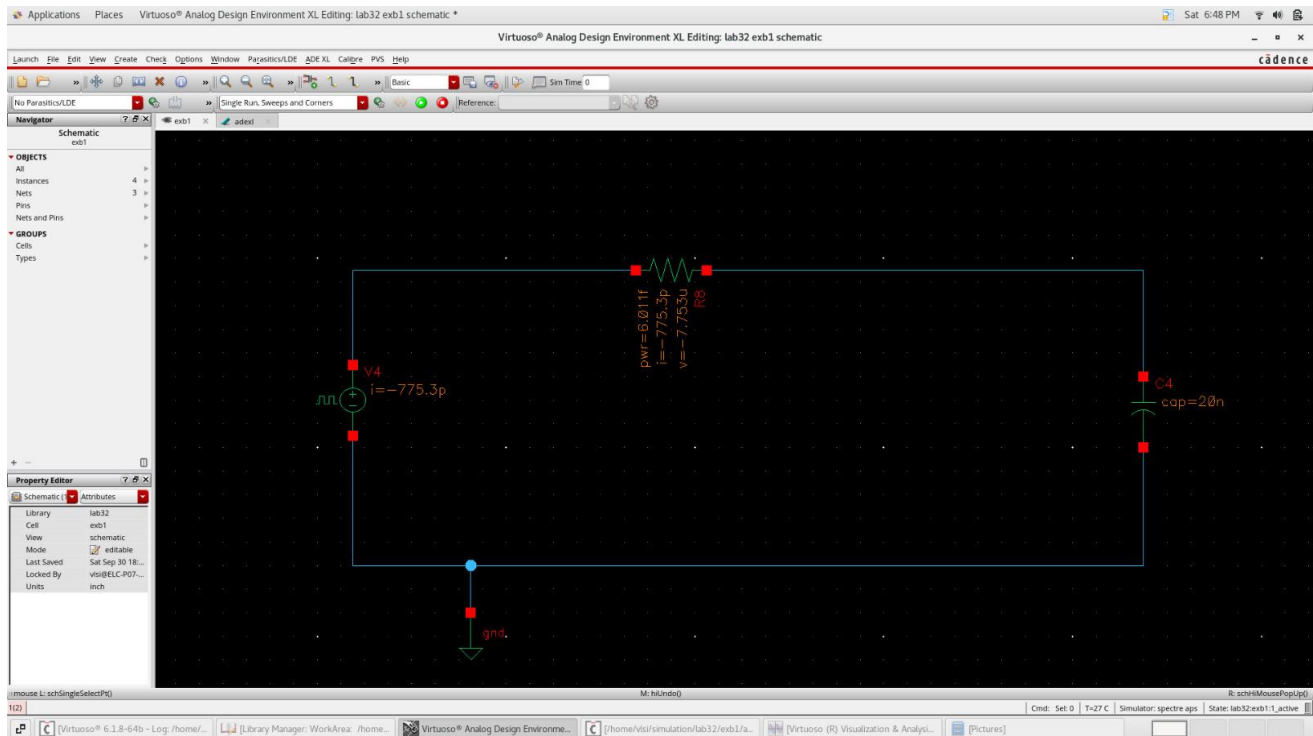

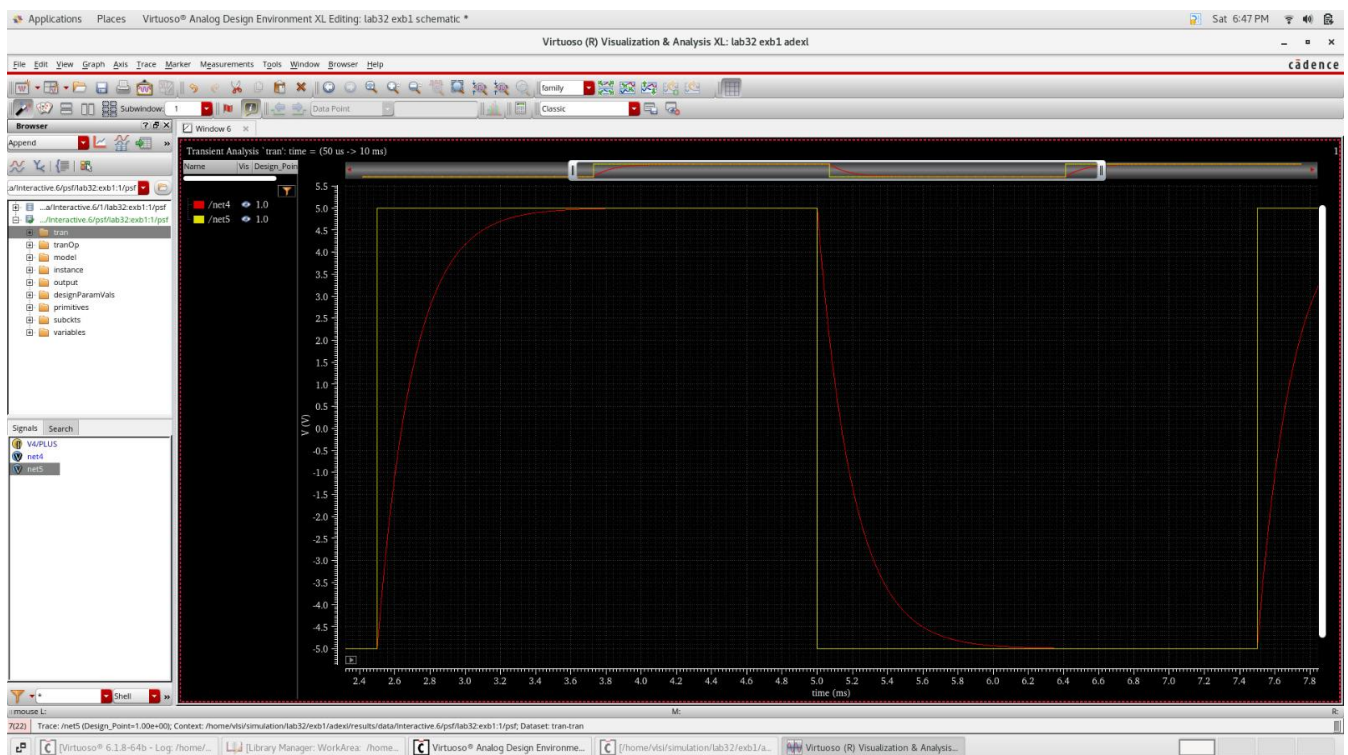
You can expect the time required analytically( $R \cdot C$ ).



## D- Transients Analysis in RL circuit:

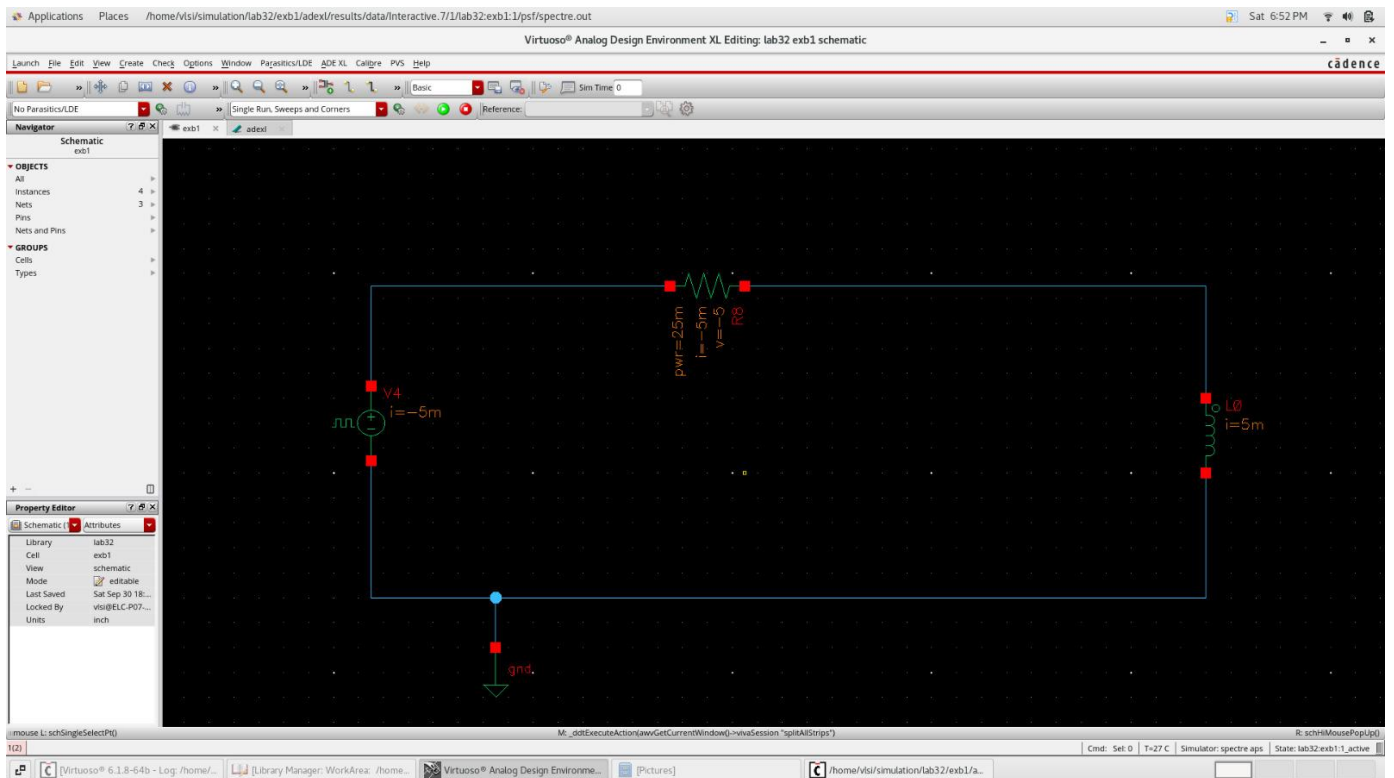


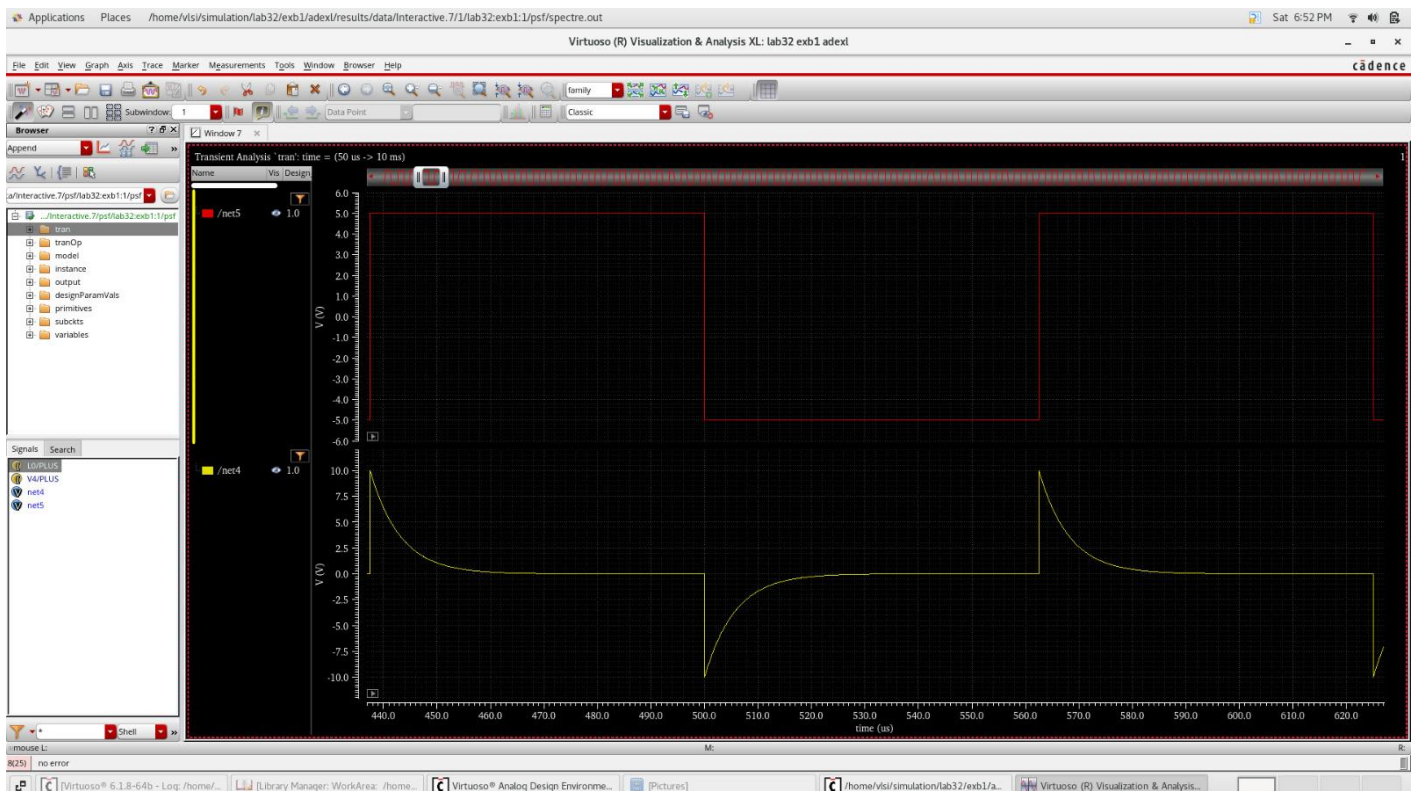**$L/R = 5.5856$  micro and theoretical  $= 5.6$  micro**






## Assignment 3

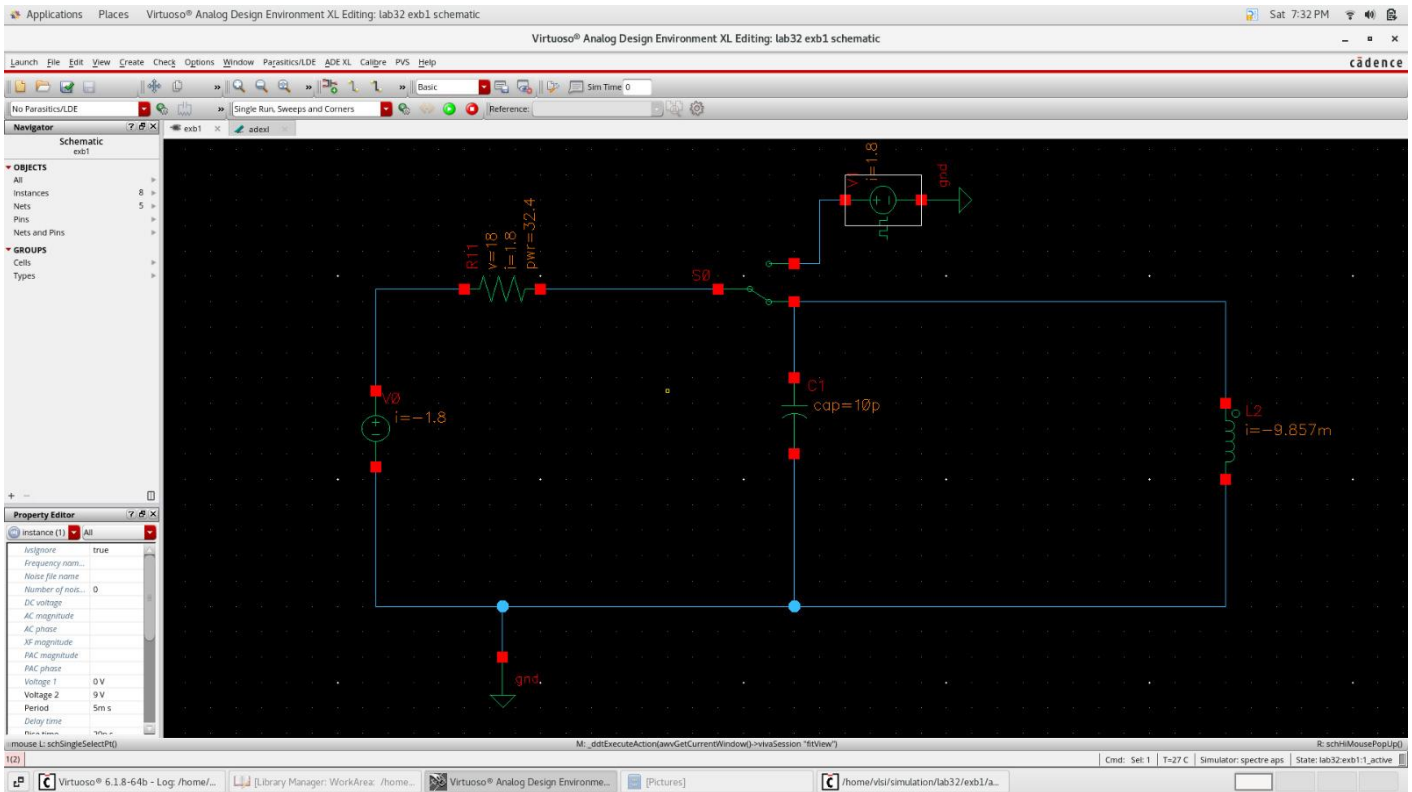


We increase the value of inductance (  $L$  ) and make the capacitance constant value ➔ We note that while we increase the  $L$  value the current reaches the zero value more later as the damping ration increases ( more oscillations starting from  $t=0$  till current reaches zero or steady state ).

L=40mH

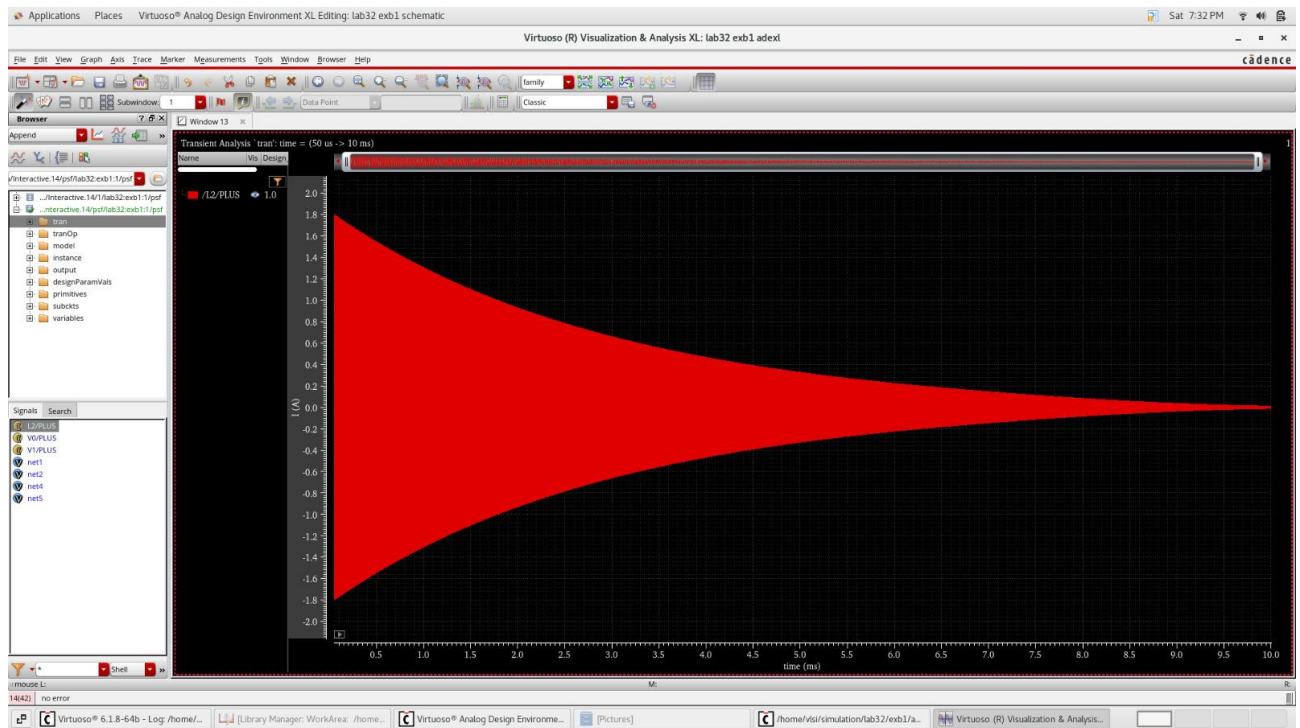

L=50mH

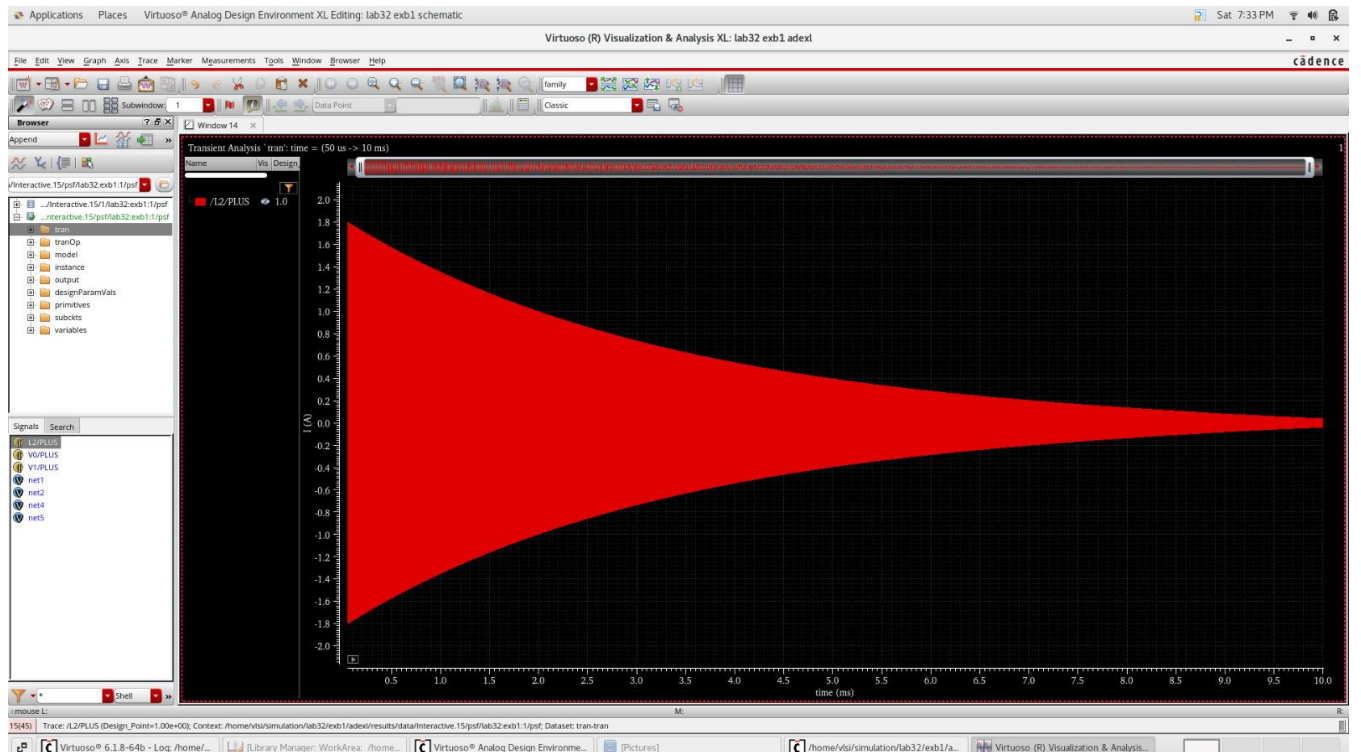

L=60mH

