


The Node-Voltage Method

1- a node as a reference node

2- We apply KCL at the nodes that results in simultaneous equations to solve for the voltages.

=> The sum of the three currents leaving node 1 must equal zero.

$$\sum i_j = 0$$

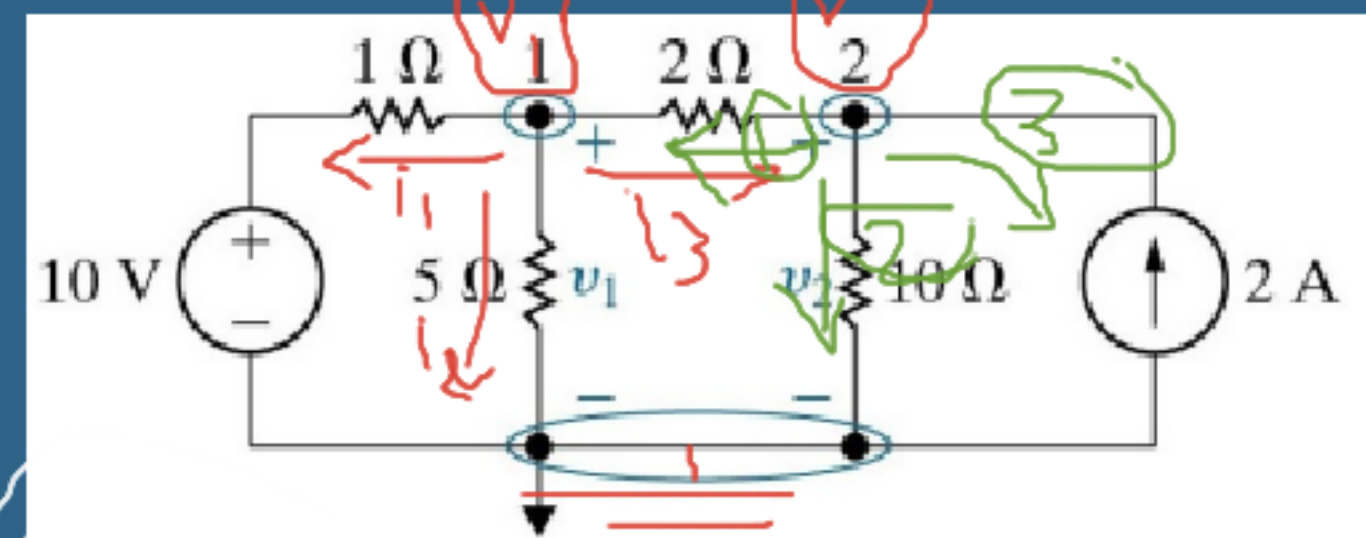

1

$$i_1 + i_2 + i_3 = 0$$

$$\frac{v_1 - 10}{1} + \frac{v_1 - 0}{5} + \frac{v_1 - v_2}{2} = 0$$

$$10v_1 - 100 + 2v_1 + 5v_1 - 5v_2 = 0 \quad (1)$$

2

$$\frac{v_2 - v_1}{2} + \frac{v_2 - 0}{10} + (-2) = 0$$


$$v_1 = 9.1V$$

$$v_2 = 10.92V$$

The Mesh-Current Method

KVL

$$-100 + 4I_1 + 10(I_1 - I_2) = 0$$

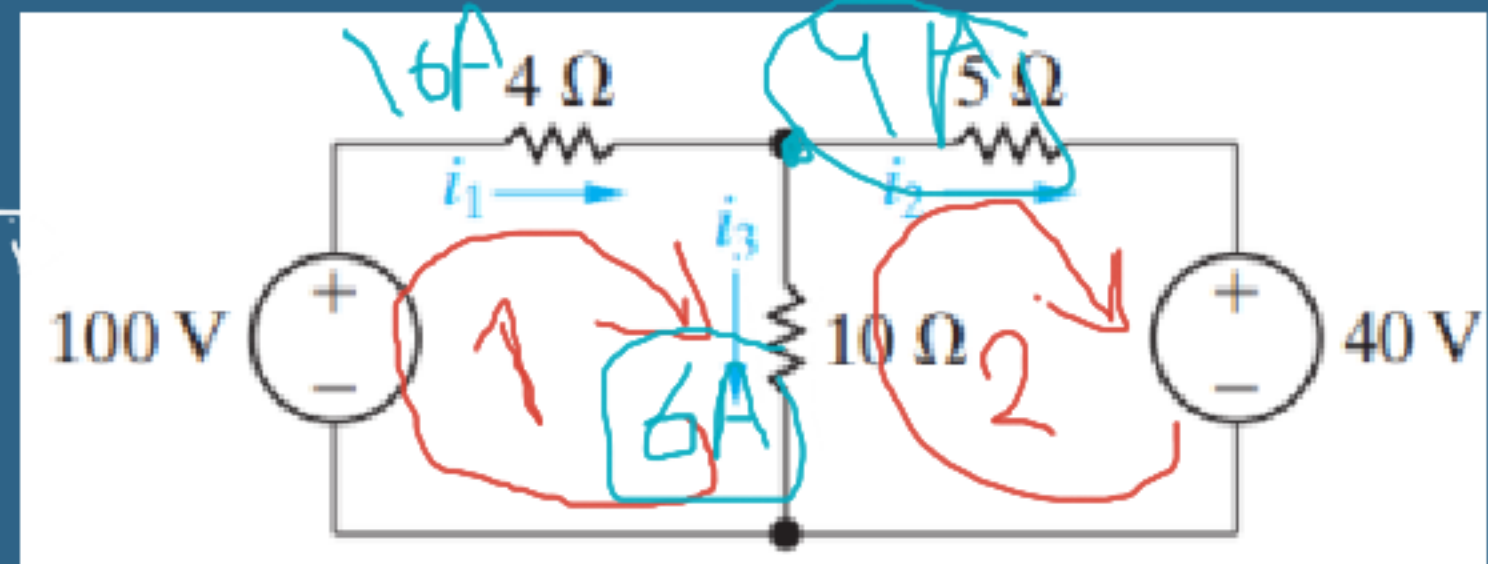

$$+40 + 5I_2 + 10(I_2 - I_1) = 0$$

$$I_1 = 10A$$

$$I_2 = 4A$$

1. **Identify the meshes** with curved directed arrows that follow the perimeter of each mesh.
2. **Label the mesh currents** for each mesh.
3. **Write the KVL equations** for each mesh.
4. **Solve the KVL equations** to find the mesh current values.
5. **Solve the circuit** using mesh currents from Step 4 to find component currents, voltages, and power values.

The Mesh-Current Method

④

$$-50 + 5(I_1 - I_3) + 20(I_1 - I_2) = 0$$


②

$$+15i_\phi + 20(I_2 - I_1) + 4(I_2 - I_3) = 0$$

③

$$1I_3 + 4(I_3 - I_2) + 5(I_3 - I_1) = 0$$

$$i_\phi = I_1 - I_2$$

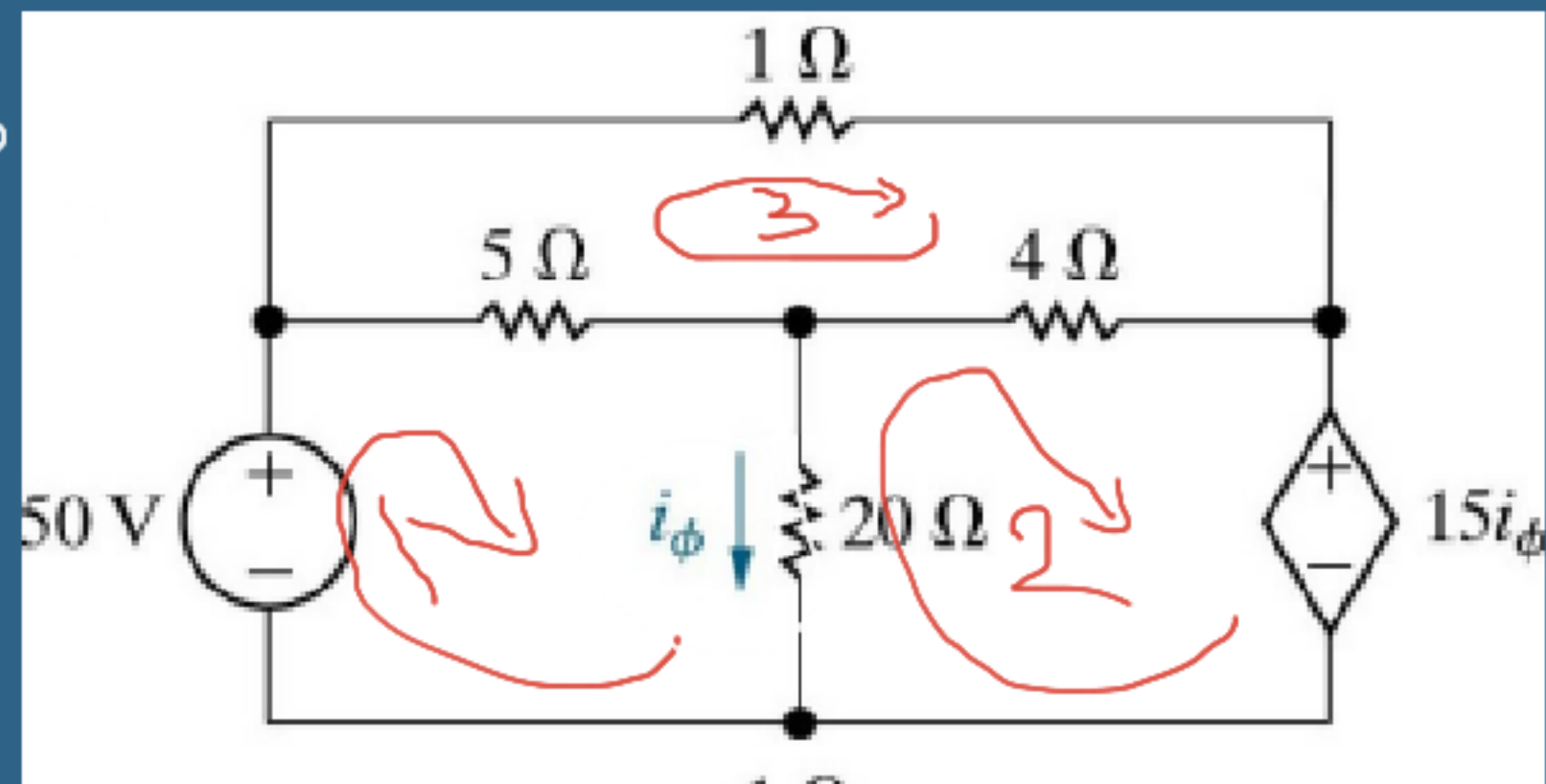

The Mesh-Current Method


$$\textcircled{1} \quad -50 + 5i_1 + 10(i_1 - i_2) = 0$$

$$\textcircled{2} \quad 10(i_2 - i_1) + 40(i_2 - i_3) = 0$$

$$i_3 = -3 \text{ A}$$


$$i_1 = 2 \text{ A}$$

$$i_2 = -2 \text{ A}$$

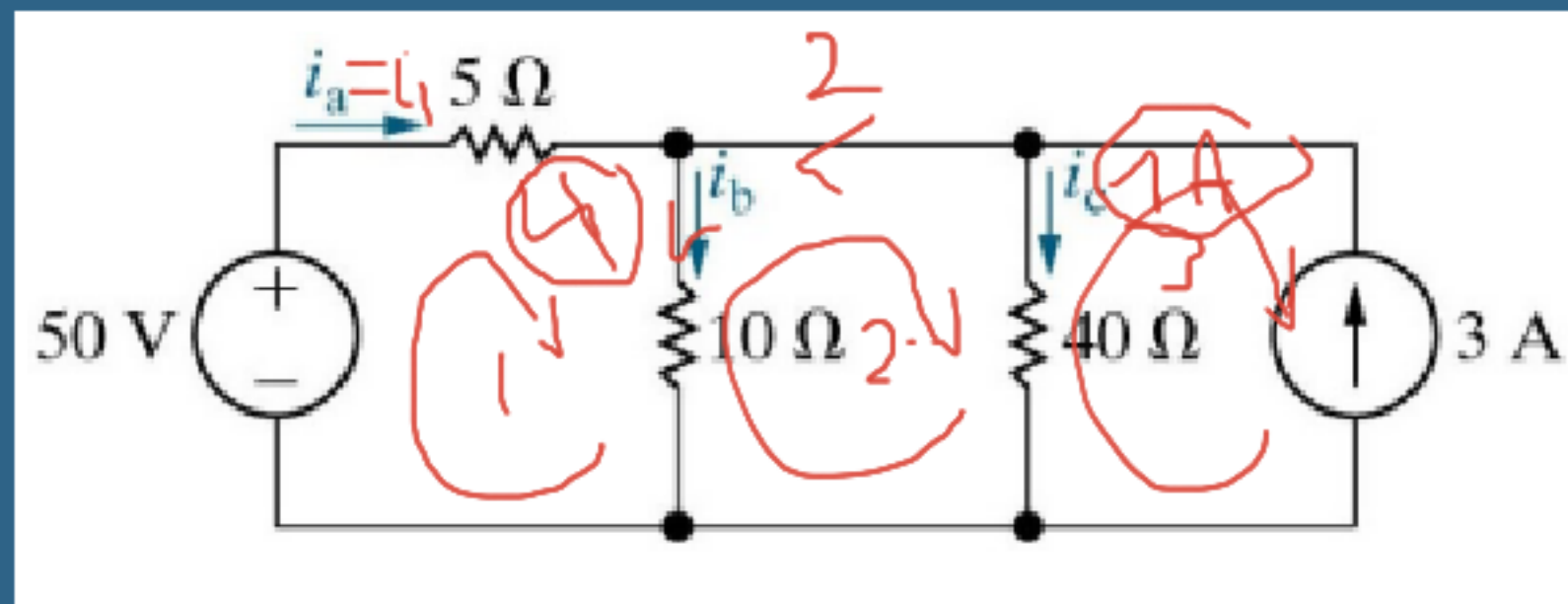

supermesh

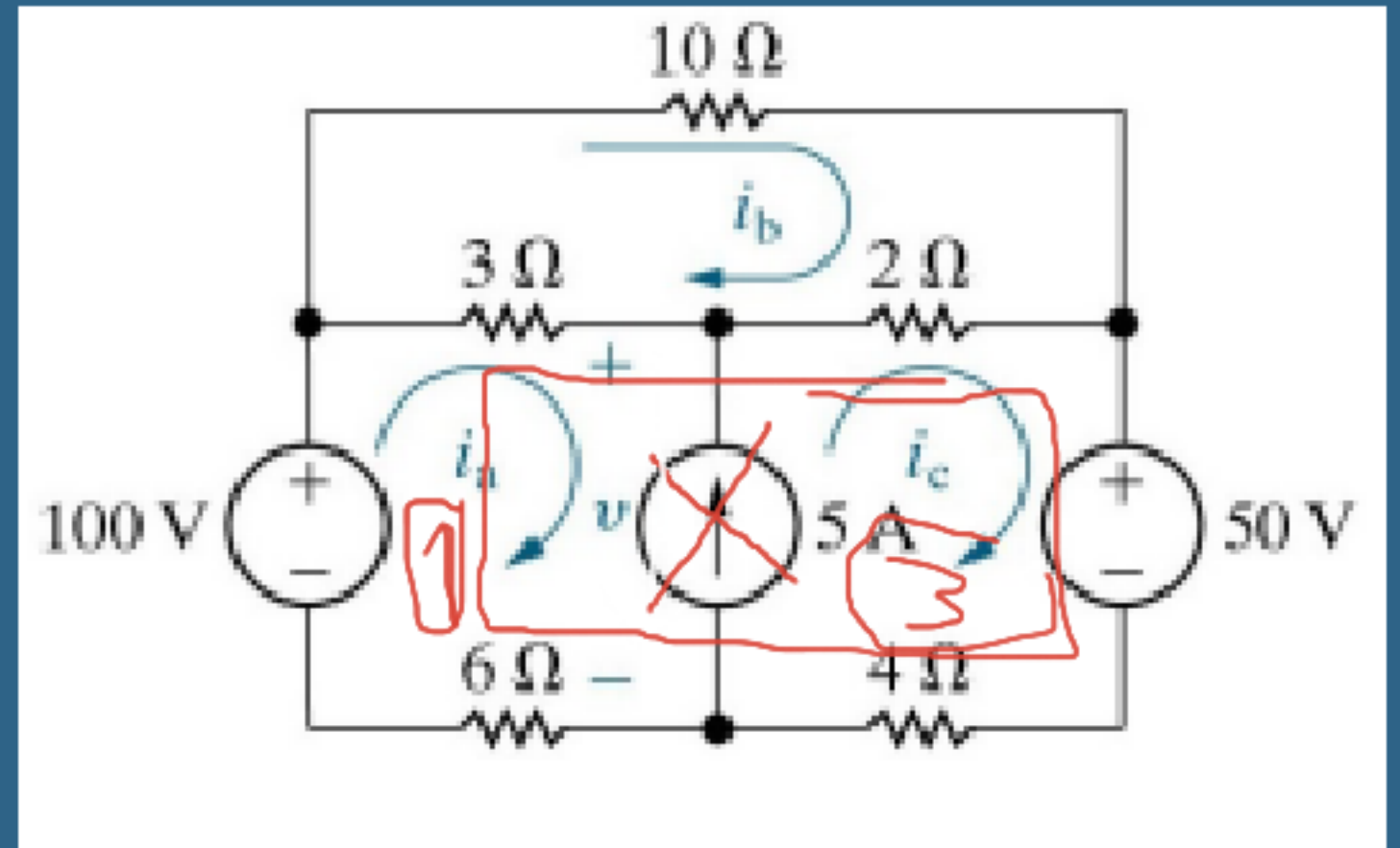When a current source is shared between two meshes, we can combine these meshes to form a supermesh, which traverses the perimeters of the two meshes and avoids the branch containing the shared current source.



① #

$$-100 + 3(i_a - i_b) + 6(i_a) + V = 0$$

②

$$10i_b + 3(i_b - i_a) + 2(i_b - i_c) = 0$$

③ +50 + 4i_c + 2(i_c - i_b) - V = 0

#


$$-100 + 3(i_a - i_b) + 2(i_c - i_b) + 50 + 4i_c + 6i_a = 0$$

I

II ✓

$$5 = i_c - i_a$$

III

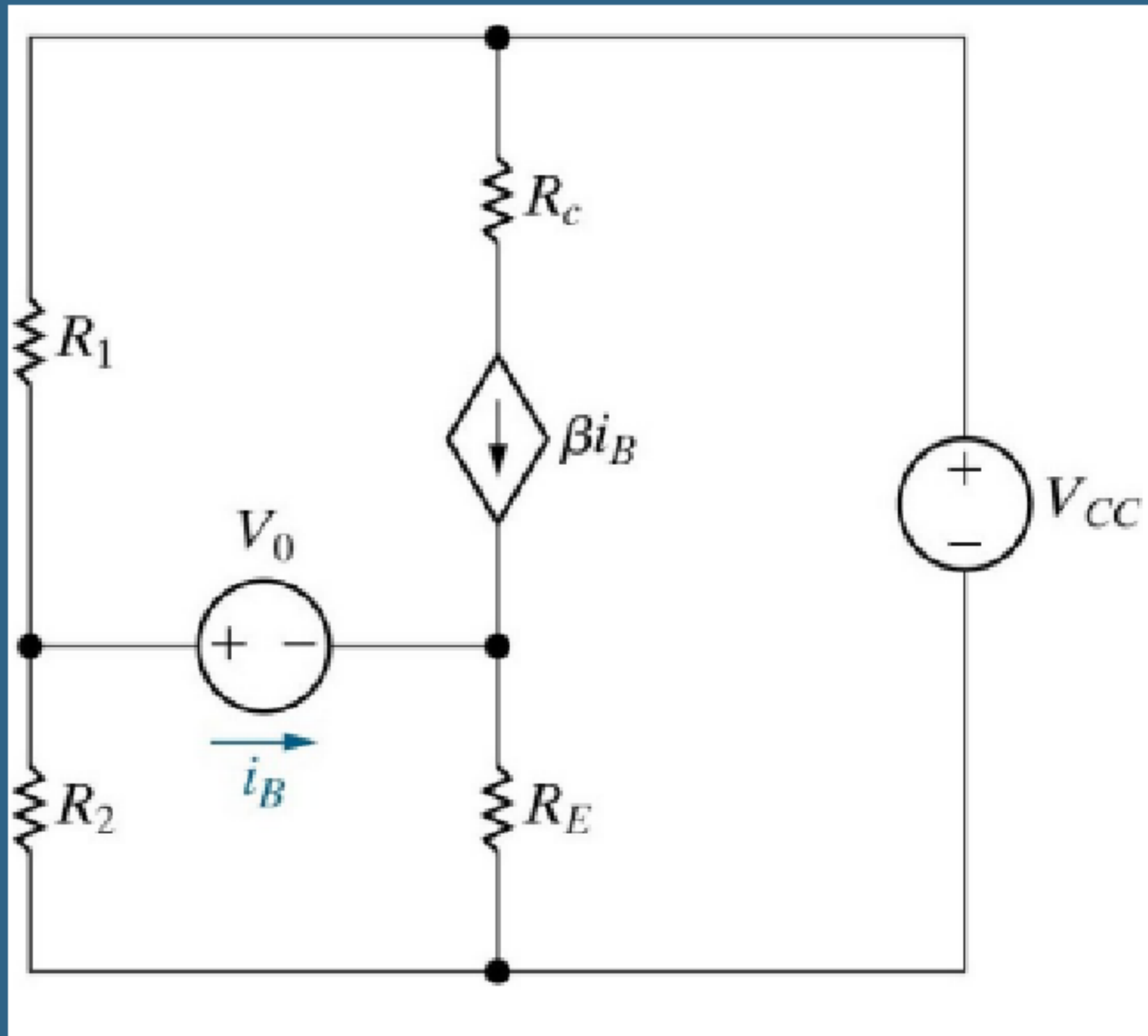

$$\beta i_B = i_a - i_c$$

