
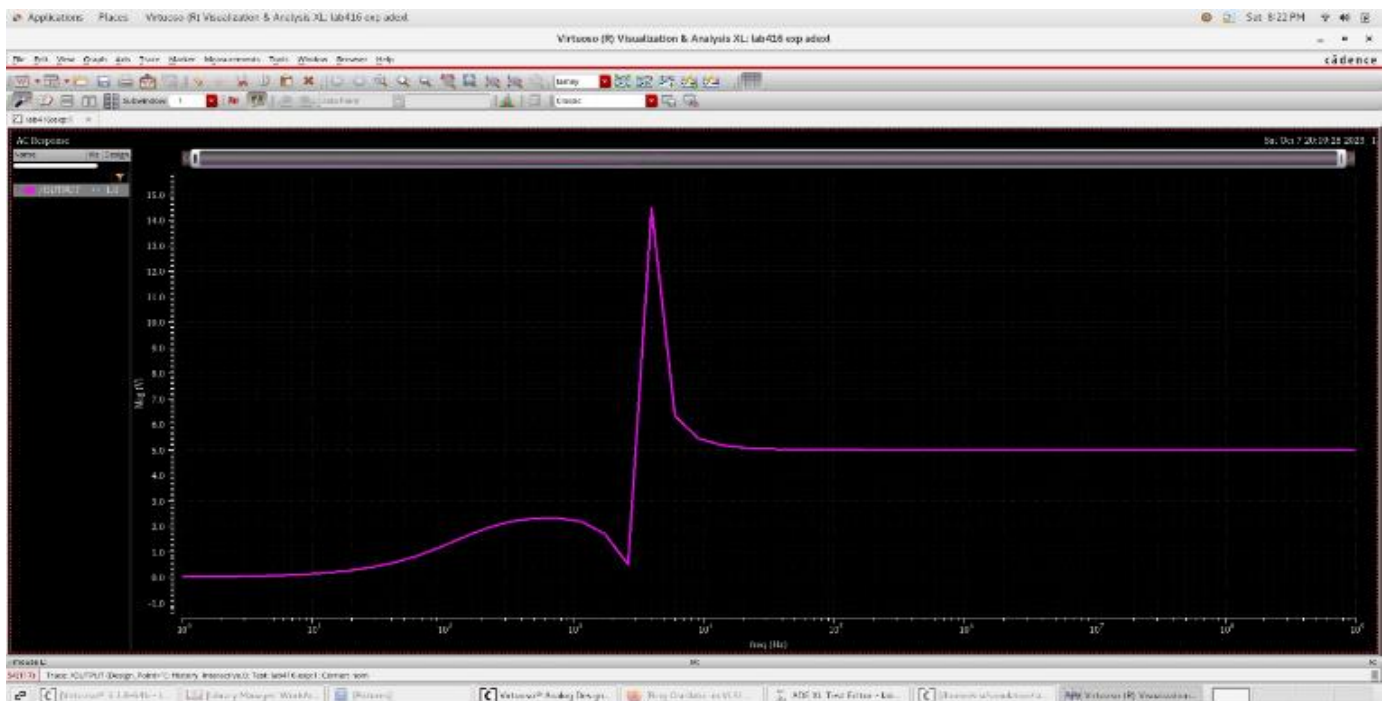


CND 101 – advanced LAB [4]

Student name: Karim Mahmoud Kamal Mohamed

Student ID: V23010174

Bonus assignment (harmonic filter)

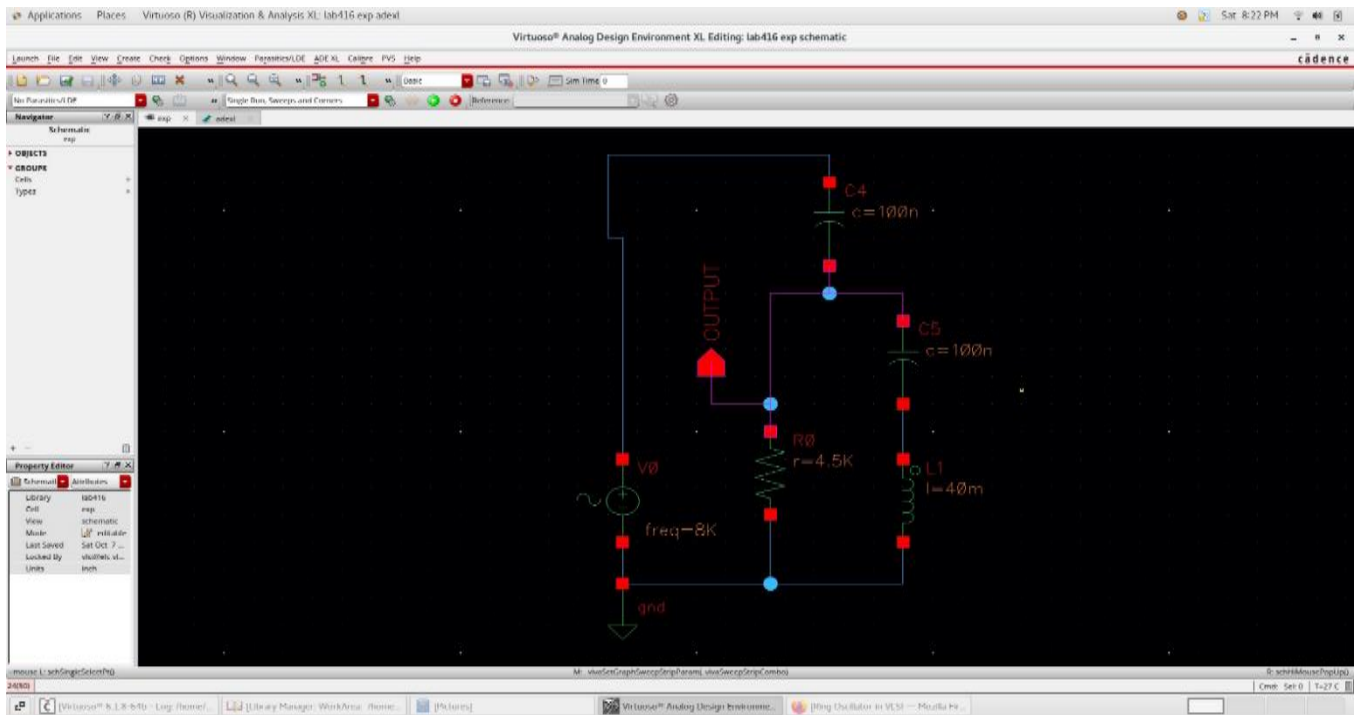



Comments

A harmonic (shunt) filter is an electronic device used in electrical power systems to mitigate and control harmonic distortion caused by nonlinear loads, such as variable speed drives, rectifiers, and other power electronics equipment.

Harmonics are unwanted sinusoidal currents or voltages at frequencies that are integer multiples (2nd, 3rd, 4th, etc.) of the fundamental frequency of the power system. Harmonic distortion can lead to a range of problems, including equipment overheating, voltage distortion, and increased energy losses.

A shunt filter is a type of harmonic filter that is connected in parallel (shunt-connected) with the power system, usually at the point where the nonlinear load is connected.

The primary function of a shunt harmonic filter is to provide a low-impedance path for harmonics to flow, diverting them away from the power source and the rest of the power system.

Key features and functions of harmonic (shunt) filters include:

1. Harmonic Absorption: Shunt filters are designed to absorb and filter out specific harmonic frequencies generated by nonlinear loads.
2. Parallel Connection: Shunt filters are connected in parallel with the nonlinear load or loads that generate harmonics. This means that the filter carries the harmonic currents, preventing them from affecting the rest of the power system.
3. Frequency Selectivity: Shunt filters are often designed to target and attenuate specific harmonic orders. This selectivity is achieved by designing the filter components to have low impedance at the target harmonic frequencies.
4. Resonance Avoidance: To prevent resonance issues, shunt filters are usually equipped with damping elements (resistors or other devices) to control the flow of harmonic currents and avoid resonance with the power system's inductance and capacitance.
5. Tuning and Design: Proper design and tuning of shunt filters are crucial to their effectiveness.
6. Losses: While shunt filters are effective at reducing harmonic distortion, they are not lossless. Some energy is dissipated as heat in the filter components, resulting in a slight reduction in system efficiency.
7. Overcurrent Protection: Shunt filters may incorporate overcurrent protection devices to safeguard against excessive currents that could damage the filter components. These protection devices can include fuses, circuit breakers, or other safety mechanisms.

Harmonic (shunt) filters are essential for maintaining the quality and reliability of electrical power in facilities with significant nonlinear loads. They help mitigate voltage distortion, reduce energy losses, and prevent overheating and premature failure of equipment in the power system. Properly designed and installed shunt filters can significantly improve power quality and minimize the adverse effects of harmonics on electrical systems.

My comments about transient & AC analysis:

AC Analysis (Steady-State Analysis):

1. Frequency Response: helps identify how the filter attenuates specific harmonic frequencies and whether it meets the requirements of the application.
2. Impedance Matching: The filter should provide a low-impedance path for the targeted harmonics while presenting a high impedance at the fundamental frequency to avoid affecting the normal power flow.
3. Selectivity: AC analysis is used to determine the selectivity of the harmonic filter. It assesses whether the filter effectively attenuates the desired harmonics while allowing the fundamental frequency and other essential frequencies to pass through with minimal loss.
4. Tuning and Resonance: to ensure that the filter components are properly tuned to the harmonic frequencies to be mitigated. It helps avoid resonance issues, where the filter could amplify rather than attenuate specific harmonics.
5. Harmonic Current Reduction: AC analysis helps assess the reduction in harmonic currents provided by the filter. Engineers can determine how much the filter suppresses the harmonic distortion, ensuring compliance with regulations and standards.

Transient Analysis (Time-Domain Analysis):

1. Startup and Transients: It assesses how the filter responds to sudden changes in load or voltage.
2. Damping and Resonance Control: It ensures that the filter can handle transient conditions without compromising system stability.
3. Inrush Currents: Managing these currents is important to prevent overloading and damage to the filter components.
4. Switching Transients: This is critical to avoid transient overvoltages and ensure proper operation.
5. Fault Response: Understanding the filter's behavior helps ensure system safety and reliability.
6. Performance During Load Variations: Transient analysis can evaluate how the filter performs under changing load conditions, ensuring that it continues to suppress harmonics effectively even as loads vary.

Both AC analysis and transient analysis help verify that the filter meets the specified requirements, operates safely, and effectively mitigates harmonic distortion while maintaining system stability.