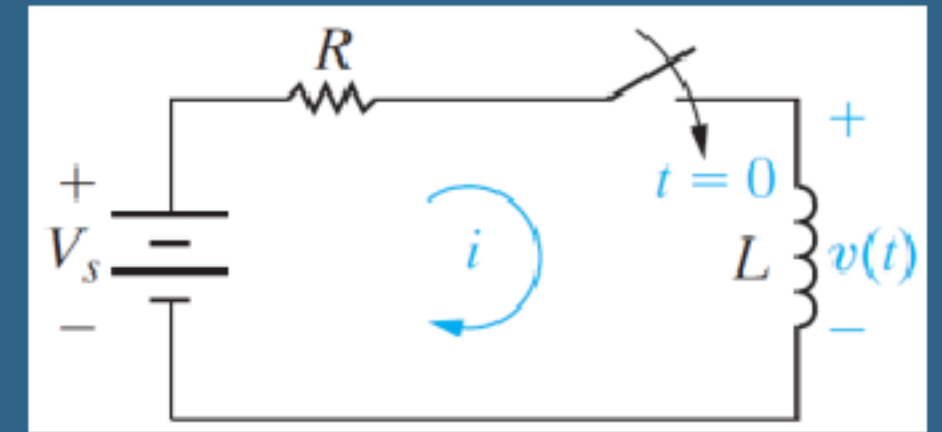


The Step Response (Transient) of an RL Circuit

The response of a circuit to the sudden application of a constant voltage or current source.



$$V_s = Ri + L \frac{di}{dt}$$

$$V_s - Ri = L \frac{di}{dt}$$

$$\left(\frac{V_s}{L} - \frac{Ri}{L} \right) dt = di$$

$$\left(i - \frac{V_s}{R} \right) \left(-\frac{R}{L} \right) dt = di$$

$$\frac{di}{i - \frac{V_s}{R}} = -\frac{R}{L} dt$$

$$\text{Let } z = i - \frac{V_s}{R}$$

$$\frac{dz}{z} = -\frac{R}{L} dt$$

$$\ln(z) = -\frac{R}{L} t$$

$$\ln\left(i - \frac{V_s}{R}\right) = -\frac{R}{L} t$$

$$\ln\left(i - \frac{V_s}{R}\right) - \ln\left(I_0 - \frac{V_s}{R}\right) = -\frac{R}{L} t$$

$$\ln\left(\frac{i - \frac{V_s}{R}}{I_0 - \frac{V_s}{R}}\right) = -\frac{R}{L} t$$

$$dz = di$$

$$\frac{i - I_f}{I_0 - I_f} = e^{-\frac{R}{L} t}$$


$$i - I_f = (I_0 - I_f) e^{-\frac{R}{L} t}$$

$$\tau = \frac{L}{R}$$

$$i(t) = I_f + (I_0 - I_f) e^{-t/\tau}$$

The Step Response (Transient) of an RL Circuit Steps:

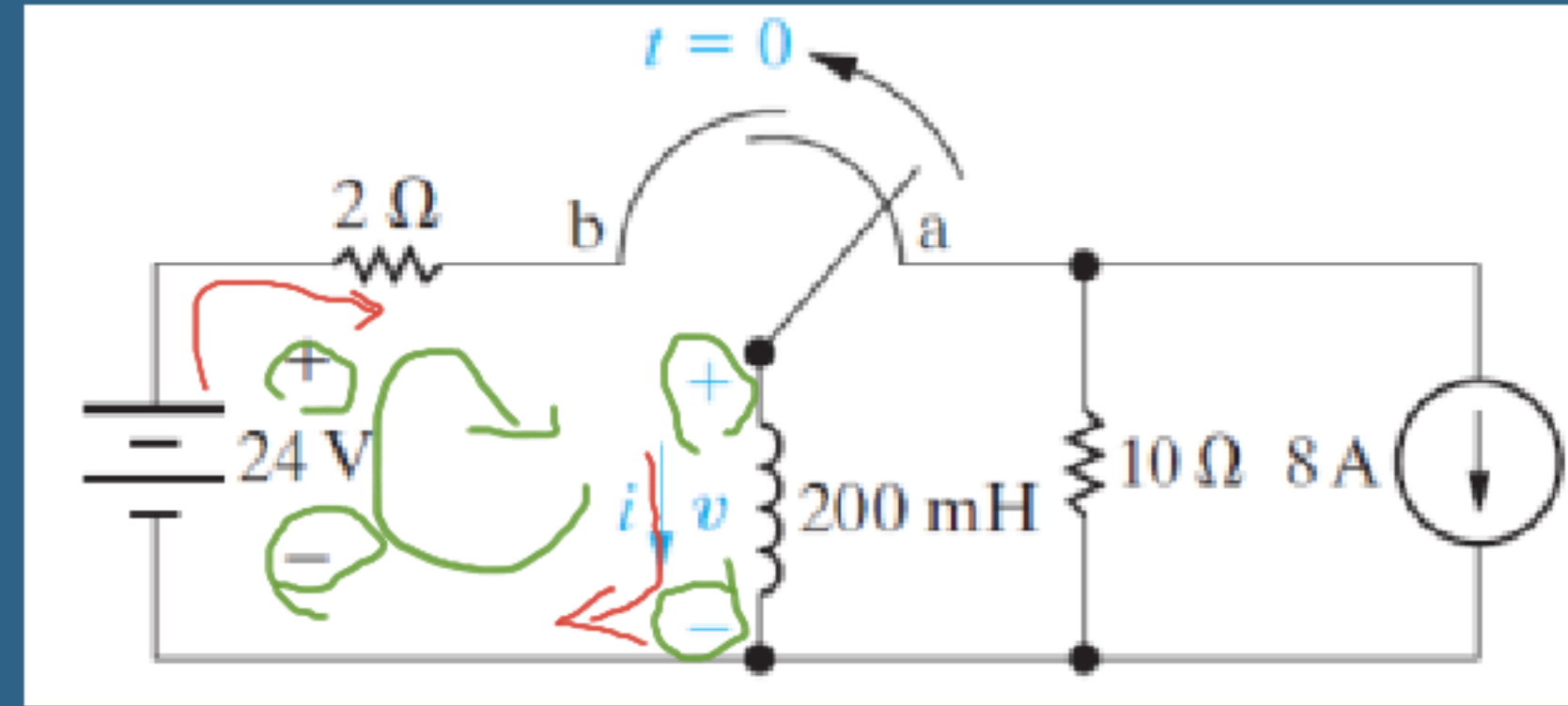- 1- Determine I_0 (usually @ $t < 0$)
- 2- Calculate $\tau \Rightarrow R_{eq}$
- 3- Calculate I_{final} ($t \rightarrow \text{infinity}$)
- 4- Write the equation of Inductor current
- 5- Calculate any required quantities



$$\rightarrow I_0 = -8A$$

$$\rightarrow \tau = \frac{L}{R} = 0.1 \text{ sec}$$

$$\rightarrow I_f = \frac{24}{2} = 12A$$


$$\rightarrow i = I_f + (I_0 - I_f) e^{-t/\tau} = 12 - 20 e^{-10t}$$

$$\rightarrow v = L \frac{di}{dt} = 40 e^{-10t}$$



The Step Response (Transient) of an RL Circuit

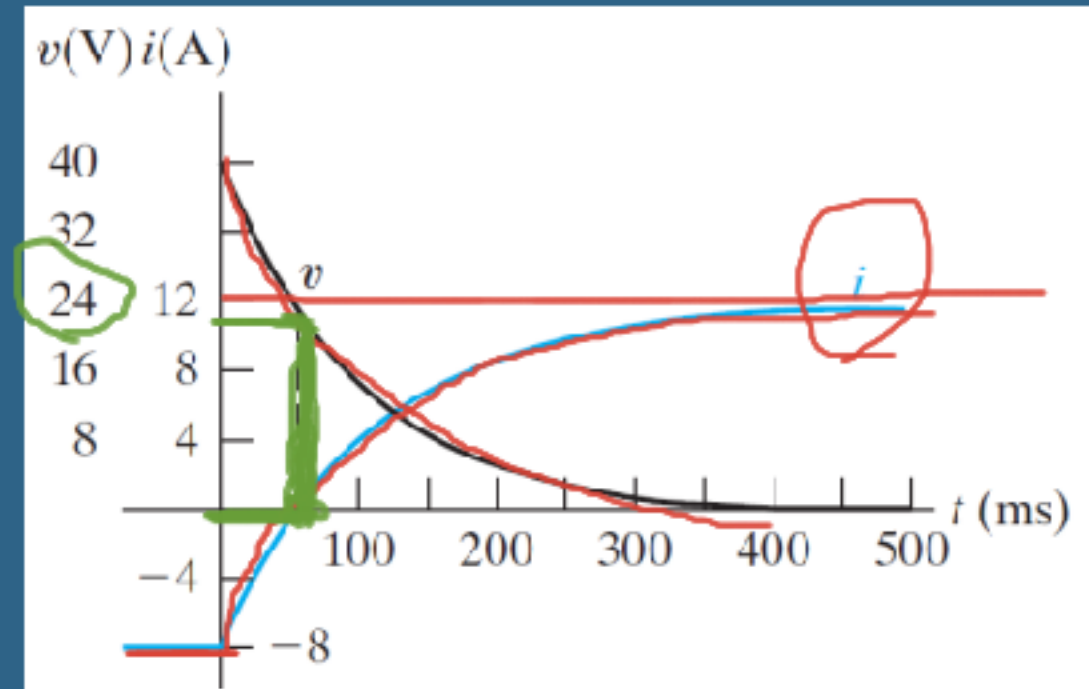- Yes. In the instant, after the switch has been moved to position b, the inductor current is 8 A counterclockwise around the newly formed closed path.
- This current causes a 16 V drop across the 2 resistors. This voltage drop adds to the 24 V drop across the source, producing a 40 V drop across the inductor.



$$24 = 40e^{-10t}$$
$$t = 51.08 \text{ ms}$$


$$24 = 40e^{-10t}$$

$$t = \frac{1}{10} \ln \frac{40}{24}$$
$$= 51.08 \text{ ms.}$$

Get V equation:


$$i(t) = \frac{V_s}{R} - \frac{V_s}{R} e^{-(R/L)t}$$

$$i_0 = 0$$

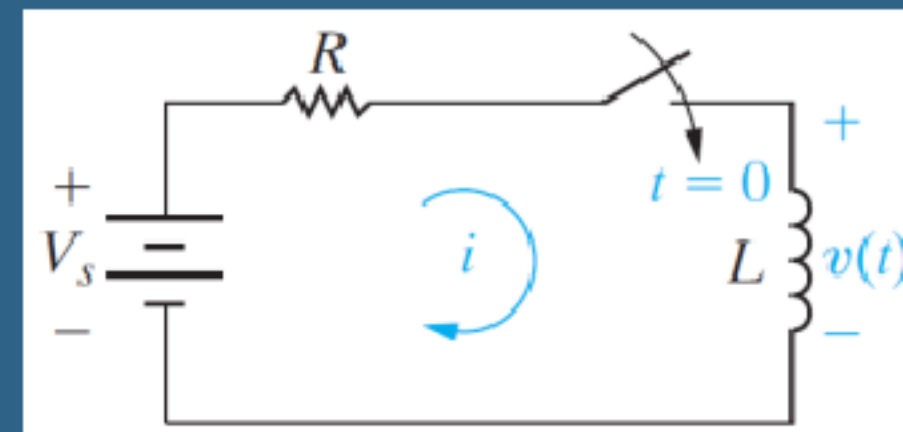

Start with $v = L \frac{di}{dt}$
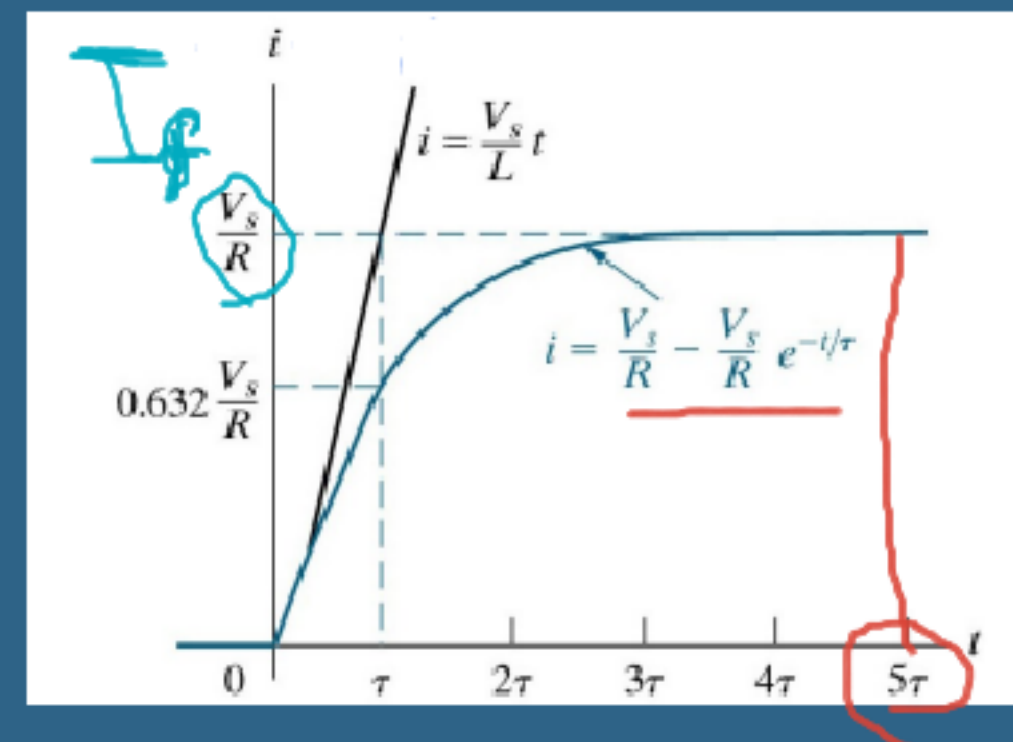
$$v = L \left(\frac{V_s}{L} - \frac{V_s}{L} e^{-(R/L)t} \right) = V_s e^{-(R/L)t}$$



$$v = V_s e^{-(R/L)t}$$

- When the initial inductor current is zero

The Step Response of an RC Circuit


Steps:

- 1- Determine V_0 (usually @ $t < 0$)
- 2- Calculate $\tau \Rightarrow R_{eq}$
- 3- Calculate V_{final} ($t \rightarrow \text{infinity}$)
- 4- Write the equation of Capacitor Voltage
- 5- Calculate any required quantities

$$C \frac{dv}{dt} + \frac{v}{R} = I_s$$

$$v = I_s R + (V_0 - I_s R) e^{-t/RC}, \quad t \geq 0.$$

$$v(t) = V_f + (V_0 - V_f) e^{-t/\tau}$$

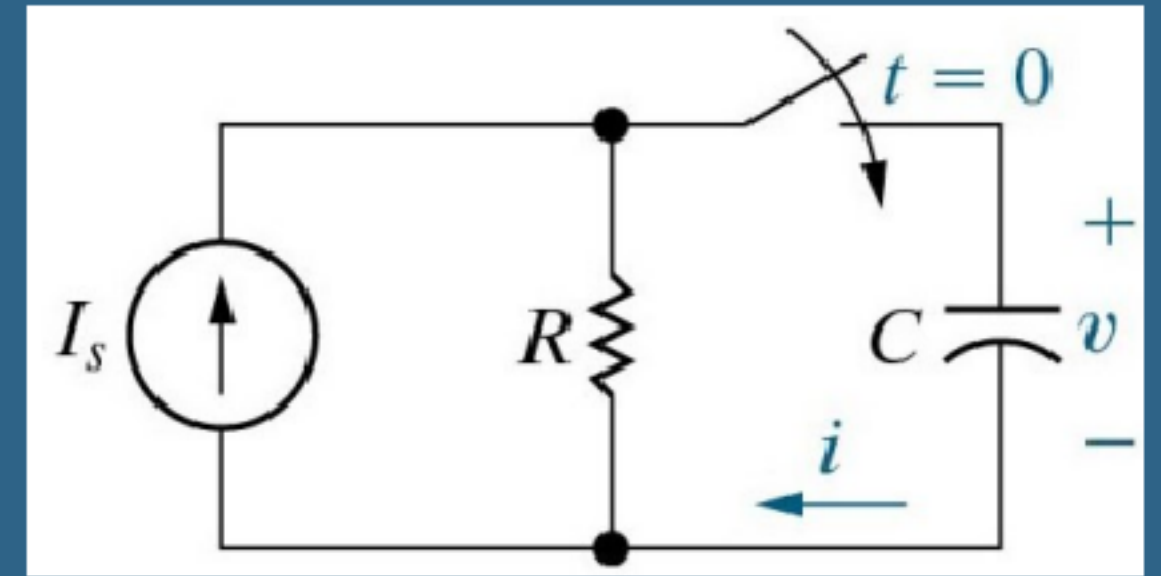

Solution

int idl
 $\rightarrow v_0 = \frac{60}{60+20} \cdot 40$


$= 30V$

$\rightarrow T = RC = 10ms$

$\rightarrow V_f = \frac{160}{160+40} (75) = -60V$



$v(t) = V_f + (V_i - V_f)e^{-t/\tau} = -60 + 90e^{-100t}$

$i = C \frac{dv}{dt} = \checkmark$

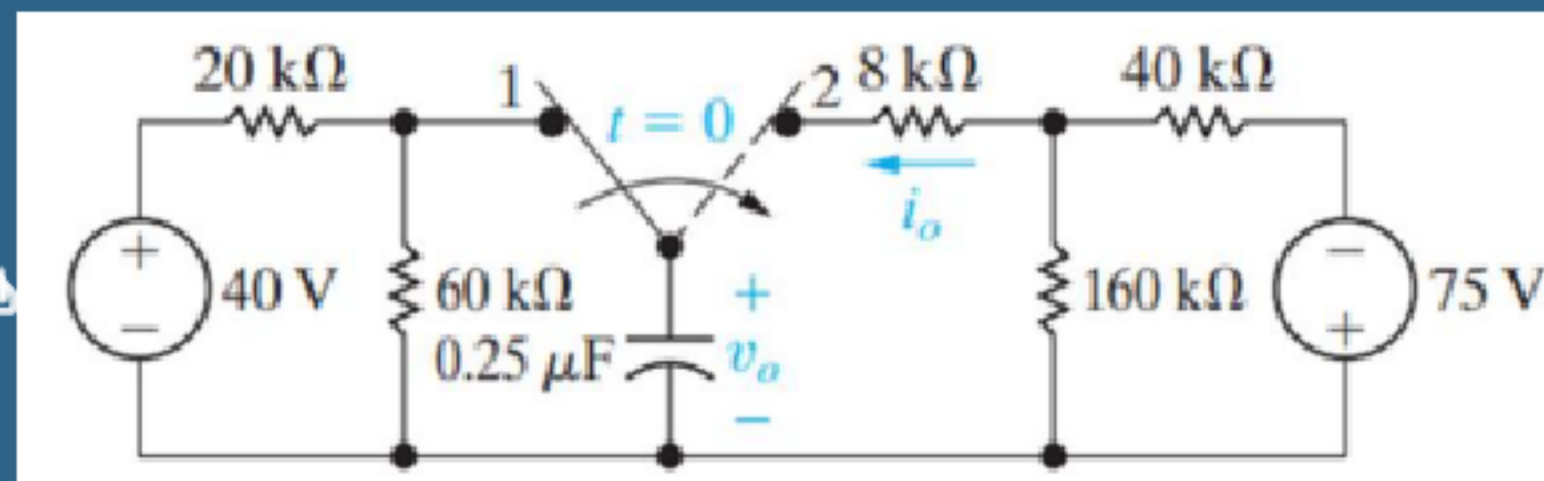

Real App () Art ifi cial Pacemaker

- The RC circuit can be used in an artificial pacemaker to establish a normal heart rhythm by generating periodic electrical impulses.
- The “controller” behaves as an o.c until the voltage drop across the capacitor reaches a preset limit.
- Once that limit is reached, the capacitor discharges its stored energy in the form of an electrical impulse to the heart, starts to recharge, and then the process repeats.

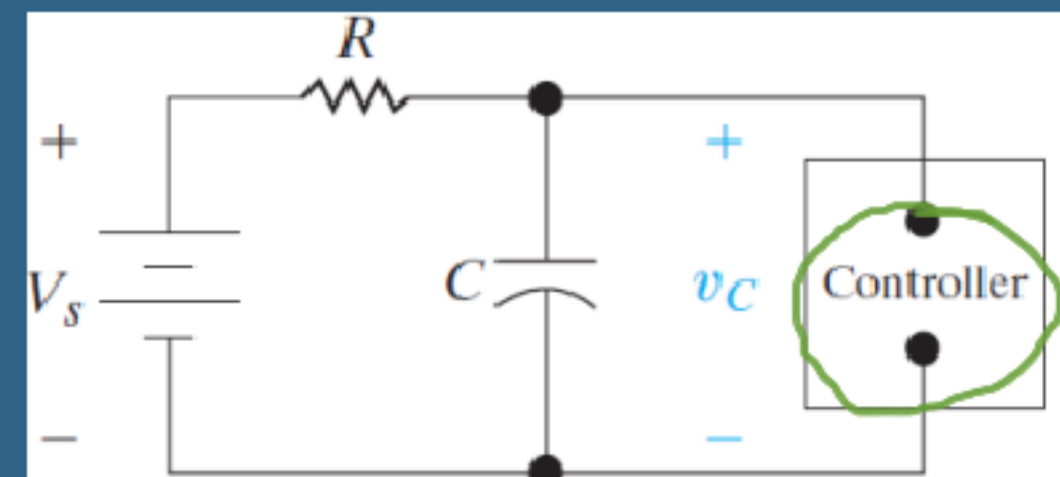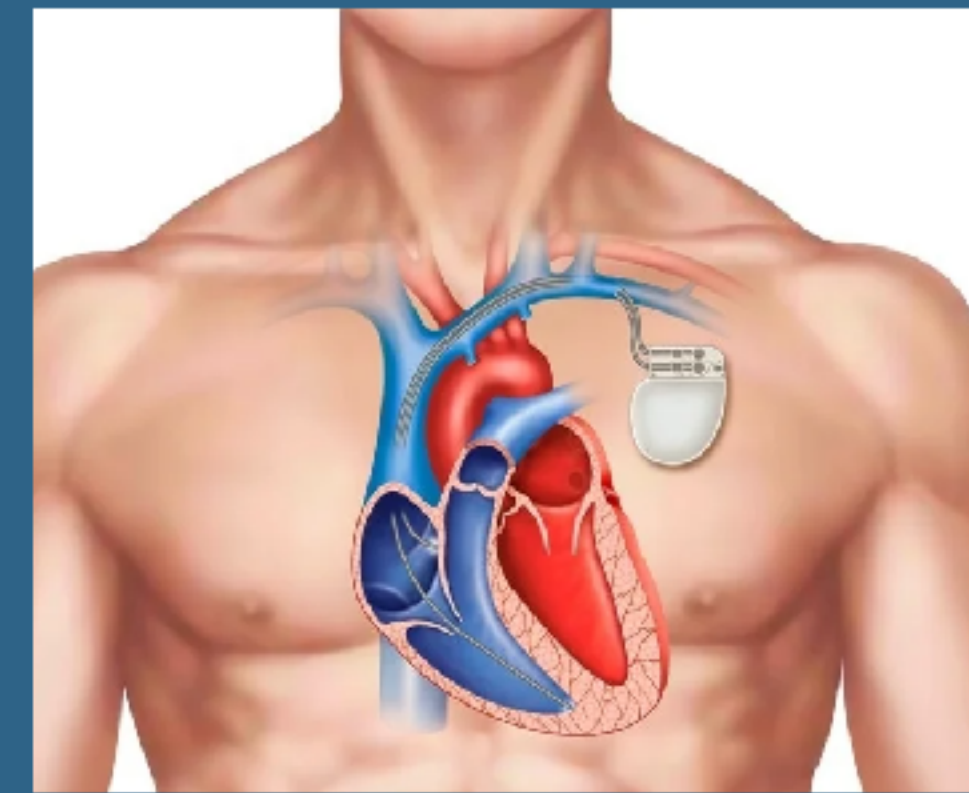

$$V_0 = v_C(0) = 0;$$

$$V_f = v_C(\infty) = V_s; \text{ and } \tau = RC.$$

$$v_o = V_f + (V_0 - V_f)e^{-t/\tau}$$

$$v_C(t) = V_s (1 - e^{-t/RC}).$$

To find H = $(1/t_c) * 60$, we should estimate t_c

$$0.75 V_s = V_s (1 - e^{-t/RC}).$$

$$H = \frac{60}{-RC \ln 0.25} \text{ [beats per minute]}$$

