

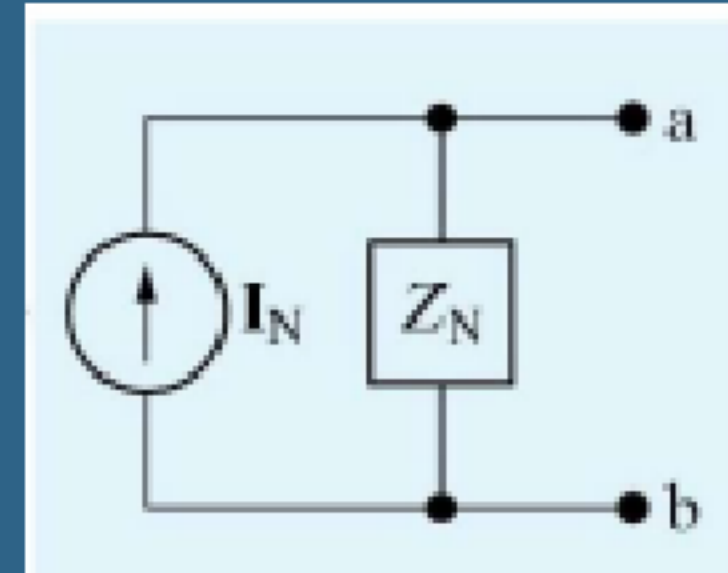


## Source transformations

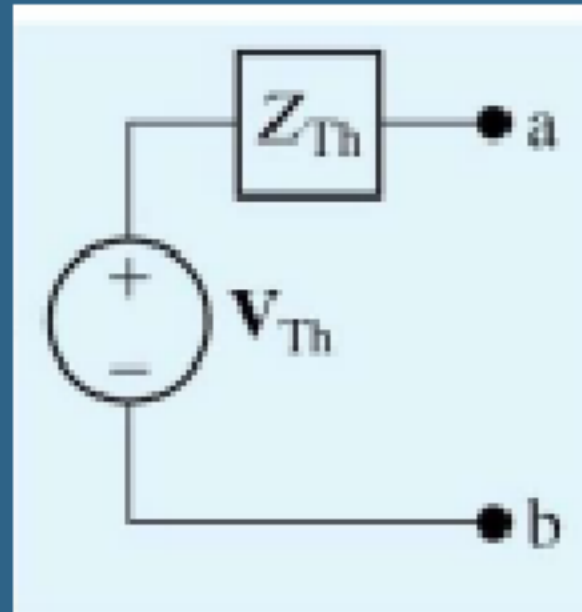

## The Node - Voltage Method

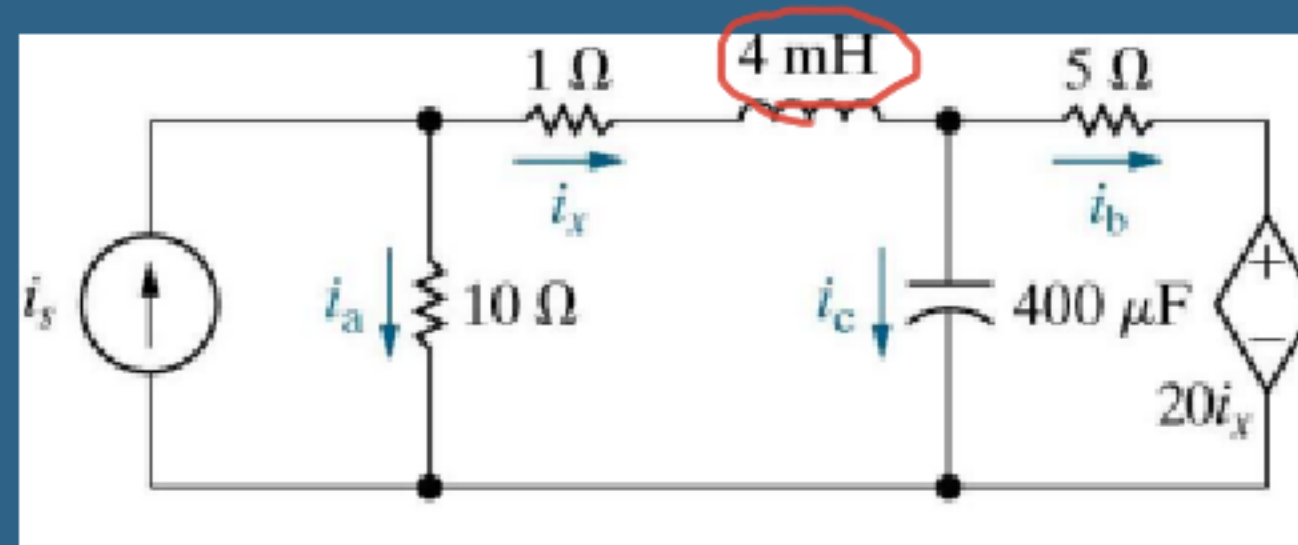


Steps:

- 1- replace the source values.
- 2- L,C to impedance.
- 3- KCL (reference node)

- Use the node-voltage method to find the branch currents  $i_a$ ,  $i_b$ , and  $i_c$  in the steady-state.
- The value of the current source in this circuit is  $i_s = 10.6 \cos(500t)$  A.

Solution

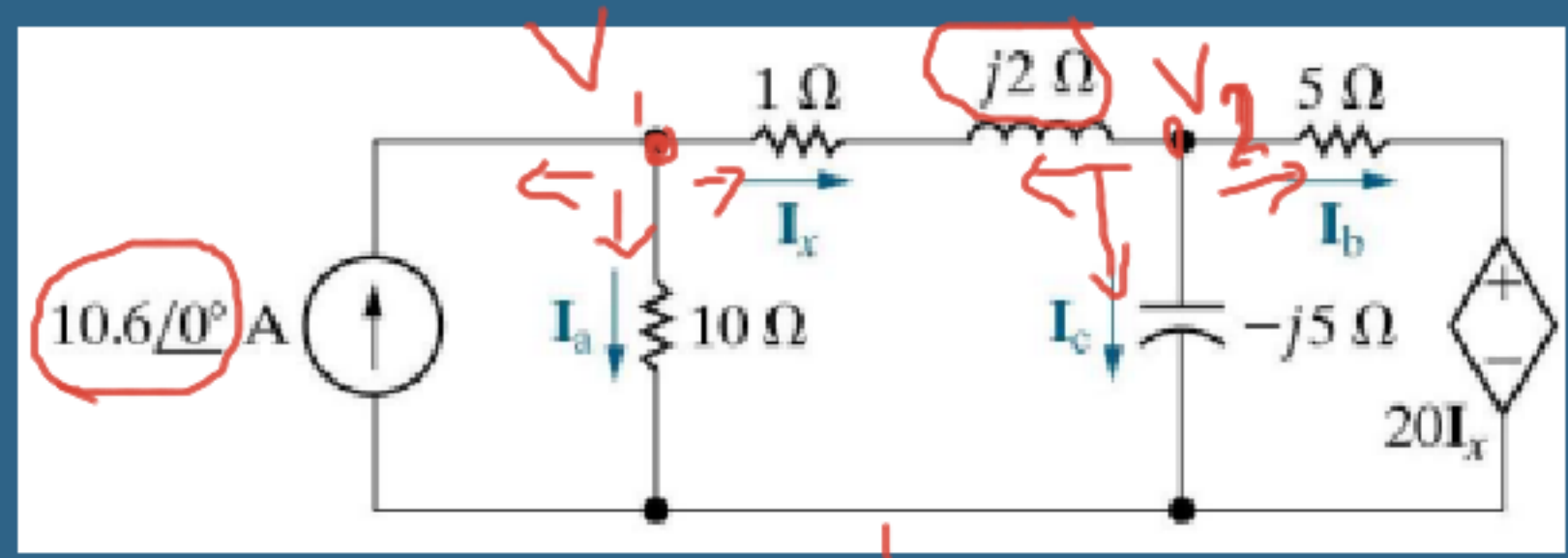

freq domain:  $\omega = 500 \text{ rad/s}$

$$L = j\omega L = 2j \Omega$$

$$C = 1/j\omega C = -5j$$

Kcl:  $-10.6 + \frac{V_1 - 0}{10} + \frac{V_1 - V_2}{1 + 2j} = 0$

$$I_x = \frac{V_1 - V_2}{1 + 2j}$$

$$\frac{V_2 - V_1}{1 + 2j} + \frac{V_2 - 0}{-5j} + \frac{V_2 - 20I_x}{5} = 0$$

$$\begin{aligned} V_1 &= 68.4 - j16.8 \text{ V,} \\ V_2 &= 68 - j26 \text{ V,} \\ I_x &= 3.76 + j1.68 \text{ A.} \end{aligned}$$

$$\mathbf{I}_a = \frac{\mathbf{V}_1}{10} = \underline{6.84 - j1.68 \text{ A}} = \underline{7.04 \angle -13.8^\circ \text{ A}},$$

$$\mathbf{I}_b = \frac{\mathbf{V}_2 - 20\mathbf{I}_x}{5} = \underline{-1.44 - j11.92 \text{ A}} = \underline{12 \angle -96.89^\circ \text{ A}},$$

$$\mathbf{I}_c = \frac{\mathbf{V}_2}{-j5} = \underline{5.2 + j13.6 \text{ A}} = \underline{14.56 \angle 69.08^\circ \text{ A}}.$$


Handwritten calculation for  $\mathbf{I}_a$ :

$$\sqrt{(6.84)^2 + (-1.68)^2} = 7.04$$

$$i_a = \underline{7.04} \cos(500t - 13.8^\circ) \text{ A},$$

$$i_b = \underline{12} \cos(500t - 96.89^\circ) \text{ A},$$
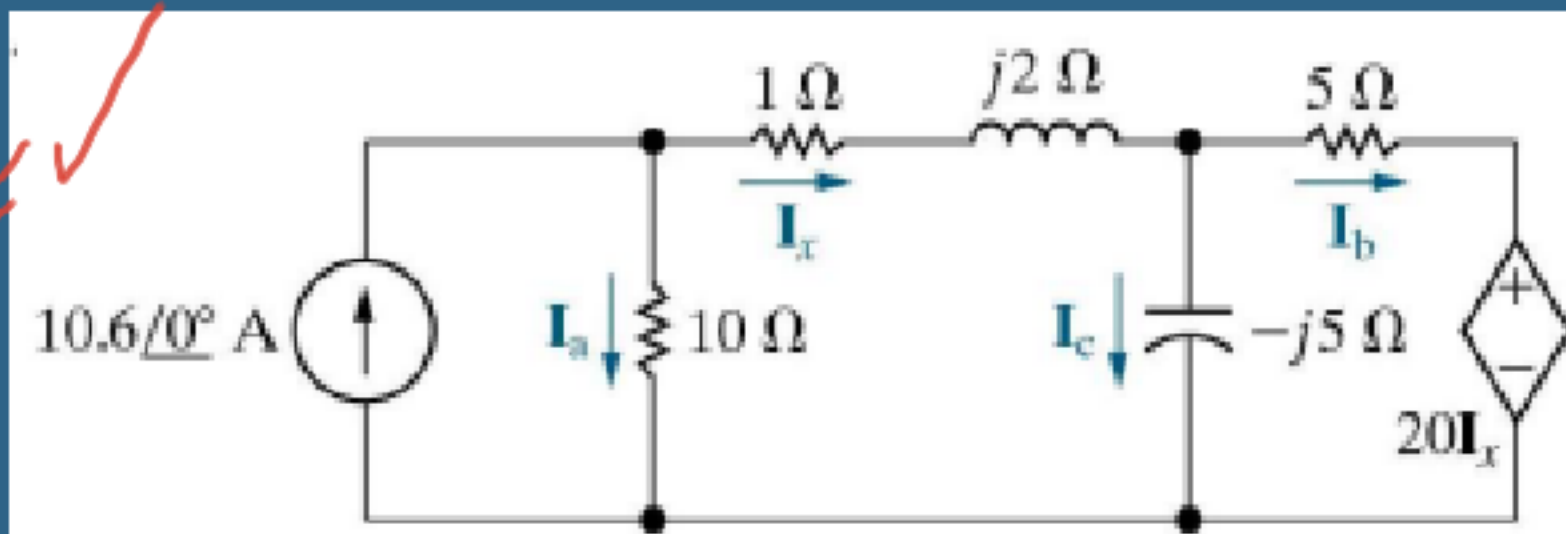
$$i_c = \underline{14.56} \cos(500t + 69.08^\circ) \text{ A}.$$




## The mesh-current method

- Use the mesh-current method to find the voltages  $V_1$ ,  $V_2$ , and  $V_3$  in the circuit

Steps:

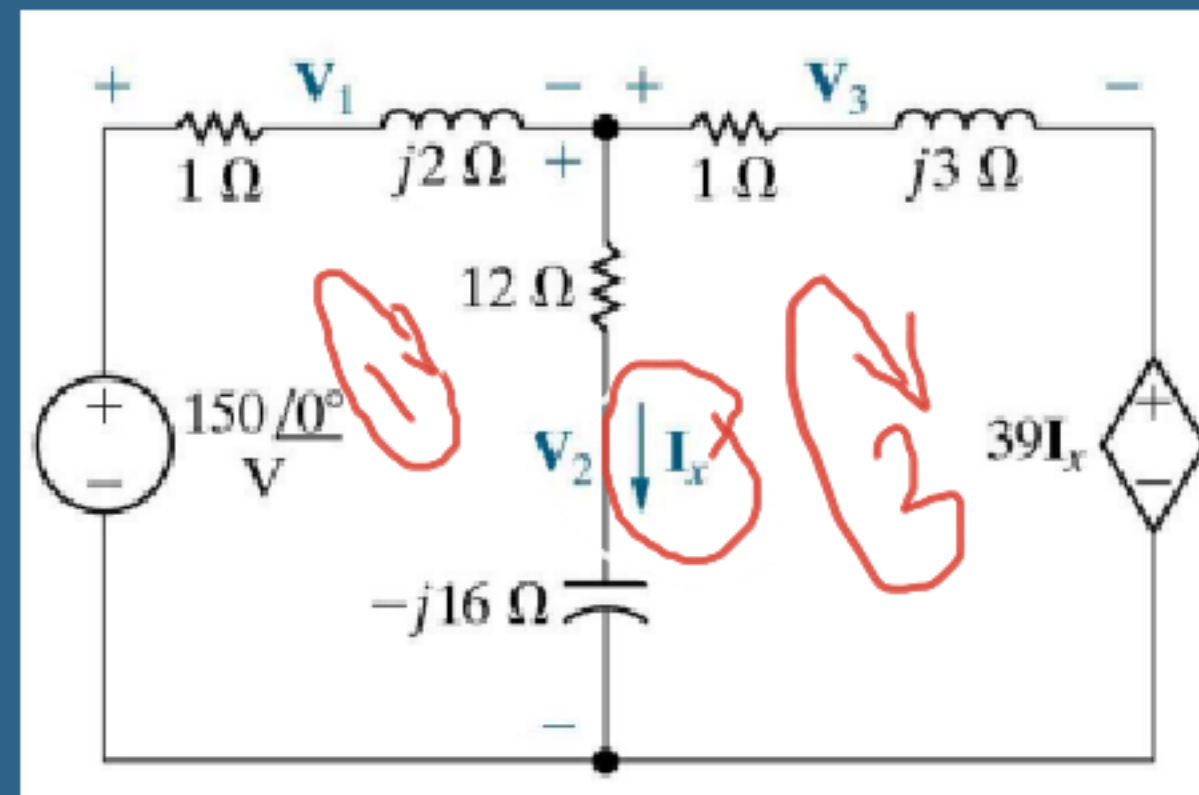- 1- replace the source values.
- 2- L,C to impedance.
- 3- KVL



$$-150 + (1 + j2)I_1 + (12 - j16)(I_1 - I_2) = 0$$

$$(12 - j16)(I_2 - I_1) + (1 + j3)I_2 = 0$$

$$+ 39I_x = 0$$

$$I_x = I_1 - I_2$$

$$I_1 = -26 - j52 \text{ A,}$$

$$I_2 = -24 - j58 \text{ A,}$$

$$I_x = -2 + j6 \text{ A.}$$

$$V_1 = (1 + j2)I_1 = 78 - j104 \text{ V,}$$

$$V_2 = (12 - j16)I_x = 72 + j104 \text{ V,}$$

$$V_3 = (1 + j3)I_2 = 150 - j130 \text{ V.}$$