

Lab 7

MOSFET (Metal-Oxide-Semiconductor Field -Effect Transistor)

Introduction:

A **MOSFET**, or **Metal-Oxide-Semiconductor Field-Effect Transistor**, is a type of **transistor** that can be **used** as a **switch** or **amplifier** in electronic circuits. It consists of a metal **gate**, an **insulating oxide layer**, and a **semiconductor channel**, and **operates** by applying a **voltage** to the **gate to control** the **flow** of **current** through the **channel**.

1-Device Characterization

The test setups for the NMOS transistor are shown in Figure 1 , which will produce the plots shown in graphs 1 and 2 , using parametric analysis.


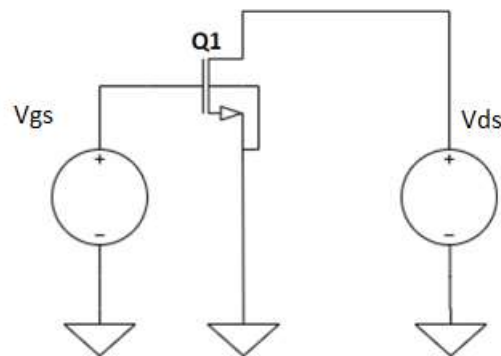


Figure 1 Active Mode circuit

Steps:

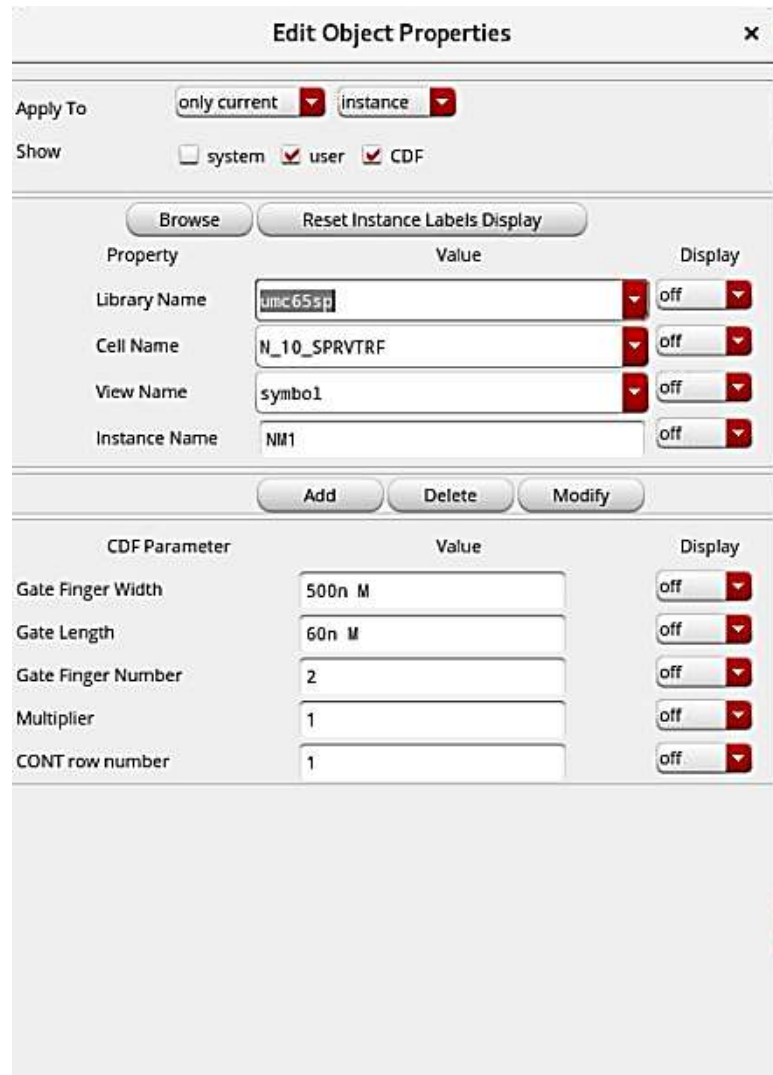- Starting cadence with normal way then :
- Create >> Instance
- Library=> UMC 65



The image shows a screenshot of the "Edit Object Properties" dialog box in a software application. The dialog has a title bar with a close button (X). It contains several sections for configuring object properties.

Apply To: A dropdown menu set to "only current" and another dropdown menu set to "instance".

Show: Checkboxes for "system" (unchecked), "user" (checked), and "CDF" (checked).

Buttons: "Browse" and "Reset Instance Labels Display".

Property Table:


Property	Value	Display
Library Name	umc65sp	off
Cell Name	N_10_SPRVTRF	off
View Name	symbol	off
Instance Name	NM1	off

Buttons: "Add", "Delete", and "Modify".

CDF Parameter Table:

CDF Parameter	Value	Display
Gate Finger Width	500n M	off
Gate Length	60n M	off
Gate Finger Number	2	off
Multiplier	1	off
CONT row number	1	off

-SCHEMATIC1:

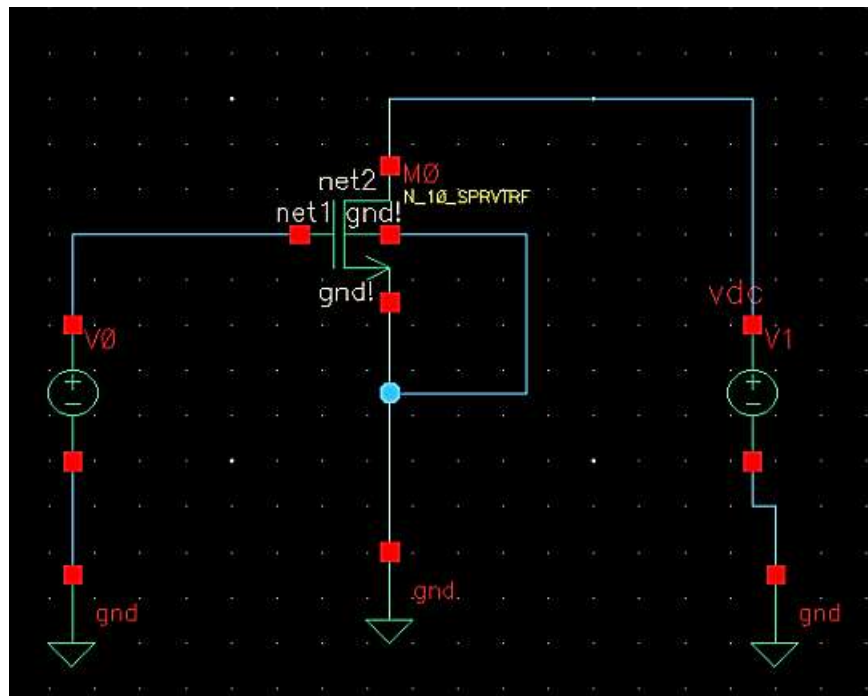

- we need to define DC analysis for getting the response of mosfet's operation
- Launch >> ADE XL window.



- on sweep 2 variables ,need to clarify the input component so we can select it by click on bottom like that:
- Choosing Analysis window =>dc
- click on =>” Save DC Operating point” icon
- Component parameter=>Select component

Choosing Analyses -- Virtuoso® Analog Design

Analysis: ☐ tran ☒ itc ☐ ac ☐ noise
☐ xf ☐ sens ☐ dcmatch ☐ stb
☐ pz ☐ rp ☐ envlp ☐ pos
☐ pac ☐ pssb ☐ pnoise ☐ pnd
☐ ptp ☐ qpss ☐ qpac ☐ qpnoise
☐ qpof ☐ qpdp ☐ hb ☐ hbac
☐ hbnoise ☐ hbap

DC Analysis
 Save DC Operating Point ☒
 Hysteresis Sweep ☐

Sweep Variable
☐ Temperature
☐ Design Variable
☒ Component Parameter
☐ Model Parameter

Component Name:
 Parameter Name:
 Select Component

Sweep Range
☒ Start-Stop Start: Stop:
☐ Center-Span

Sweep Type
☒ Automatic

Add Specific Points ☐

Enabled ☒ Options...

-Schematic Window => vds Source =>OK.

Choosing Analyses -- ADE L (11)

Analysis: ☐ tran ☒ dc ☐ ac ☐ noise
☐ xf ☐ sens ☐ dcmatch ☐ acmatch
☐ stb ☐ pz ☐ lf ☐ sp
☐ envlp ☐ pss ☐ pac ☐ pstb
☐ pnoise ☐ pxf ☐ psp ☐ qpss
☐ qpac ☐ qpnoise ☐ qpxf ☐ qpsp
☐ hb ☐ hbac ☐ hbstb ☐ hbnoise
☐ hbap ☐ hbxf

DC Analysis
 Save DC Operating Point ☒
 Hysteresis Sweep ☐

Sweep Variable
☐ Temperature
☒ Design Variable
☐ Component Parameter
☐ Model Parameter

Variable Name:
 Select Design Variable

Sweep Range
☒ Start-Stop Start: Stop:
☐ Center-Span

Sweep Type
☒ Linear
☐ Step Size
☒ Number of Steps

Add Specific Points ☐

Add Points By File ☐


Enabled ☒ Options...

OK Cancel Defaults Apply Help

-Run from XL's window

-Final Results

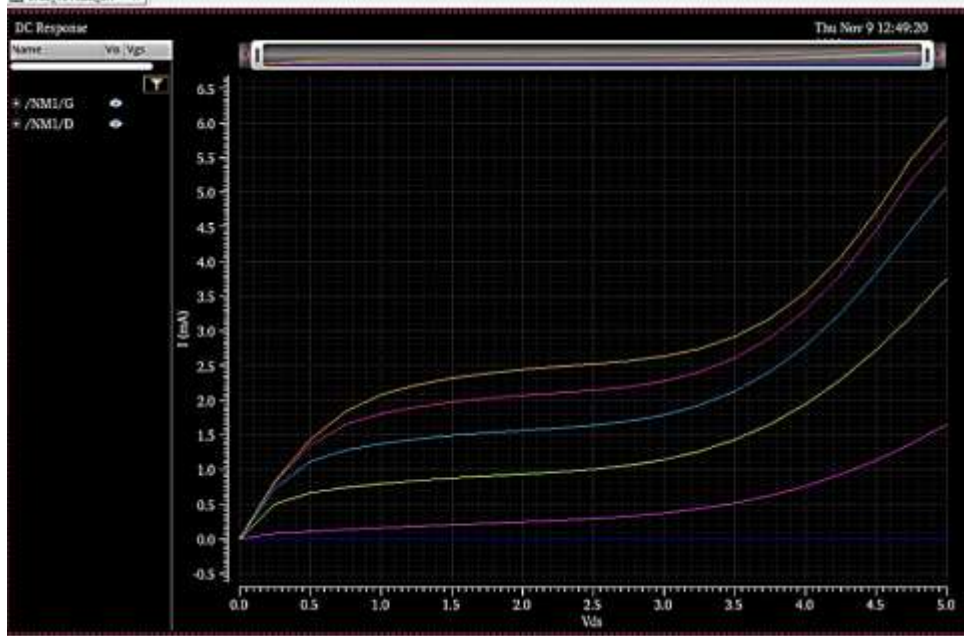Graph 1 (I/V_{ds} Characteristic for select regions of mosfet)



Note that : the output curve will be linear for 2 stages , the second stage due to the library of MOSFET selecting breakdown voltage of MOSFET at almost 4v so after that voltage ,MOSFET will act as resistor

➤ Replacing the main sweep variables as shown below

Choosing Analyses -- ADE L (2) x

Analysis

<input type="radio"/> tran	<input checked="" type="radio"/> dc	<input type="radio"/> ac	<input type="radio"/> noise
<input type="radio"/> xf	<input type="radio"/> sens	<input type="radio"/> dcmatch	<input type="radio"/> acmatch
<input type="radio"/> stb	<input type="radio"/> pz	<input type="radio"/> lf	<input type="radio"/> sp
<input type="radio"/> envlp	<input type="radio"/> pss	<input type="radio"/> pac	<input type="radio"/> pstb
<input type="radio"/> pnoise	<input type="radio"/> pxf	<input type="radio"/> psp	<input type="radio"/> qpss
<input type="radio"/> qpac	<input type="radio"/> qpnoise	<input type="radio"/> qpxf	<input type="radio"/> qpss
<input type="radio"/> hb	<input type="radio"/> hbac	<input type="radio"/> hbstb	<input type="radio"/> hbnoise
<input type="radio"/> hbsp	<input type="radio"/> hbxf		

DC Analysis

Save DC Operating Point ☒

Hysteresis Sweep ☐

Sweep Variable

☐ Temperature

☒ Design Variable

☐ Component Parameter

☐ Model Parameter

Variable Name

Select Design Variable


Sweep Range

☒ Start-Stop

Start Stop

☐ Center-Span

Sweep Type



☐ Step Size

☒ Number of Steps

Add Specific Points ☐

Add Points By File ☐


Enabled ☒

Options...

OK Cancel Defaults Apply Help

At $V_{ds}=1,2,3\text{volts}$

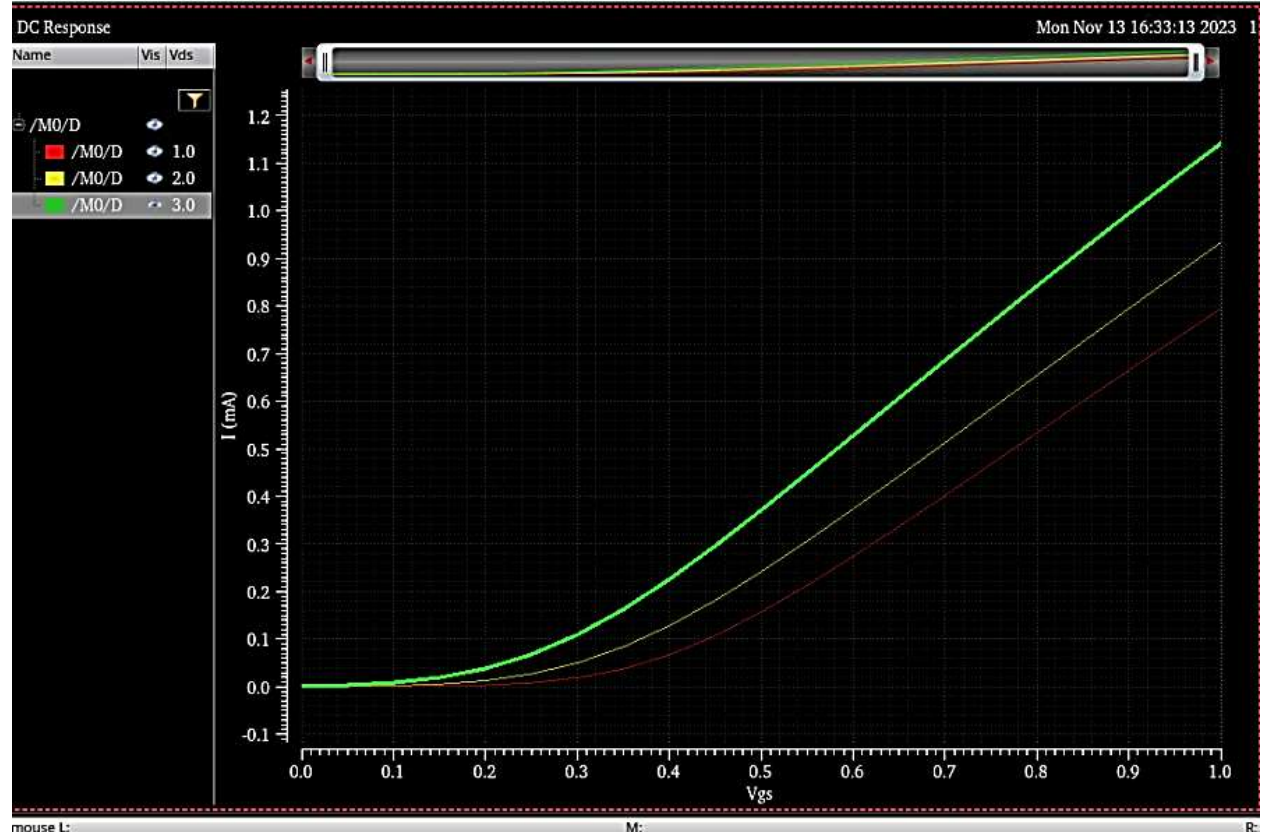Graph 2(I/V_{gs} for select the operating point of gate voltage)



From the above 2 curves we suggest to work on $V_{ds}=3\text{volts}$ and V_{gs} started from 0.1volts

2-Types of MOSFET Amplifiers

MOSFET amplifiers are available in three types like **common source (CS)**, **common gate (CG)**, and **common drain (CD)**, where each type along with its configuration is discussed below.

2-a Common Source

The common source circuit provides a medium input and output impedance levels. Both current and voltage gain can be described as medium, but the output is the inverse of the input, i.e. 180° phase change. This provides a good overall performance and as such it is often thought of as the most widely used configuration.

The **common-source** MOSFET amplifier is related to the **CE (common-emitter)** amplifier of **BJT**. This is **very popular** due to **high gain** and **larger signal amplification** can be **achieved**.


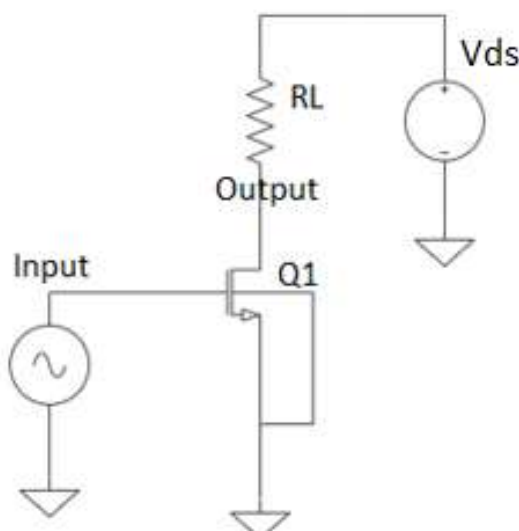


Figure 2 Common Source Circuit

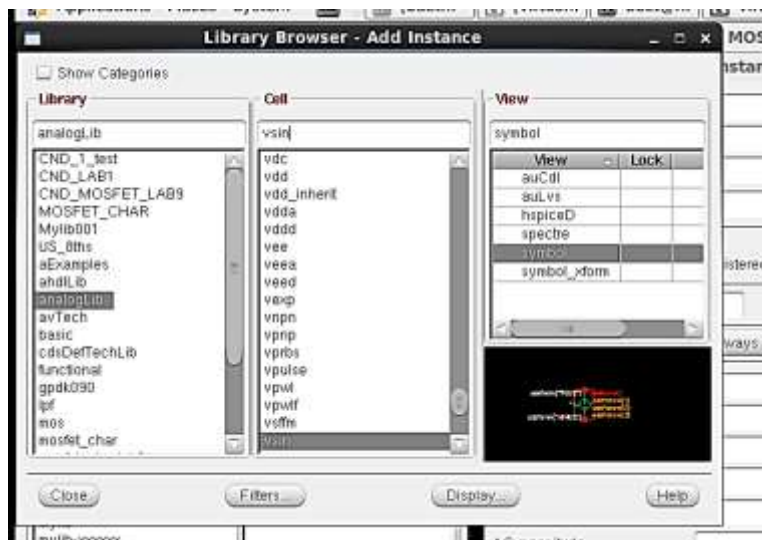

Edit Object Properties x

Apply To only current instance

Show ☐ system ☒ user ☒ CDF

Browse
Reset Instance Labels Display


Property	Value	Display
Library Name	analogLib	off
Cell Name	vsource	off
View Name	sybo1	off
Instance Name	V2	off

Add
Delete
Modify


User Property	Master Value	Local Value	Display
lvignore	TRUE		off

CDF Parameter	Value	Display
DC voltage	600m V	off
Source type	sine	off
Frequency name 1		off
Frequency 1	1K Hz	off
Amplitude 1 (Vpk)	100m V	off
Phase for Sinusoid 1		off
Sine DC level		off
Delay time		off
Display second sinusoid	<input type="checkbox"/>	off
Display multi sinusoid	<input type="checkbox"/>	off
Display modulation params	<input type="checkbox"/>	off
Display small signal params	<input type="checkbox"/>	off
Display temperature params	<input type="checkbox"/>	off
Display noise parameters	<input type="checkbox"/>	off
Multiplier		off

- SCHEMATIC 2:

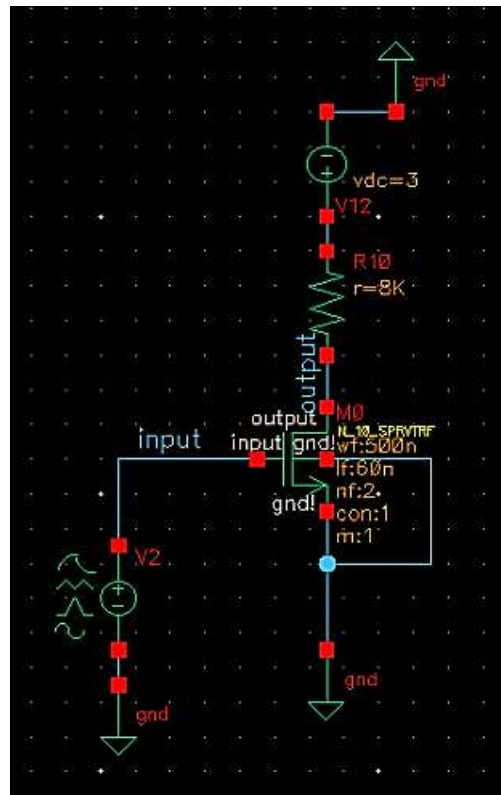


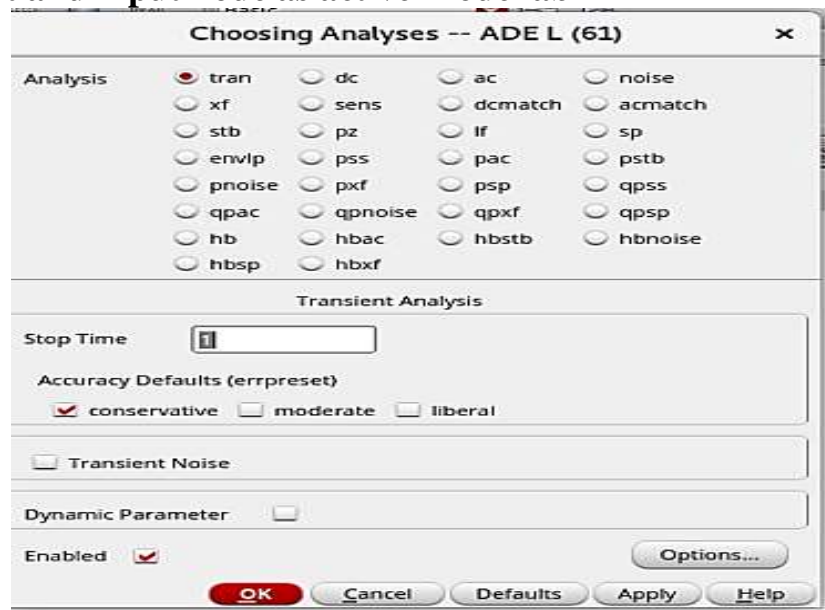-select output and input node as active-mode lab



-Final Results:-

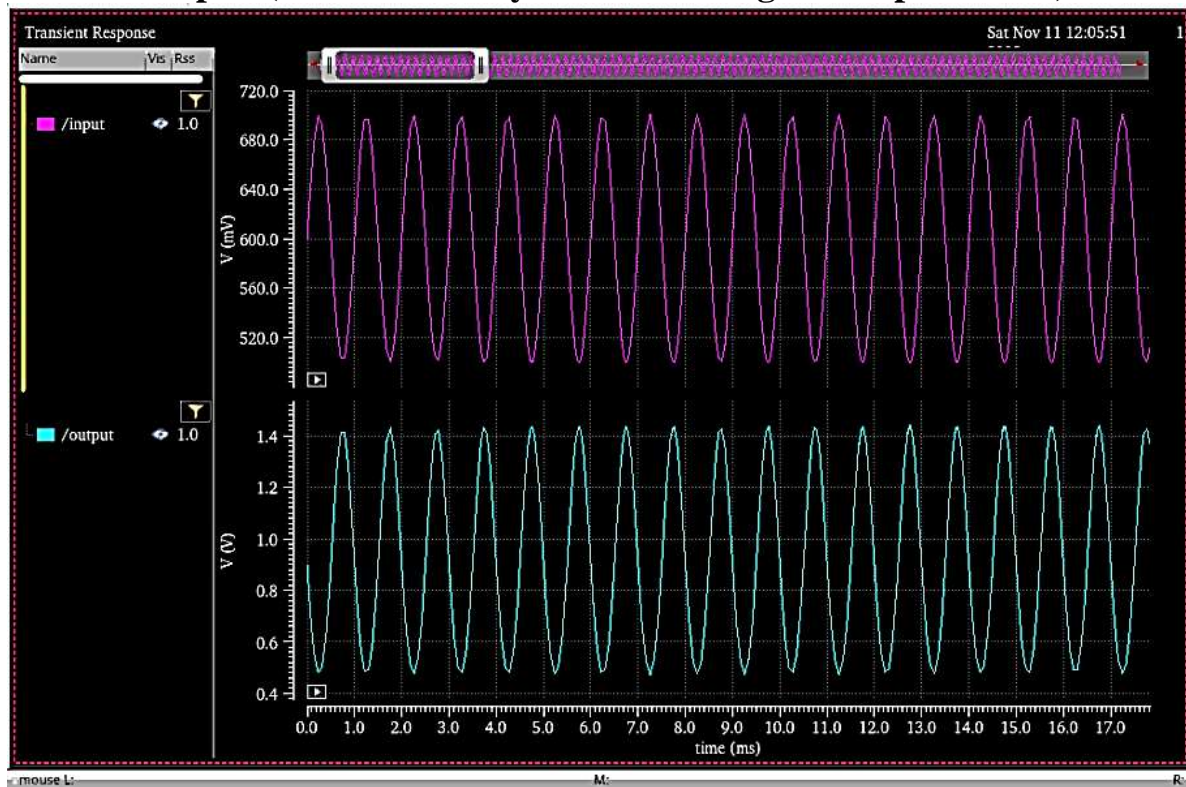Graph 3(Transient analysis for checking the amplification)



➤ Making Ac analysis to check the output voltage gain

Choosing Analyses -- ADE L (61)

Analysis	<input type="radio"/> tran	<input type="radio"/> dc	<input checked="" type="radio"/> ac	<input type="radio"/> noise
	<input type="radio"/> xf	<input type="radio"/> sens	<input type="radio"/> dcmatch	<input type="radio"/> acmatch
	<input type="radio"/> slb	<input type="radio"/> pt	<input type="radio"/> lf	<input type="radio"/> sp
	<input type="radio"/> envlp	<input type="radio"/> pss	<input type="radio"/> pac	<input type="radio"/> pstb
	<input type="radio"/> pnoise	<input type="radio"/> pxf	<input type="radio"/> psp	<input type="radio"/> qpss
	<input type="radio"/> qpac	<input type="radio"/> qpnoise	<input type="radio"/> qpxf	<input type="radio"/> qpsp
	<input type="radio"/> hfb	<input type="radio"/> hfbac	<input type="radio"/> hfbstb	<input type="radio"/> hfbnoise
	<input type="radio"/> hbfb	<input type="radio"/> hfbxf		

AC Analysis

Sweep Variable

☒ Frequency

☐ Design Variable

☐ Temperature

☐ Component Parameter

☐ Model Parameter

☐ None

Sweep Range

☒ Start-Stop

☐ Center-Span

Start: 1 Stop: 10G

Sweep Type

☒ Linear

☐ Step Size

☒ Number of Steps

Add Specific Points ☐

Add Points By File ☐

Specialized Analyses

☒ None

Enabled ☐

Options...

OK Cancel Defaults Apply Help

None

Sweep Range

☒ Start-Stop Start Stop

☐ Center-Span

Sweep Type

☒ Step Size

☐ Number of Steps


Add Specific Points ☐

Add Points By File ☐

Specialized Analyses

None ☒

Graph 4 (voltage gain)

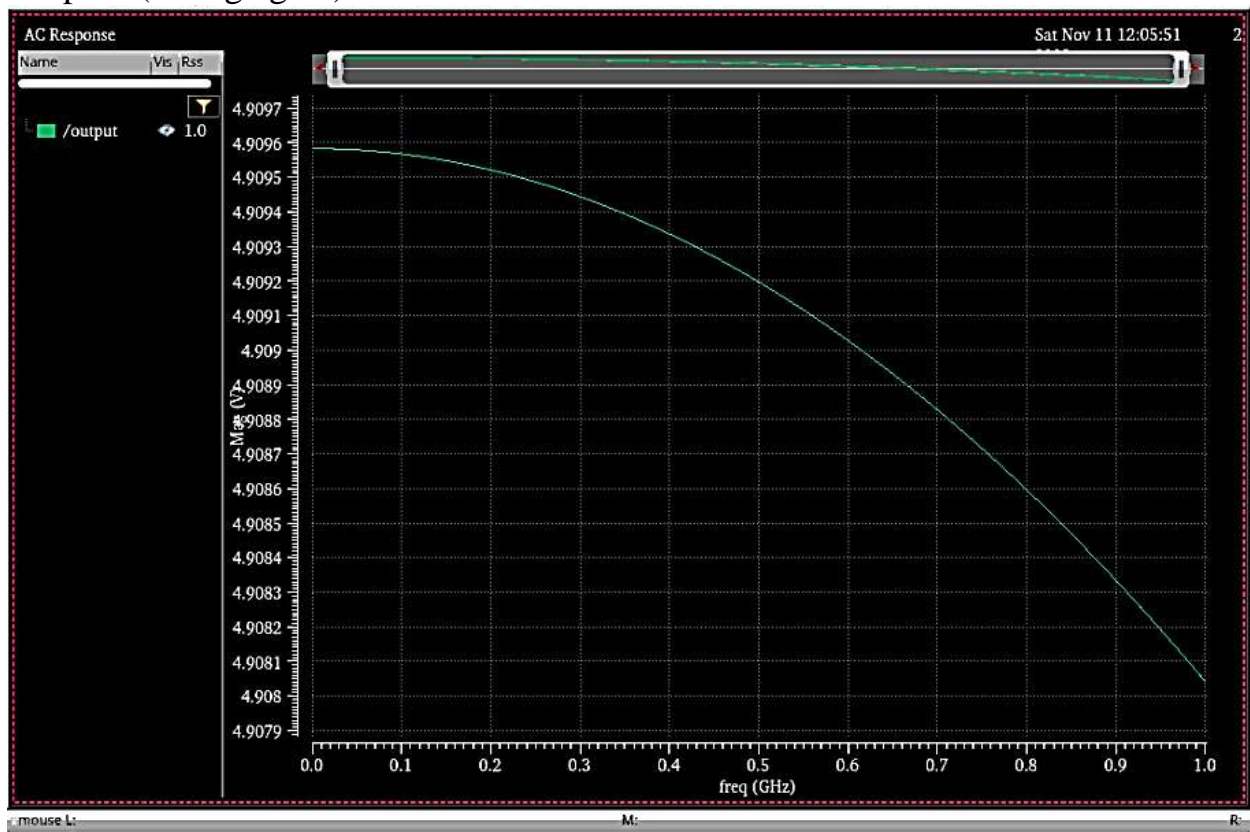

2-b Common gate

Common gate FET configuration provides a low input impedance while offering a high output impedance. As the gate is grounded, this acts as a barrier between input and output providing high levels of isolation, preventing feedback, especially at very high frequencies.

Although the voltage gain is high, the current gain is low and the overall power gain is also low when compared to the other FET circuit configurations available.

The other salient feature of this configuration is that the input and output are in phase.

Note that: although gate have to be grounded, we have to make voltage difference between gate and source = 1v so MOSFET can work

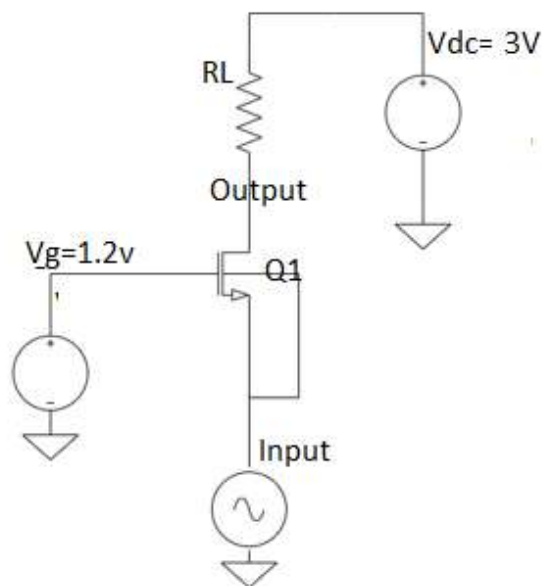


Figure 3 Common Gate Circuit

Steps:

Same properties of component (input sine wave) and setup of analysis (even transient or AC) then:-

x
Edit Object Properties

Apply To only current instance

Show ☐ system ☒ user ☒ CDF

Browse
Reset Instance Labels Display


Property	Value	Display
Library Name	analogLib	off
Cell Name	vsource	off
View Name	symbol	off
Instance Name	V0	off

Add
Delete
Modify


User Property	Master Value	Local Value	Display
lvignore	TRUE		off

CDF Parameter	Value	Display
DC voltage	750m V	off
Source type	sine	off
Frequency name 1		off
Frequency 1	1K Hz	off
Amplitude 1 (Vpk)	200m V	off
Phase for Sinusoid 1		off
Sine DC level		off
Delay time		off
Display second sinusoid	<input type="checkbox"/>	off
Display multi sinusoid	<input type="checkbox"/>	off
Display modulation params	<input type="checkbox"/>	off
Display small signal params	<input type="checkbox"/>	off
Display temperature params	<input type="checkbox"/>	off
Display noise parameters	<input type="checkbox"/>	off


SCHEMATIC 3:

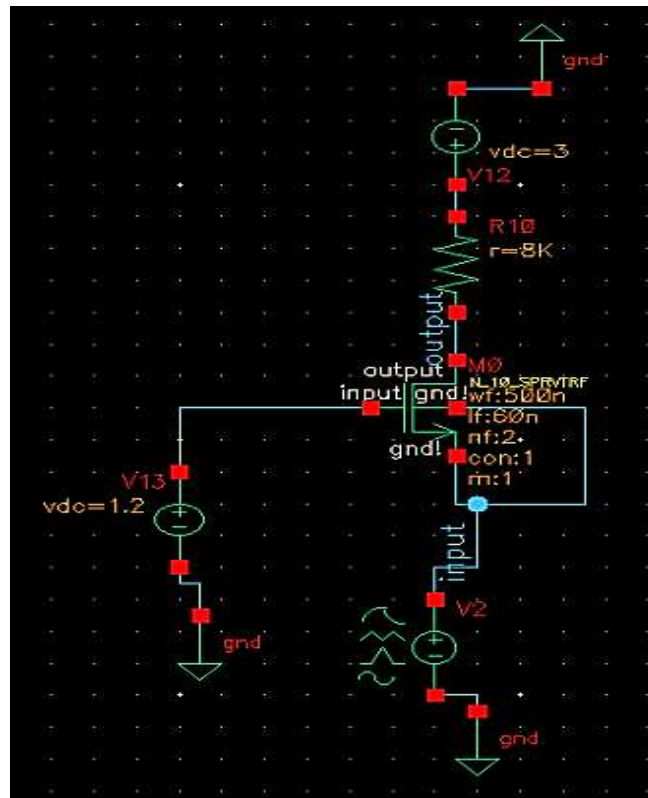

-Final Results Graph 5

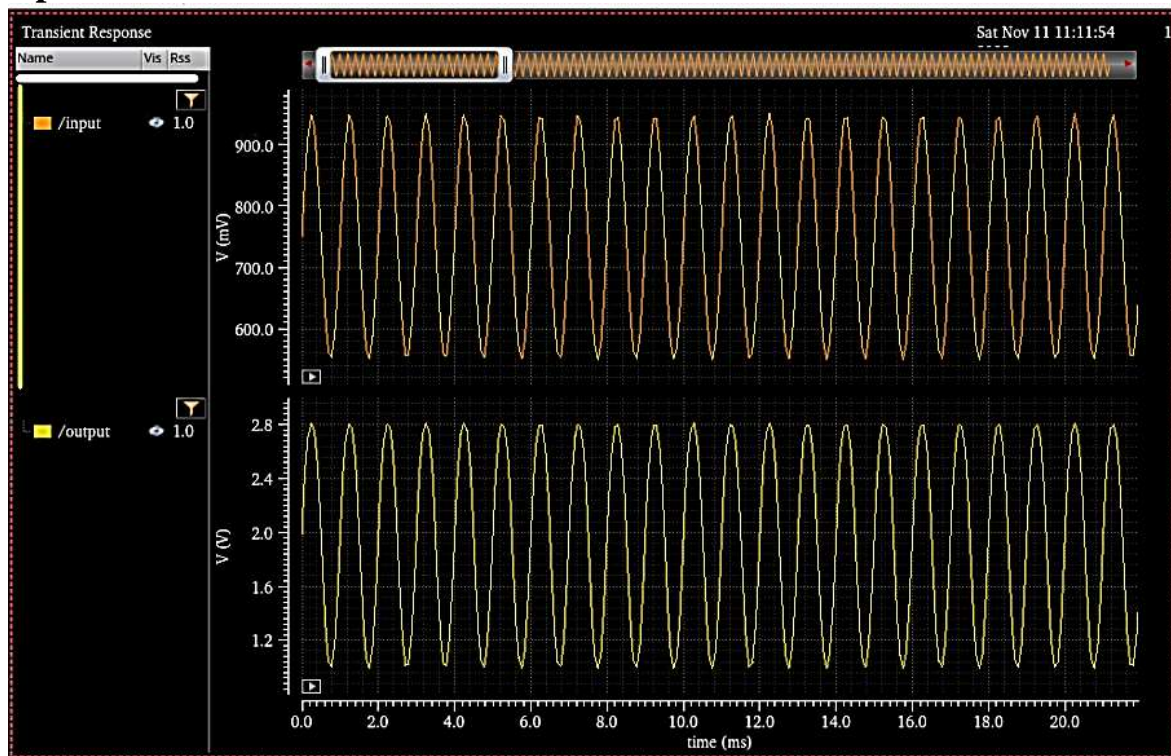

Graph 6

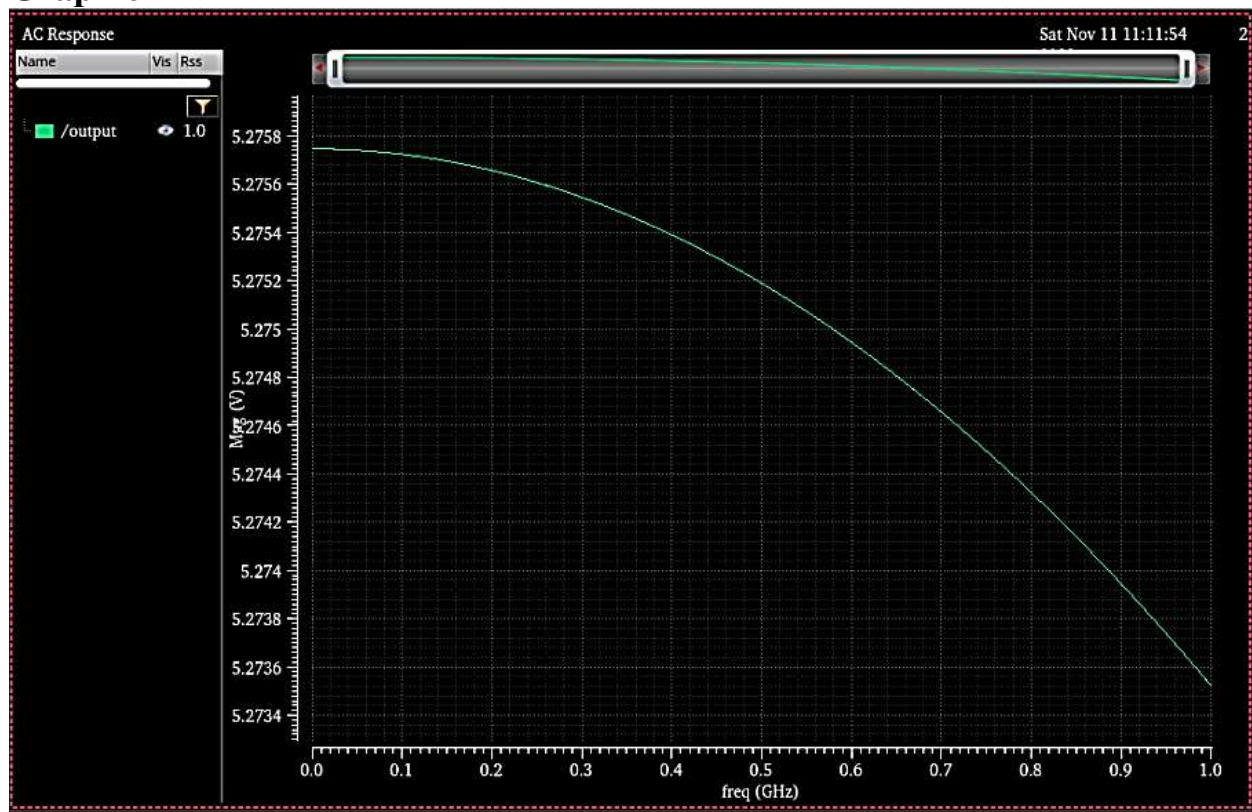

2-c Common drain

Like the transistor emitter follower, the FET source follower configuration itself provides a high level of buffering and a high input impedance. The actual input resistance of the FET itself is very high as it is a field effect device. This means that the source follower circuit is able to provide excellent performance as a buffer.

The voltage gain is unity, although current gain is high. The input and output signals are in phase.

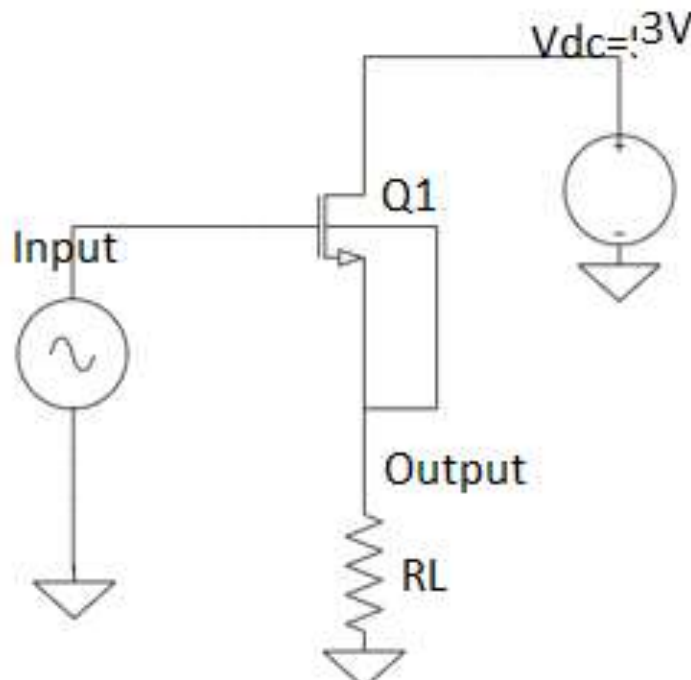


Figure 4 Common Drain Circuit

✕

Edit Object Properties

Apply To only current instance

how ☐ system ☒ user ☒ CDF

Browse Reset Instance Labels Display


Property	Value	Display
Library Name	analogLib	off
Cell Name	vsourse	off
View Name	symbol	off
Instance Name	V2	off

Add Delete Modify


User Property	Master Value	Local Value	Display
Ivsignore	TRUE		off

CDF Parameter	Value	Display
IC voltage	2 V	off
source type	sine	off
Frequency name 1		off
Frequency 1	1K Hz	off
Amplitude 1 (Vpk)	2 V	off
Phase for Sinusoid 1		off
Sine DC level		off
Delay time		off
display second sinusoid	<input type="checkbox"/>	off
display multi sinusoid	<input type="checkbox"/>	off
display modulation params	<input type="checkbox"/>	off
display small signal params	<input type="checkbox"/>	off
display temperature params	<input type="checkbox"/>	off
display noise parameters	<input type="checkbox"/>	off
multiplier		off


-SCHEMATIC 4:

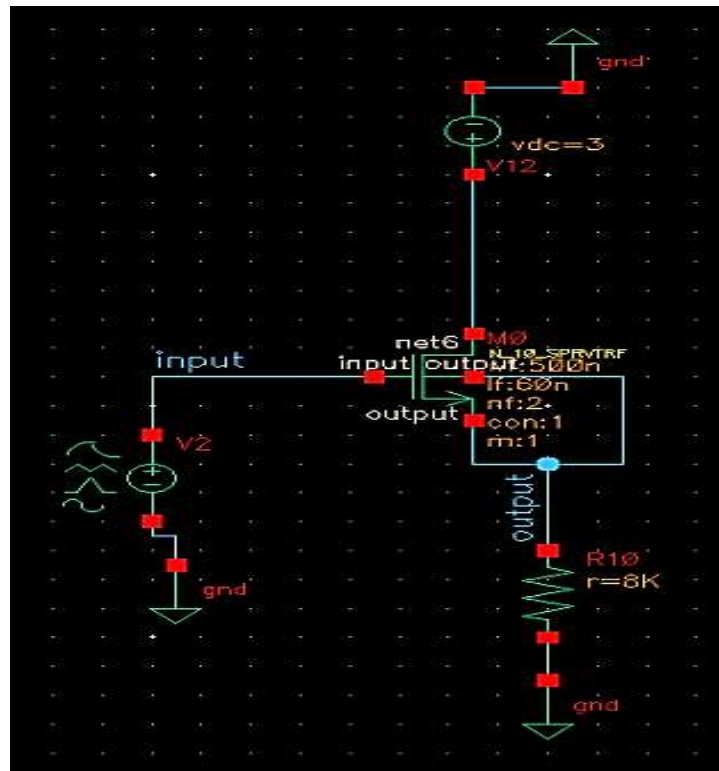

-Final Results Graph 7

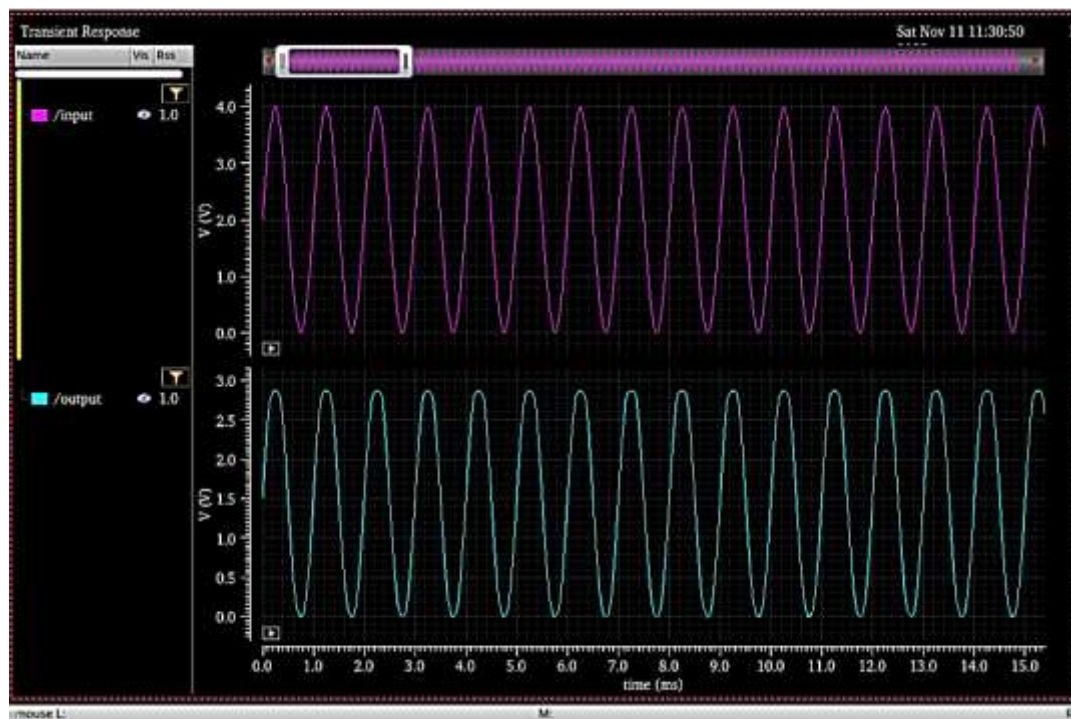


Graph 8

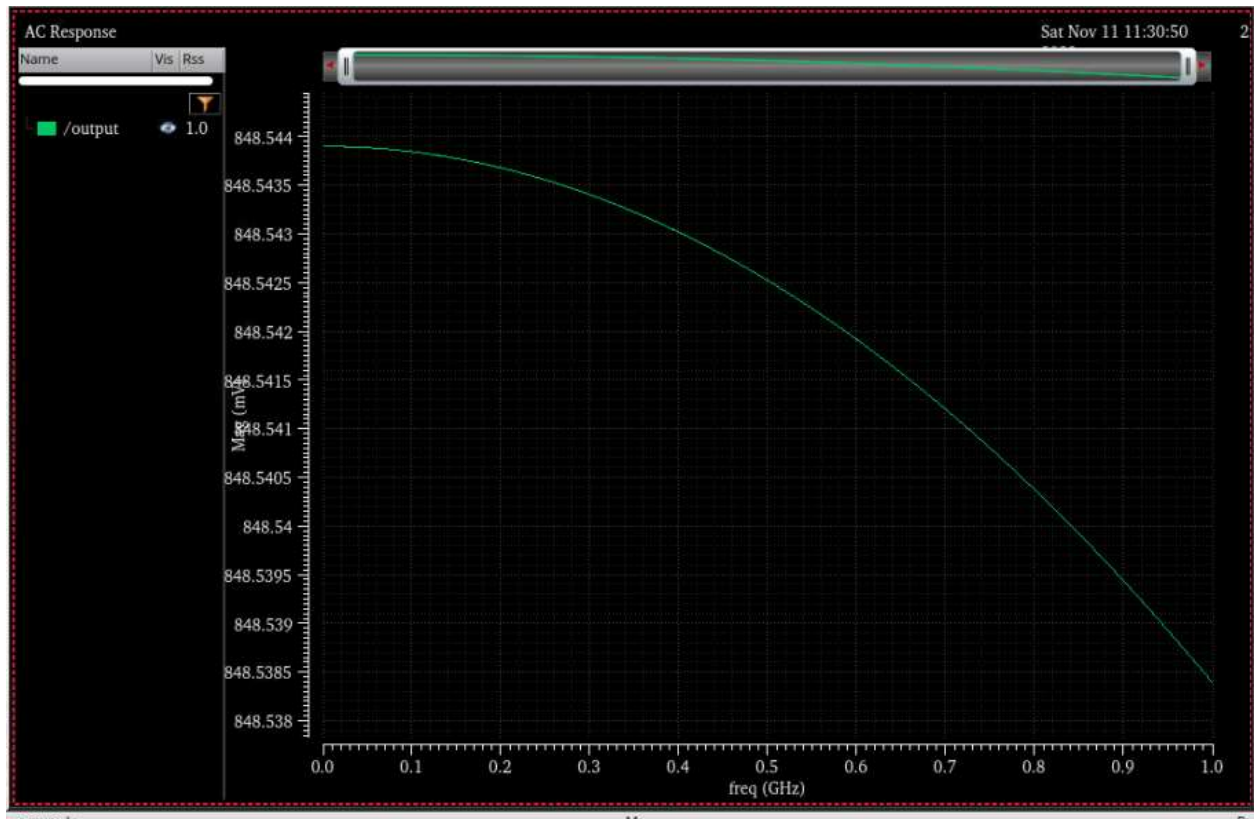

Assignment 7

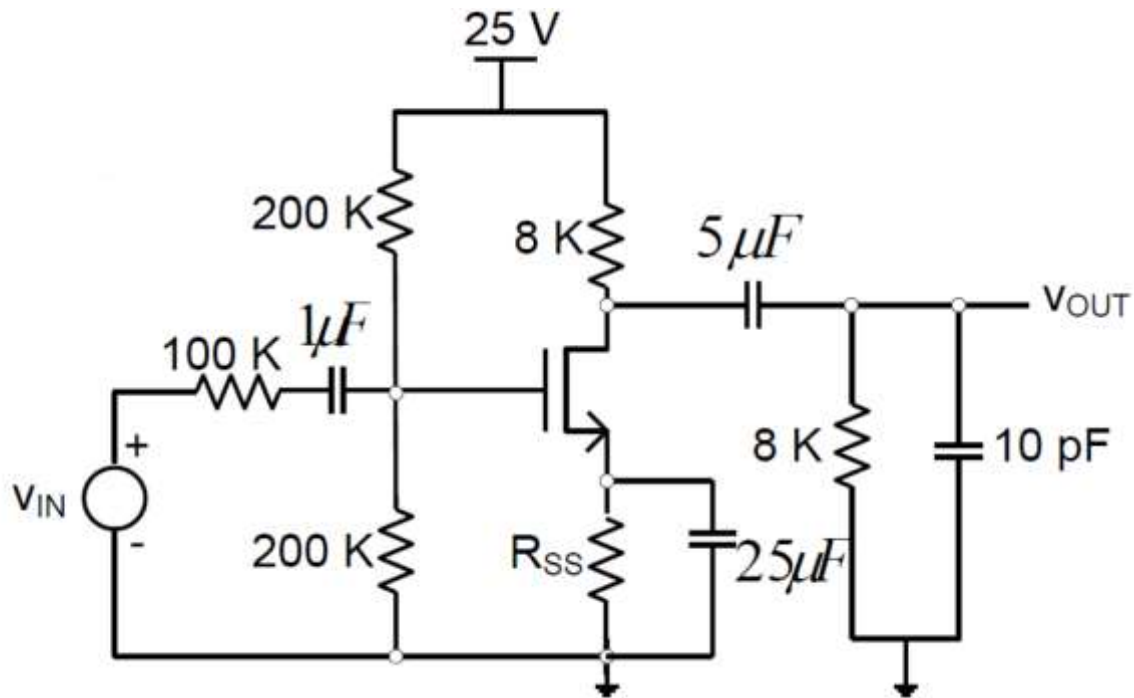Using cadence simulation build the below circuit and answer the following question using the simulator.



P.S.: Create a .scs file including the following model library at the adexl to save the parameters of the Mosfet and to make it easier to analyze.

```
save*:gm sigtype=dev
save*:gds sigtype=dev
save*:id sigtype=dev
save*:vgs sigtype=dev
save*:vds sigtype=dev
save*:vth sigtype=dev
save*:vdsat sigtype=dev
save*:gmbs sigtype=dev
save*:region sigtype=dev
```

Q1) Using DC sweep find the value of RSS that will make the current $I_D = 2.75 \text{ mA}$. Report the Graph RSS vs I_D

Q2) 2- After setting the Value of RSS Report the DC operating points of the MOSFET I_D , V_{gs} , V_{ds} , g_m , region of operation and v_{th}

Q3) Find the input resistance and output resistance of the amplifier mid-band.

Bonus 7

Q4) If it's desired to attach $100\ \Omega$ resistance instead of $8K$ load resistance and maintain the same gain of the amplifier at the same value, then what type of the amplifier stage should be inserted between this one and the load. (Justify your answer using graph simulations)