

$$\frac{V_1 - 25}{100} + \frac{V_1 - V_2}{100} + \frac{V_1 - V_2}{100} = 0$$


$$3V_1 - 2V_2 + 0 = 25 \quad (1)$$

$$\frac{V_2 - V_1}{100} + \frac{V_2 - V_3}{100} = 0$$

$$-V_1 + 2V_2 - V_3 = 0 \quad (2)$$

$$\frac{V_3 - V_2}{100} + \frac{V_3 - V_2}{100} + \frac{V_3 - 0}{100} = 0$$

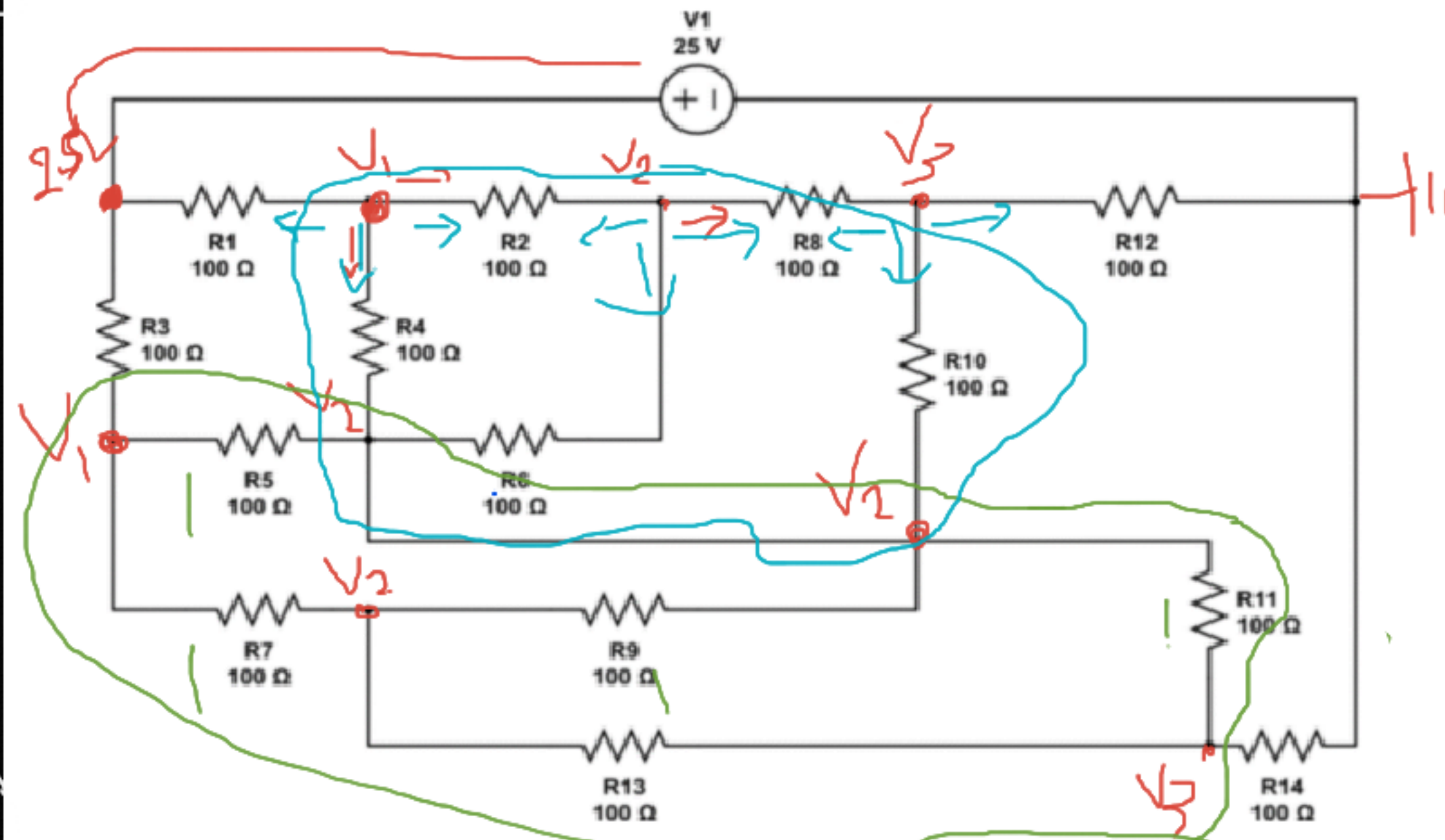
1- Using Nodal Analysis, calculate the current through each resistor and the voltage across each resistor.




$$V_2 + 3V_3 = 0 \quad (3)$$



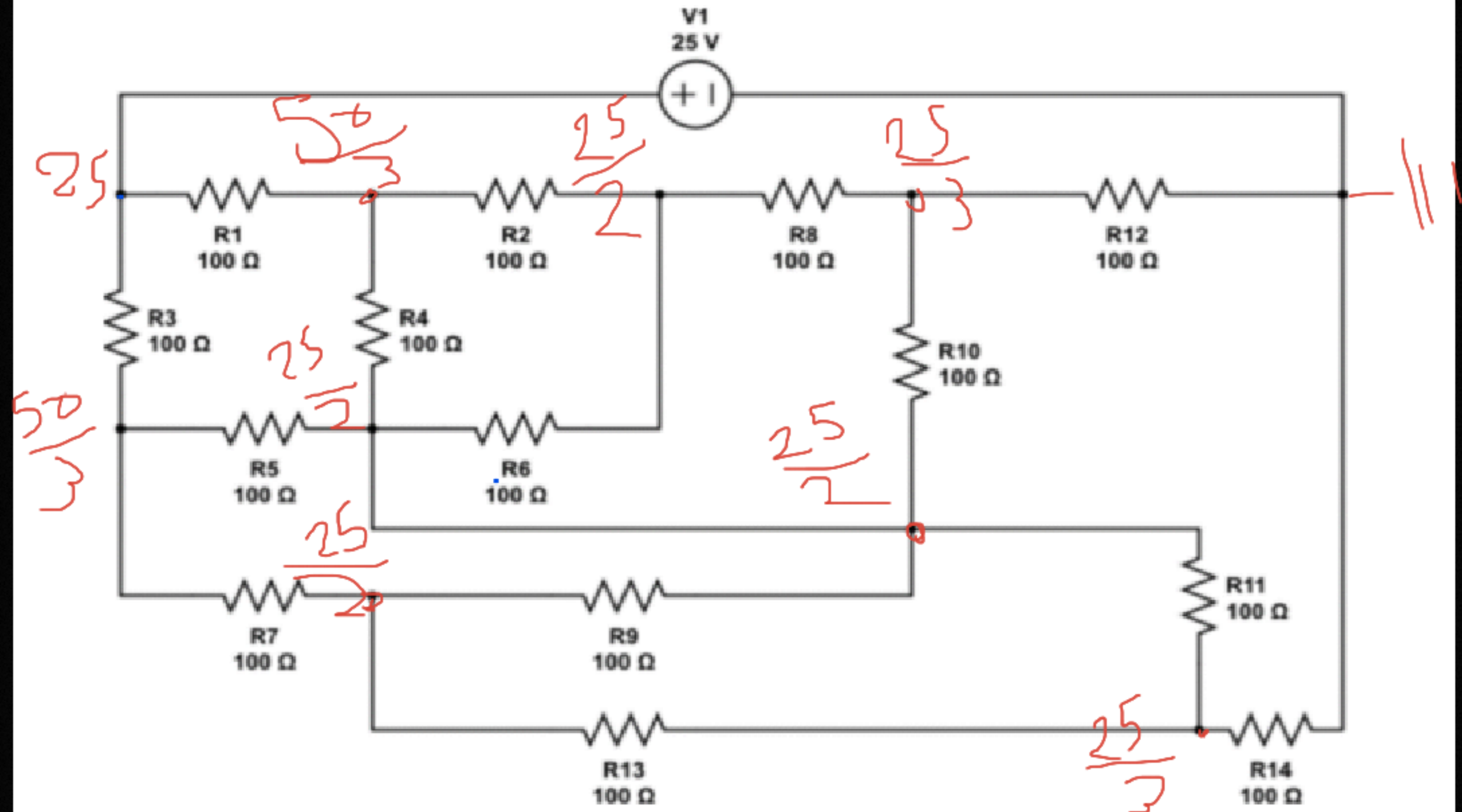1- Using Nodal Analysis, calculate the current through each resistor and the voltage across each resistor.



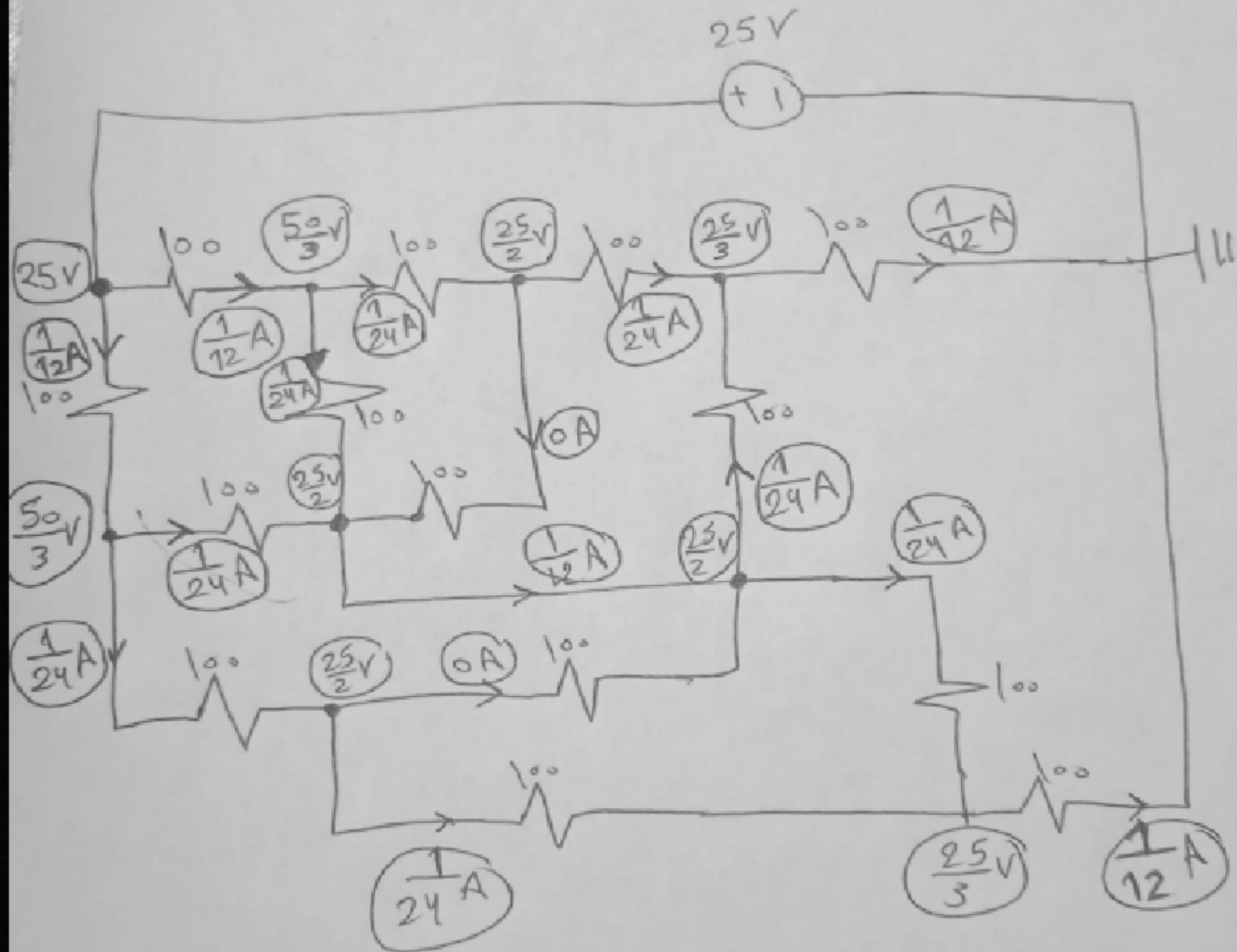



Thevenin:

$$\frac{V_1 - 710}{15} + \frac{V_1 - V_2}{5} - 0.1V_\Delta = 0 \quad (1)$$


$$\frac{V_2 - V_1}{5} + \frac{V_2 + 3i_\Delta}{8} = 0 \quad (2)$$

$$V_\Delta = 110 - V_1 \quad (3)$$

$$V_{Th} = 55V$$

2- The variable resistor  $R_O$  in the following circuit is adjusted until it absorbs maximum power from the circuit.

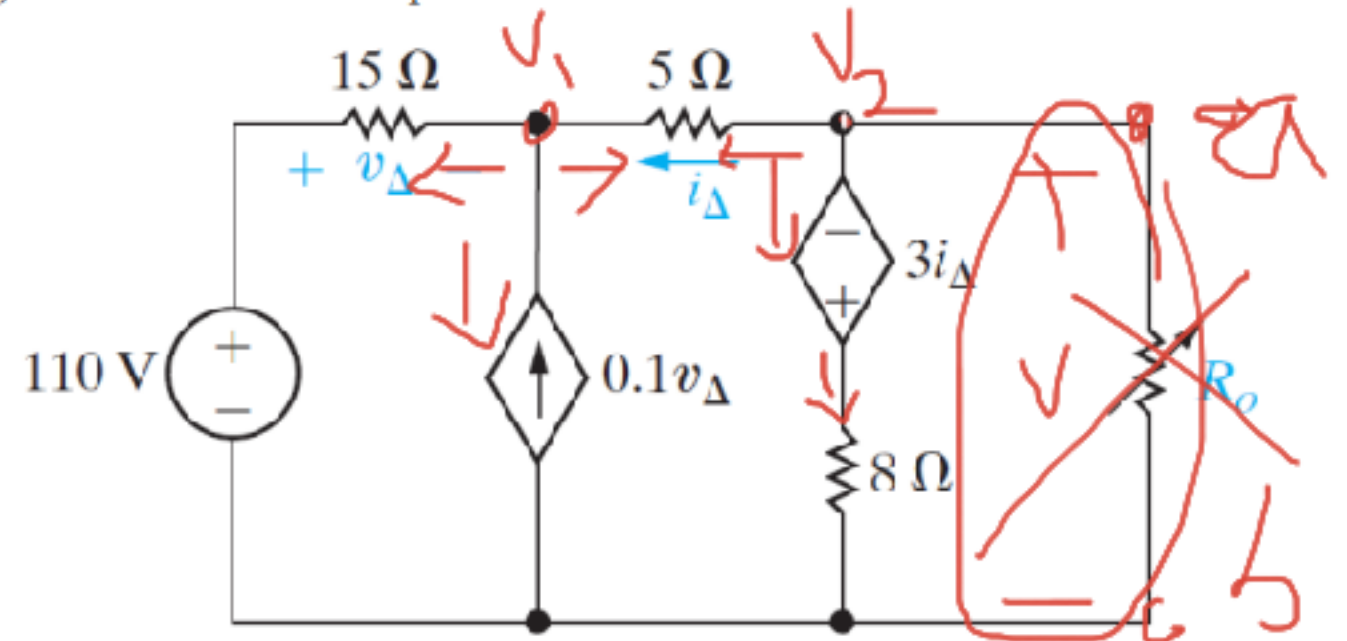
- Find the Thevenin and Norton equivalents with respect to the terminals a,b
- Find the value of  $R_O$ .
- Find the maximum power.



$$i_\Delta = \frac{V_2 - V_1}{5} \quad (4)$$



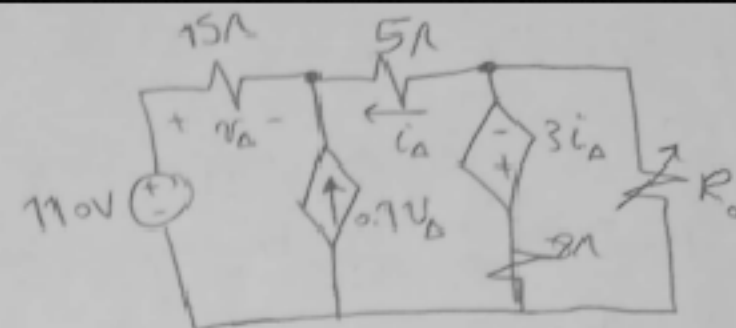- ② a) Thevenin, Norton  
 b)  $R_o = ?$   
 c) Max power




Solution

To get  $V_{th} \rightarrow$  open circuit

Nodal Analysis

$$\frac{V_1 - 110}{15} + \frac{V_1 - V_2}{5} - 0.1V_A = 0 \rightarrow (1) \quad (*15)$$
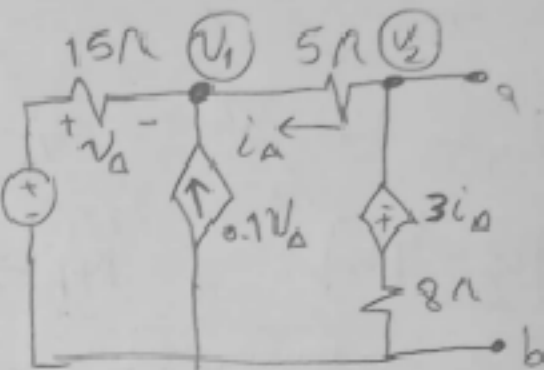
$$\frac{V_2 - V_1}{5} + \frac{V_2 + 3i_A}{8} = 0 \rightarrow (2) \quad (*40)$$



$i_A = \frac{V_2 - V_1}{5}$ ,  $V_A = 110 - V_1 \rightarrow$  Substituted in (1) & (2)

$$V_1 - 110 + 3V_1 - 3V_2 - 15 \cdot 0.1(110 - V_1) = 0$$

$$5.5V_1 - 3V_2 = 110 + 1.5 \cdot 110 \quad (I)$$

$$8V_2 - 8V_1 + V_2 + 3\left(\frac{V_2 - V_1}{5}\right) = 0 \quad (*5)$$

$$40V_2 - 40V_1 + 5V_2 + 3V_2 - 3V_1 = 0$$

$$48V_2 = 43V_1 \quad (II)$$

Solving (I) & (II)  $\rightarrow \therefore V_2 = 55V$

$\therefore V_{th} = 55V$  #



Norton  $I_N$


$$\frac{V_1 - 110}{15} + \frac{V_1 - 5}{0} = 0 \quad \text{--- } 0.1 V_\Delta = 0$$

$$V_\Delta = 110 - V_1$$

$$V_1 = 56V$$

2- The variable resistor  $R_O$  in the following circuit is adjusted until it absorbs maximum power from the circuit.

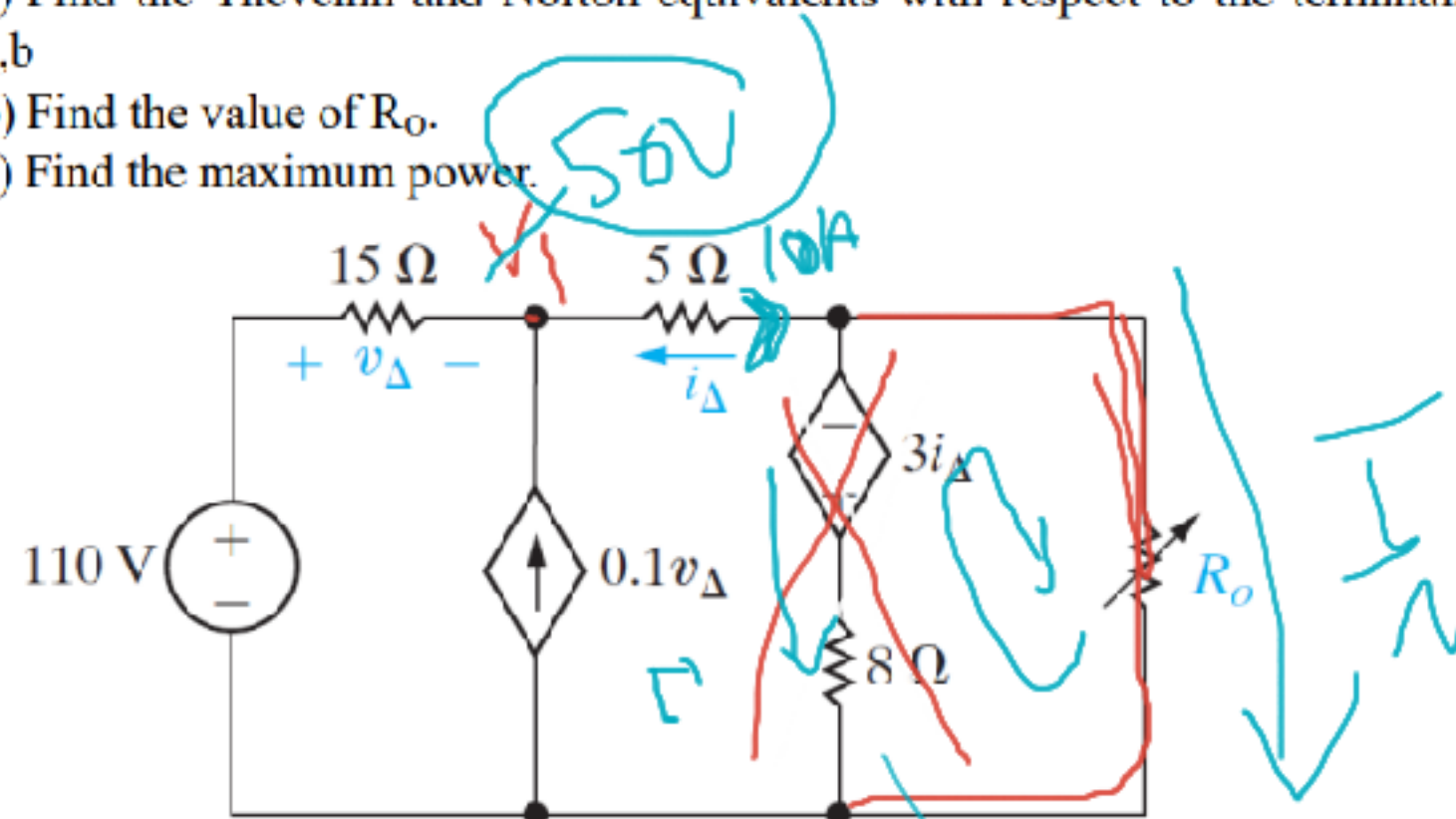- Find the Thevenin and Norton equivalents with respect to the terminals a,b
- Find the value of  $R_O$ .
- Find the maximum power.



$$I_\Delta = -10A$$

$$I = \frac{30}{8}$$

$$8I + 3I_\Delta = 0$$

$$I_N = 10 - \frac{30}{8} = 13.75A$$



$$\frac{\sqrt{I}}{R}$$

Norton:

$$\frac{V_1 - 110}{15} + \frac{V_1 - 0}{5} - 0.1 V_\Delta = 0$$

$$V_\Delta = 110 - V_1$$




$$\therefore \frac{V_1 - 110}{15} + \frac{V_1}{5} - 0.1(110 - V_1) = 0$$

$$\therefore V_1 = 50V$$

$$i_\Delta = -10A$$

$$-3i_\Delta + 8I_3 = 0 \rightarrow I_3 = \frac{-30}{8}$$
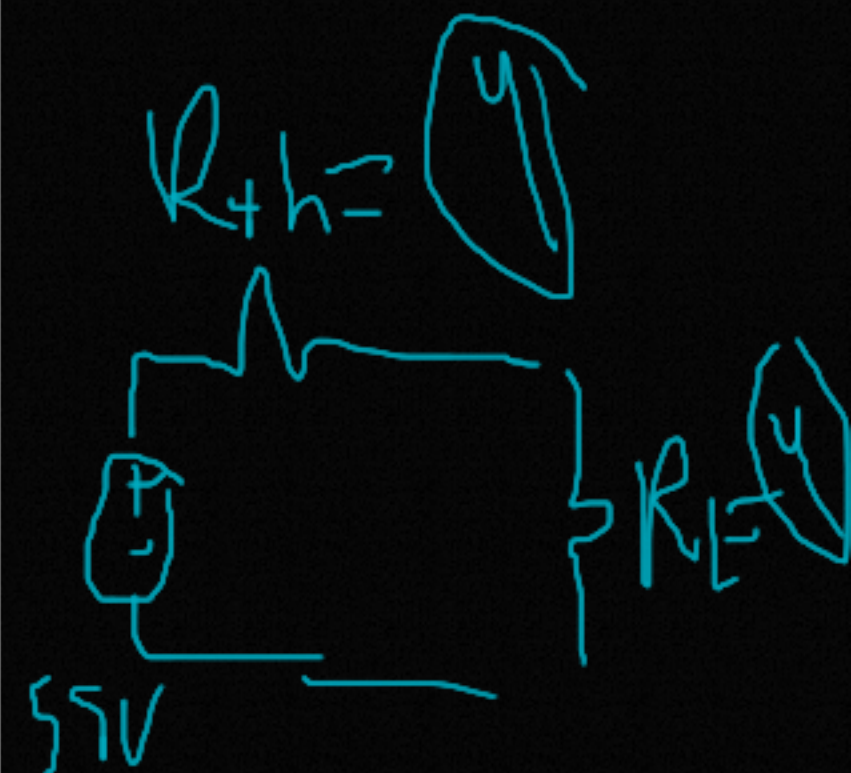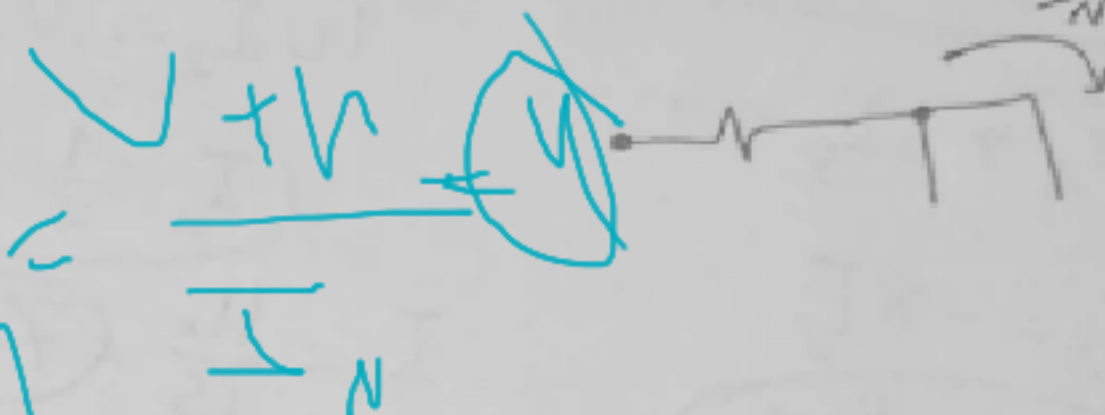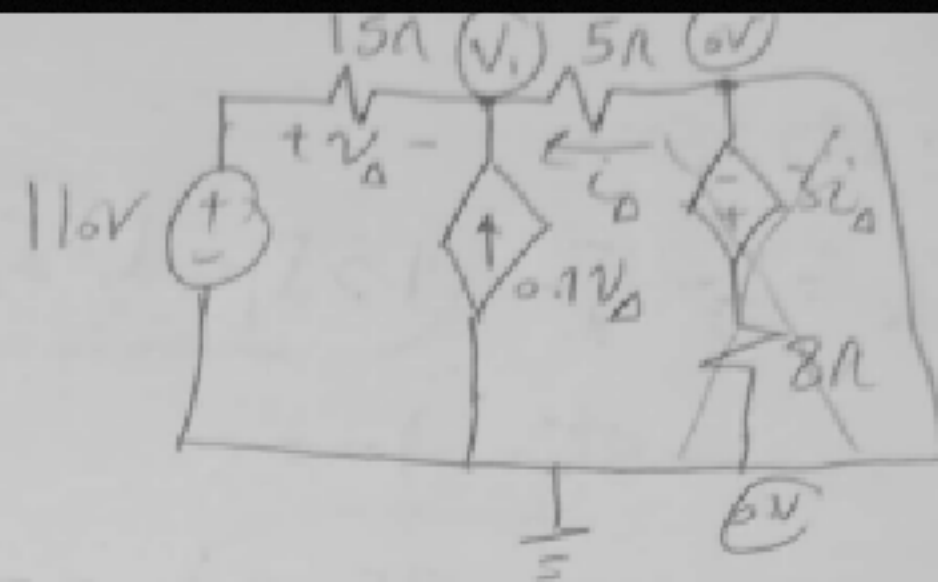
$$10 = I_N - \frac{30}{8} \rightarrow I_N = 13.75A$$



$$\frac{(55/2)^2}{4}$$

$$= \checkmark$$




$$\alpha = \frac{V_x}{V_s} = \frac{1}{5} = 0.2$$

$$\beta = \frac{V_y}{V_s} = \frac{3.75}{5} = 0.75$$

$$X = (1 - \alpha) * 480 = 384 \quad \text{or } 800$$

$$Y = (1 - \beta) * 800 = 200$$

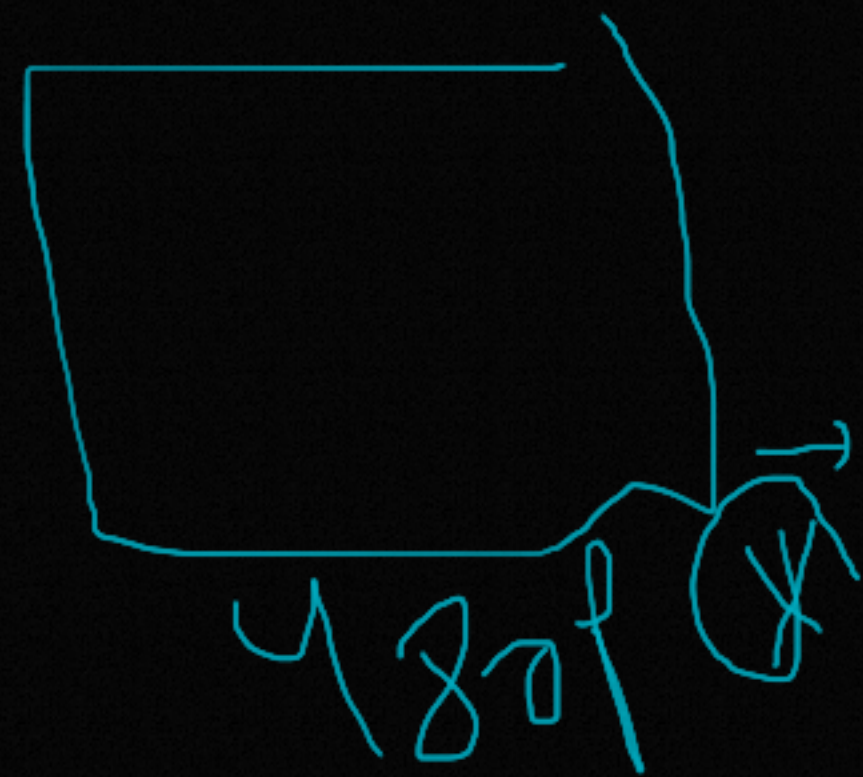

3- A resistive touch screen has 5 V applied to the grid in the x-direction and in the y-direction. The screen has 480 pixels in the x-direction and 800 pixels in the y-direction. When the screen is touched, the voltage in the x-grid is 1 V and the voltage in the y-grid is 3.75 V.)

a) Calculate the values of  $\alpha$  and  $\beta$ .

b) Calculate the x- and y-coordinates of the pixel at the point where the screen was touched.



$$\boxed{3} \quad V_x = \alpha V_s \Rightarrow \alpha = \frac{V_x}{V_s} = \frac{1}{5} = \boxed{0.2}$$

$$\textcircled{a} \quad V_y = \beta V_s \Rightarrow \beta = \frac{V_y}{V_s} = \frac{3.75}{5} = \boxed{0.75}$$

$$\textcircled{b} \quad X = (1 - \alpha) P_x = (1 - 0.2) * 480 = \boxed{384}$$

$$Y = (1 - \beta) P_y = (1 - 0.75) * 800 = \boxed{200}$$

The touch occurred in the upper right corner of the screen