




Handwritten Assignments 3

Question 1:

A resistor, denoted as R_i , is added in series with the inductor as shown in the figure on the left.

- Derive the expression for $H(s)$ where $H(s) = V_o / V_i$
- At what frequency will the magnitude of $H(j\omega)$ be maximum?
- What is the maximum value of the magnitude of $H(j\omega)$?
- At what frequency will the magnitude of $H(j\omega)$ equal its maximum value divided by $\sqrt{2}$?
- Assume a resistance of 300Ω is added in series with the 50 mH inductor in the circuit in the figure on the right. Find ω_c , $H(j0)$, $H(j\omega_c)$, $H(j0.2\omega_c)$, and $H(j5\omega_c)$.

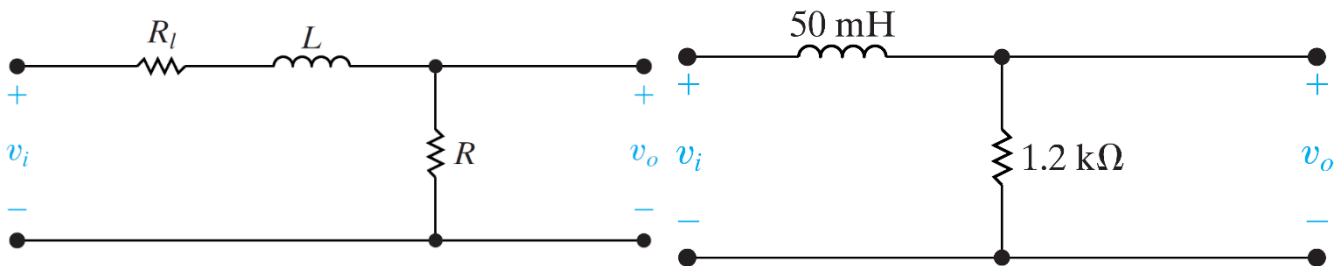

Question 2:

A bandpass filter has a center, or resonant, frequency of 50 krad/s and a quality factor of 4. Find the band-width, the upper cutoff frequency, and the lower cut-off frequency. Express all answers in kilohertz.

Question 3:

A block diagram of a system consisting of a sinusoidal voltage source, an RLC series bandpass filter, and a load is shown in Fig. P14.32. The internal impedance of the sinusoidal source is $80 + j\omega$, and the impedance of the load is $480 + j\omega$. The RLC series bandpass filter has a 20 nF capacitor, a center frequency of 50 krad/s , and a quality factor of 6.25.

- Draw a circuit diagram of the system.
- Specify the numerical values of L and R for the filter section of the system.
- What is the quality factor of the interconnected system?
- What is the bandwidth (in hertz) of the interconnected system?

