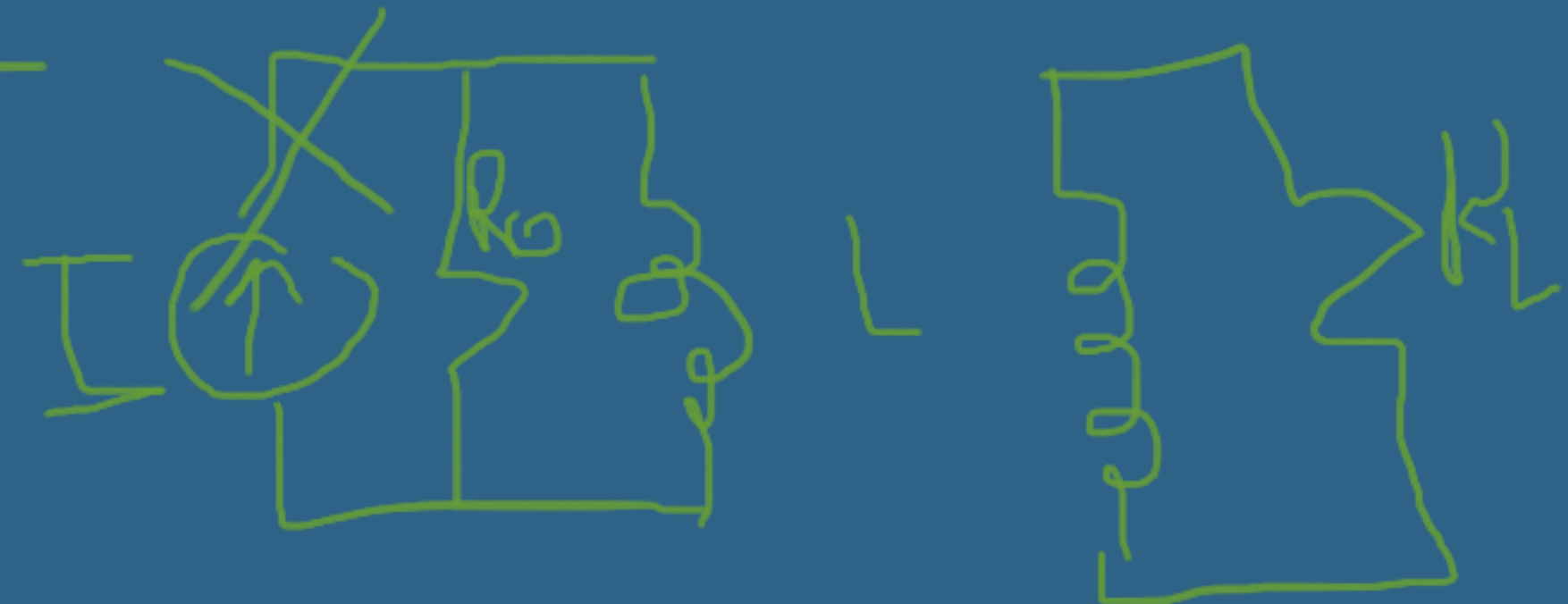


Response of RL and RC circuits

Magnetic

→ electric

- we established that inductors and capacitors can store energy.
- We analyze RL and RC circuits for I & V \Rightarrow when energy is either released or acquired by an inductor or capacitor in response to an abrupt change in a dc voltage or current source.
- Natural Response: When an inductor or capacitor is abruptly disconnected from its dc source, we find I & V that arise when stored energy in an inductor or capacitor is suddenly released to a resistive network.
- Step Response: We find the I & V that arise when energy is being acquired by an inductor or capacitor when a dc voltage or current source is suddenly applied



Natural Response of RL and RC circuits

- We assume that the independent current source generates a constant current I_s and that the switch has been in a closed position for a long time.

Therefore, before the stored energy is released,

$$L \frac{di}{dt} + Ri = 0,$$




- The inductor behaves like a short circuit.
- The whole current is in inductive branch and No current in R or R_o.

$$i(t) = I_0 e^{-(R/L)t}, \quad t \geq 0.$$

$$\tau = \frac{L}{R}$$

- The time constant is an important parameter for first order circuits. You can express the time elapsed after switching as an integer multiple of t .
- one-time constant after the inductor begins releasing its stored energy to the resistor, the current has been reduced to approximately 0.37 of its initial value.

t	$e^{-t/\tau}$	t	$e^{-t/\tau}$
τ	3.6788×10^{-1}	6τ	2.4788×10^{-3}
2τ	1.3534×10^{-1}	7τ	9.1188×10^{-4}
3τ	4.9787×10^{-2}	8τ	3.3546×10^{-4}
4τ	1.8316×10^{-2}	9τ	1.2341×10^{-4}
5τ	6.7379×10^{-3}	10τ	4.5400×10^{-5}

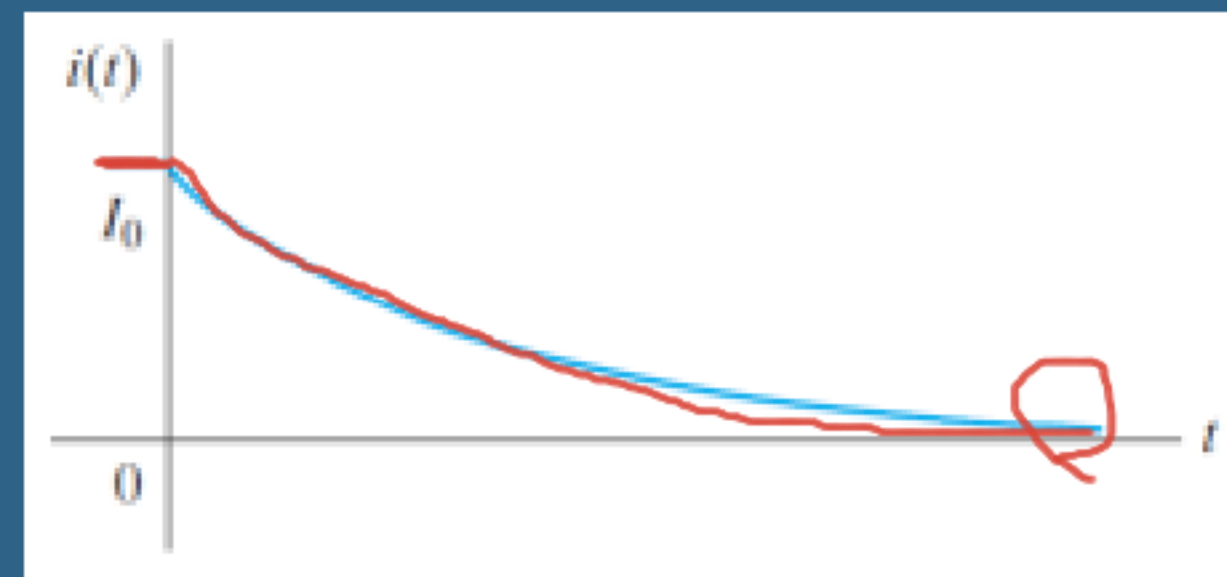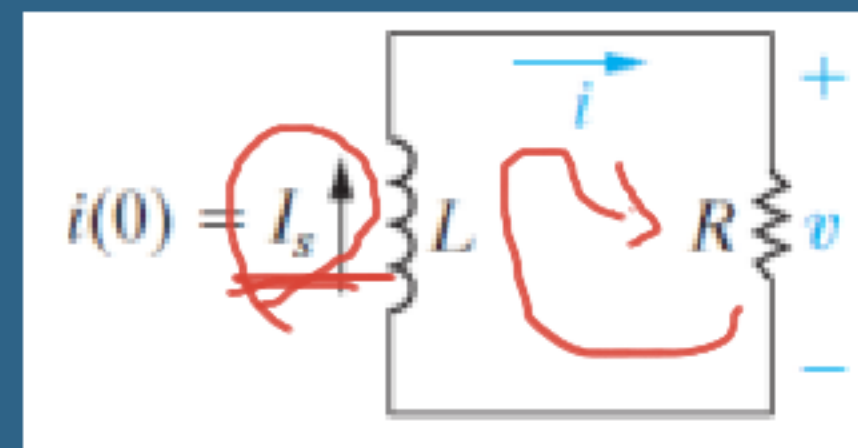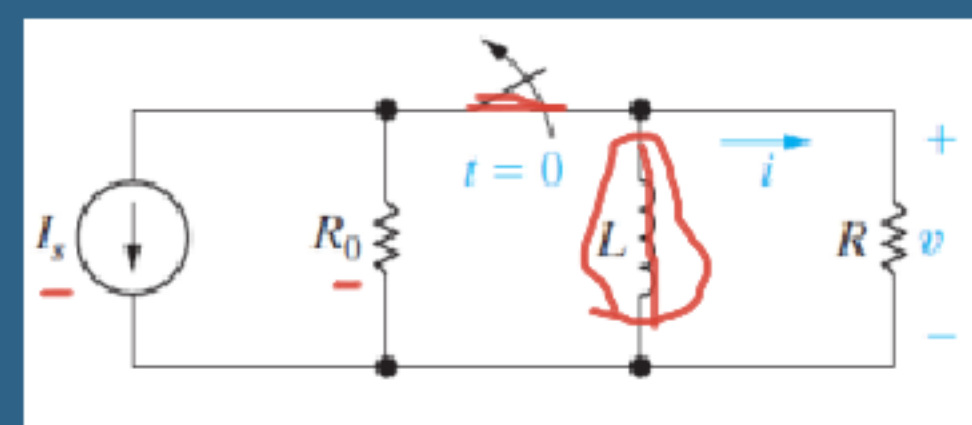

$$L \frac{di}{dt} + Ri = 0$$

$$L \frac{di}{dt} = -Ri$$

$$L \frac{di}{dt} dt = -Ri dt$$

$$\int_{i_0}^i \frac{1}{i} di = \int_0^t \frac{-R}{L} dt$$

$$\ln\left(\frac{i}{i_0}\right) = \frac{-R}{L} t$$

$$\ln(i) - \ln(i_0) = \frac{-R}{L} t$$

$$\ln\left[\frac{i(t)}{i_0}\right] = \frac{-R}{L} t$$

$$\frac{i(t)}{i_0} = e^{\frac{(-R/L)t}{-R/L}} = e^{-\frac{R}{L}t}$$

$$i(t) = i_0 e^{-\frac{R}{L}t}$$

Natural Response of RL and RC circuits

Steps:



- 1- Determine i_o (usually @ $t < 0$)
- 2- Calculate time constant (τ) ==> don't forget Req
- 3- Write equation of Inductor
- 4- Calculate any required quantity.

Solution

$$\begin{aligned} \rightarrow i_L &= 20 \text{ A} \\ \rightarrow \tau &= ? \Rightarrow \frac{L}{R} = \frac{2}{10} = 0.2 \text{ s} \\ R_{eq} &= (10 \parallel 40) + 2 = 10 \Omega \\ \rightarrow i_L(t) &= I_0 e^{-t/\tau} = 20 e^{-5t} \end{aligned}$$

The switch in the circuit shown in Fig. 7.6 has been closed for a long time before it is opened at $t = 0$. Find

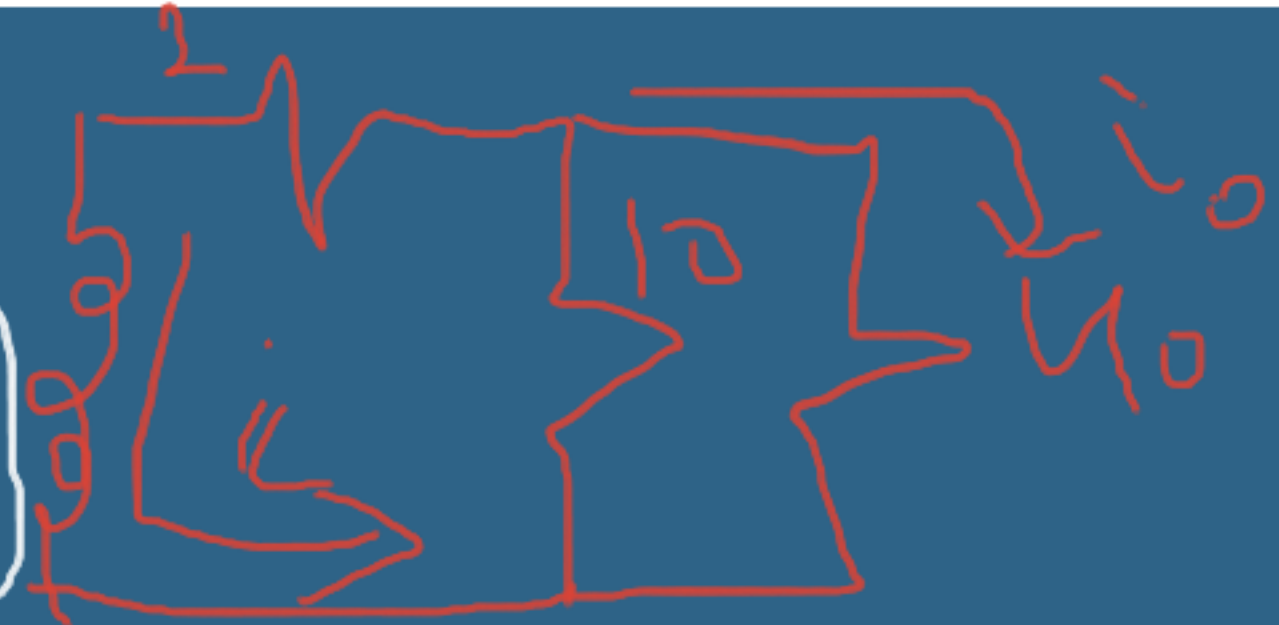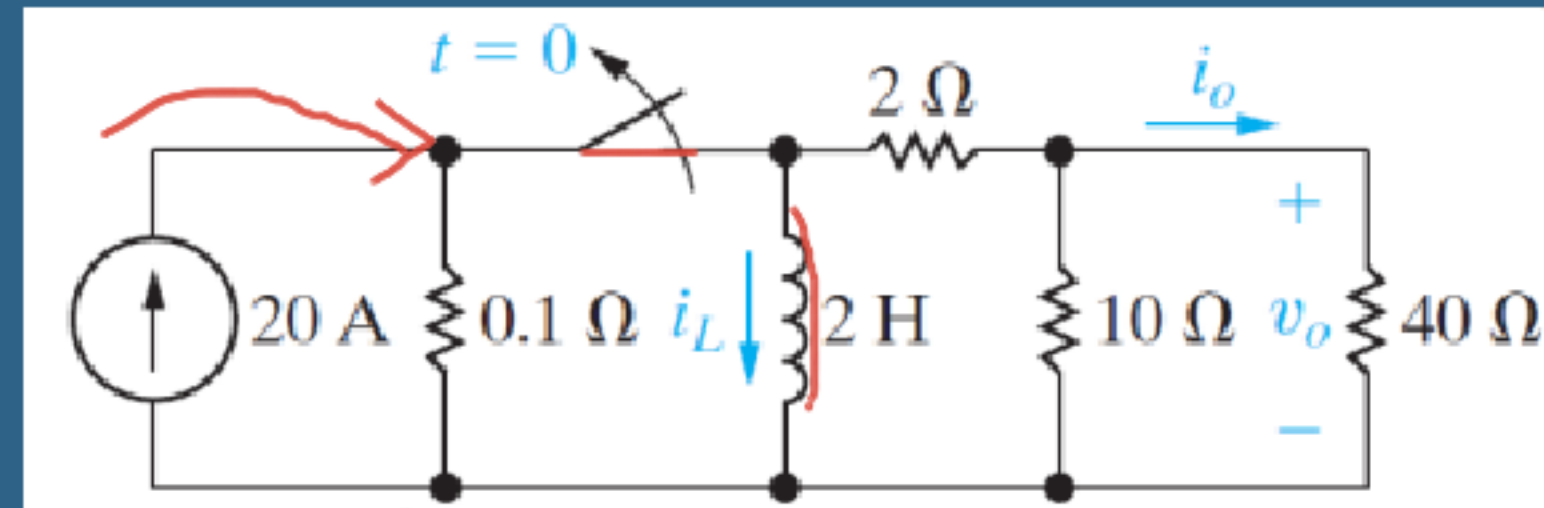- a) $i_L(t)$ for $t \geq 0$, ✓
- b) $i_o(t)$ for $t \geq 0^+$,
- c) $v_o(t)$ for $t \geq 0^+$,
- d) the percentage of the total energy stored in the 2 H inductor that is dissipated in the 10 Ω resistor.




$$I_0 = \frac{10}{10 + 40} (I_s - 1)$$

$$= -4 e^{-5t}$$

$$v_o(t) = i_o(t) R = -16 e^{-5t} \text{ V}$$

$$P_{10\Omega} = \frac{V_o^2}{10} = 256 e^{-10t} \text{ watt}$$
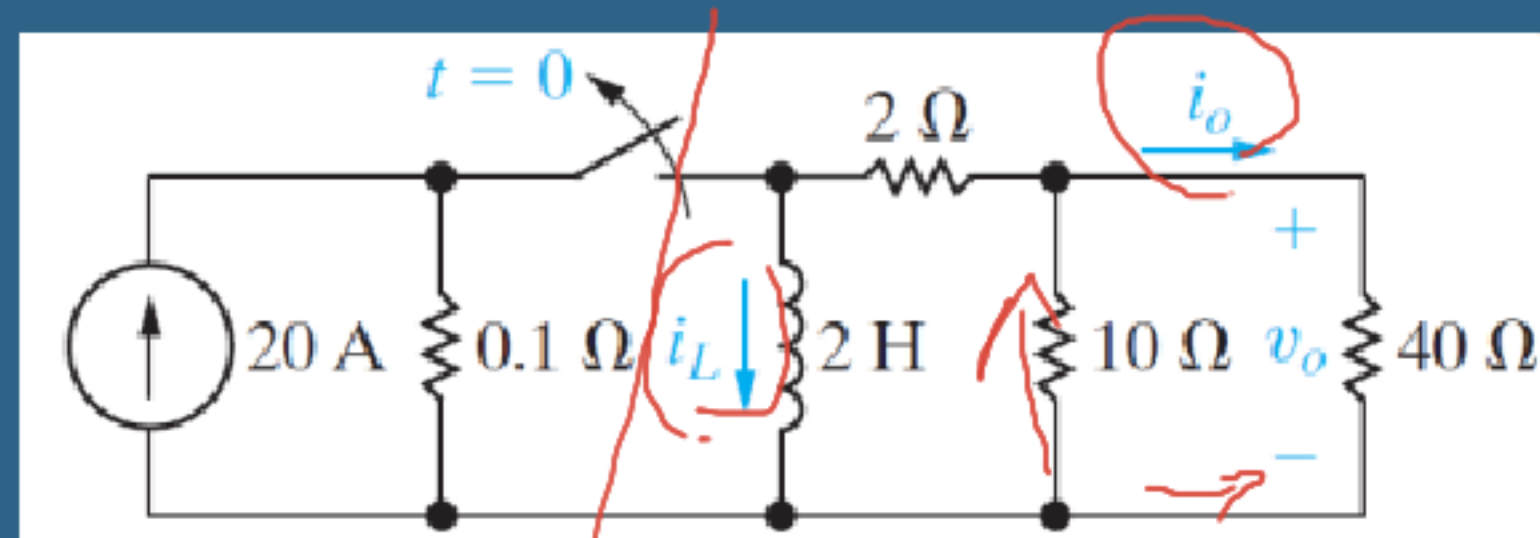
$$W_{10\Omega} = \int_0^{\infty} P dt = 256 \text{ J}$$



$$W = \int p dt$$

$$P = \frac{dW}{dt}$$

$$W(0) = \frac{1}{2} L i_o^2$$

$$= \frac{1}{2} (2) (20)^2 = 400 \text{ J}$$

The natural response of an RC Circuit


$$C \frac{dv}{dt} + \frac{v}{R} = 0$$

KCL


$$C \frac{dv}{dt} = -\frac{v}{R}$$

$$\frac{1}{v} dv = -\frac{1}{RC} dt$$


$$v(t) = v_0 e^{-t/\tau}$$

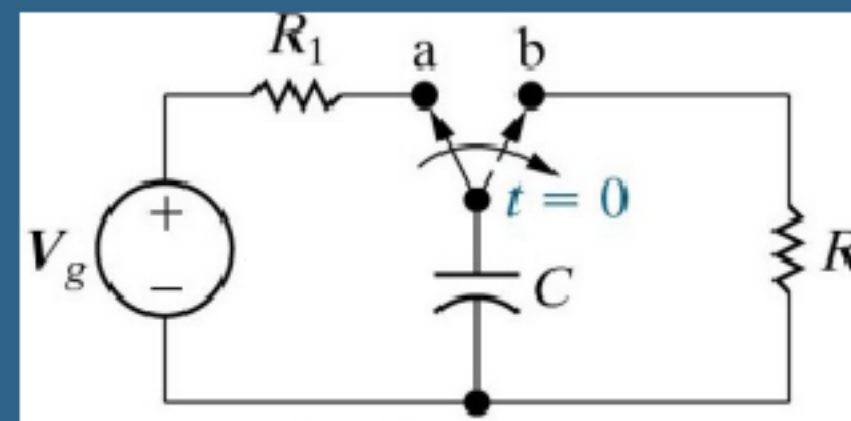

$$\tau = RC$$

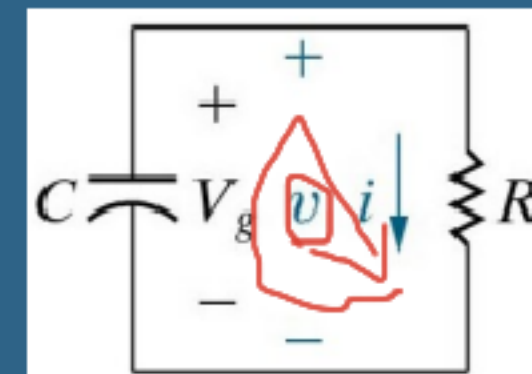

$$v(t) = V_0 e^{-t/\tau}$$

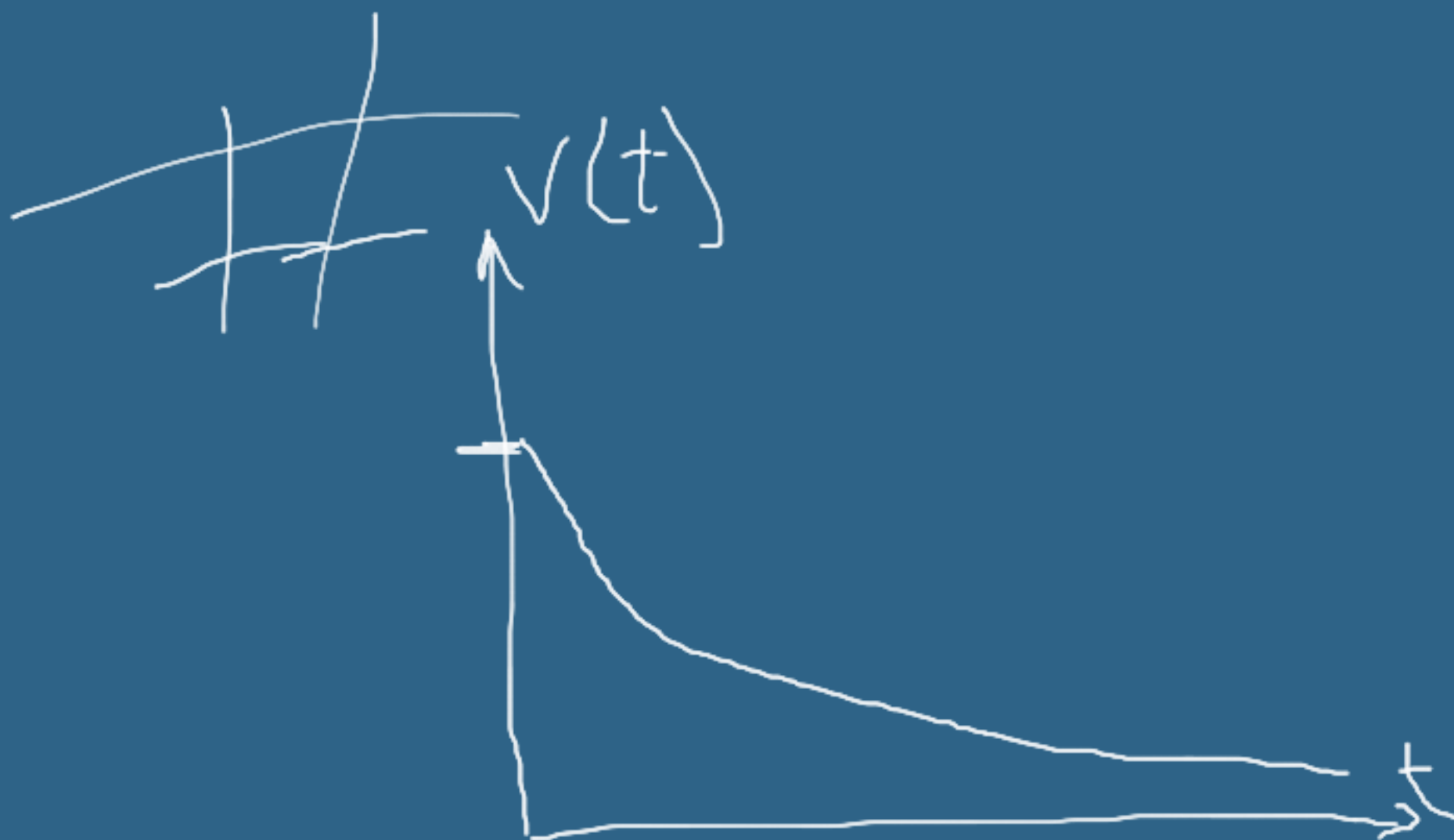


The natural response of an RC Circuit

Steps:

- 1- Determine V_0 (usually @ $t < 0$)
- 2- Calculate time constant (τ) ==> don't forget Req
- 3- Write equation of ~~Inductor~~ V_C
- 4- Calculate any required quantity.

The switch in the circuit shown in Fig. 7.15 has been in position x for a long time. At $t = 0$, the switch moves instantaneously to position y . Find

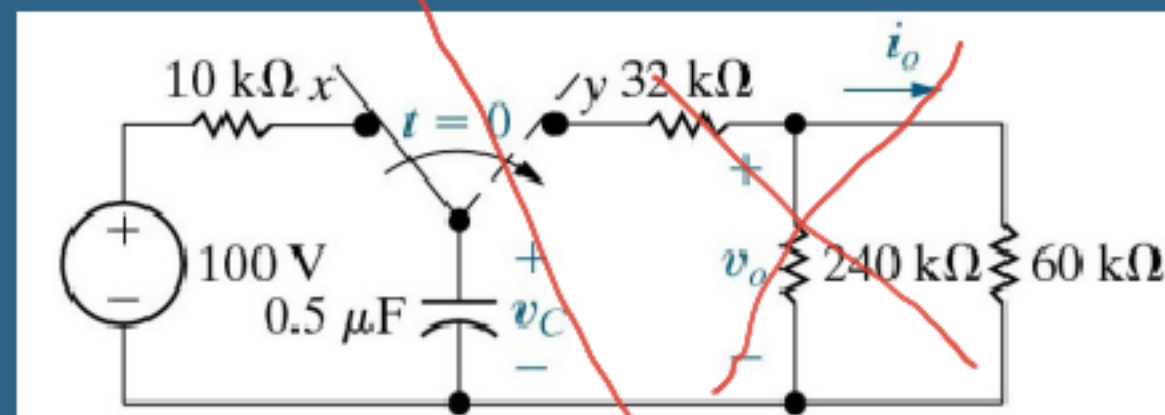- a) $v_C(t)$ for $t \geq 0$,
- b) $v_o(t)$ for $t \geq 0^+$,
- c) $i_o(t)$ for $t \geq 0^+$, and
- d) the total energy dissipated in the $60 \text{ k}\Omega$ resistor.



Handwritten calculations:


$$\rightarrow V_0 = 100 \text{ V}$$

$$\rightarrow \tau = ? \rightarrow R_{eq} = 60 \parallel 240 + 32 = 80 \text{ k}\Omega$$

$$R_C = 10 \text{ k}\Omega$$

$$\rightarrow V_C(t) = 100 e^{-25t}$$
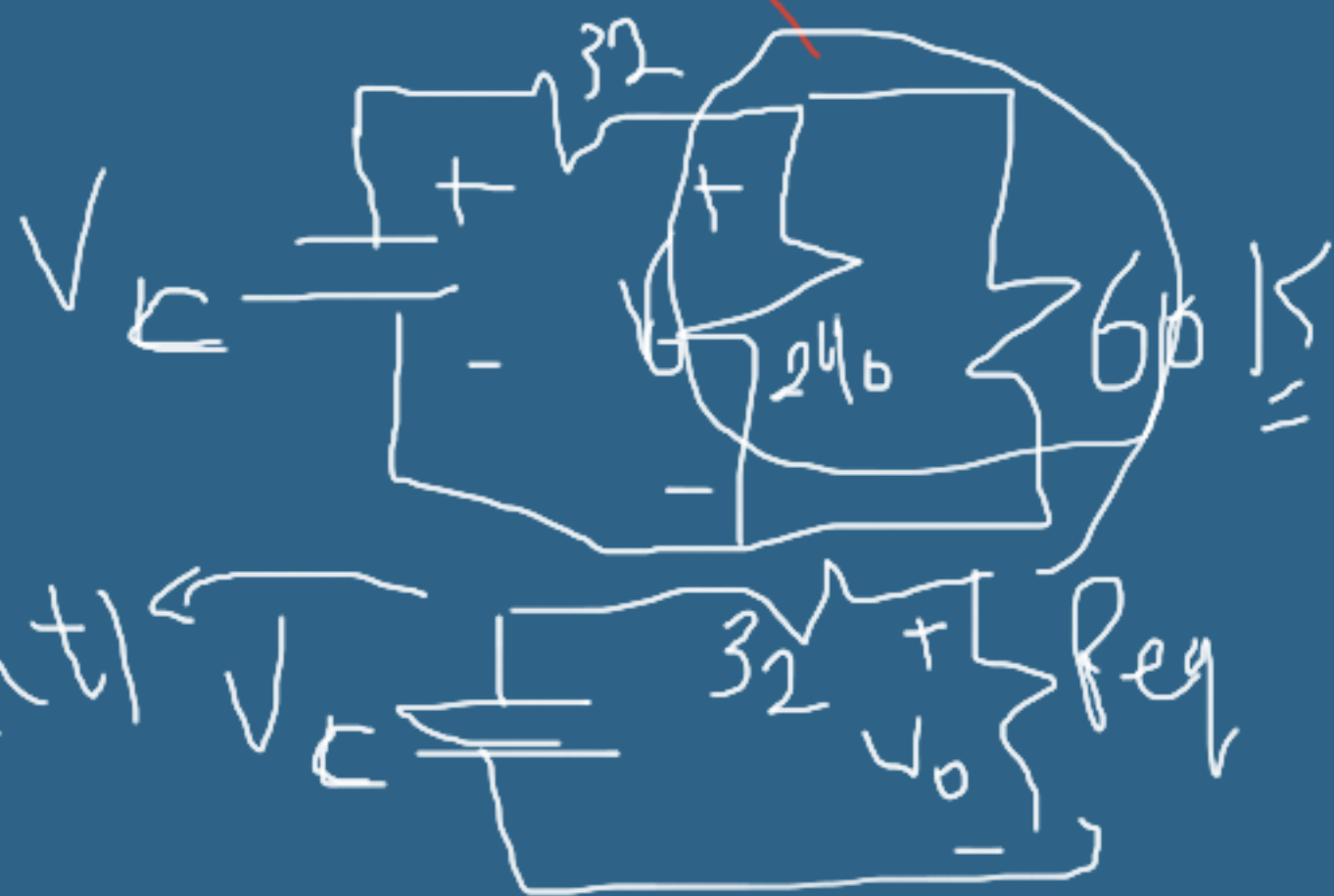
$$V_o(t) = \frac{240 \parallel 60}{240 \parallel 60 + 32} V_C(t)$$



$$i_{out}(t) = \frac{v_{out}(t)}{60k\Omega} = \boxed{e^{-25} \text{ mA}}$$

$$P_{60k\Omega} = i_{out}^2 R = \boxed{60 e^{-50t} \text{ watt}}$$

$$W_{60k\Omega} = \int_0^{\infty} P dt = \boxed{1.2 \text{ mJ}} \quad \#$$