

## Delta-to-Y Equivalent Circuit (simplifying techniques)


proof:

Let's assume:

$$R_{ab} = (R_a + R_b) \parallel R_c = R_1 + R_2 \quad ①$$

$$R_{bc} = (R_b + R_c) \parallel R_a = R_2 + R_3 \quad ②$$
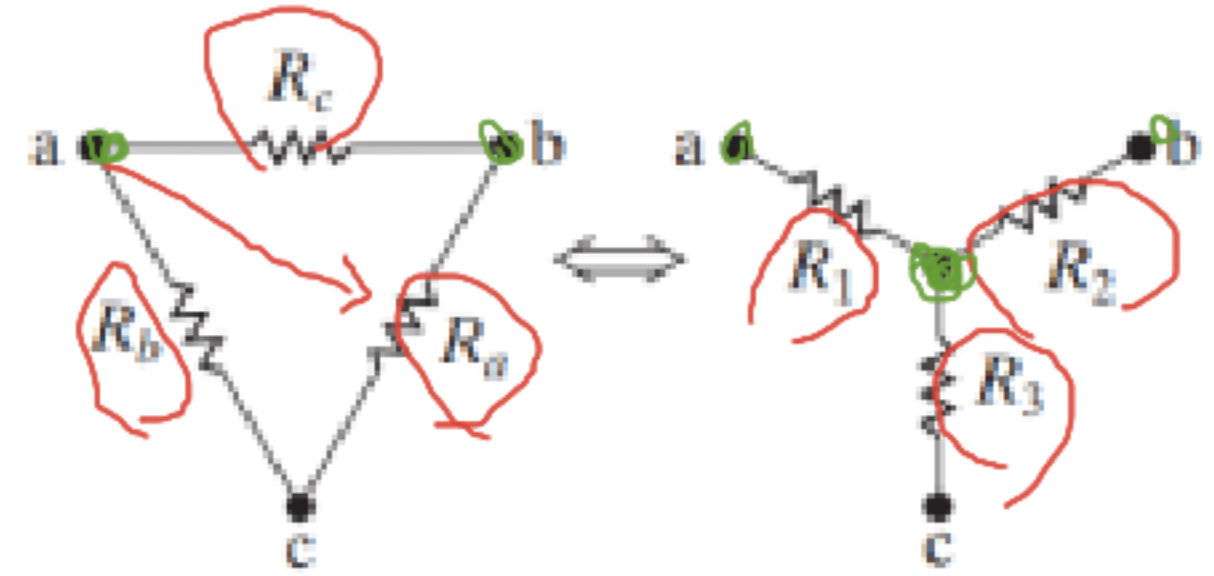
$$R_{ca} = (R_c + R_a) \parallel R_b = R_1 + R_3 \quad ③$$



$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c}$$

$$R_2 = \frac{R_c R_a}{R_a + R_b + R_c}$$


$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

# Proof of Delta to Y

$$R_{ab} = (R_a + R_b) \parallel R_c = R_1 + R_2 \quad (1)$$

$$R_{bc} = (R_b + R_c) \parallel R_a = R_2 + R_3 \quad (2)$$
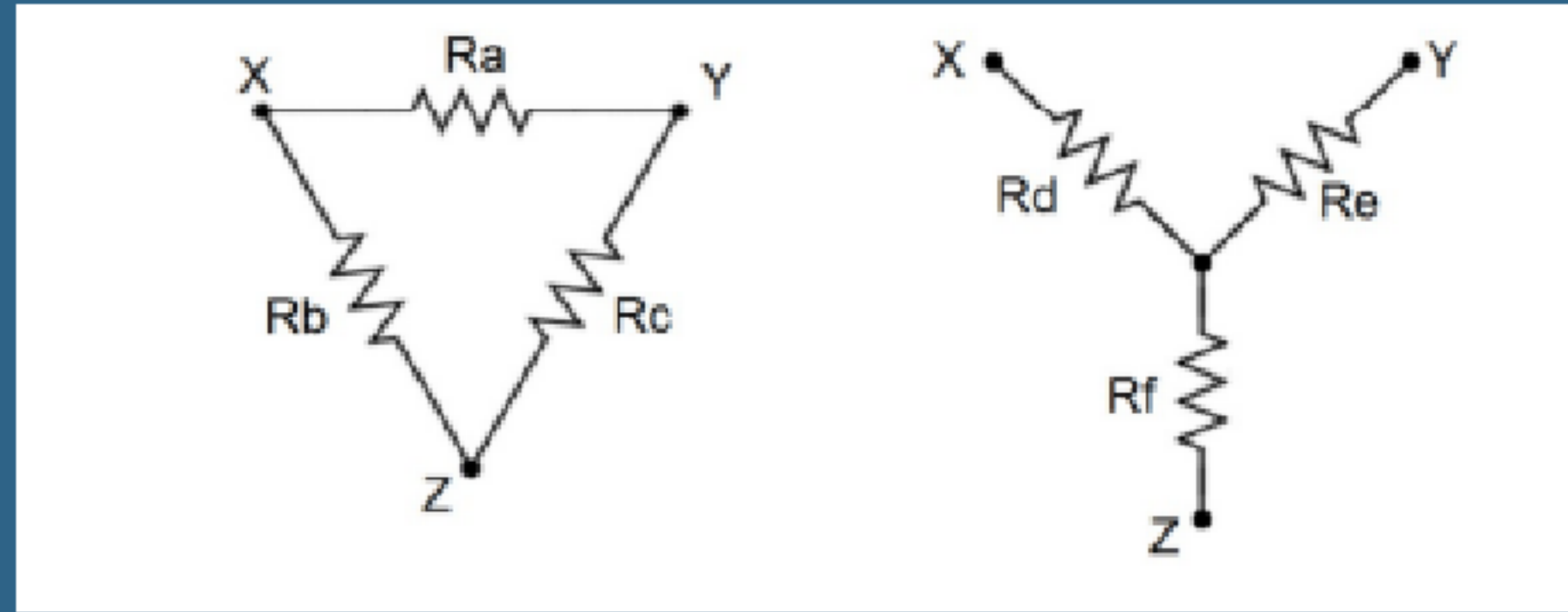
$$R_{ca} = (R_c + R_a) \parallel R_b = R_1 + R_3 \quad (3)$$



$$R_{XY} = R_d + R_e = R_a \parallel (R_b + R_c) \quad \text{eq. 1}$$

$$R_{XZ} = R_d + R_f = R_b \parallel (R_a + R_c) \quad \text{eq. 2}$$

$$R_{ZY} = R_e + R_f = R_c \parallel (R_b + R_a) \quad \text{eq. 3}$$

$$R_d = R_a R_b / (R_a + R_b + R_c) \quad \text{eq. 4}$$

Similarly,

$$R_e = R_a R_c / (R_a + R_b + R_c) \quad \text{eq. 5}$$

$$R_f = R_b R_c / (R_a + R_b + R_c) \quad \text{eq. 6}$$

eg. 1 - eq. 3  $R_1 + R_2 = R_1 + R_3$

$$R_2 + R_3 = (R_a + R_b) \parallel R_c = (R_c + R_a) \parallel R_b \quad (4)$$

$$(4) + (2): 2R_2 = \dots + (R_b + R_c) \parallel R_a \quad (3)$$

$$\begin{array}{l} \text{RHS} \\ (R_a + R_b) \parallel R_c \rightarrow \begin{array}{|l} \cancel{R_c} \parallel \cancel{R_a + R_b} \\ \hline R_a + R_b + R_c \end{array} \quad (1) \end{array}$$

$$\begin{array}{l} (R_c + R_a) \parallel R_b \rightarrow \begin{array}{|l} \cancel{R_b} \parallel \cancel{R_a + R_c} \\ \hline R_a + R_b + R_c \end{array} \quad (2) \\ \hline \begin{array}{|l} 2R_a R_c \\ \hline R_a + R_b + R_c \end{array} = 2R_2 \end{array}$$

$$\begin{array}{l} (R_b + R_c) \parallel R_a \rightarrow \begin{array}{|l} \cancel{R_a} \parallel \cancel{R_b + R_c} \\ \hline R_a + R_b + R_c \end{array} \quad + (3) \end{array}$$



## Proof of Y to Delta


$$R_d / R_c = (R_a R_b / (R_a + R_b + R_c)) / (R_a R_c / (R_a + R_b + R_c)) = R_a R_b / R_a R_c = R_b / R_c$$

Therefore,

$$R_b / R_c = R_d / R_e$$

$$R_b = R_c R_d / R_e$$

$R_a \Rightarrow R_c, R_d, R_e$

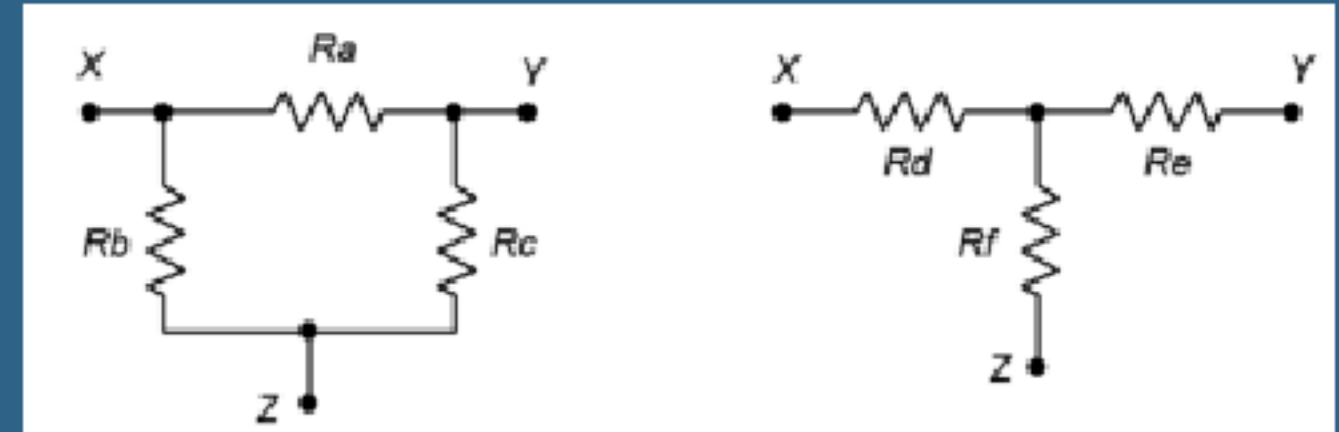

$$R_d = R_a R_b / (R_a + R_b + R_c) \quad \text{eq. 4}$$

Similarly,

$$R_e = R_a R_c / (R_a + R_b + R_c) \quad \text{eq. 5}$$



$$R_f = R_b R_c / (R_a + R_b + R_c) \quad \text{eq. 6}$$

This process can be repeated for eq. 4 and 6 to obtain an expression for  $R_a$ . The two expressions for  $R_a$  and  $R_b$  can then be substituted into eq. 4 to obtain an expression for  $R_c$  that utilizes only  $R_d$ ,  $R_e$  and  $R_f$ . A similar process is followed for  $R_a$  and  $R_b$  resulting in:

$$R_a = (R_d R_e + R_e R_f + R_d R_f) / R_f$$

$$R_b = (R_d R_e + R_e R_f + R_d R_f) / R_e$$
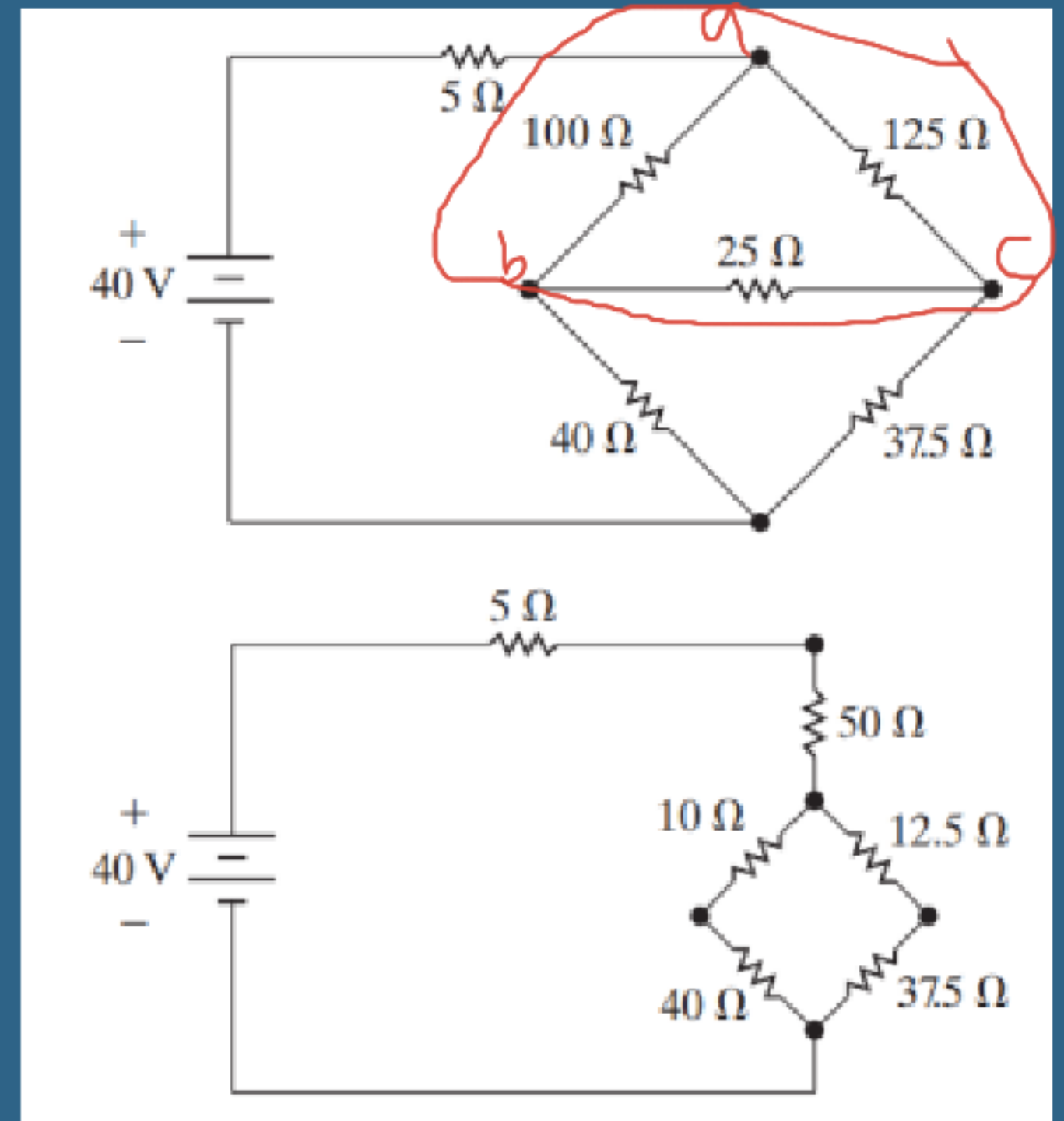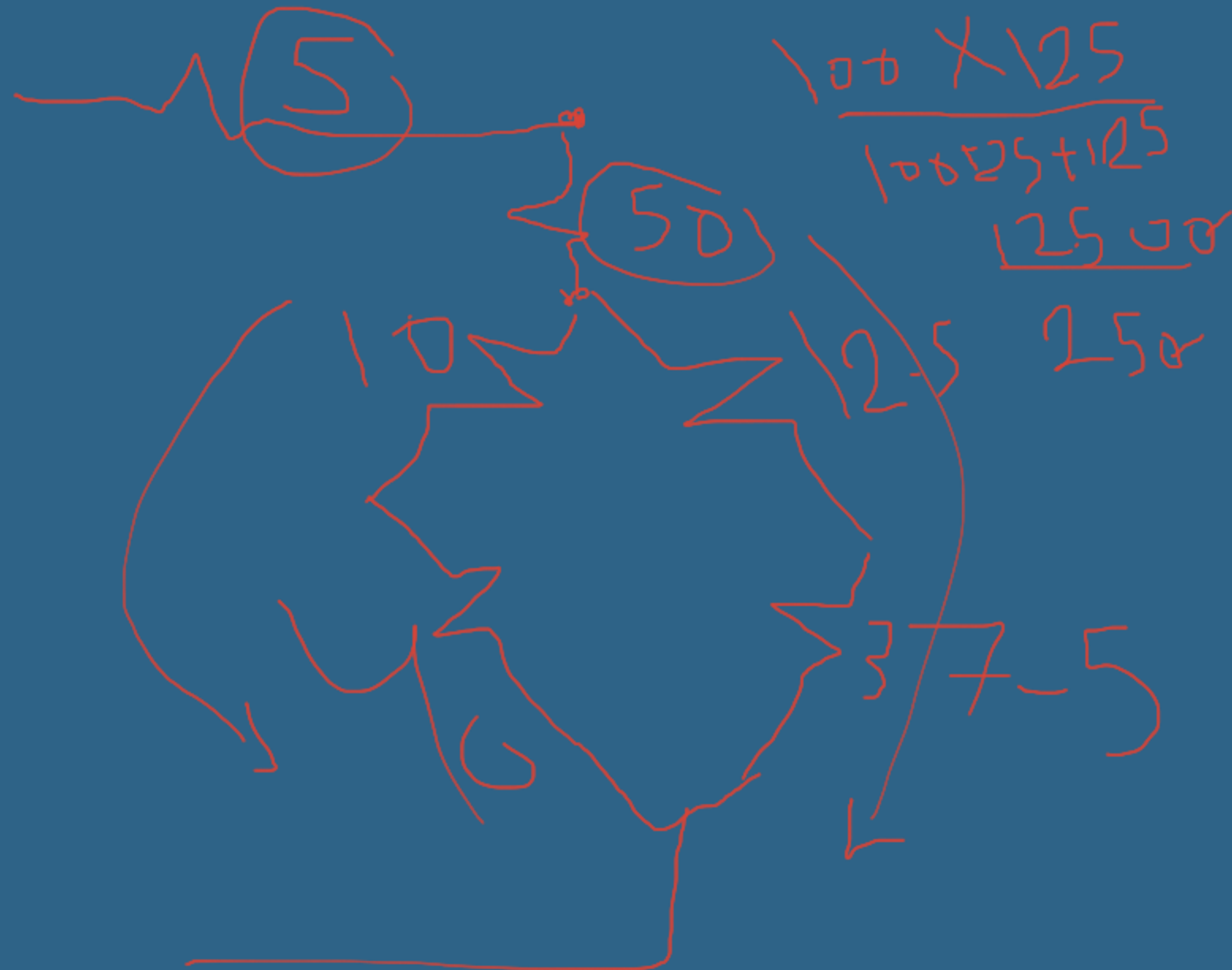
$$R_c = (R_d R_e + R_e R_f + R_d R_f) / R_d$$




# Source Transformations (simplifying techniques)

- A source transformation allows a voltage source in series with a resistor to be replaced by a current source in parallel with the same resistor or vice versa.
  - We assume that both circuits are loaded with the same load resistance  $R_L$ .
- In order to be equivalent the current through  $R_L$  should be the same in both circuits



$$i_L = \frac{v_s}{R + R_L}$$


$$i_L = \frac{R}{R + R_L} i_s$$

$$i_s = \frac{v_s}{R}$$

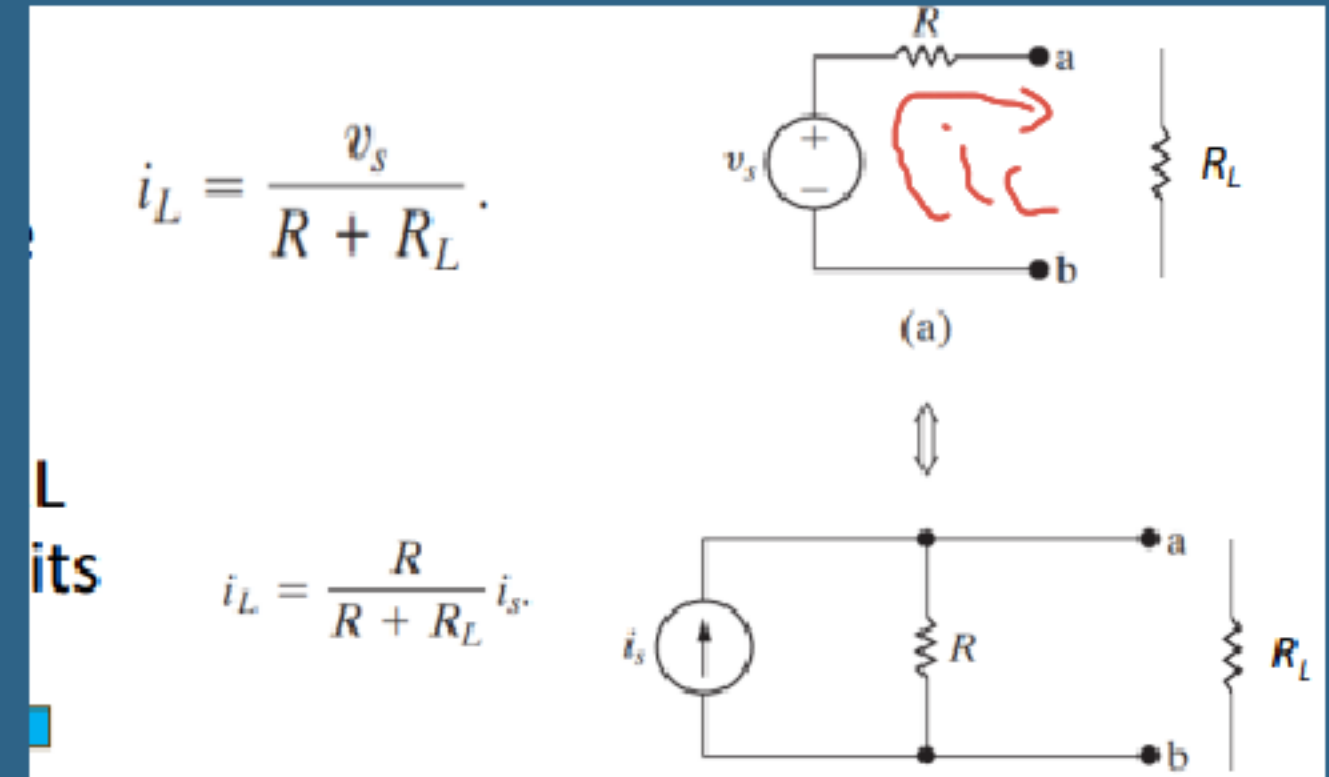


# Source Transformations

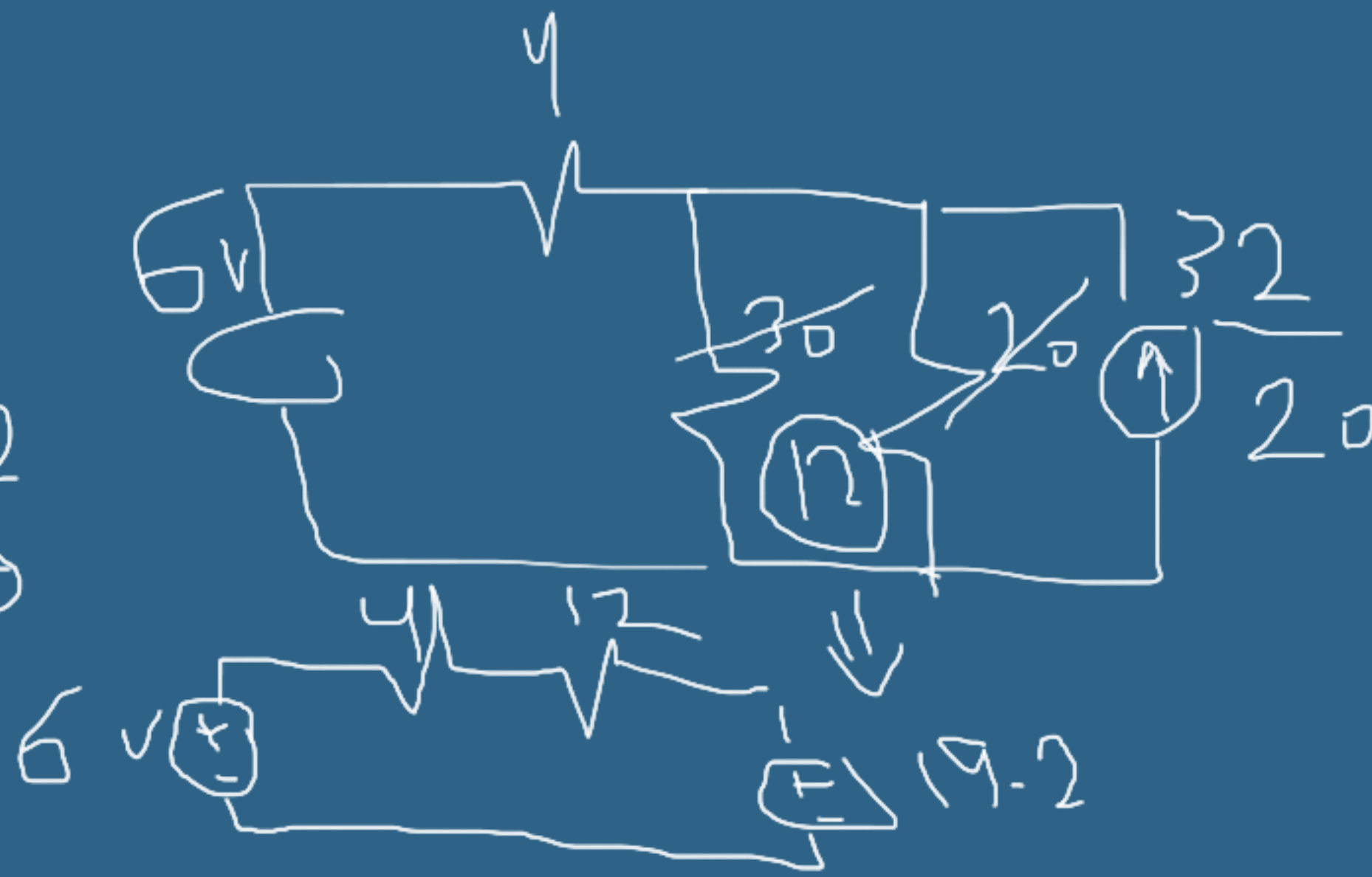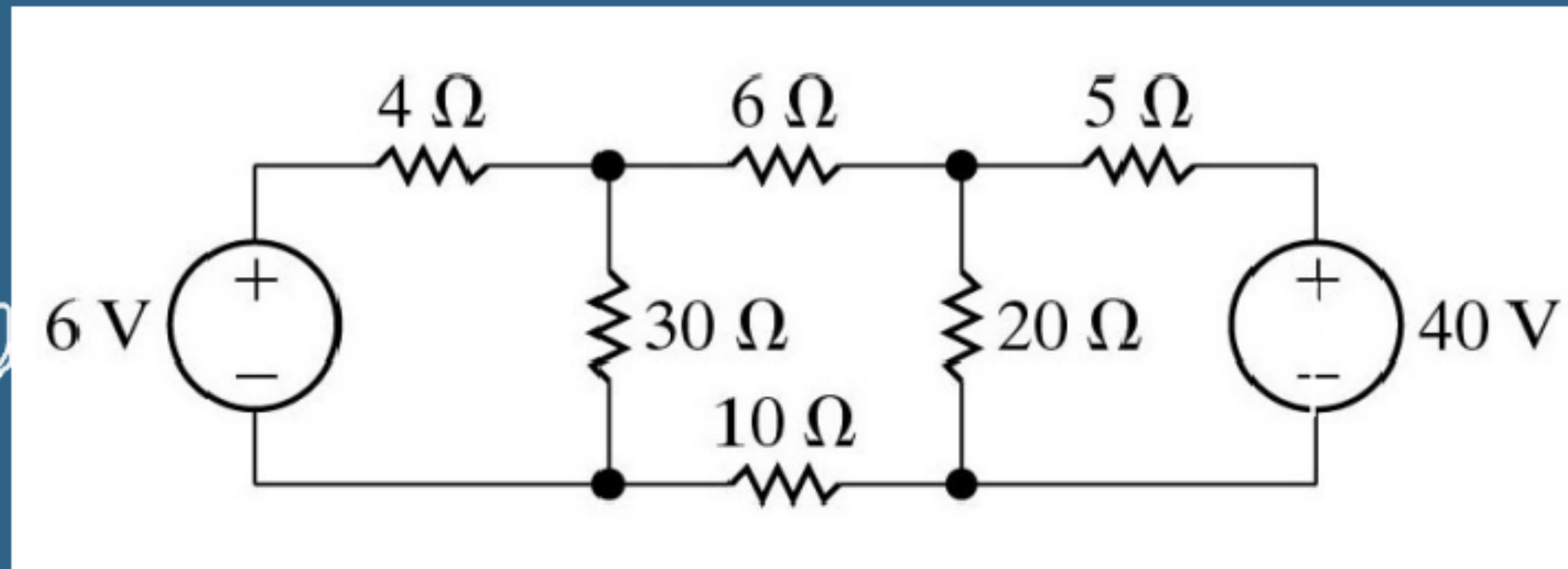


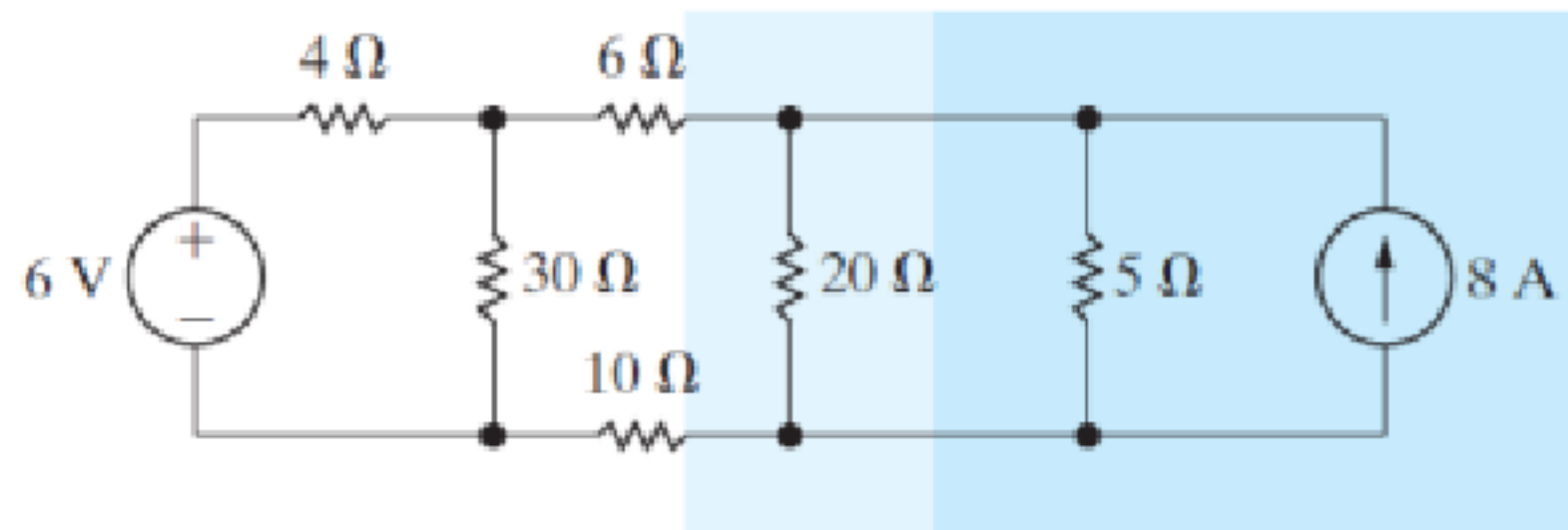


(a) First step

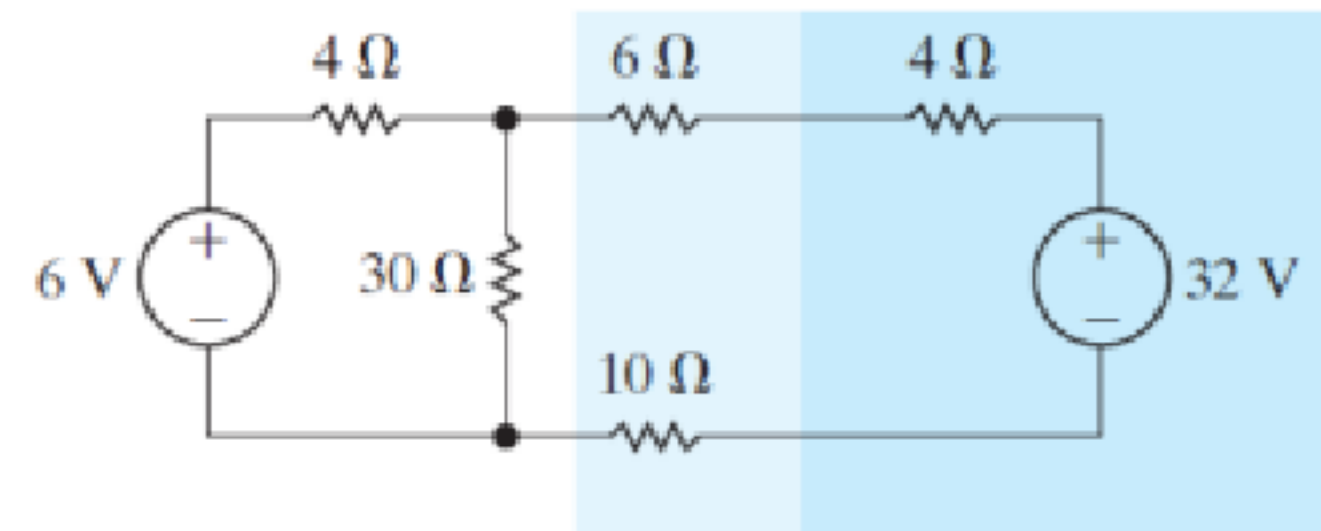

(b) Second step

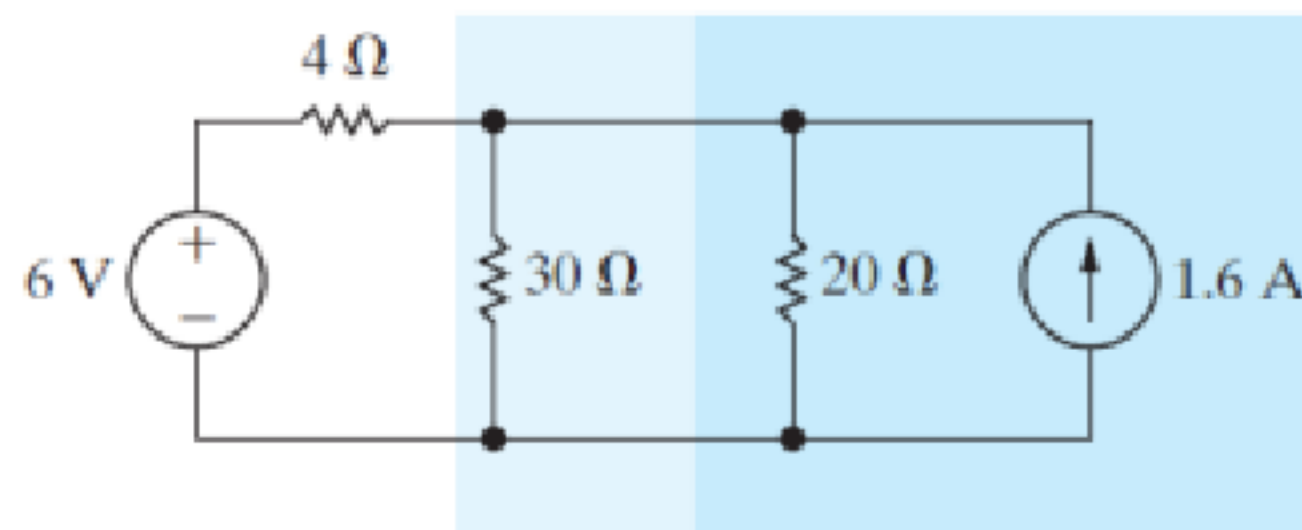

(c) Third step

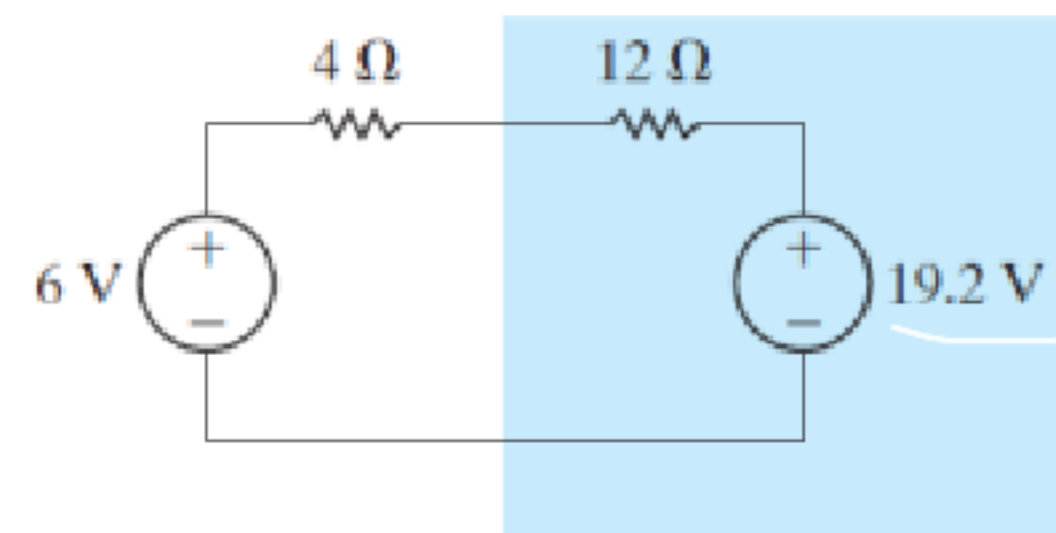

(d) Fourth step