



## Handwritten Assignments 2

1- The two series-connected capacitors in Fig. 1 are connected to the terminals of a black box at

$t = 0$ . The resulting current for is known to be  $800e^{-25t} \mu\text{A}$ .

a) Replace the original capacitors with an equivalent capacitor and find  $v_o(t)$  for  $t \geq 0$ .

b) Find  $v_1(t)$  for  $t \geq 0$ .

c) Find  $v_2(t)$  for  $t \geq 0$ .

d) How much energy is delivered to the black box in the time interval  $0 \leq t \leq \infty$

e) How much energy was initially stored in the series capacitors?

f) How much energy is trapped in the ideal capacitors?

g) Show that the solutions for  $v_1$  and  $v_2$  agree with the answer obtained in (f).

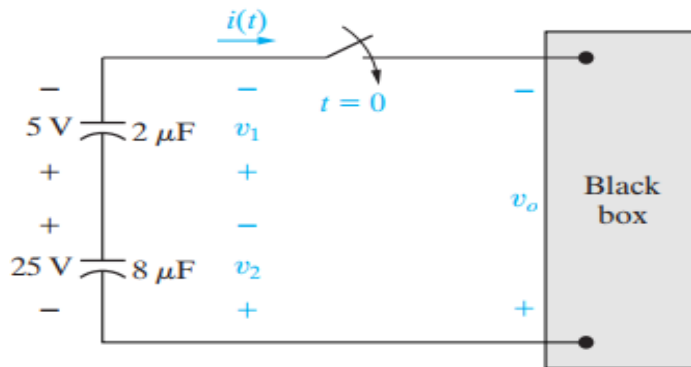


Fig. 1

2- In the circuit shown in Fig .2, the switch has been in position a for a long time. At  $t=0$ , it moves instantaneously from a to b.

a) Find  $i(t)$  for  $t \geq 0$ .

b) What is the total energy delivered to the resistor?

c) How many time constants does it take to deliver 95% of the energy found in (b)?

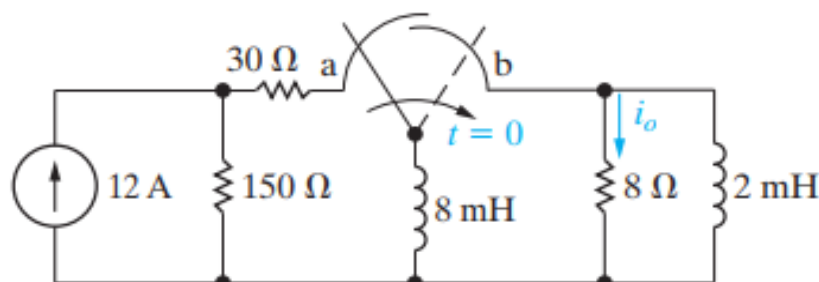


Fig .2

3- The switch in the circuit in Fig. 3 has been in the left position for a long time. At  $t=0$ , it moves to the right position and stays there.

- Find the initial voltage drop across the capacitor.
- Find the initial energy stored by the capacitor.
- Find the time constant of this circuit for  $t > 0$ .
- Write the expression for the capacitor voltage  $v(t)$  for  $t \geq 0$ .

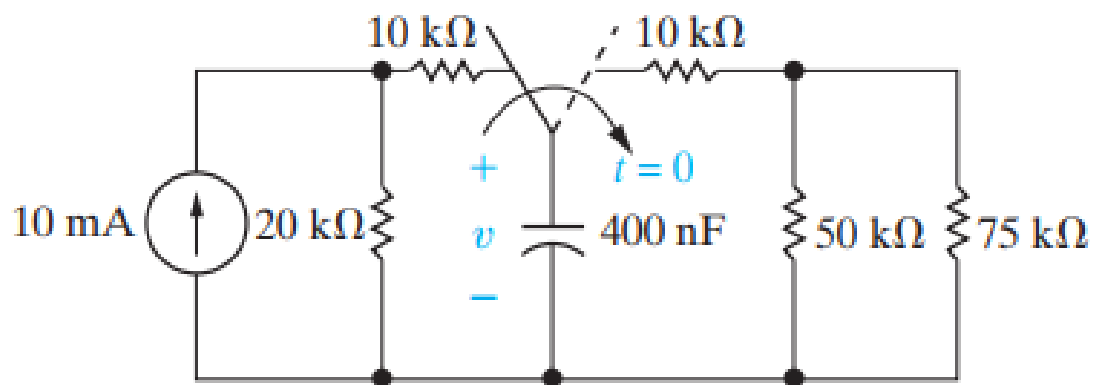


Fig. 3