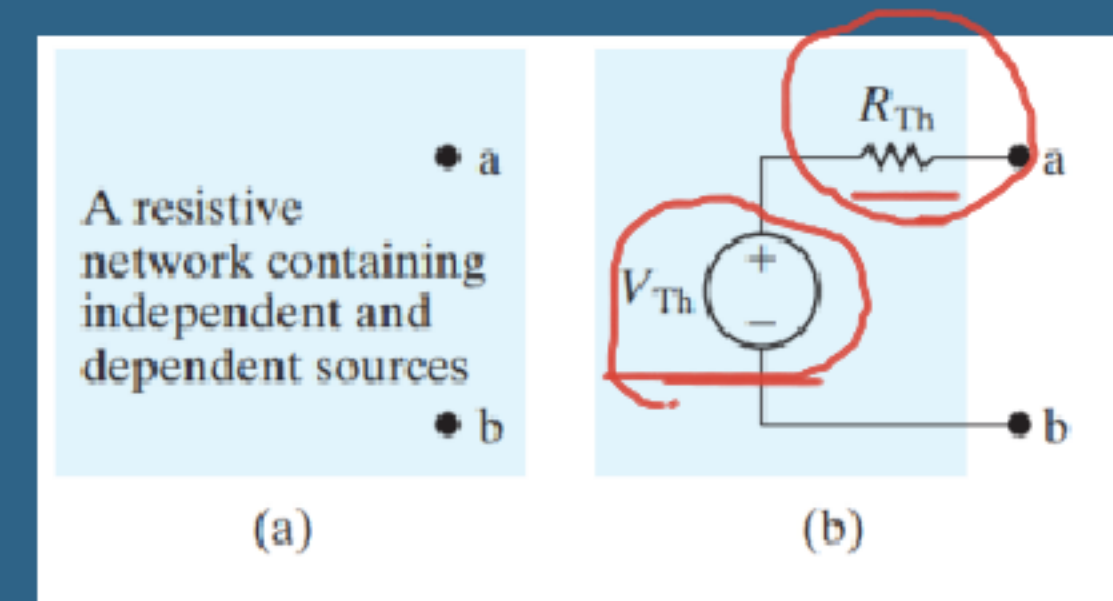



- # Thevenin Equivalent Circuit
- Thevenin and Norton equivalents are circuit simplification techniques.
 - These equivalent circuits retain no information about the internal behavior of the original circuit and focus only on terminal behavior.
 - Thevenin equivalent circuit is an independent voltage source in series with a resistor, which replaces an interconnection of sources and resistors.



This series combination of V_{Th} and R_{Th} is equivalent to the original circuit in the sense that, if we connect the same load across the terminals a,b of each circuit, we get the same voltage and current at the terminals of the load.

=> In order to get the Thevenin voltage V_{Th} , we assume an open circuit condition at the terminals and deduce the voltage at the terminals. Then we assume a short circuit at the terminals and compute the current I_{sc} from which we find the R_{th} .

$$R_{th} = \frac{V_{Th}}{I_{sc}}$$

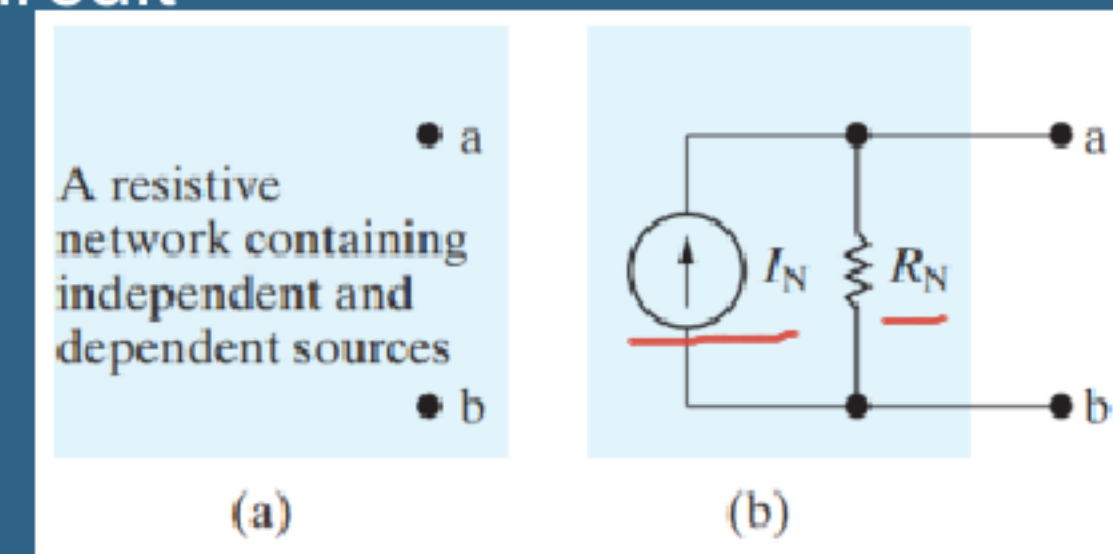


- Example: Finding a Thevenin Equivalent:

① O.C. to get V_{th}

$$\frac{V_x - 25}{5} + \frac{V_x - 0}{20} - 3 = 0 \quad \boxed{V_x = 32V}$$

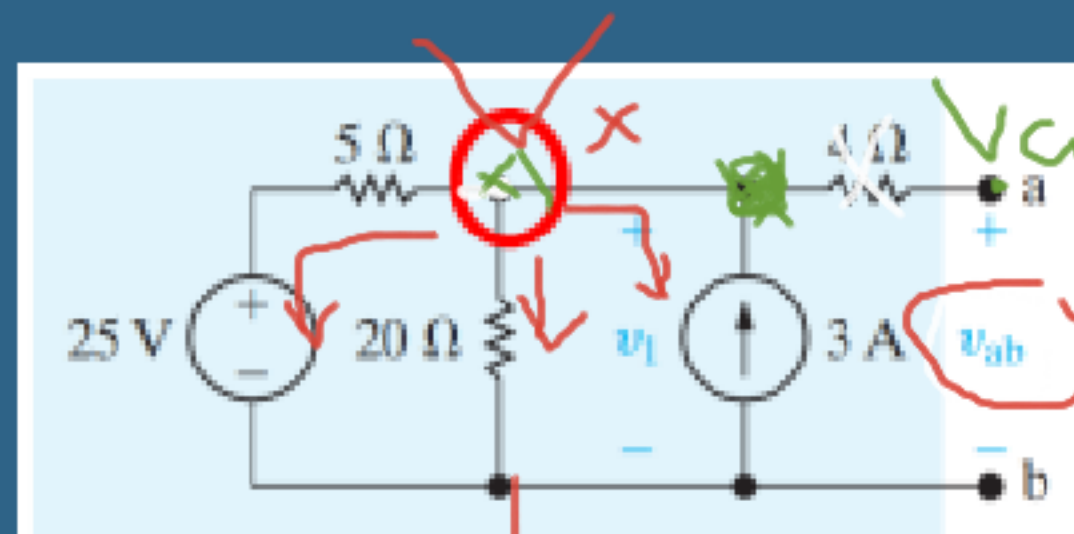Note: $V_a = V_x$ $V_{ab} = V_a - V_b = V_a = 32V$ $\xrightarrow{V_{th}}$




② $I_{s.c.}$:

$$\frac{V_y - 25}{5} + \frac{V_y - 0}{20} - 3 + \frac{V_y - 0}{4} = 0$$


$$V_2 = 16V$$

$$i_{sc} = \frac{V_2 - 0}{4} = \frac{16}{4} = 4A$$

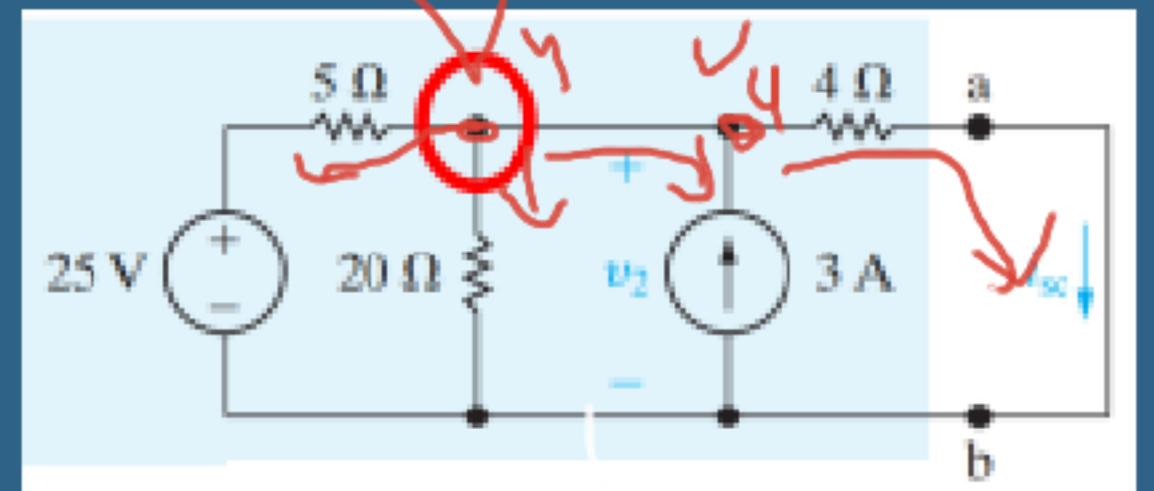
$$R_{th} = \frac{V_{th}}{i_{sc}} = \frac{32}{4} = 8\Omega$$



\equiv

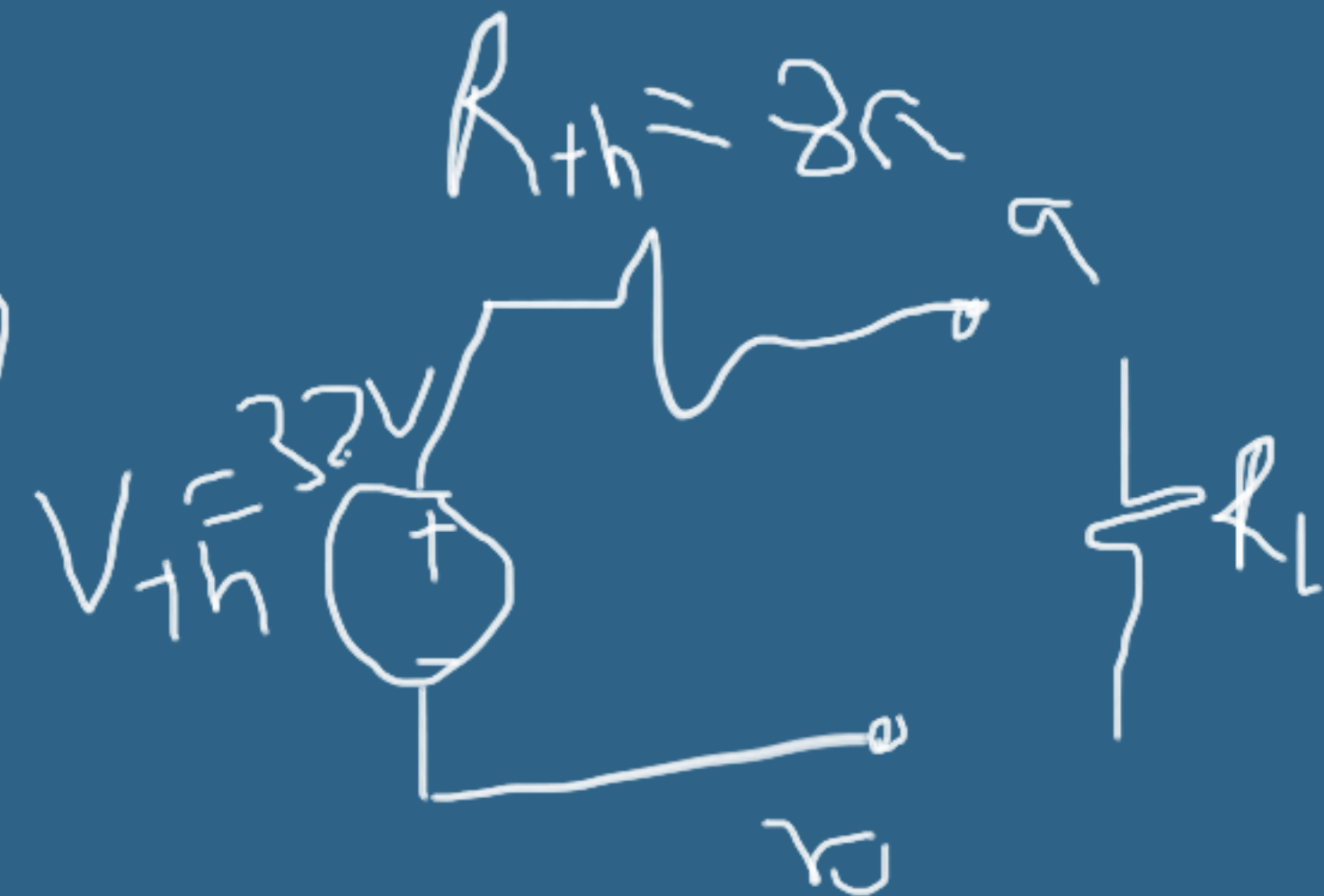

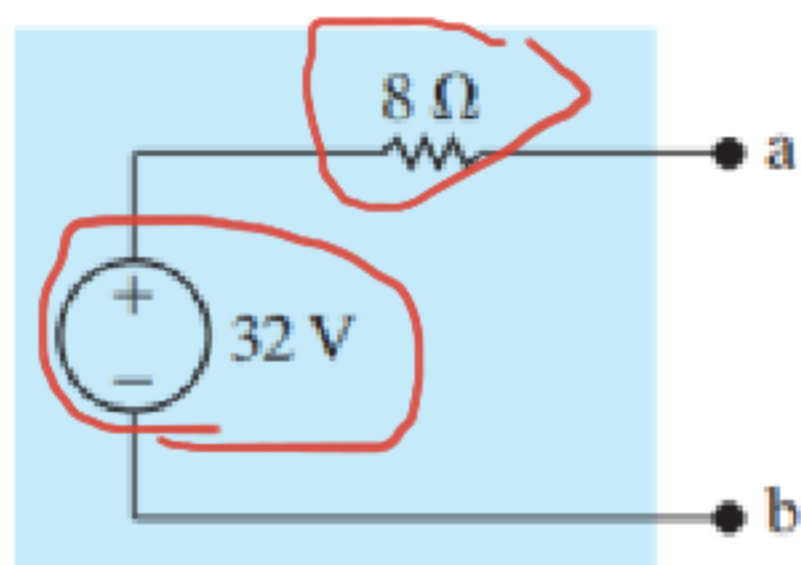
$$I = \frac{V}{R} = \frac{32}{8} = 4 \text{ A}$$



Thevenin equivalent circuit


Source
Transformation

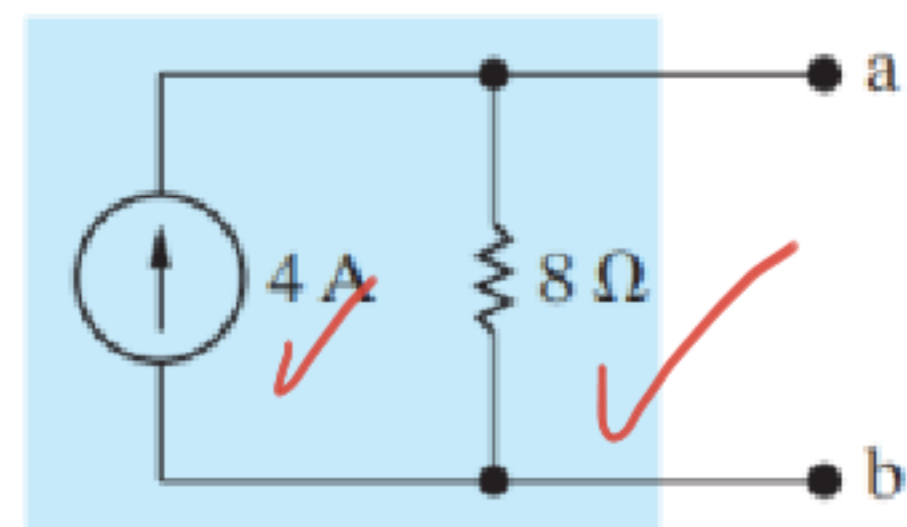

Norton equivalent circuit

Norton

$$\frac{5 \times 20}{5 + 20}$$

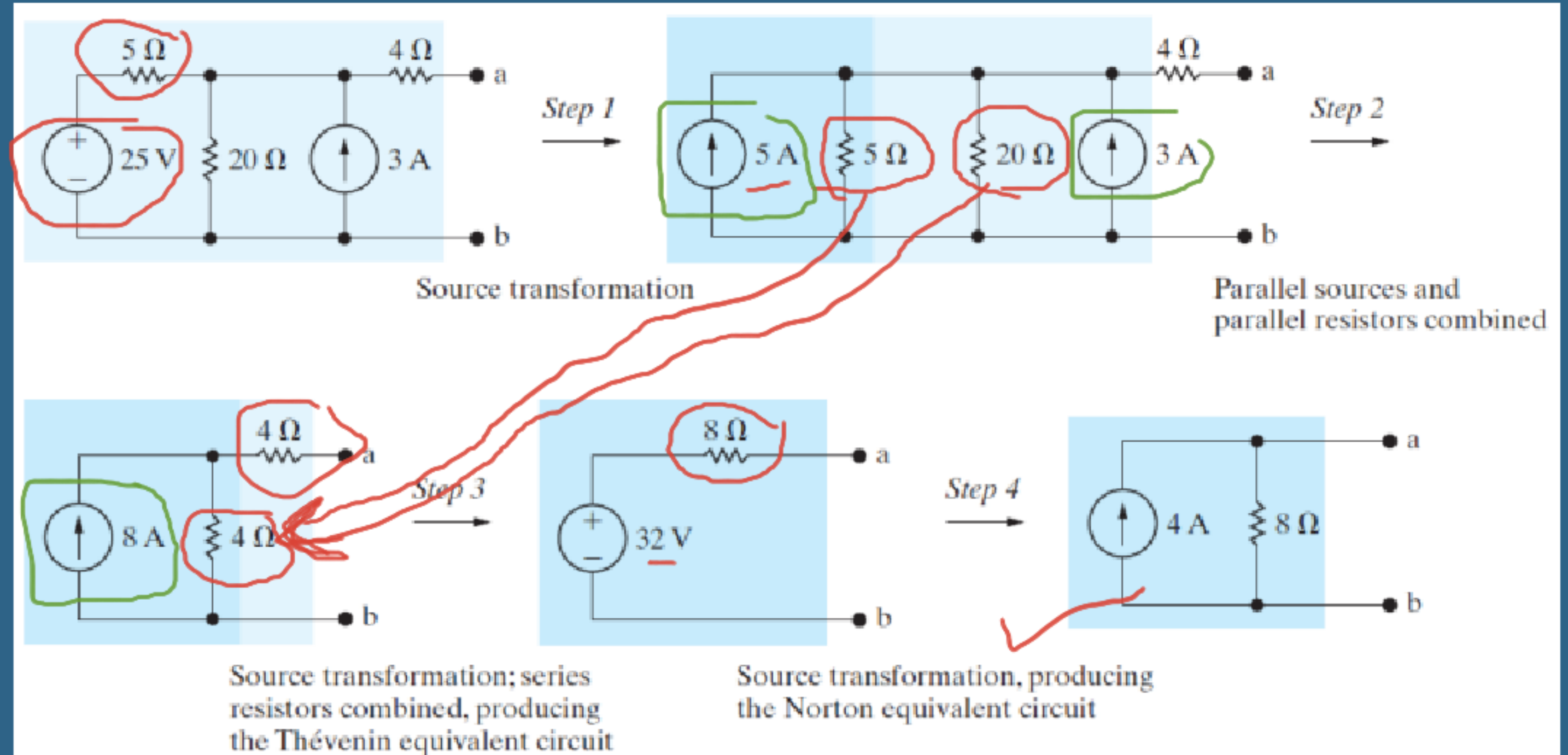


Thévenin Equivalent of a Circuit with a Dependent Source

① $V_{th} = 0.5$

$$V_{th} = V_{ab} = V_a = (-20i)(25) \\ = -500i$$

$$-5 + 2000i + 3(-500i) \rightarrow 0 = 0.1A$$

$$V_{th} = -5V$$

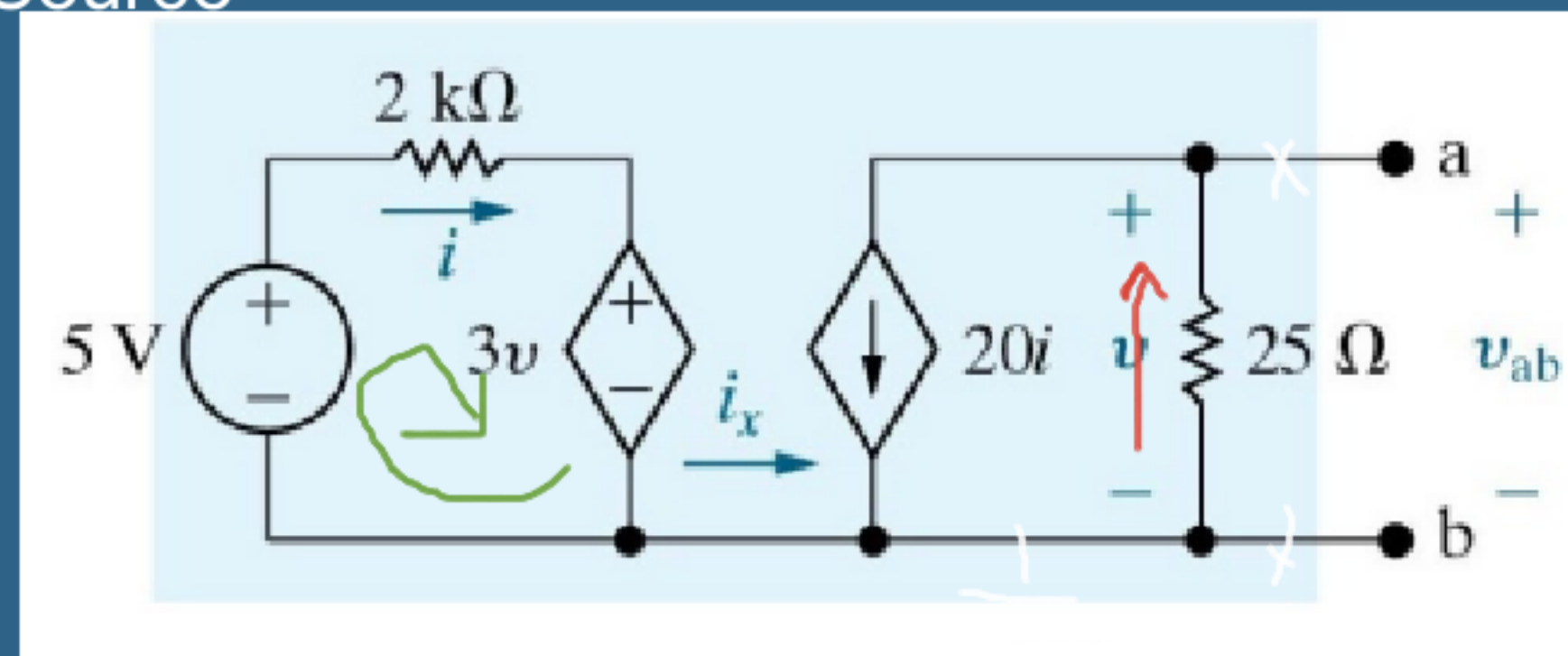


② $i_{s.c}$

$$i_{s.c} = -20 i$$

$$i = \frac{5 - 3V}{2000} = \frac{5}{2000} = \left(\frac{1}{400} \right) A$$

$$i = -\frac{1}{20} A$$

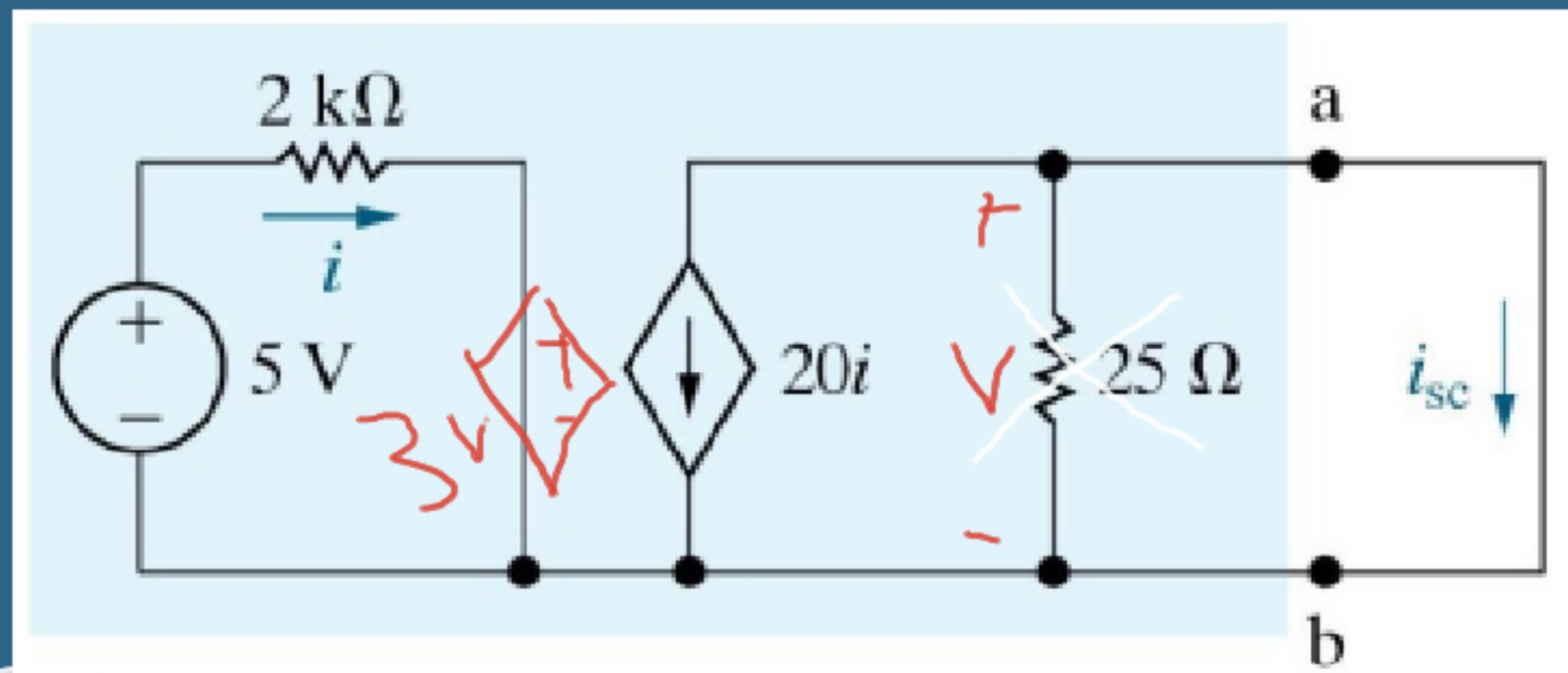
$$R_{th} = \frac{V_{th}}{i_{s.c}} = \frac{-5}{\left(\frac{-1}{20} \right)} = \left(100 \Omega \right)^*$$



Maximum Power Transfer

- In Communication systems information (data) is transmitted via electric signals, the power available at the transmitter or detector is limited.

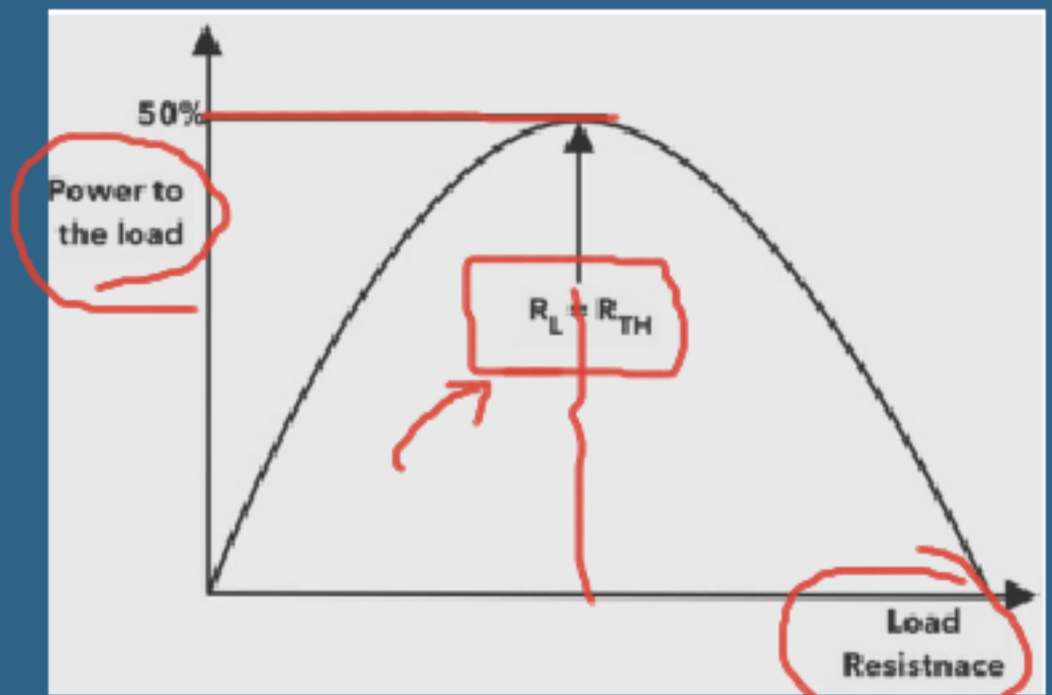Thus, transmitting as much of this power as possible to the receiver (load) is desirable.




Derivation

$$P_L = V_L I = I^2 R_L = \left(\frac{V_{th}}{R_L + R_{th}} \right)^2 R_L$$

$$I = \frac{V_{th}}{R_{th} + R_L}$$

$$\frac{dP_L}{dR_L} = 0$$

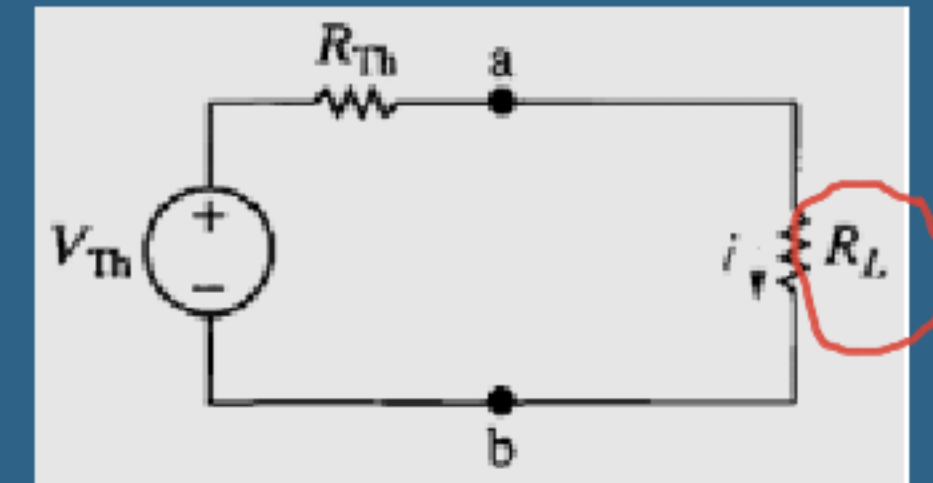

$$\underline{p} = \underline{i^2 R_L} = \left(\frac{V_{Th}}{\cancel{R_{Th}} + R_L} \right)^2 R_L.$$

$$R_L = R_{Th}$$

$$\frac{dp}{dR_L} = V_{Th}^2 \left[\frac{(R_{Th} + R_L)^2 - R_L \cdot 2(R_{Th} + R_L)}{(\cancel{R_{Th} + R_L})^4} \right]$$

$$= 0$$

$$p_{max} = \frac{V_{Th}^2}{4R_L^2} - R_L$$

$$= \frac{V_{Th}^2}{4R_L}$$

$$p_{max} = \frac{V_{Th}^2 R_L}{(2R_L)^2} = \frac{V_{Th}^2}{4R_L}$$

Maximum Power Transfer



$$V_{Th} = \frac{150}{180} (360) = 300 \text{ V}$$

$$R_{Th} = \frac{(150)(30)}{180} = 25 \Omega$$

$R_L = R_{Th}$

$$P_{max} = \left(\frac{300}{50} \right)^2 (25) = 900 \text{ W}$$
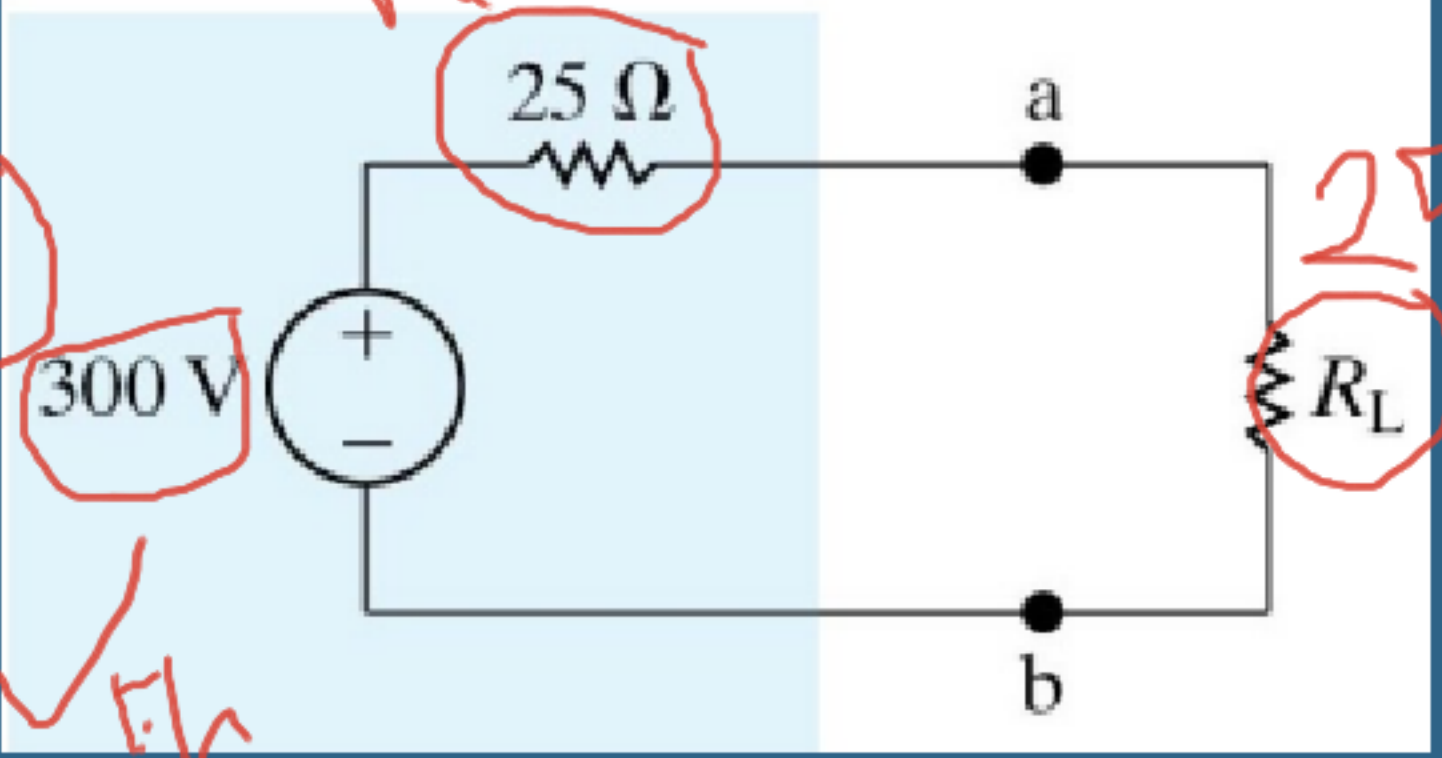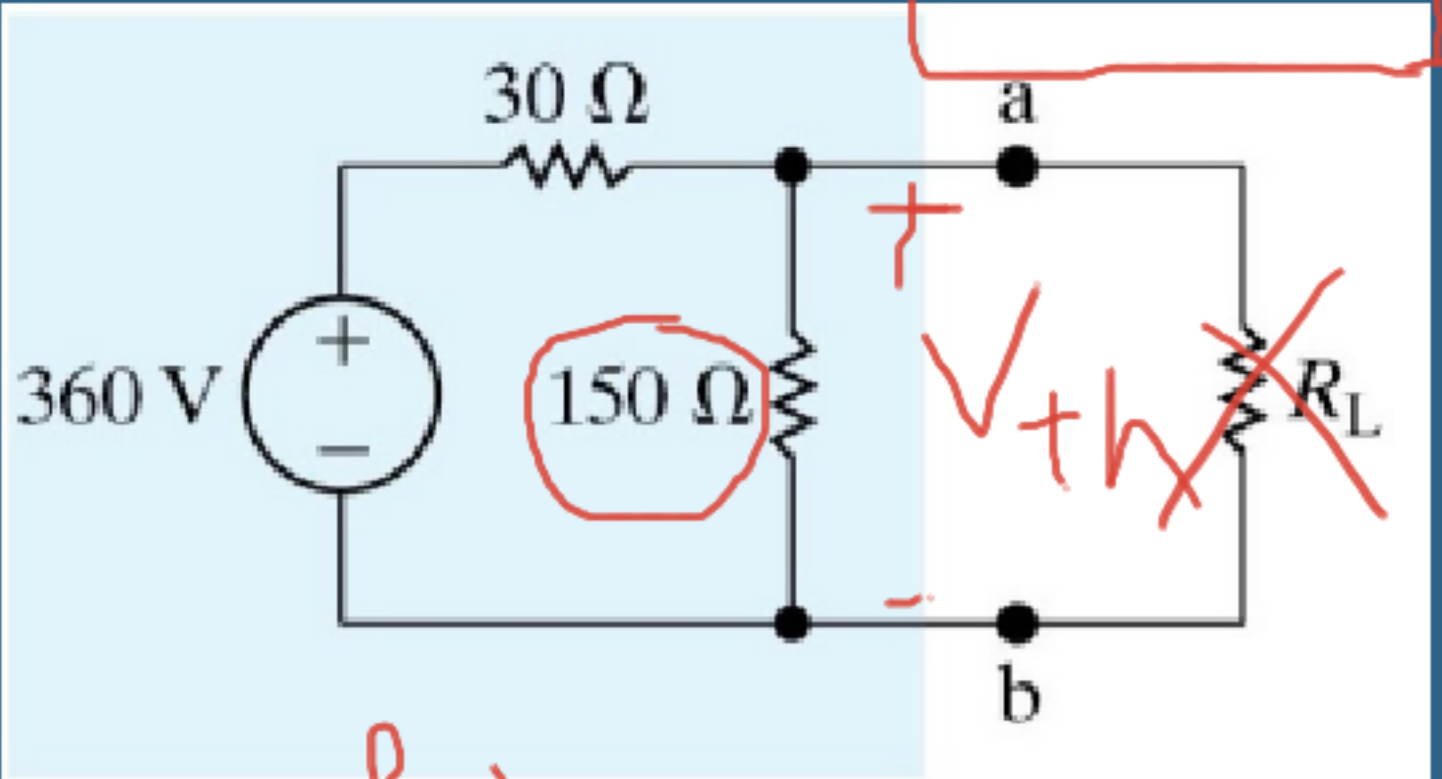
$$v_{ab} = \left(\frac{300}{50} \right) (25) = 150 \text{ V}$$



$$v_{ab} = \left(\frac{300}{50} \right) (25) = 150 \text{ V}$$

$$i_s = \frac{360 - 150}{30} = \frac{210}{30} = 7 \text{ A}$$

$$p_s = -i_s(360) = -2520 \text{ W}$$

$$\frac{900}{2520} \times 100 = 35.71\%$$

