



Lab 6

Zener Diode and BJT Transistor

Introduction:


A diode is an electrical device that allows current to move through it in one direction with far greater ease than in the other. When placed in a simple battery-lamp circuit, the diode will either allow or prevent current through the lamp, depending on the polarity of the applied voltage.

A- ZENER DIODE CHARACTERISTICS

A **Zener diode** is a **silicon** semiconductor device that allows **current** to flow in either **direction**.

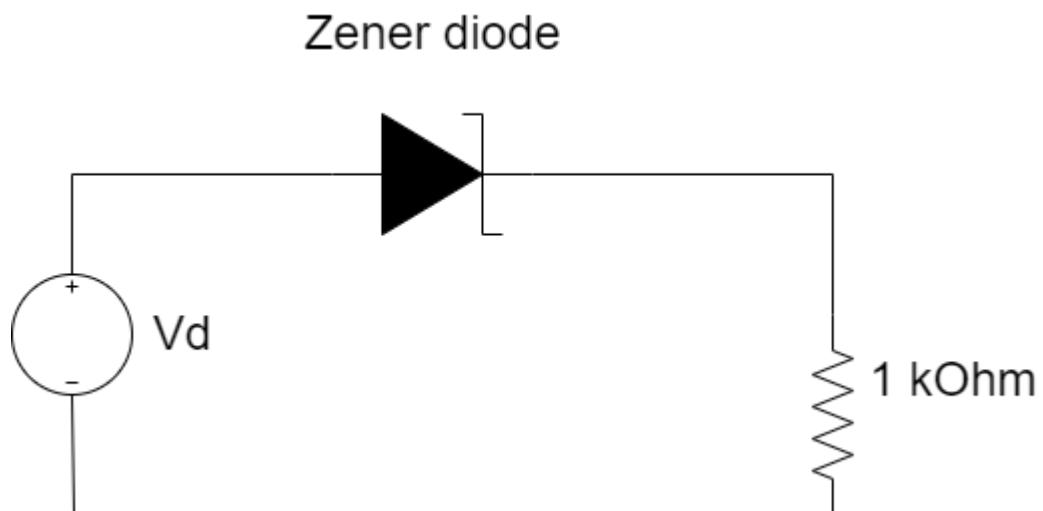
I. Experiment:

- You are required to **simulate** this circuit to **plot I-V** characteristics of **Zener** diode.




II. Simulation procedures:

- Draw SCHEMATIC:

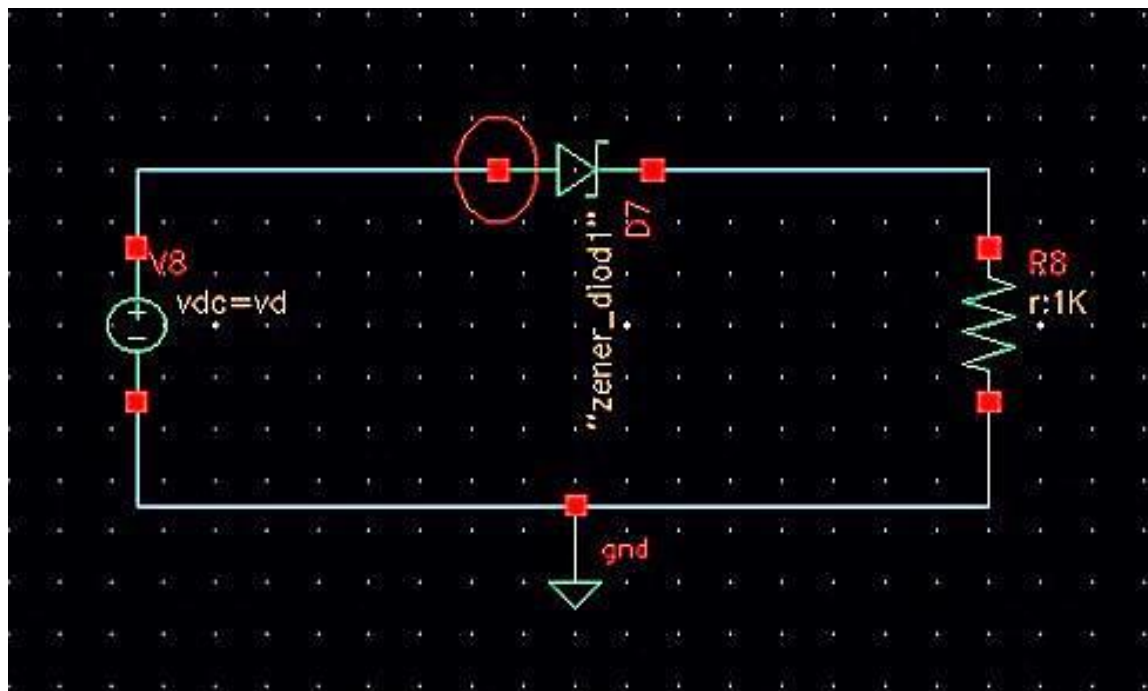

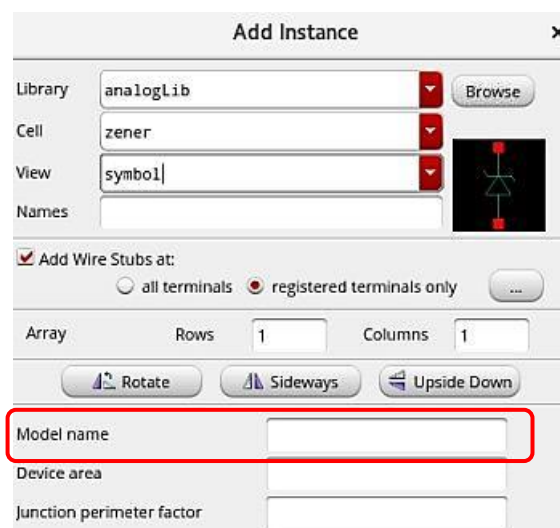- For the **zener diode** just repeat the **step** to the **add instance** because here is the **difference**. **YOU WANT FIND THE ZENER DIODE ON THE TECHNOLOGY UMC.**
- To **solve** this **problem** just grab the **Zener** diode from **analoglib**.





NO SPICE MODEL == EMPTY SYMBOL

- To solve this another problem you will have to **create your own Zener diode spice model**.
- Open terminal and type \$cat>filename.scs
- Copy the following spice code:



```
simulator lang = spice
.model zener_diod1 d
+ bv = 5.5
+ cj = 9.353E-14
+ level=1
+ is=1e-20 n=0.2118 ibv=1e-3
+ rs=91.5316 tcv=-1.600e-03 eg=0.1 xti=0
+ mj=0.3552 pb=0.8144
```
- Now copy the Model Zener_diod1 to the **Model Name Section**. Just select the diode and **press Q** from your keyboard.



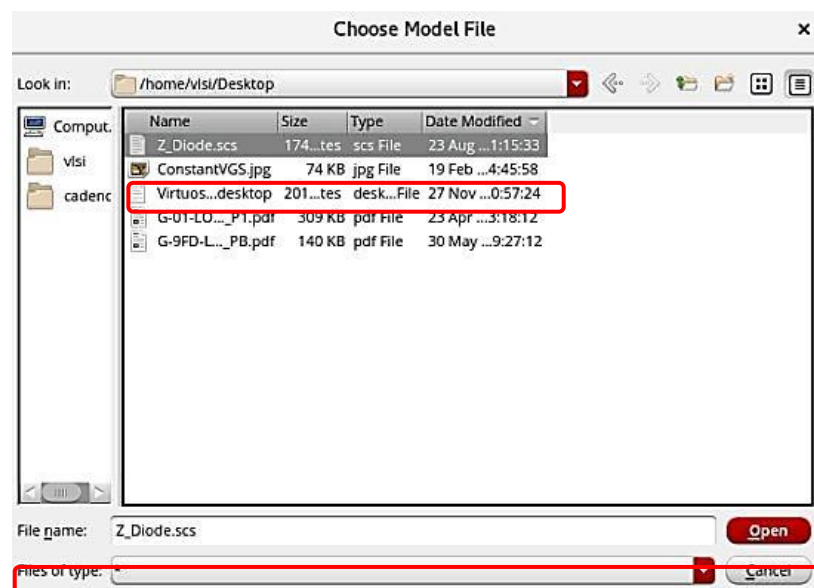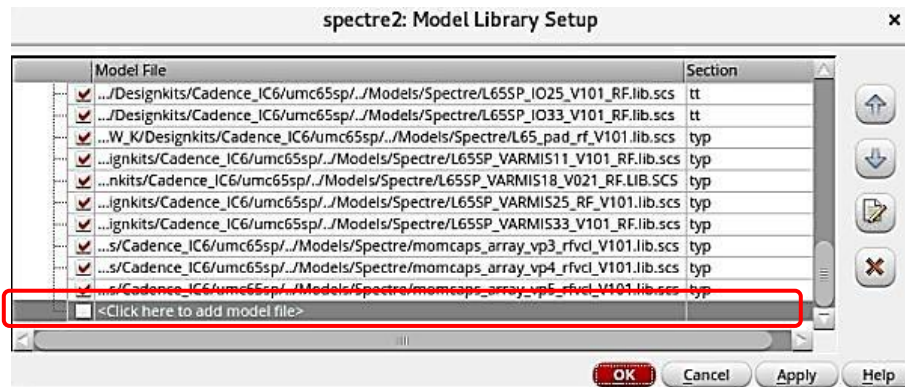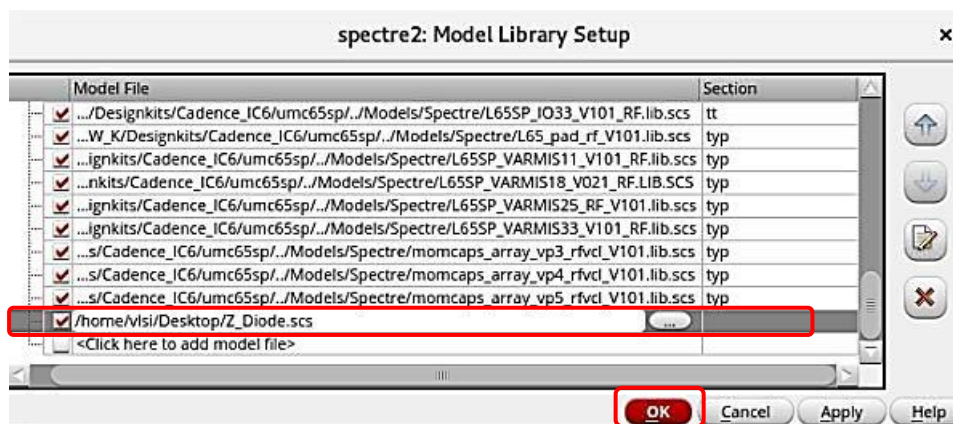- Now Open the ADEL again as before but **now we need to add the Spice file to its library.**
 - You can do this by choosing: **Setup >> Model Libraries**. A new window will open:





Now click **OK** for it to be **ADDED**.



Note: You have to add spice file of Zener in each cell

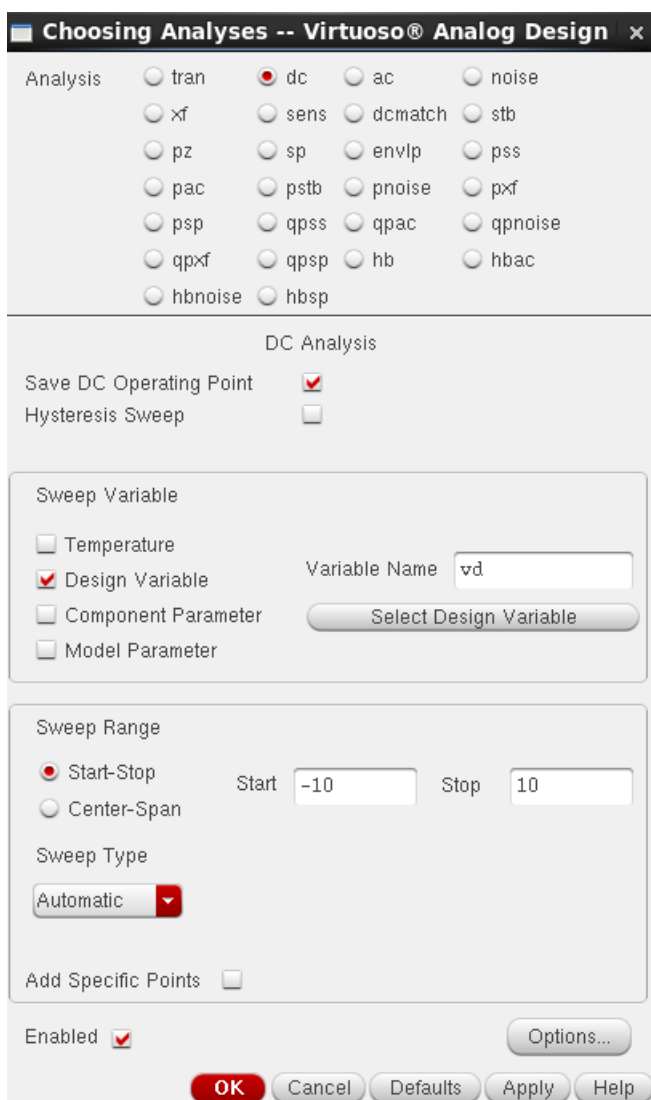9. Now to show its characteristics just apply dc analysis and sweep on the input value between ranges (-10,10).




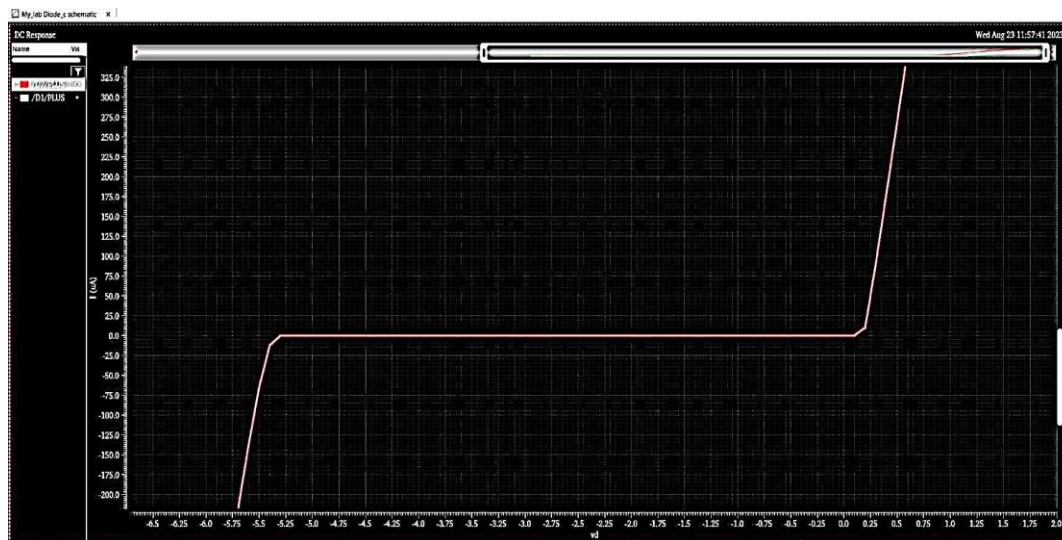

10-Get the break up and down voltage of Zener diode from output curve.

B-ZENER DIODE AS A REGULATOR

SCHEMATIC:

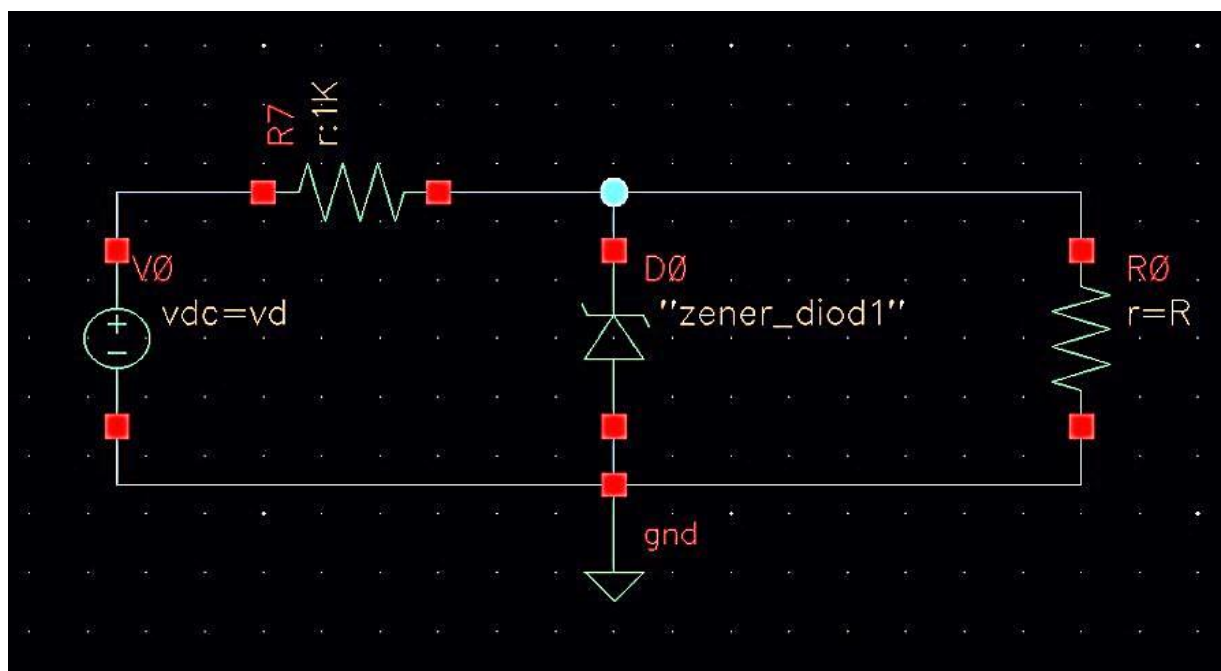

- For the Resistor **change its value to a variable R** so we could SWEEP it.

- To vary the value of **R** first **add** it to **Design Variables** as we did **before**. Now **assign** a **value** to it as we did before.

Design Variables		
	Name	Value
1	R	500
2	vd	10

- Now add the **Dc sweep Analysis** for **vd** but this time it won't be automatic.

Sweep Range

☒ Start-Stop Start Stop

☐ Center-Span

Sweep Type

 ☒ Step Size

☐ Number of Steps

Add Specific Points ☐

Add Points By File ☐

Sweep Range

☒ Start-Stop Start Stop

☐ Center-Span

Sweep Type

 ☐ Step Size

☒ Number of Steps

Add Specific Points ☐

Add Points By File ☐

Click to add variable

Click to add test

☒ Global Variables

☒ R 10k, 20k, 30k


☒ vd 1

Click to add variable


☒ Parameters

- Add the output as we did before **but this time choose any of the resistor nodes**.
- Now to **vary** the **resistance R** you will need to **open** the **parametric analysis**. Just choose:

Tools >> Parametric Analysis...

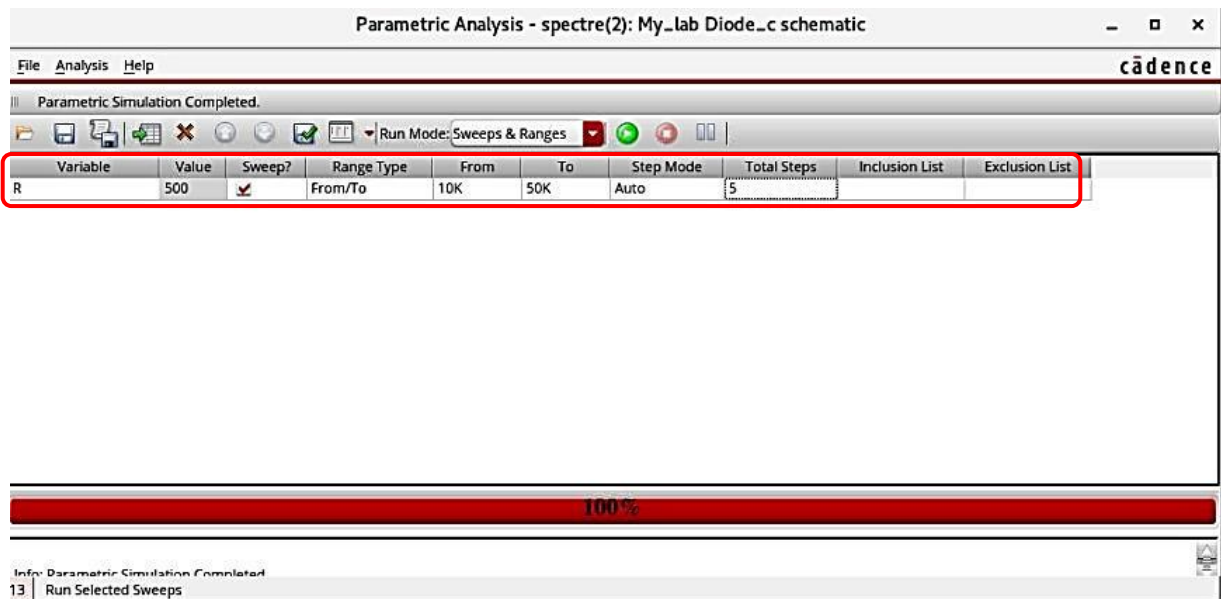

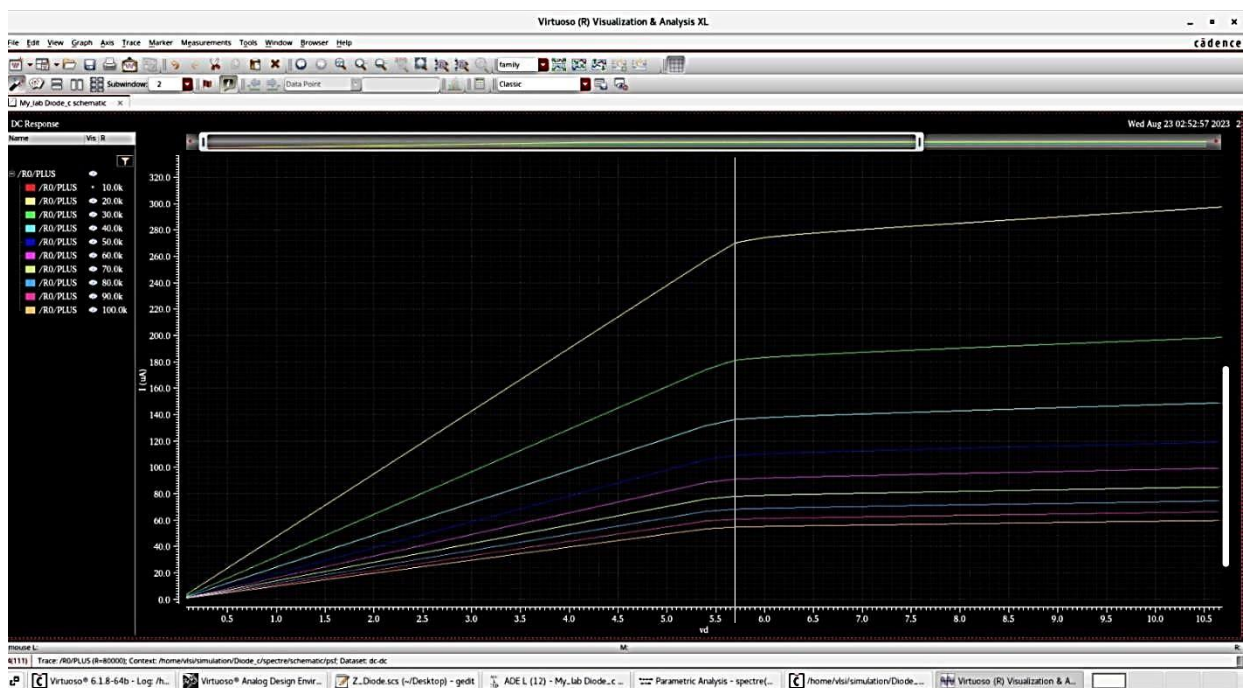Now click the green button to **start simulation** .




B-Bipolar Junction Transistors



Introduction



Bipolar transistors work as current-controlled current regulators. In other words, transistors restrict the amount of current passed according to a smaller, controlling current.

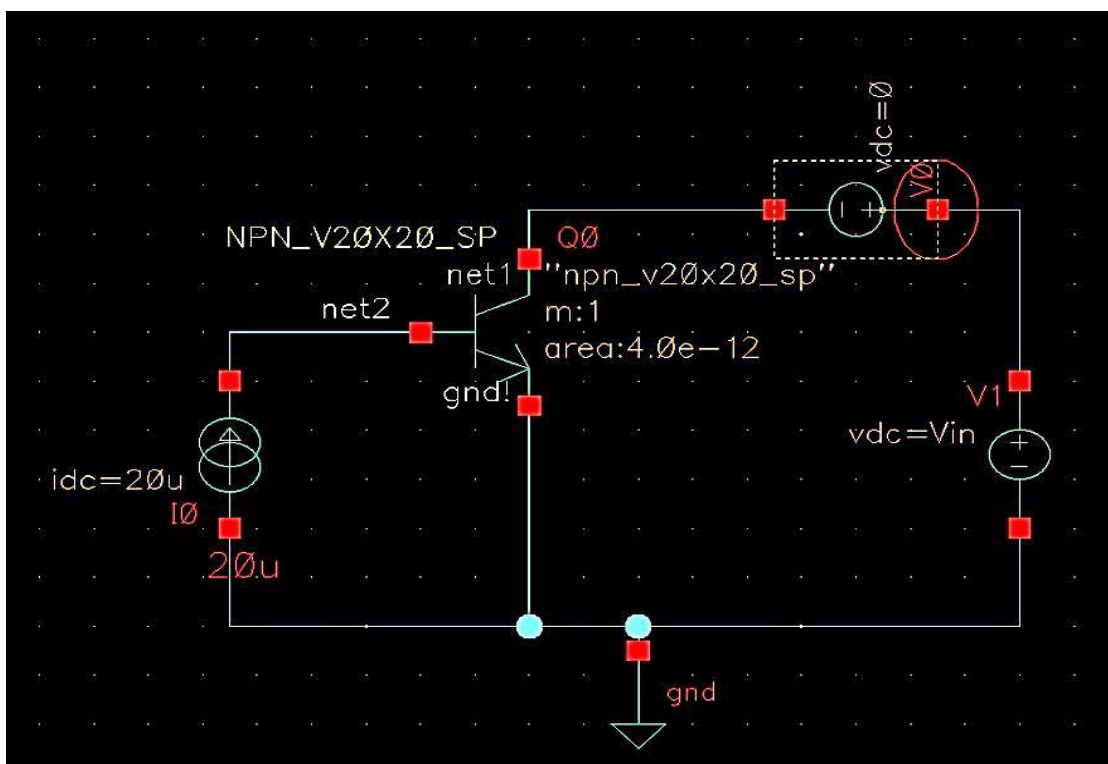1. Active-mode operation


Set the current source (I_{dc}) at a constant value of $20\ \mu\text{A}$, then vary the voltage source (V_1) over a range of 0 to 2 volts and monitor how much current goes through it.



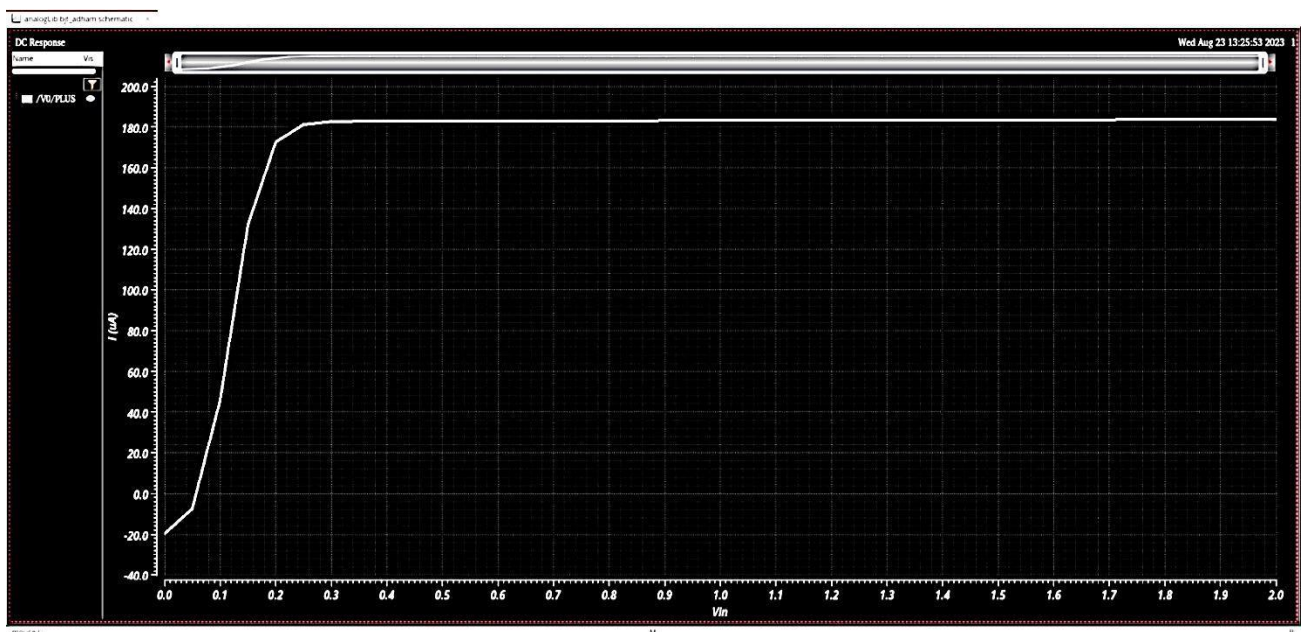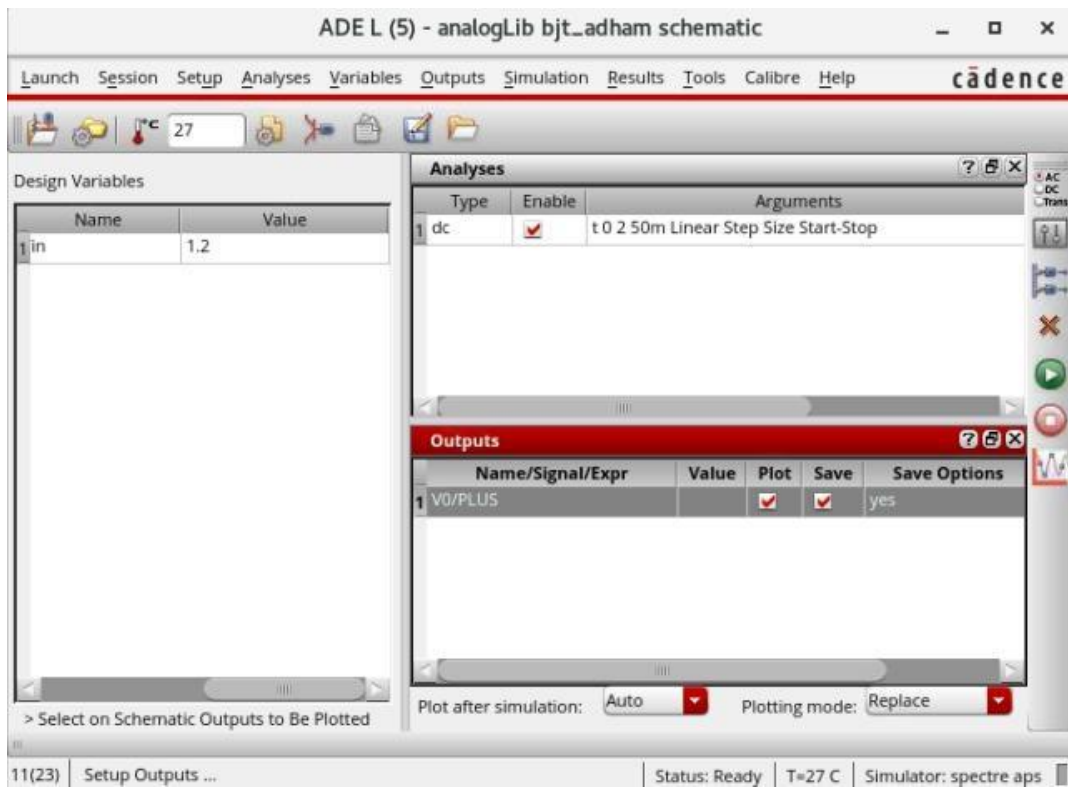

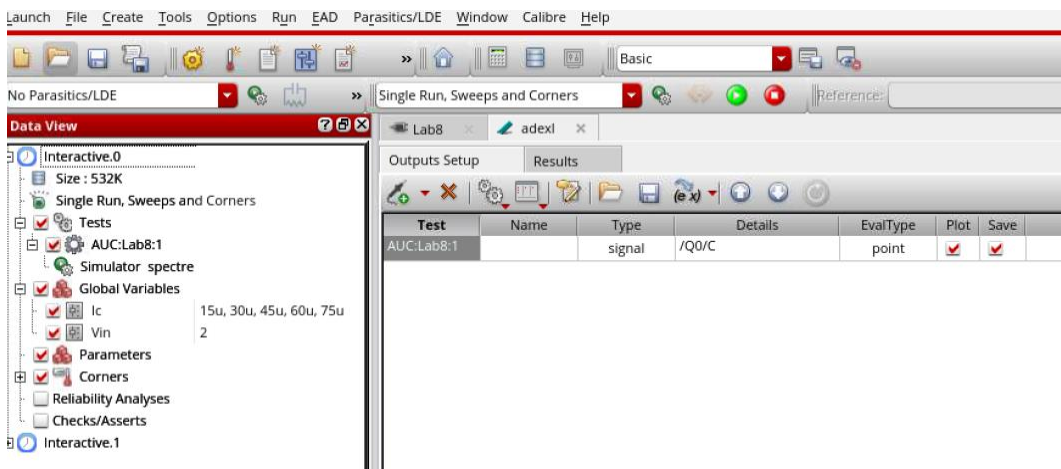
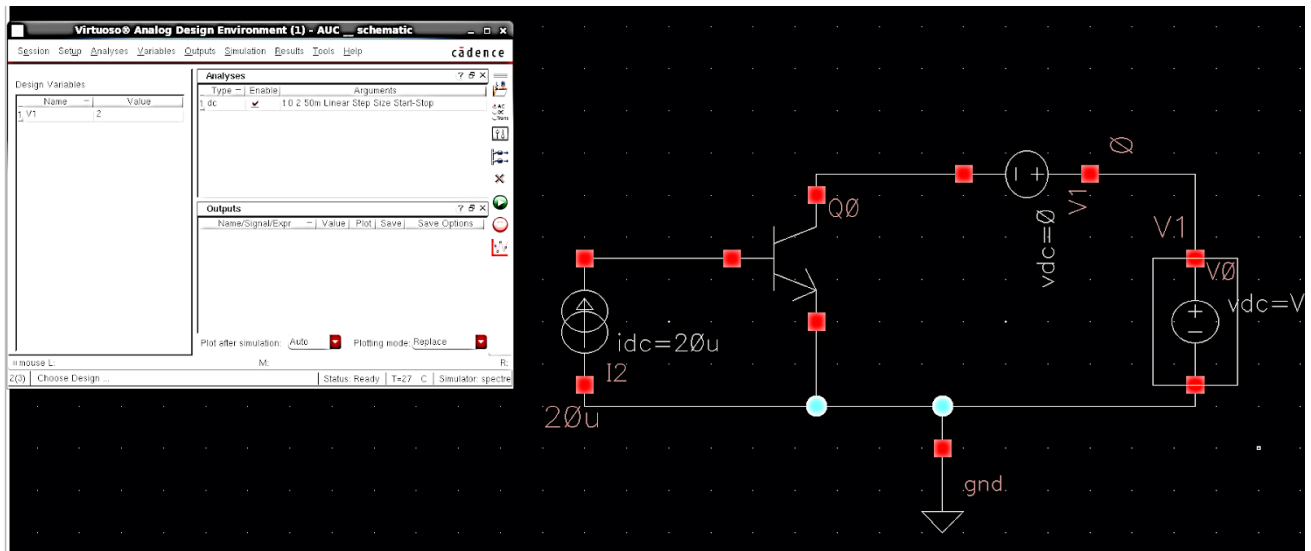


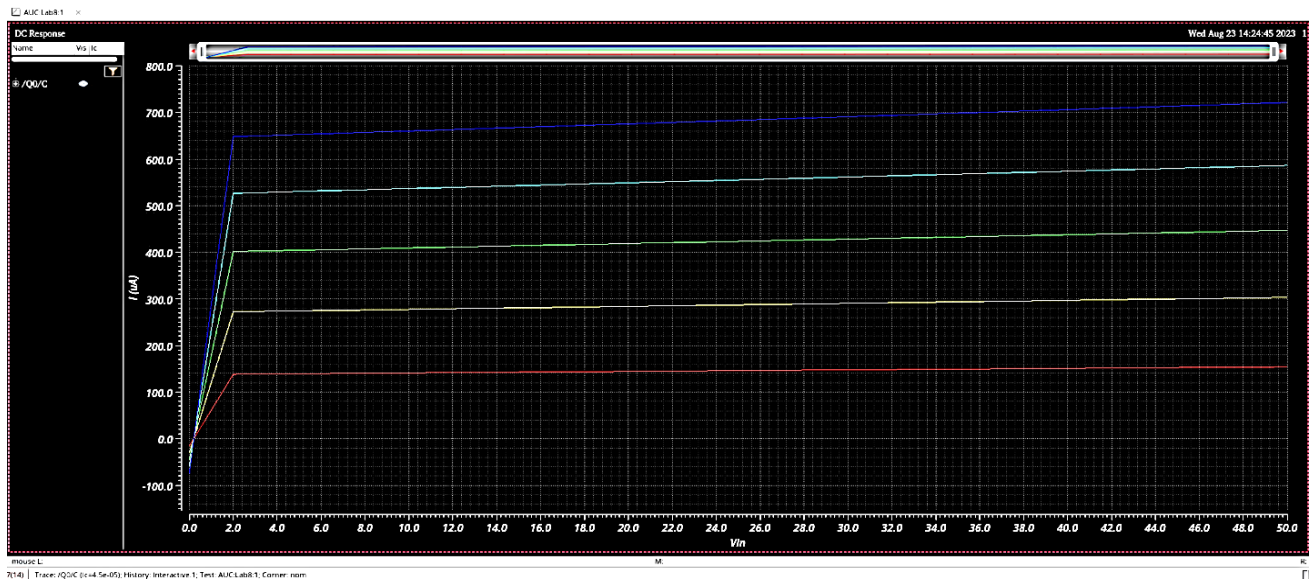if we increase the controlling (I_{dc}) current from $20\mu\text{A}$ to $75\mu\text{A}$, once again sweeping the battery (V_1) voltage from 0 to 50 volts and graphing the collector current in Figure below.



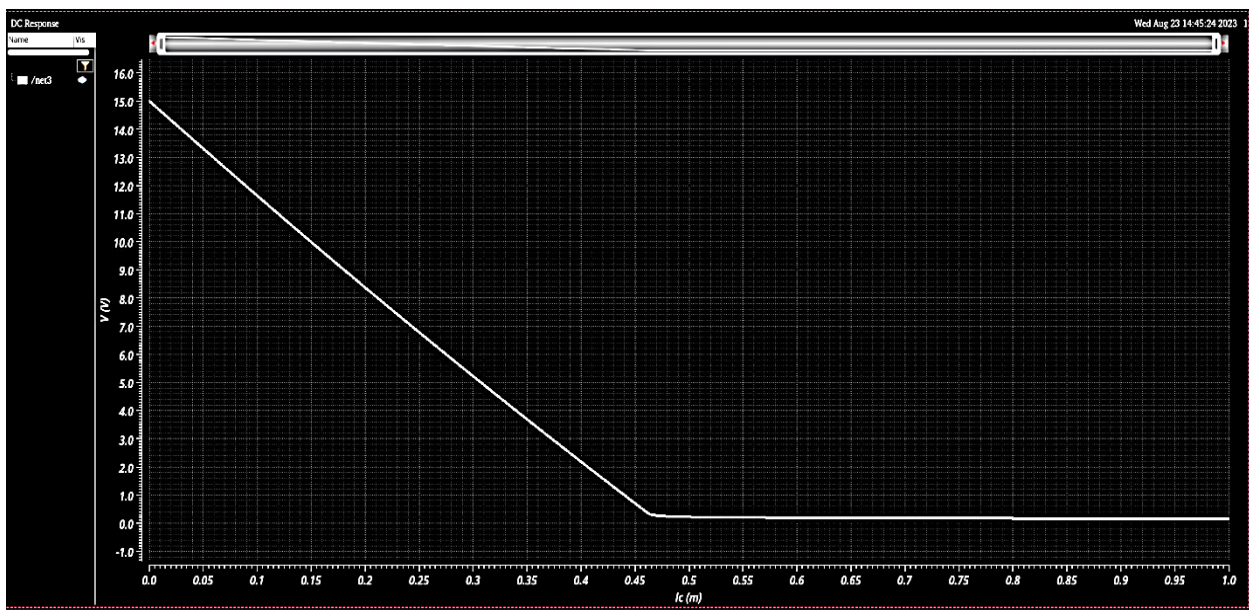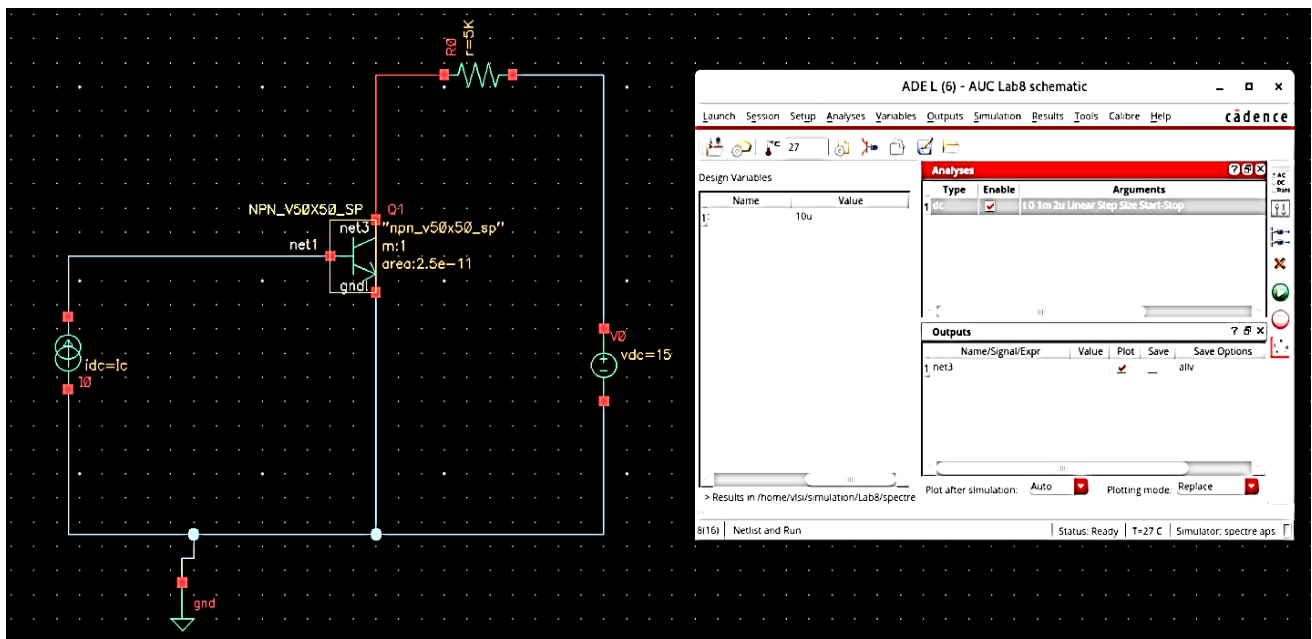
2. The common-emitter amplifier

The input and output signals both share a connection to the emitter.




At the beginning of the simulation in the figure above where the current source is outputting zero current, the transistor is in cutoff mode and the full 15 volts from the battery is shown at the amplifier output. As the current begins to increase, the output voltage proportionally decreases, until the transistor reaches saturation at $30\text{ }\mu\text{A}$ of base current (3 mA of collector current). Notice how the output voltage trace on the graph is perfectly linear until the point of saturation, where it never quite reaches zero.


3. The common-collector amplifier

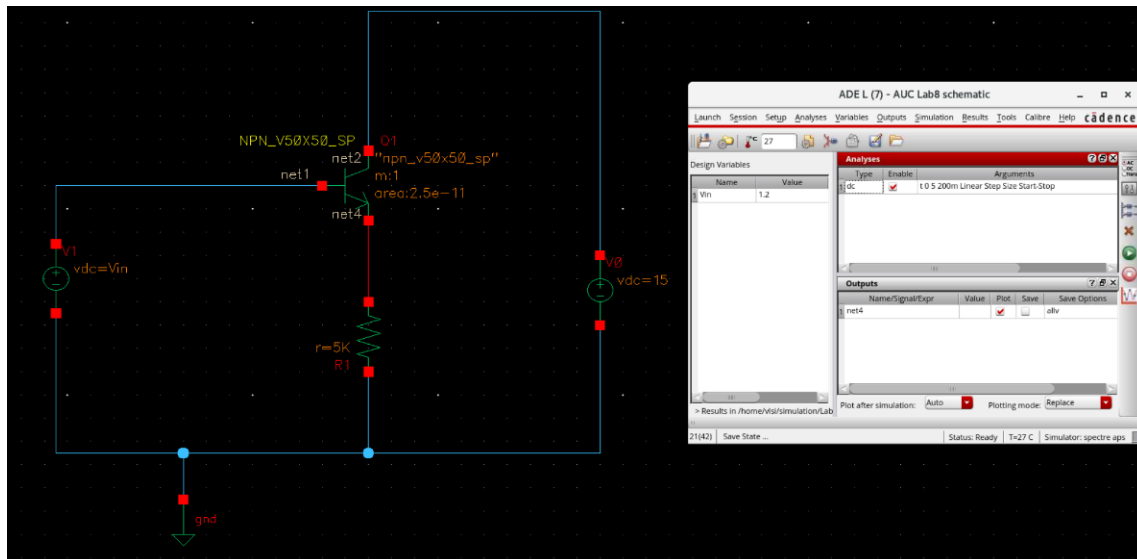

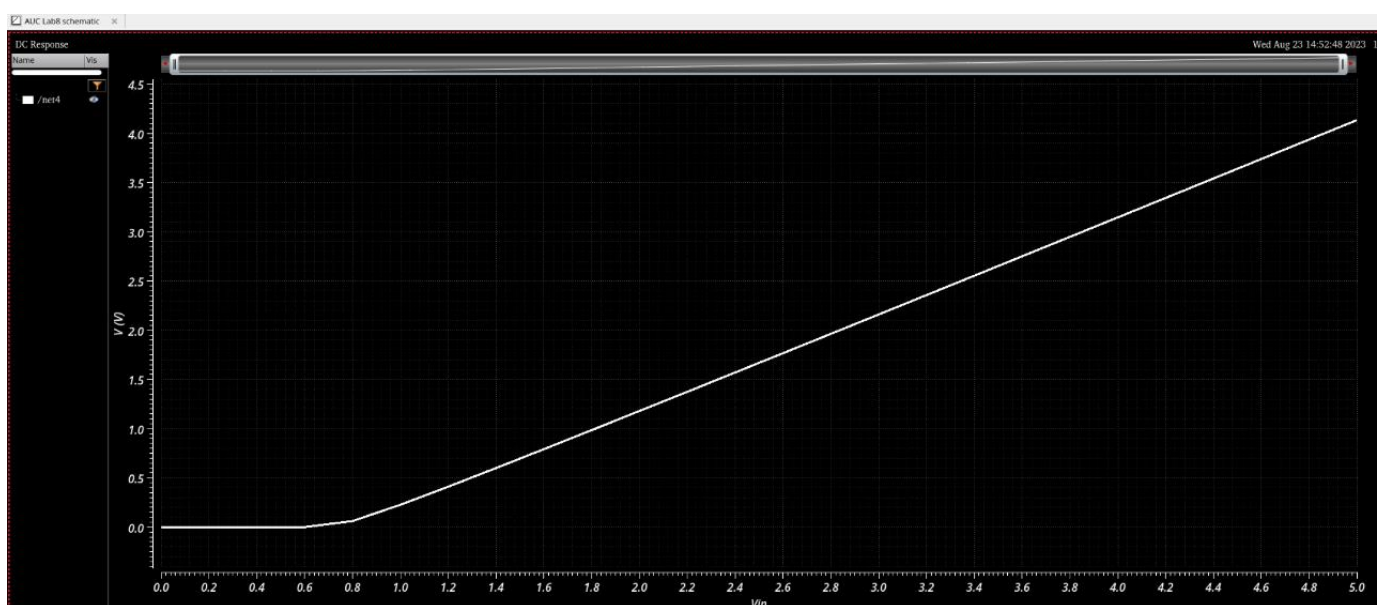
Unlike the common-emitter amplifier from the previous section, the common-collector produces an output voltage *direct* rather than *inverse* proportion to the rising input voltage. This amplifier has a voltage gain of almost unity (1), or 0 dB. This holds true for transistors of any β value, and for load resistors of any resistance value.



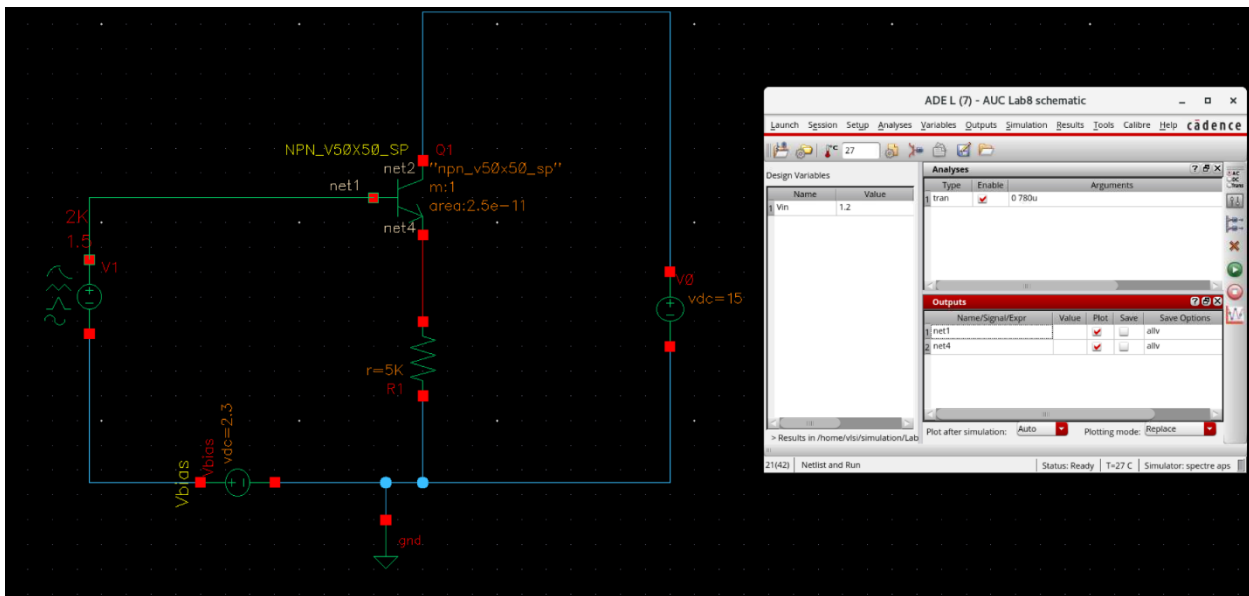
The common-collector amplifier circuit is also known as the *voltage-follower*



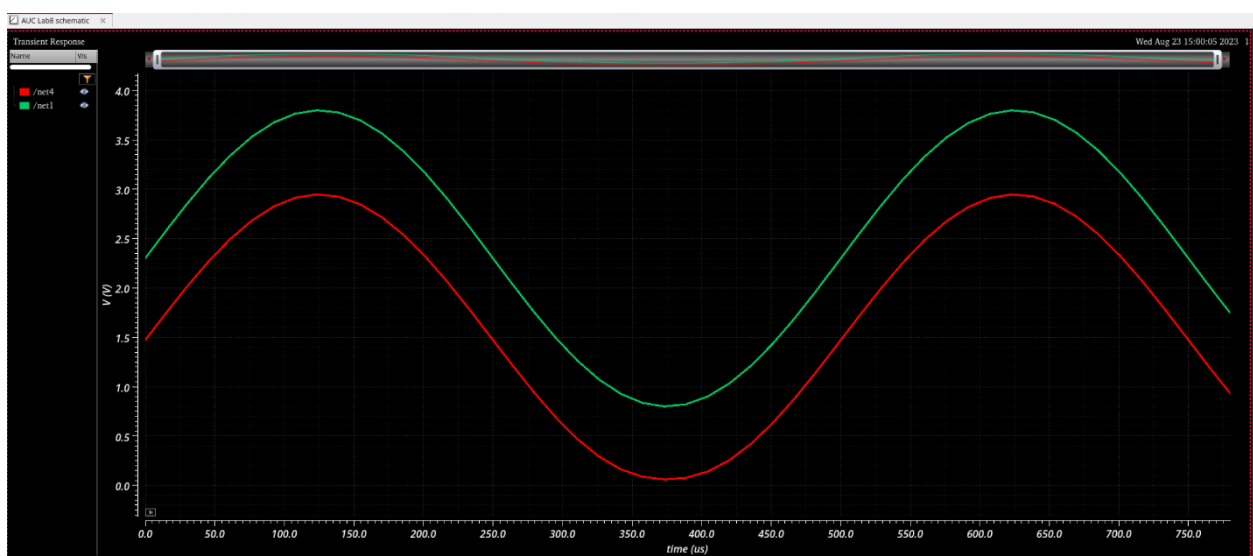
A DC voltage must be added to the AC input signal to keep the transistor in its active mode during the entire cycle. The results of the simulation in Figure below shows that the output follows the input. The output is the same peak-to-peak amplitude as the input. Though, the DC level is shifted downward by one V_{BE} diode drop.



4. The common-base amplifier

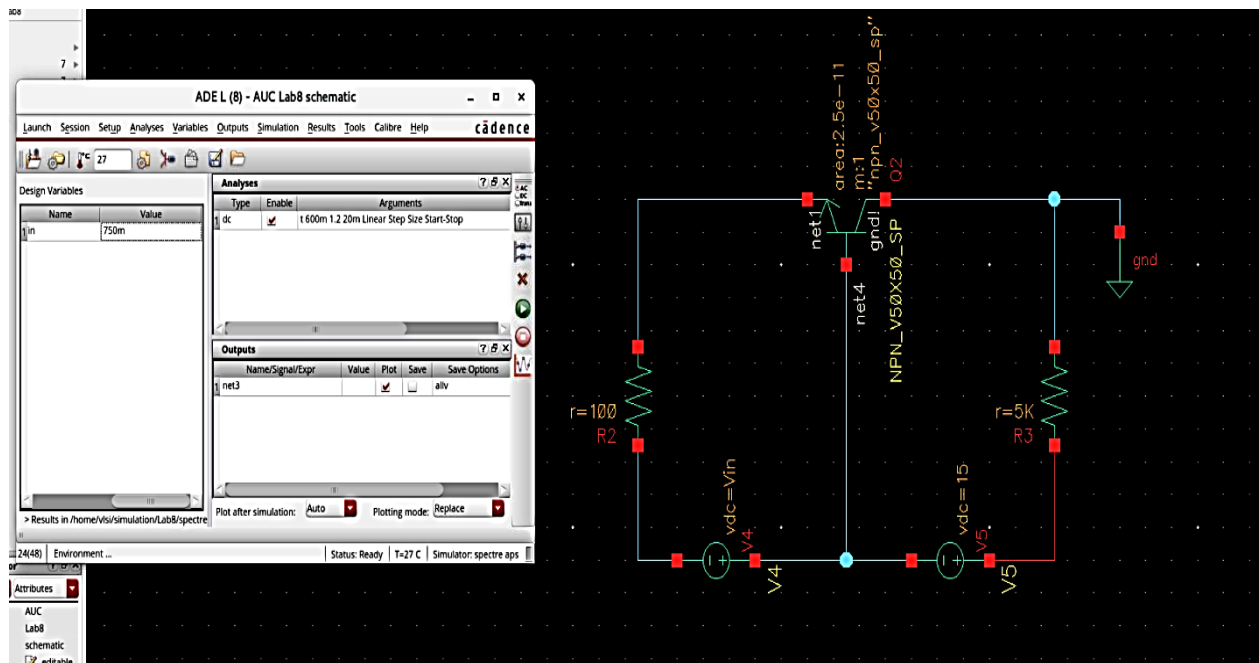


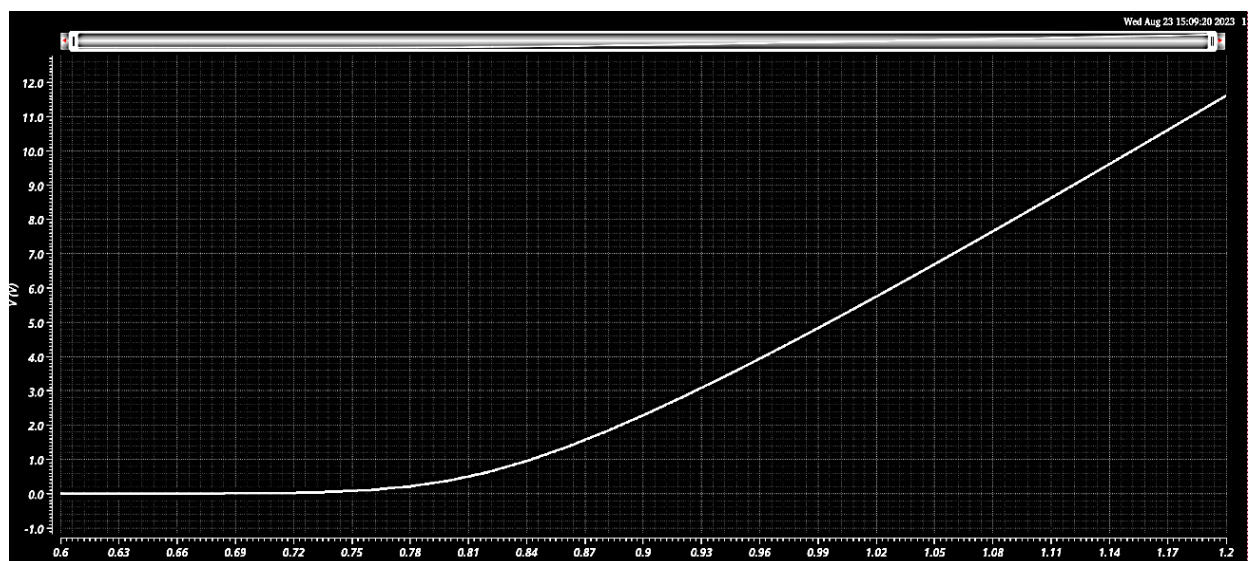
As we know, the emitter current is greater than any other current in the transistor, being the sum of base and collector currents. Because the input current exceeds all other currents in the circuit, including the output current, the current gain of this amplifier is less than 1. In other words, it attenuates current rather than amplifying it.



Notice in the figure above that the output voltage goes from practically nothing (cutoff) to 15.75 volts (saturation) with the input voltage being swept over a range of 0.6 volts to 1.2 volts. The output voltage plot doesn't show a rise until about 0.7 volts at the input and cuts off (flattens) at about 1.12 volts input. This represents a rather large voltage gain with an output voltage span of 15.75 volts and an input voltage span of only 0.42 volts: a gain ratio of 37.5, or 31.48 dB.

AC Input:

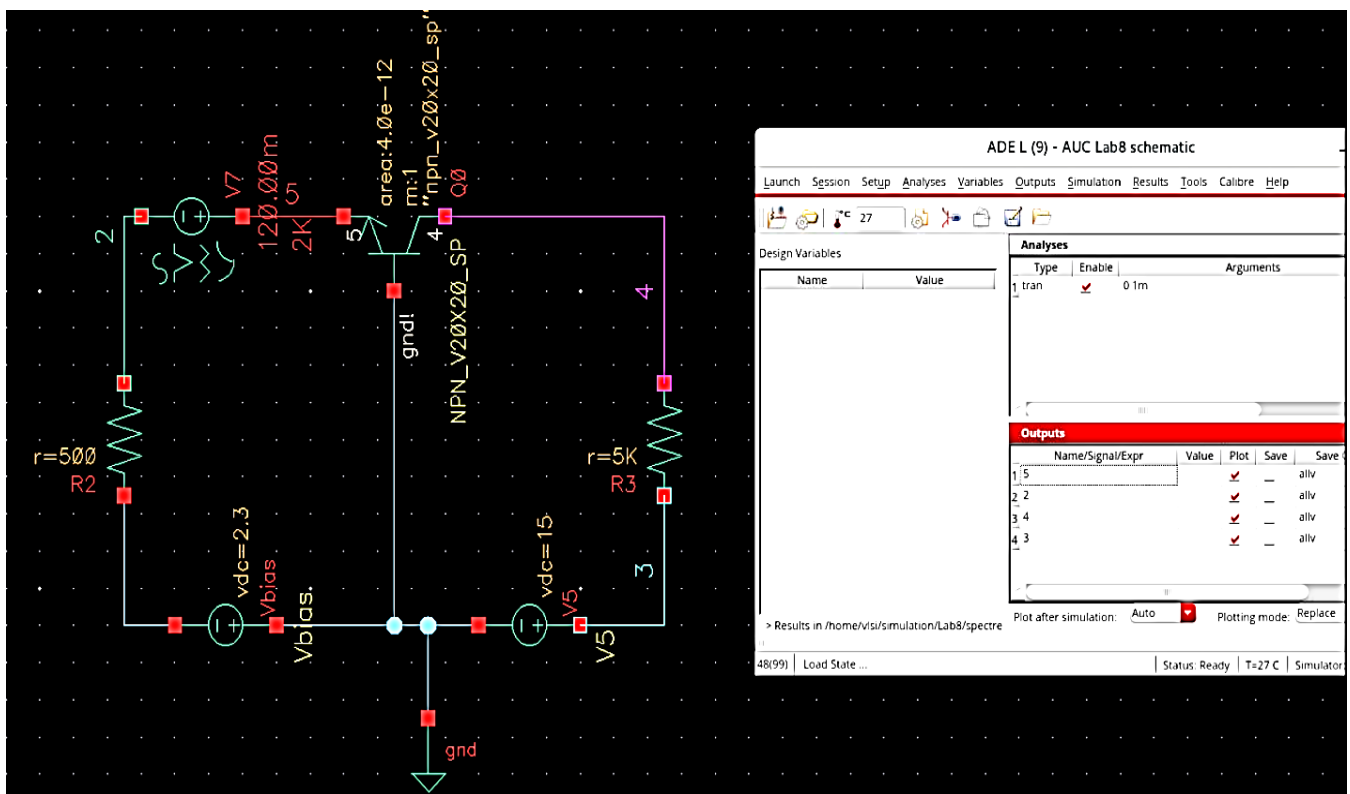

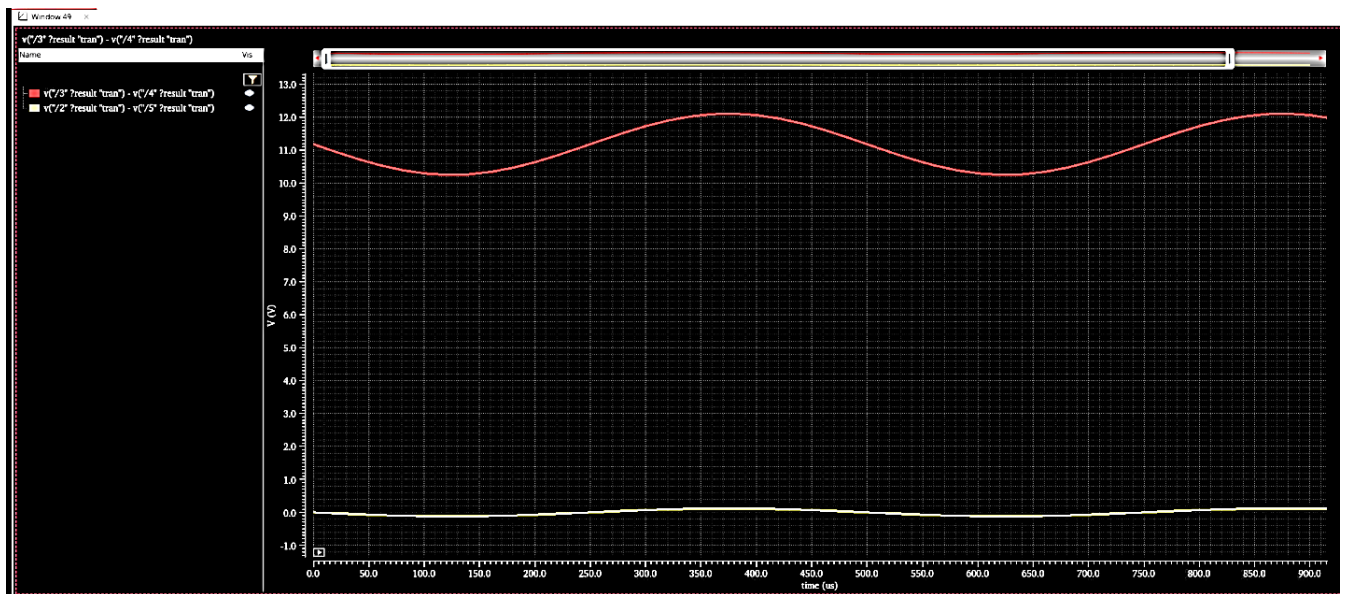

As we can see, the input and output waveforms in Figure below are in phase with each other. This tells us that the common-base amplifier is non-inverting with a high voltage gain.

Assignment 6

- Design a simple Series voltage regulator with BJT, Zener diode , resistance and load .
- Simulate the circuit below using cadence virtuoso.
- Try to run as same as steps of Zener regulator that we done before with mentioning your own comments.
- Compare between voltage regulator circuits(with bjt and with only zener) by advantages and dis advantages.

Bonus 6

- Design a **Transistor based Capacitance multiplier** with single transistor, capacitor, resistor, Ac source and putting load resistance =1kohm
- Record the output and input wave form with mention your comments
- Try to optimize your output curve

(load resistance not contained to design)