


High-pass filters

=> passes signals at frequencies higher than the cutoff frequency.


RC Circuit

$$Z_C = \frac{1}{j\omega C}$$

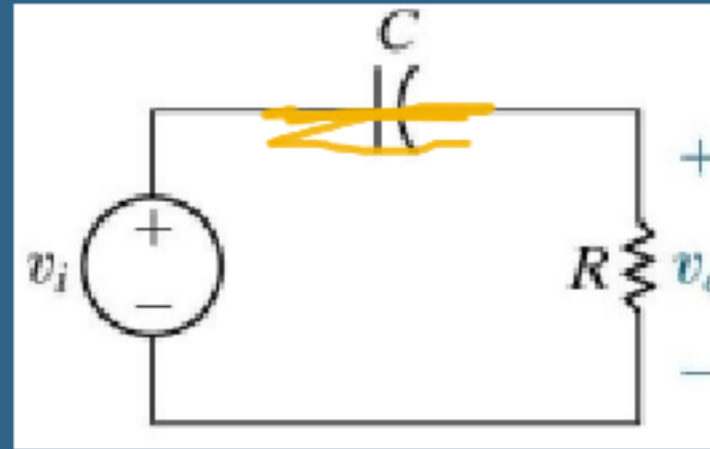
=> At $\omega = \infty$, the capacitor behaves as a s.c.,
so the capacitor voltage is zero.




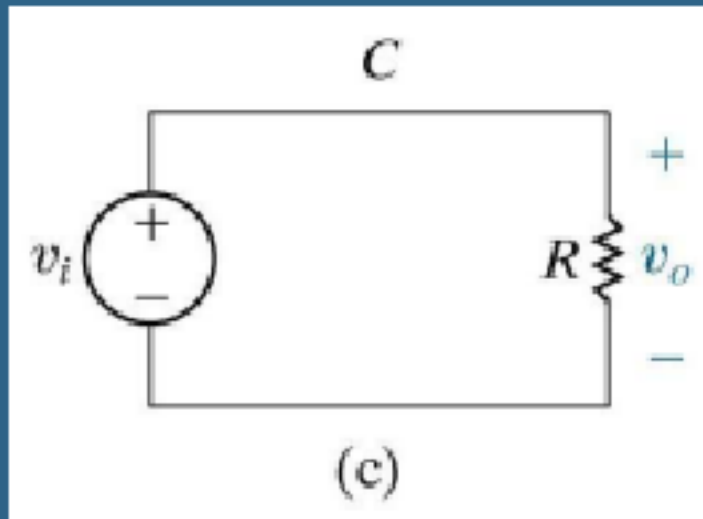
=> At $\omega = 0$, the capacitor behaves as an o.c.,
so no current on R.




high freq

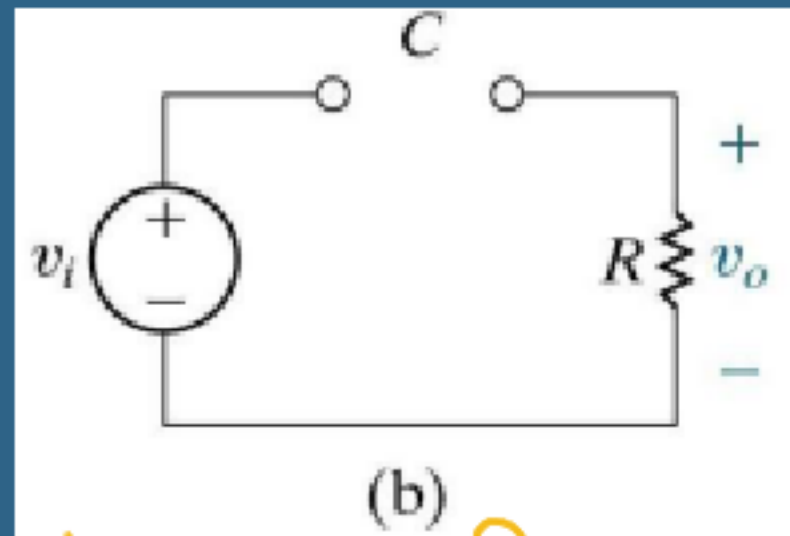

low freq

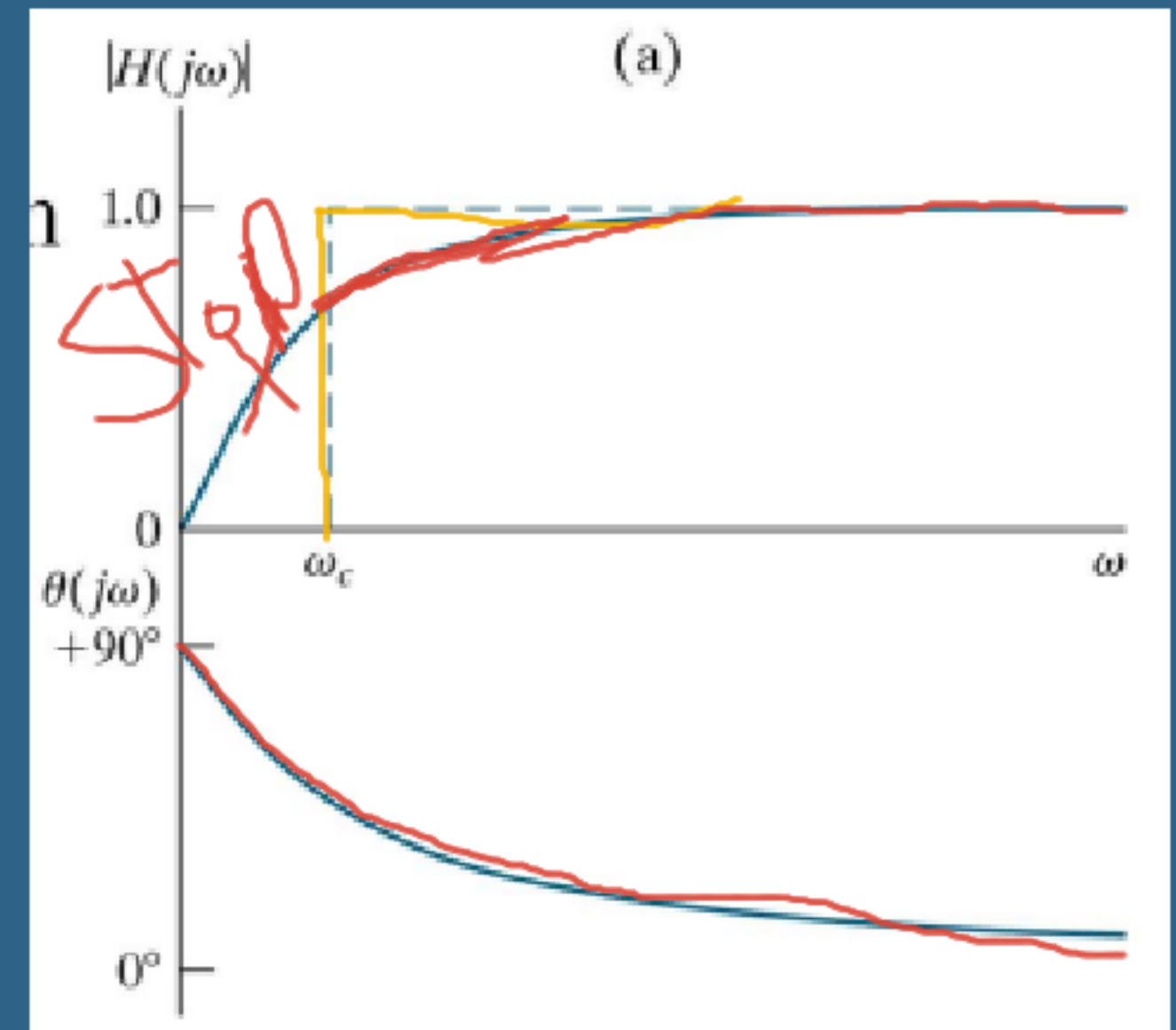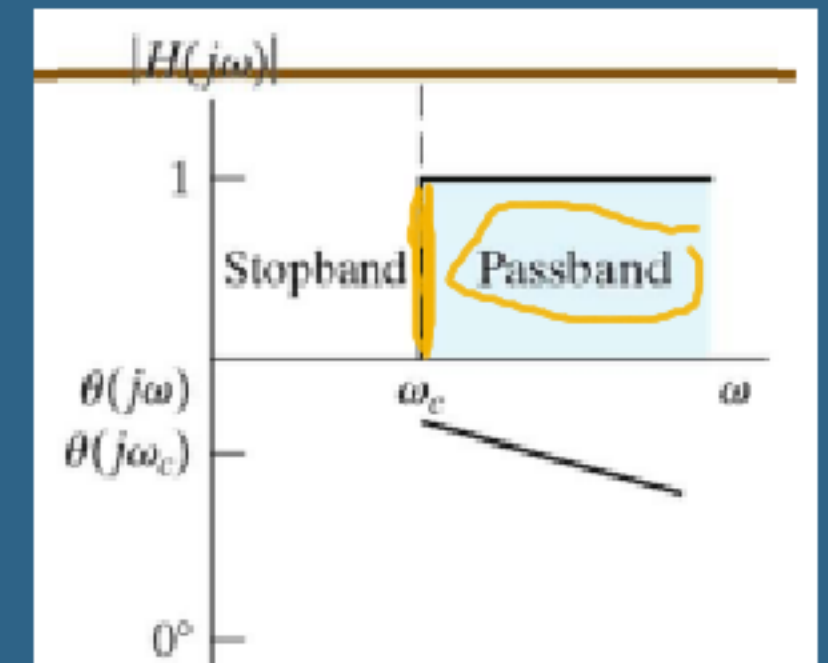


High-pass filters

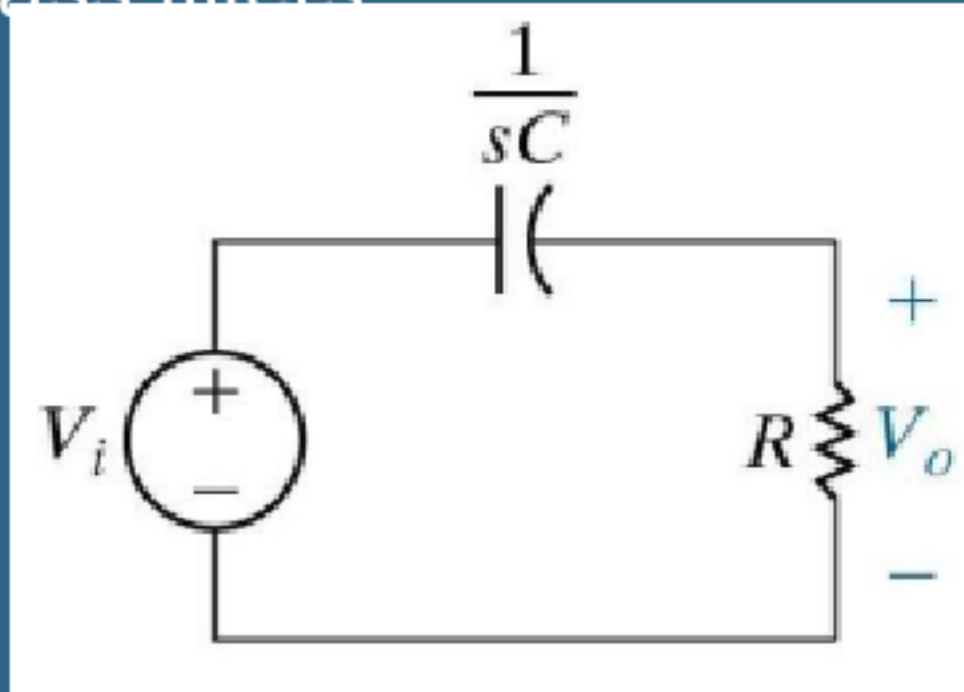

$$H(s) = \frac{s}{s + 1/RC}$$

$$\omega_c = 1/RC$$

$$= \frac{V_o}{V_i}$$

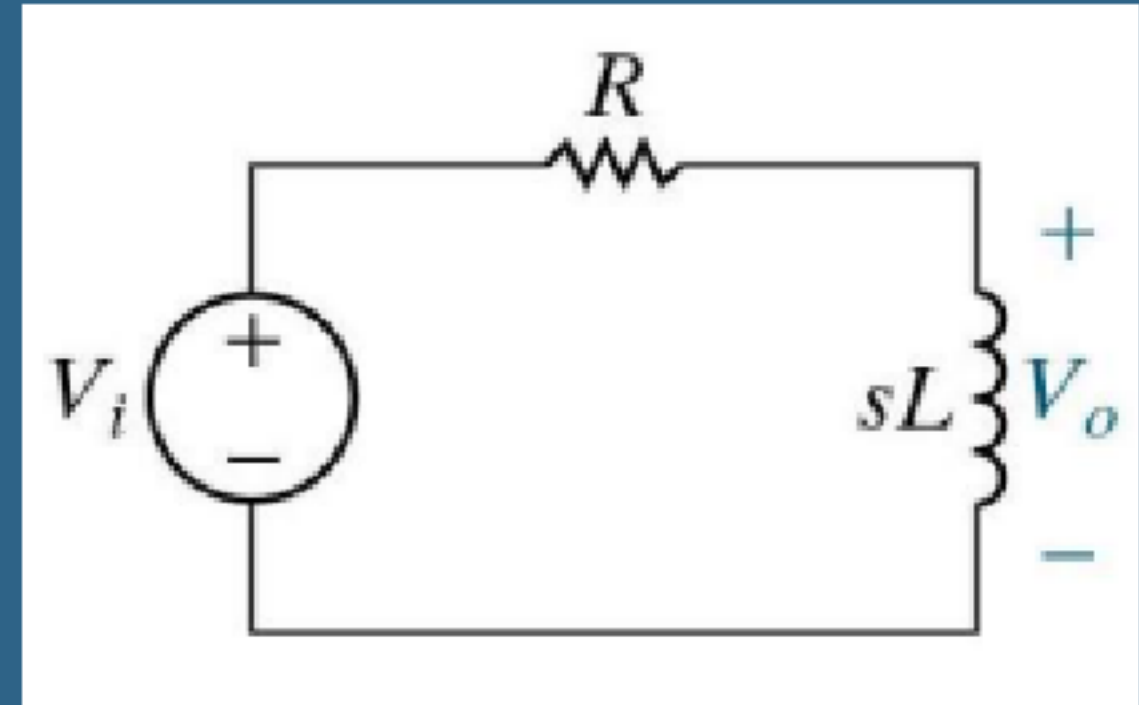

$$H(s) = \frac{s}{s + R/L}$$

$$\omega_c = R/L$$


$$= \frac{V_o}{V_i}$$

$$H(s) = \frac{s}{s + \omega_c}$$

Band-pass filters

==> passes a source voltage to the output only when the source frequency is within the band defined by the two cutoff frequencies.

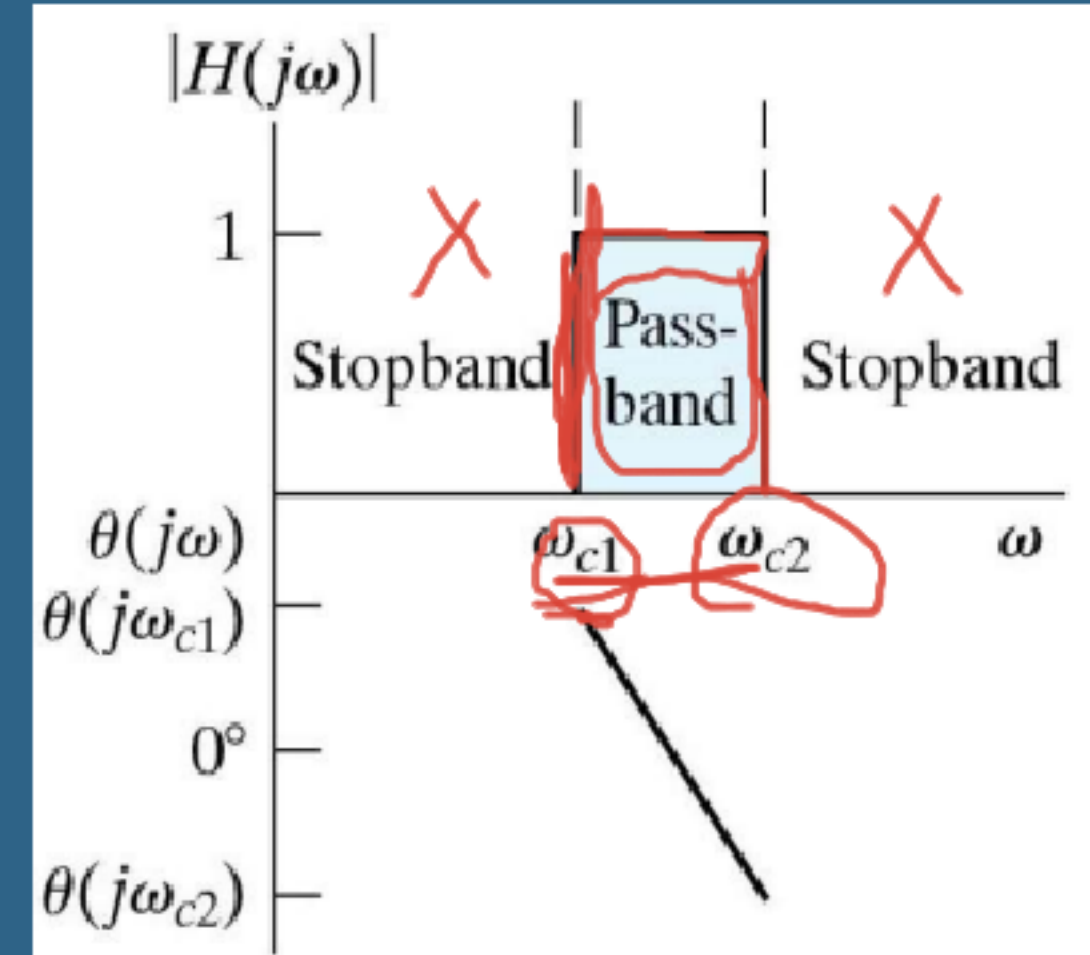
==> Ideal bandpass filters have two cutoff frequencies.



Series RLC Circuit

==> At $\omega = 0$: the capacitor behaves like an o.c., and the inductor behaves like a s.c.

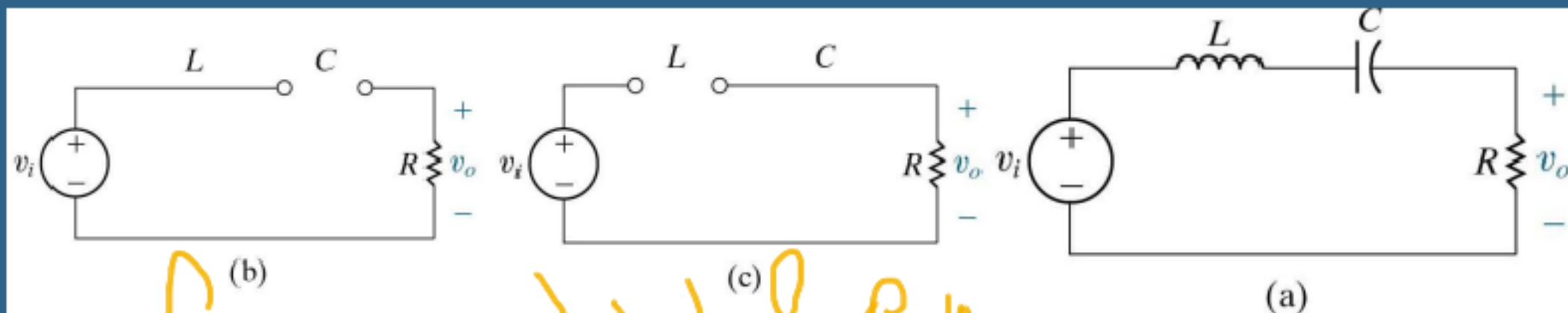==> At $\omega = \infty$, the capacitor behaves like a s.c., and the inductor behaves like an o.c.



low freq high freq

$$\omega_o = \sqrt{\frac{1}{LC}}$$

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$

$$\omega_o = \sqrt{\omega_{c1} \cdot \omega_{c2}}$$

$$\beta = \omega_{c2} - \omega_{c1}$$

$$\beta = \frac{R}{L}$$



Bandwidth

RELATIONSHIP AMONG QUALITY FACTOR
CENTER FREQUENCY AND BANDWIDTH


$$Q = \frac{\omega_o}{\beta}$$

QUALITY FACTOR, SERIES RLC FILTERS

$$Q = \sqrt{\frac{L}{R^2 C}}$$

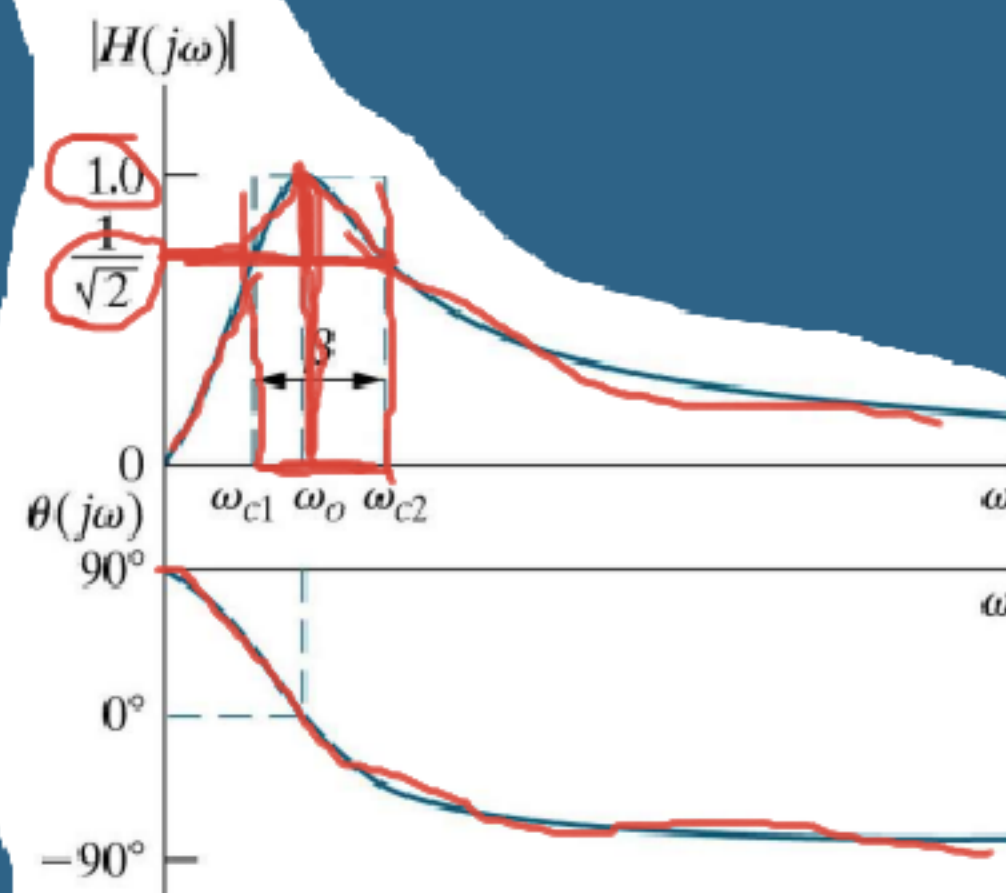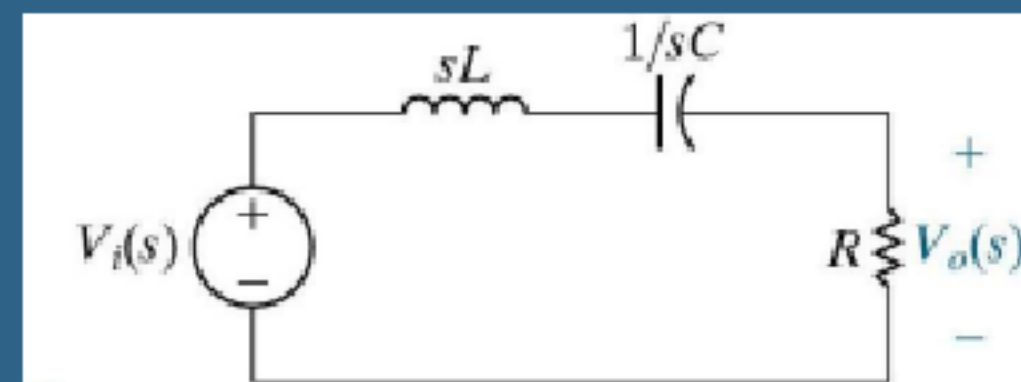

Series RLC Circuit

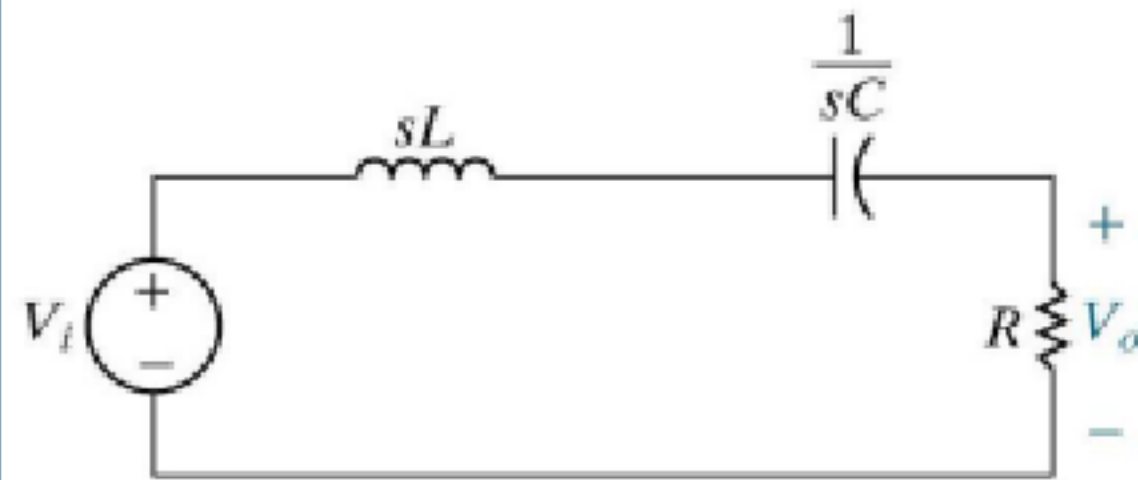


$$H(s) = \frac{(R/L)s}{s^2 + (R/L)s + 1/LC}$$

$$\checkmark \omega_o = \sqrt{1/LC}$$

$$\beta = R/L$$

Voltage Divider

Parallel LC Circuit

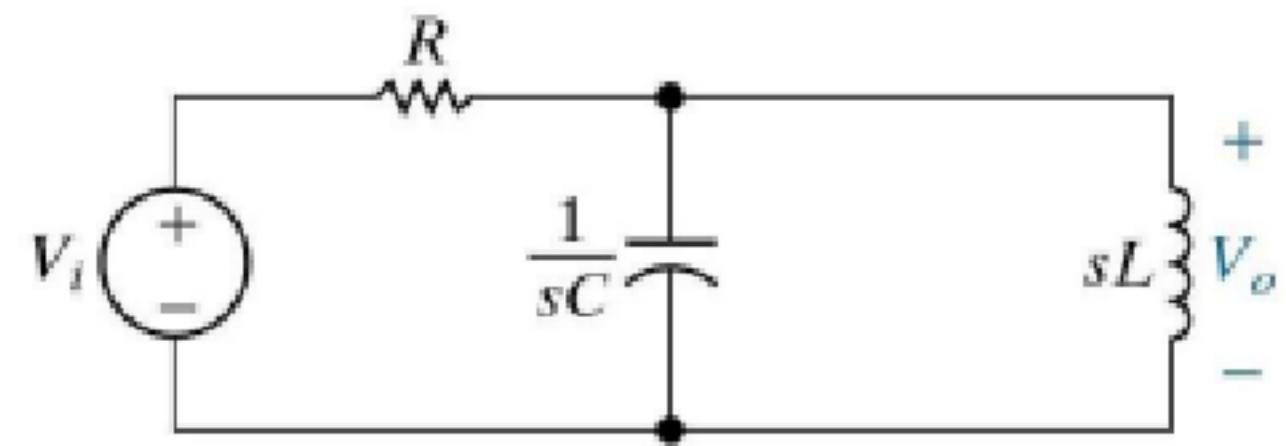

$$H(s) = \frac{s/RC}{s^2 + s/RC + 1/LC}$$

$$\checkmark \omega_o = \sqrt{1/LC}$$



$$\beta = 1/RC$$

Band-reject filter

passes a source voltage to the output only when the source frequency is outside the band defined by the two cutoff frequencies.




\Rightarrow At $\omega = 0$: the capacitor behaves like an o.c., and the inductor behaves like a s.c.

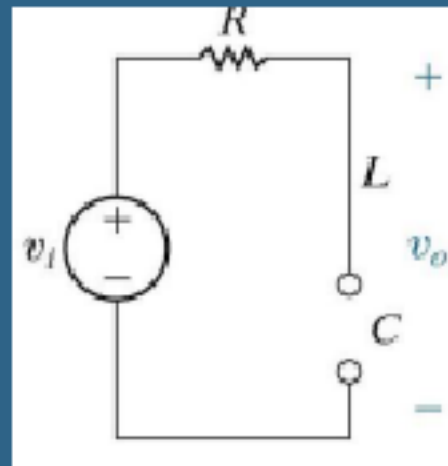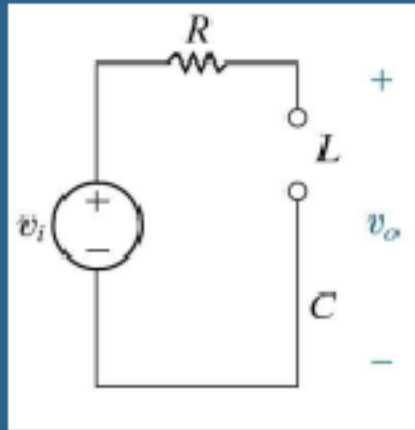\Rightarrow At $\omega = \infty$: the capacitor behaves like a s.c., and the inductor behaves like an o.c.



high

low

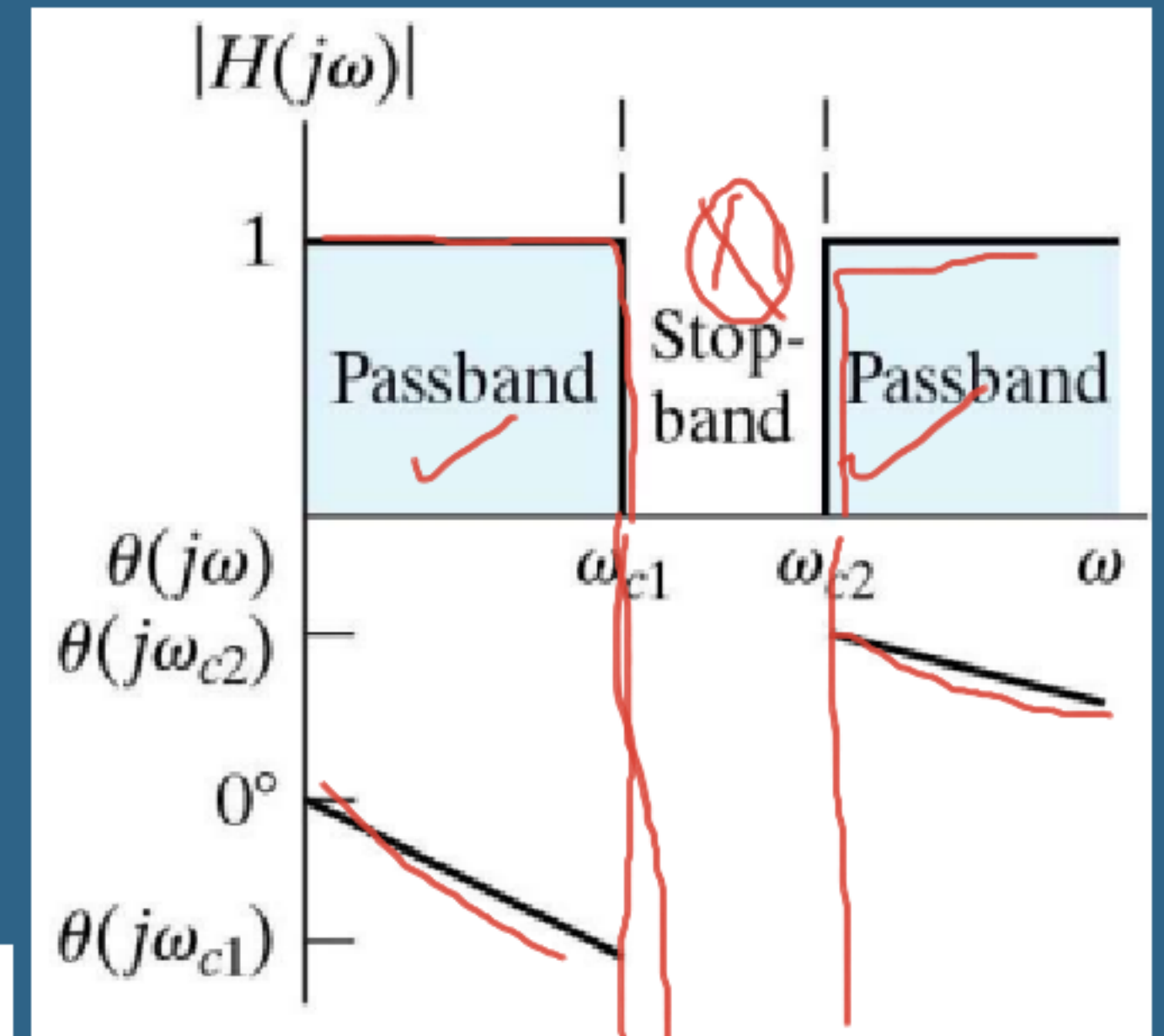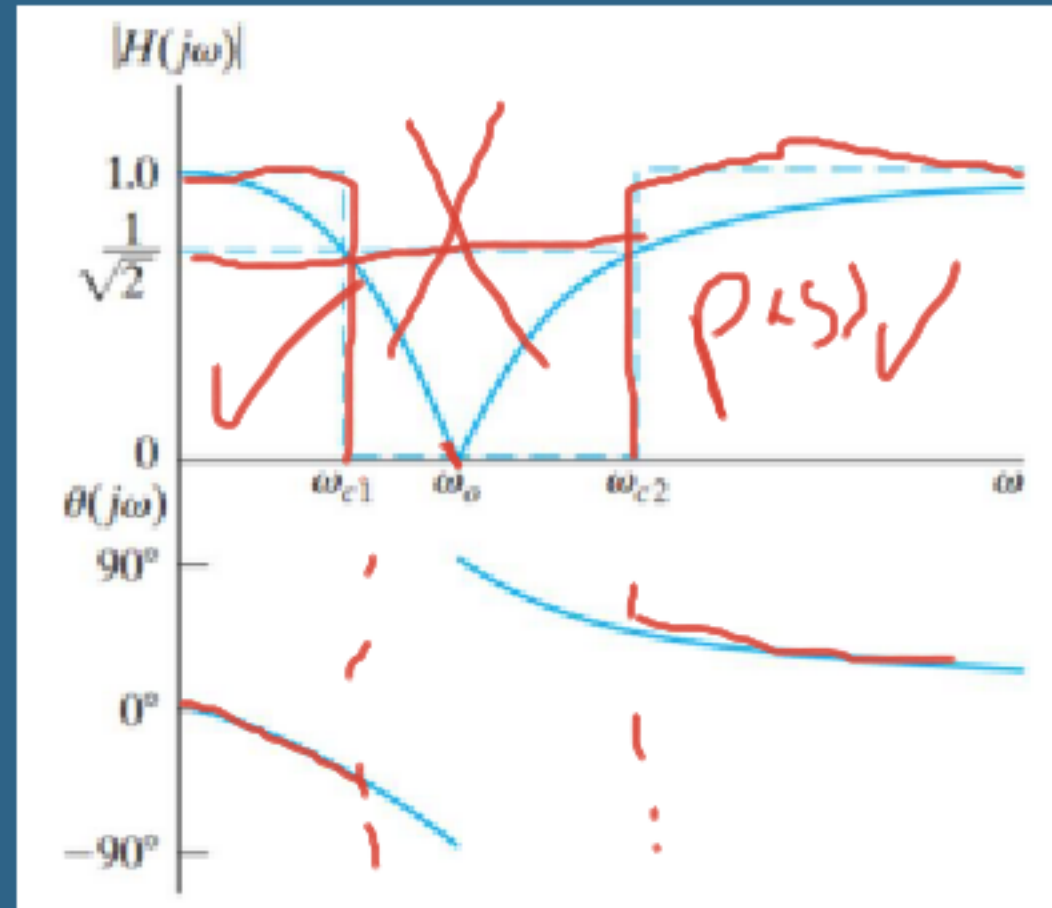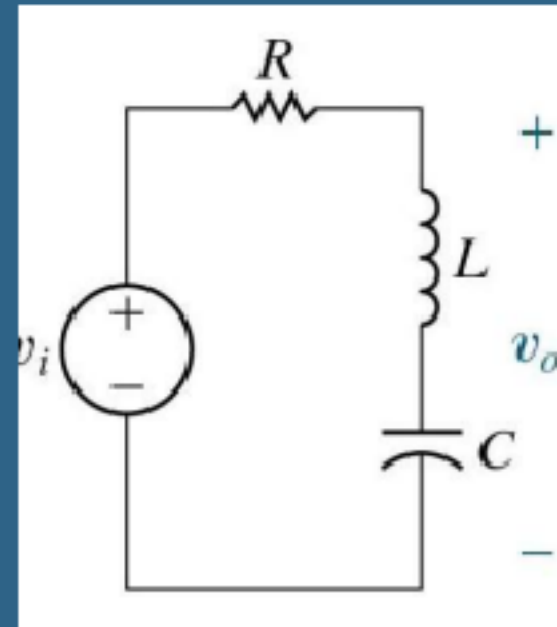

Filter Design Process

