
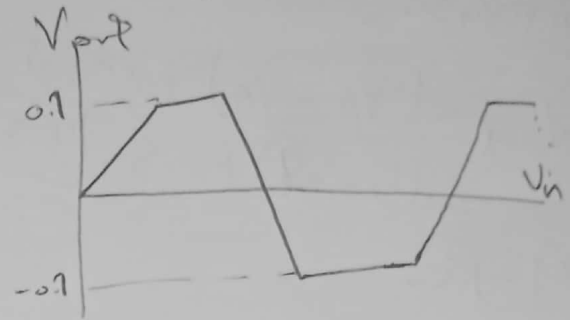


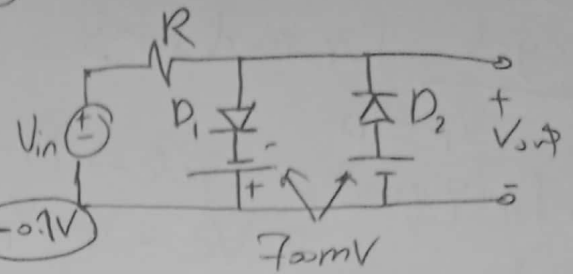Q1 @ $V_{in} > 0$

$$0.7 - 0.8 + V_{out} \therefore V_{out} = 0.1V$$


@ $V_{in} < 0$, $-0.7 + 0.8 + V_{out} \rightarrow V_{out} = -0.1V$



Q2 During +ve cycle of V_{in}

Diodes D_2, D_3 are off due to reverse biased


So $V_{out} = 0$

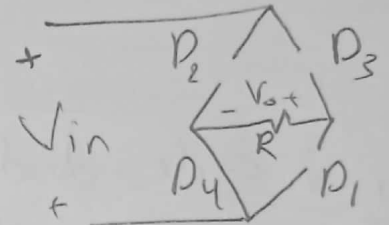

During -ve cycle of V_{in} :

D_1, D_3 are conducting (short circuit)

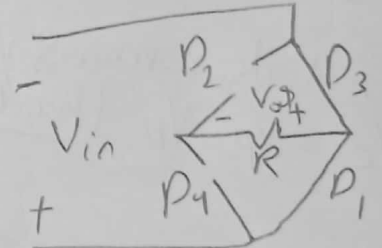$V_o = 0V$ no current flows through load resistor



\Rightarrow The full wave rectifier will not work properly as $V_o = 0V$
The V_o is zero in both (+ve) & (-ve) cycles.

Q3


+ve cycle : forward bias

$V_c = V_p - V_0$
after first quarter cycle \rightarrow the diode become
in reverse bias & $V_c = V_p - V_0$


$$V_{max} = (V_p - V_0) + \text{initial } V_c$$

$$= (5 - 0.8) + 0.5 = \boxed{4.7 \text{ V}}$$

$$T = RC$$

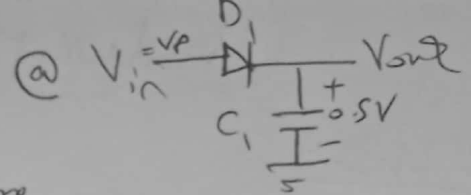

2

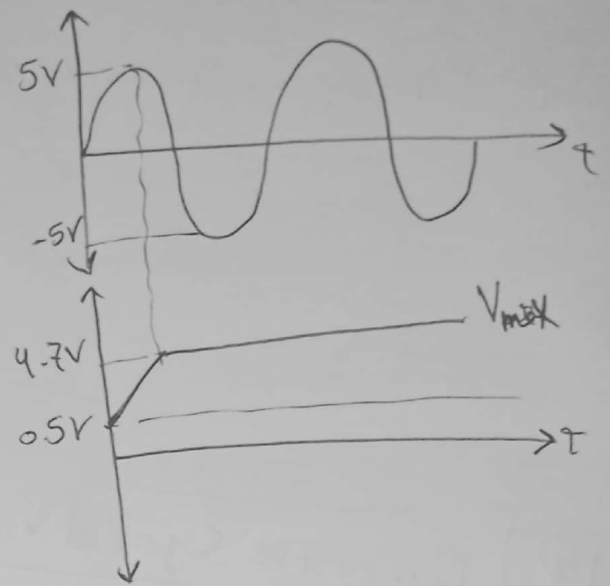

For -ve cycle : diode in forward bias

$V_c = V_p - V_0$, after 1st quarter cycle
 \rightarrow diode remains in reverse bias
 $V_c = V_p - V_0$ (holds)

$$V_{max} = (V_p - V_0) - \text{initial } V_c$$

$$= (5 - 0.8) - 0.5 = \boxed{3.7 \text{ V}} \#$$

